



02/02/03

Modification for a Kenwood R2000 to get relative good DRM conversion reception:

Simple 467kHz crystal controlled down mixer linked behind the first FM IF stage (base Q33). The filter F5 bandwidth at this point is ~15kHz and is activated in position FM ! The power for the mixer stage could simply be derived from the AN7809 voltage regulator.

