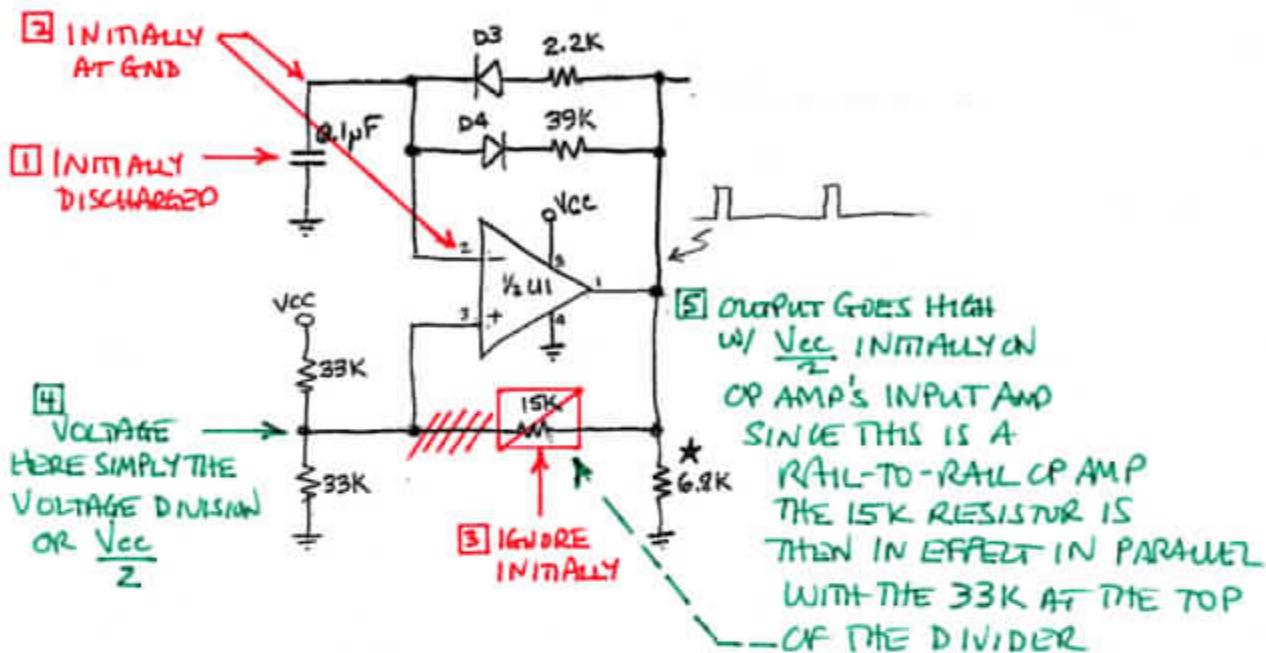


SOME NOTES FOR W2AEW'S VIDEO  
 #231: CIRCUIT FUN: STAIRSTEP  
GENERATOR USING 555 AND OP AMPS  
 (KL0S)


(A)



\* NOTE: THIS 6.8K RESISTOR IS NOT NEEDED IF THE OP AMP USED IS A GOOD RAIL-TO-RAIL DEVICE. SOME OP AMPS MAY NEED A PULL-DOWN RESISTOR AT THE OUTPUT TO FUNCTION CORRECTLY.


(B)

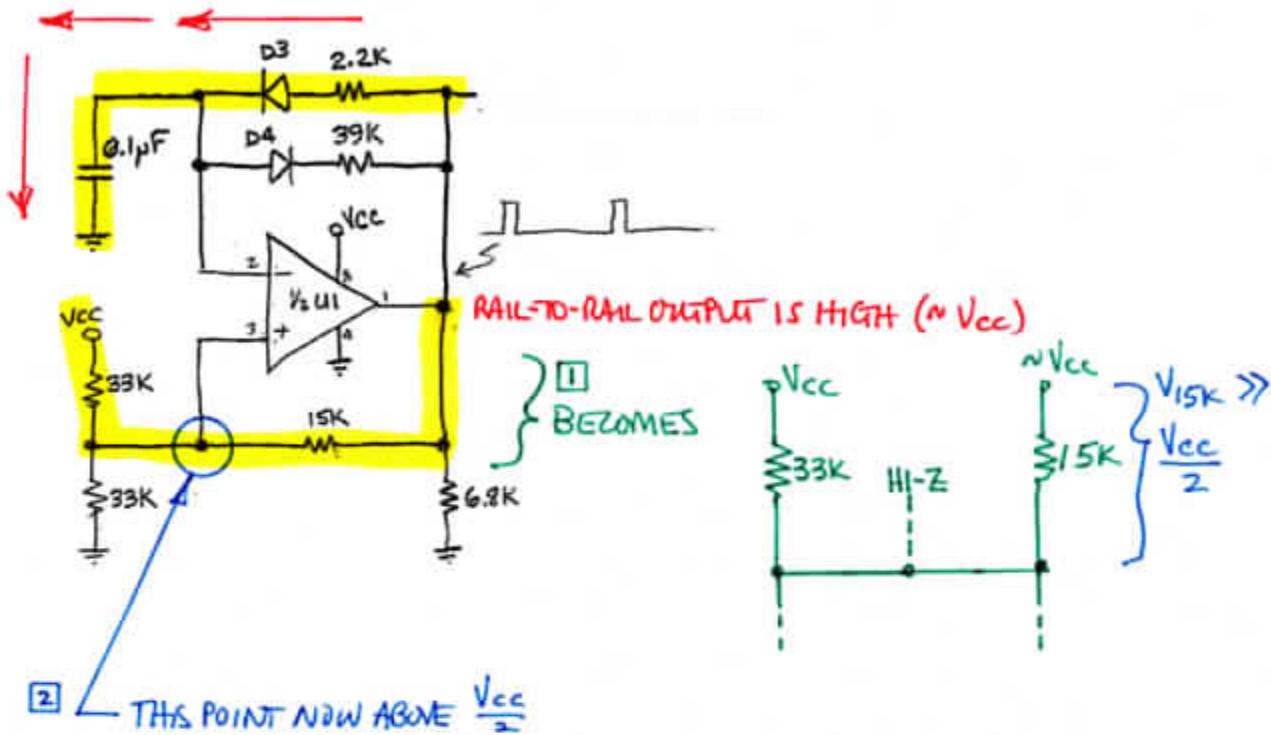② WITH OUTPUT INITIALLY HIGH CURRENT FLOWS VIA D<sub>3</sub> AND BEGINS TO CHARGE THE 0.1 $\mu$ F CAPACITOR




(C)

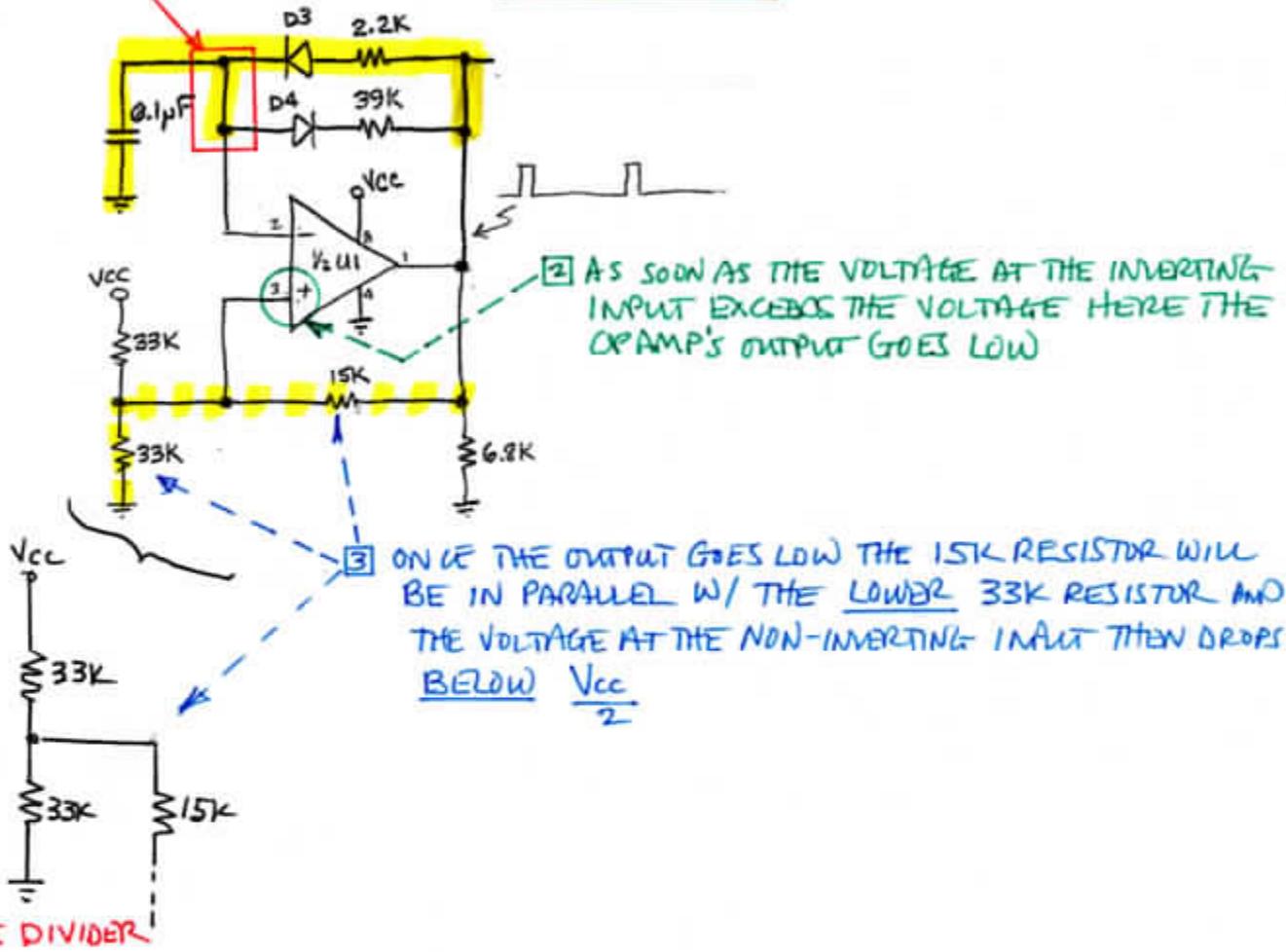① AS THE  $0.1\mu F$  CAPACITOR CHARGES THE VOLTAGE AT THIS POINT RISES UNTIL THAT VOLTAGE EQUALS AND THEN EXCEEDS THE VOLTAGE AT THE OP AMP'S NON-INVERTING (+) INPUT




ONCE THE VOLTAGE AT THE INVERTING INPUT (-) BECOMES MUCH HIGHER THAN THAT AT THE NON-INVERTING INPUT (+) [SINCE 15K IS IN EFFECT || TO THE LOWER 33K RESISTOR]


D

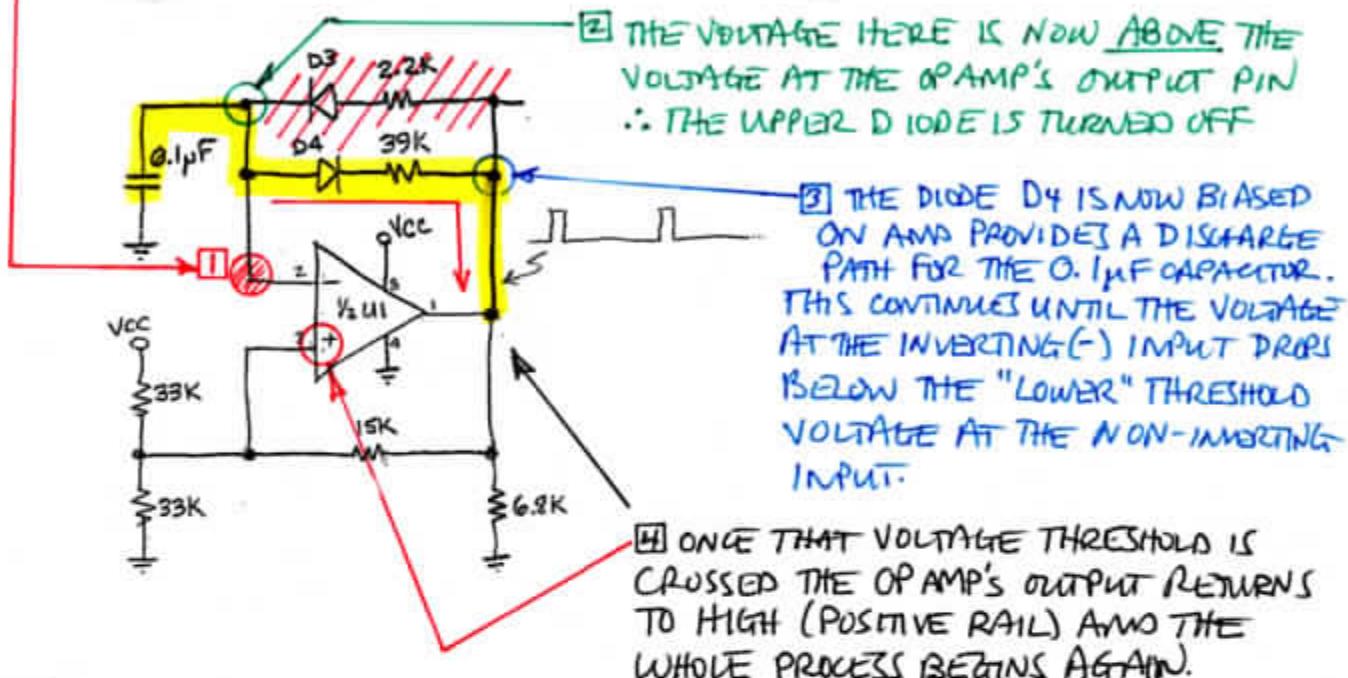

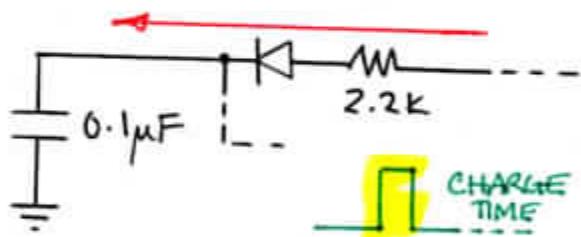- 1 THE TWO "STEERING DIODES" ARE USED TO CONTROL HOW QUICKLY THE 0.1 $\mu$ F CAPACITOR IS CHARGED AND THEN DISCHARGED



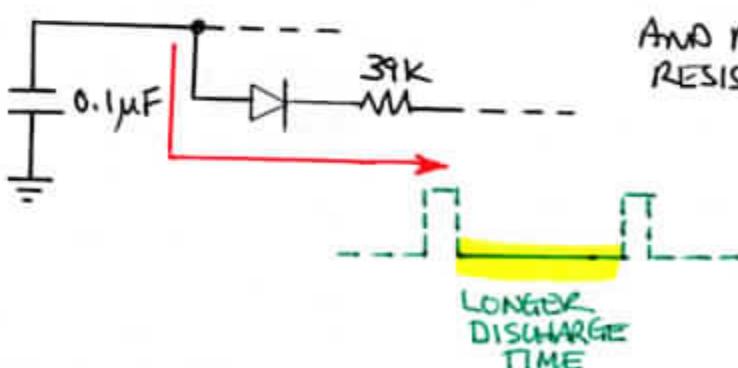HERE THE CAPACITOR CHARGES MORE QUICKLY SINCE WE'RE GOING THRU A RELATIVELY SMALL 2.2K RESISTOR



AND MORE SLOWLY THRU THE 39K RESISTOR

$$[39\text{k} \gg 2.2\text{k}]$$


- 1 PULSE WIDTH AND REPETITION RATE CAN BE CHANGED BY ADJUSTING THE VALUES OF THE 2.2K AND 39K RESISTORS.
- 2 TO CHANGE AND MAINTAIN THE RATIO SIMPLY CHANGE THE CAPACITOR.

(E)

- THE "STEPS" OF THE CIRCUIT ARE CREATED USING A 555 TIMER  
(COULD HAVE USED THE SAME OPAMP RELAXATION OSCILLATOR)
- A LOW DUTY-CYCLE PULSE TRAIN

**① INITIAL CHARGING  
PATH FOR THE 10nF  
CAPACITOR**

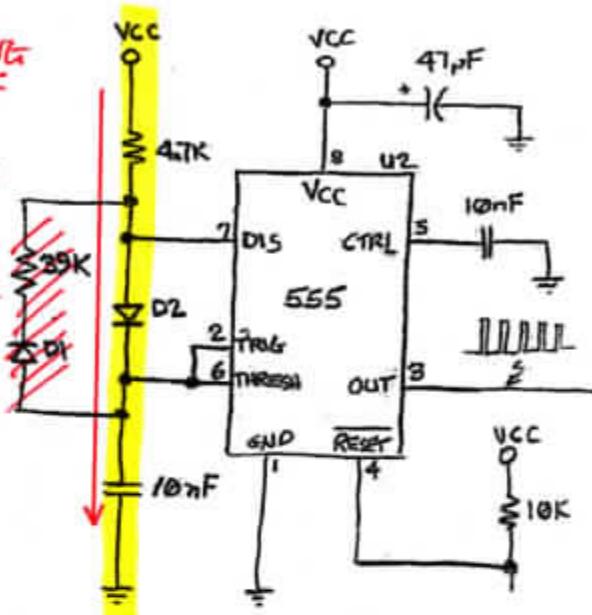- THE CHARGE PATH IS THRU THE SMALLER 4.7K RESISTOR
- ∴ A SHORTER CHARGE TIME (PULSE) AND IS ESSENTIALLY THE "ON TIME" OF THE OUTPUT.



**② ONCE THE VOLTAGE AT THE THRESHOLD - TRIGGER PINS RISES SUFFICIENTLY THE TIMER RESETS AND THE VOLTAGE ON THE 10nF CAP BLEEDS OFF VIA THE TIMER'S DISCHARGE PIN.**


- THE DISCHARGE PATH THRU THE HIGHER VALUE RESISTOR CREATES A LONGER "OFFTIME"

- ADJUSTING THESE VALUES CHANGES THE PULSE WIDTH AND REPETITION RATE.

\* THE VALUE OF USING A 555 IS THAT IT CAN BE STARTED AT A PARTICULAR TIME AND THUS BE SYNCHRONIZED WITH THE OTHER RELAXATION OSCILLATOR

THE "THRESHOLD" IS  $\frac{2}{3}$  OF  $V_{CC}$  AT WHICH POINT THE DISCHARGE IS TURNED ON — WHEN THE VOLTAGE FALLS TO  $\frac{1}{3}$  OF  $V_{CC}$  THE DISCHARGE FUNCTION DISENGAGES AND THE CHARGING CYCLE BEGINS AGAIN.

(F)

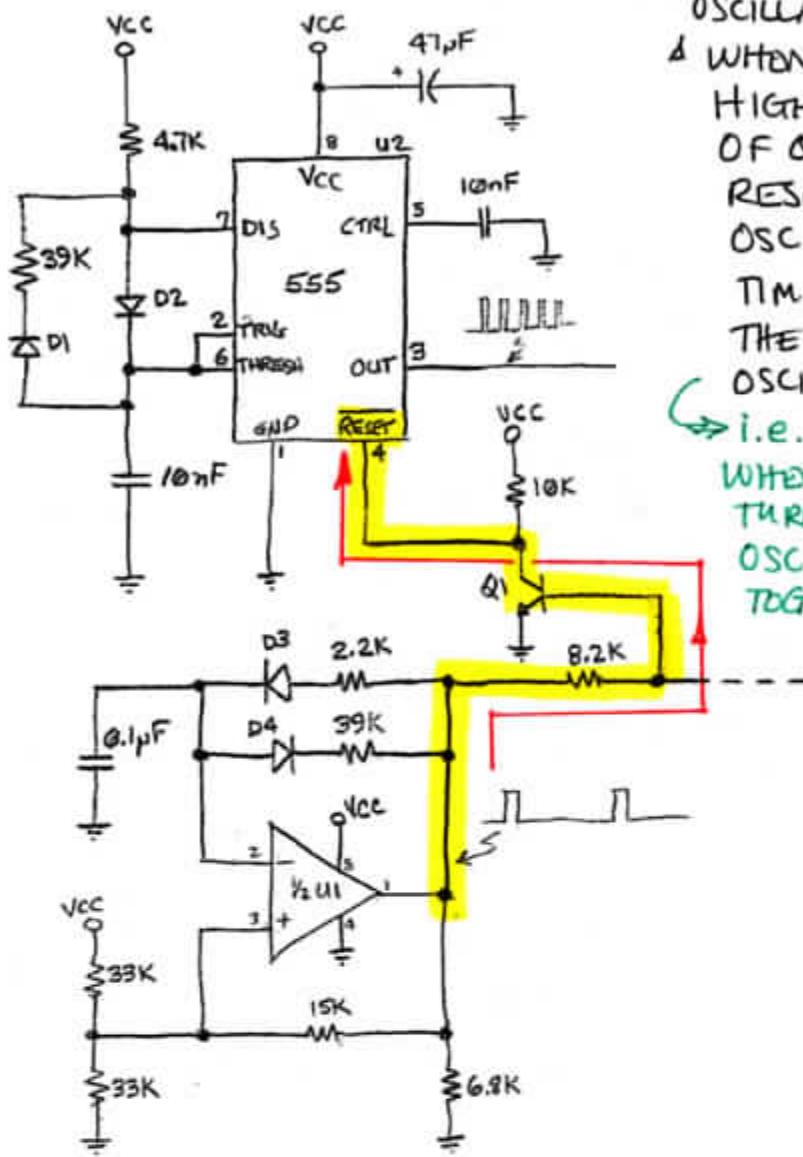

- 1 TRANSISTOR Q1 IS BEING DRIVEN BY THE OP AMP RELAXATION OSCILLATOR'S OUTPUT
- 2 WHEN THE OP AMP'S OUTPUT GOES HIGH IT PULLS DOWN THE COLLECTOR OF Q1 THUS GROUNDING THE 555 RESET PIN AND BEGINNING ITS OSCILLATOR ACTION; THE 555 TIMER STARTS ESSENTIALLY WITH THE SAME PERIOD AS THE OPAMP OSCILLATOR ACTION.
- ↳ i.e. THE FIRST "STEP" BEGINS WHEN THE OP AMP OSCILLATOR TURNS ON; THAT'S HOW THE TWO OSCILLATORS ARE SYNCHRONIZED TOGETHER.



?

SO HOW DO THE TWO OSCILLATORS COMBINE TO CREATE THE STAIRSTEP SIGNAL?


G

A THIS PART OF THE CIRCUIT IS CONFIGURED AS A PULSE INTEGRATOR OR ACCUMULATOR [SEE THE "DEBOO INTEGRATOR" WHICH IS BASED ON

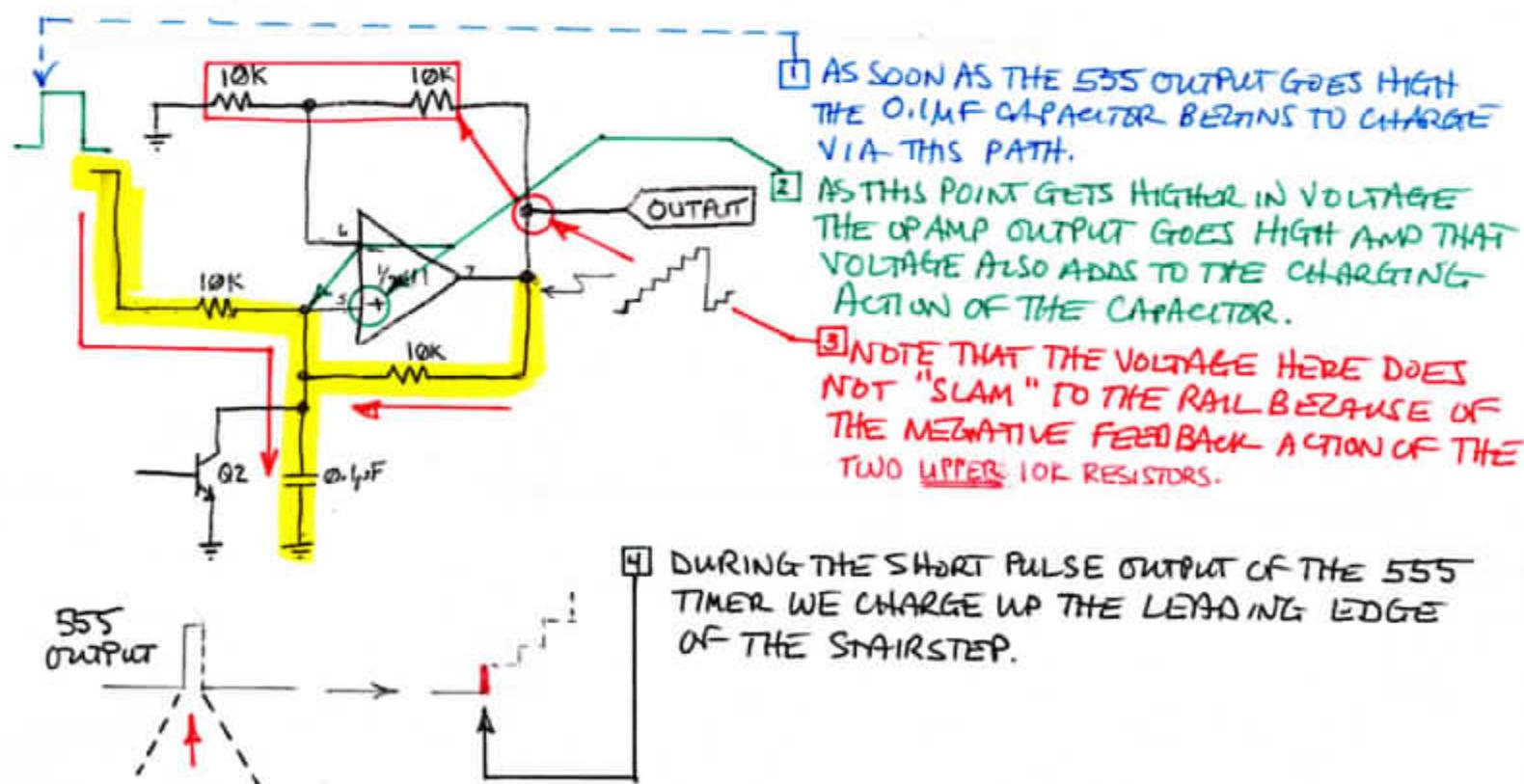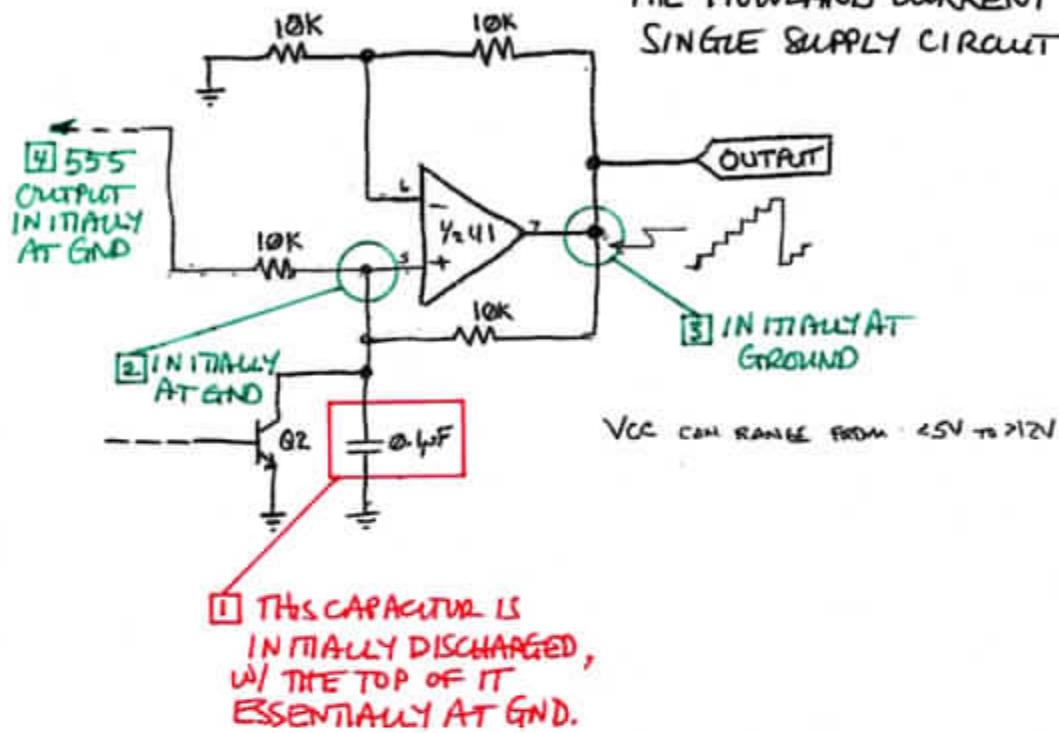
THE HOWLAND CURRENT SOURCE — GOOD FOR A SINGLE SUPPLY CIRCUIT SINCE IT'S NON-INVERTING]



(H)

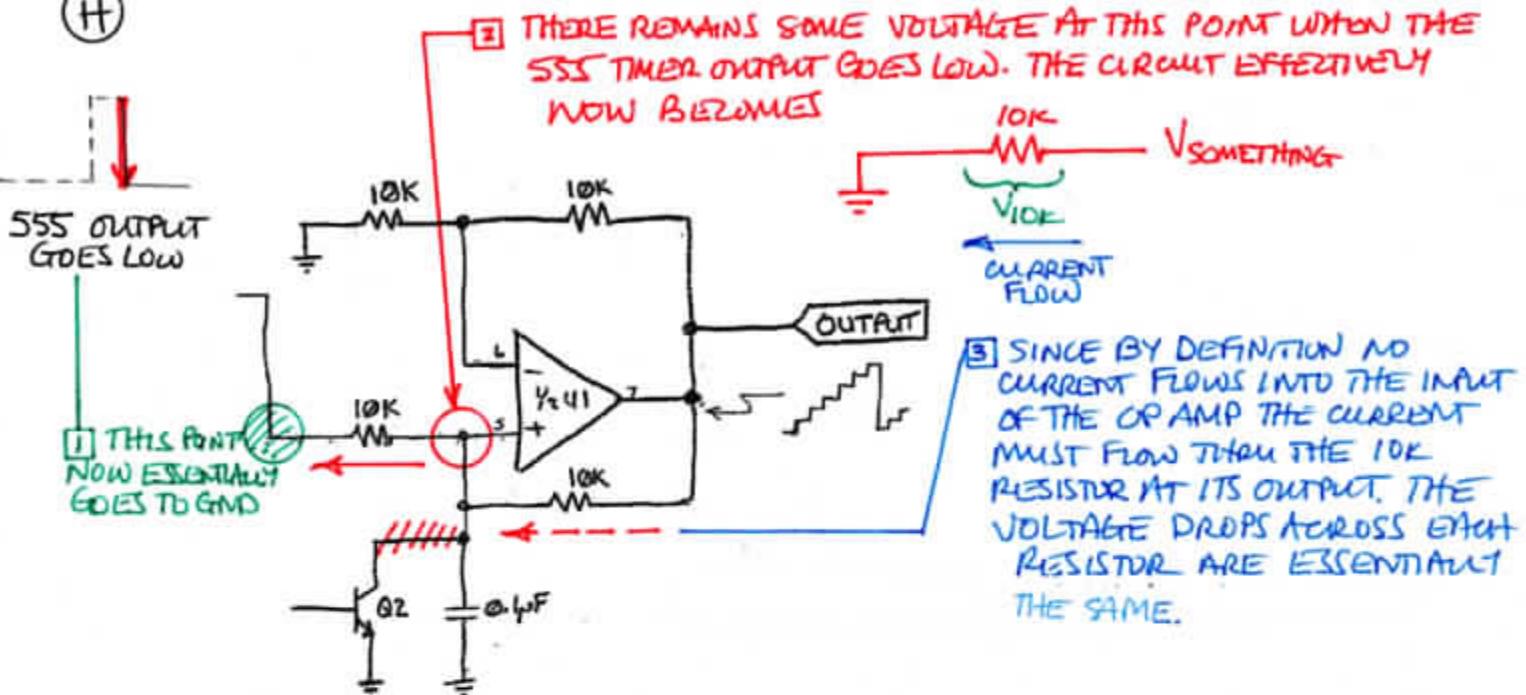

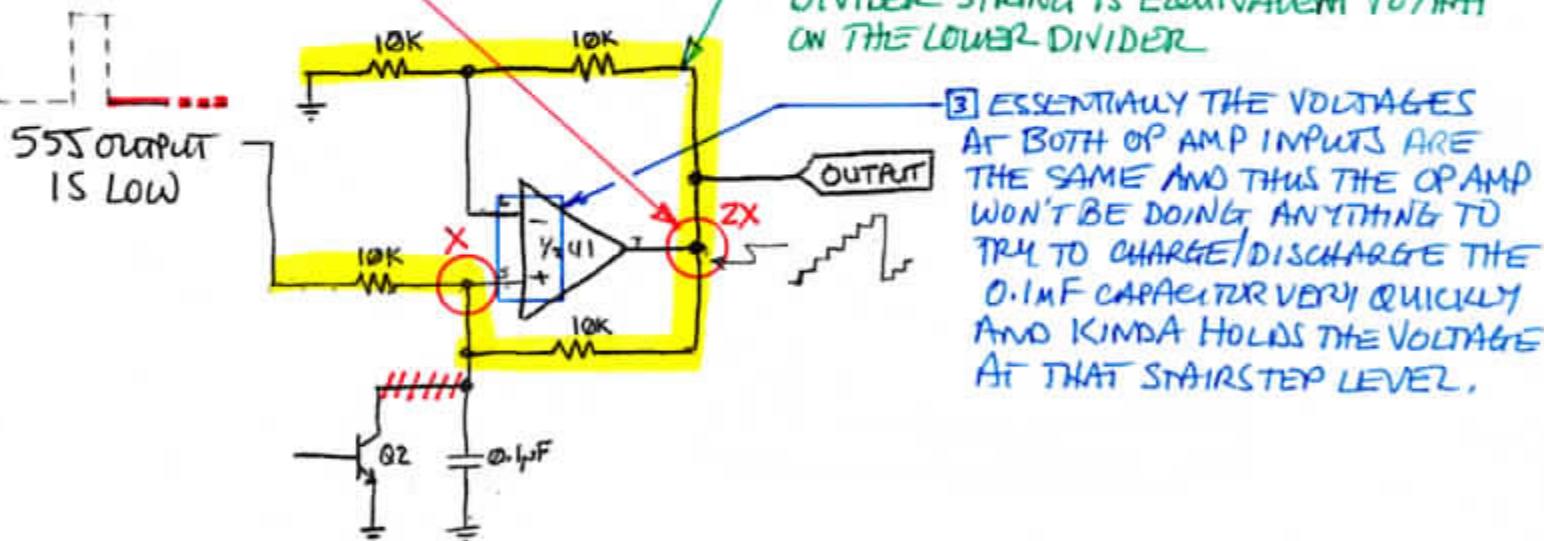
1 WITH THE VOLTAGE AT THE NON-INVERTING INPUT OF THE OP AMP CONSIDERED "X" THEN THE VOLTAGE AT THE OP AMP OUTPUT MUST BE  $\sim 2X$ .



2 SO WHEN THE 555 TIMER OUTPUT IS LOW THE OP-AMP OUTPUT REMAINS STATIC. THERE WILL BE SOME MINOR DROP OFF DUE TO LEAKAGE BUT NOT A SIGNIFICANT AMOUNT.

3 WHEN THE 555 OUTPUT GOES HIGH AGAIN THE CAPACITOR BEGINS TO CHARGE AGAIN THEREBY ADDING TO THE VOLTAGE ALREADY PRESENT AND CREATES THE NEXT STAIRSTEP; WHEN THE 555 OUTPUT GOES LOW AGAIN THE CIRCUIT AGAIN HOLDS THIS HIGHER VOLTAGE.

(I)

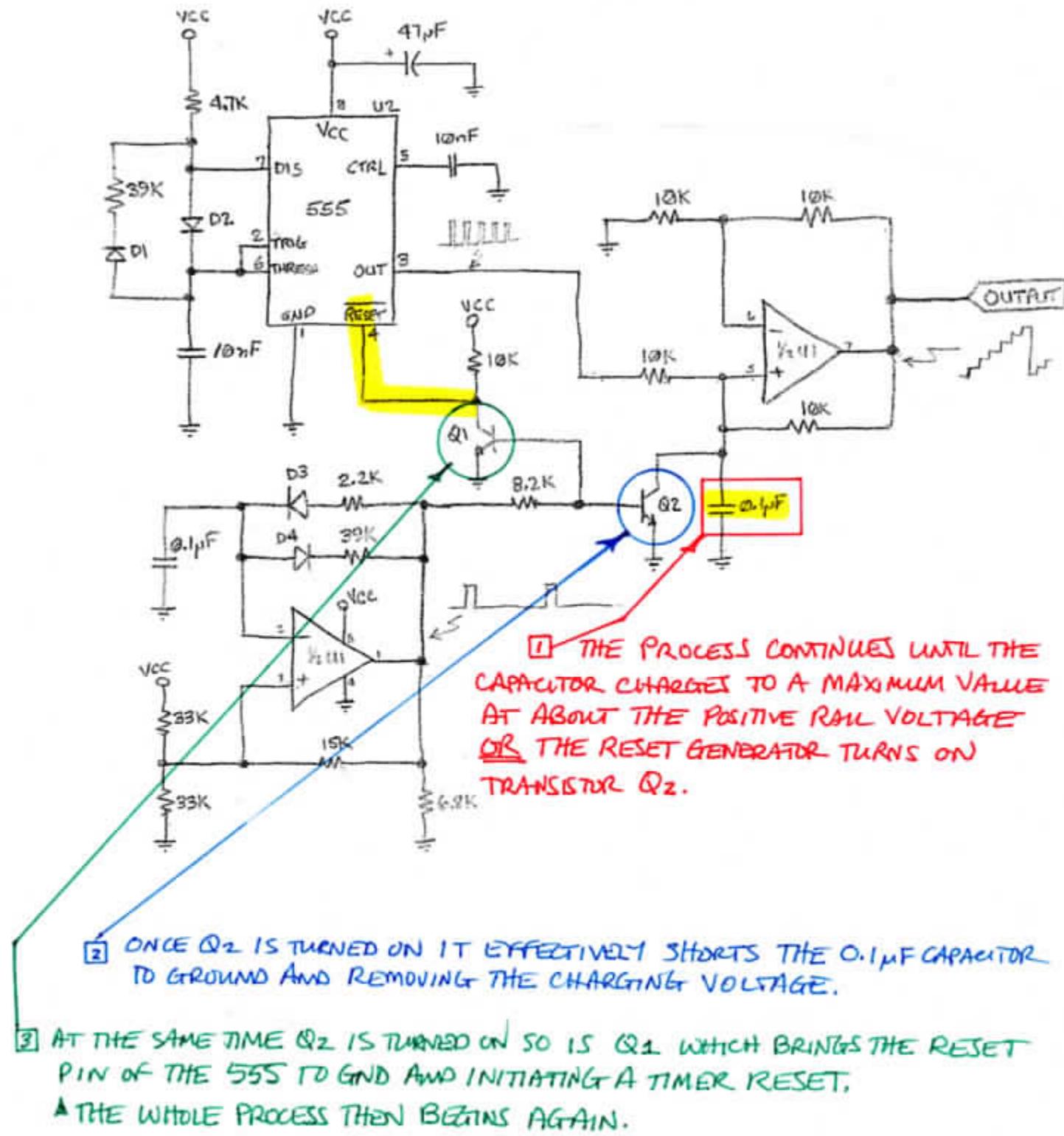

- SO THIS CIRCUIT PROVIDES STAIR STEPS FROM NARROW PULSES, RESET BY ANOTHER PULSE → CREATES AN ANALOG STAIRSTEP GENERATOR WITH NO MEMORY OR DIGITAL A/D CONVERTER.