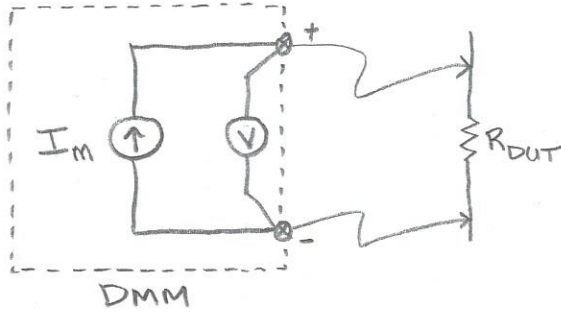


# 4-WIRE RESISTANCE MEASUREMENT (KELVIN CONNECTION)

W2AEW


## BACKGROUND

- How DMMs MAKE RESISTANCE MEASUREMENTS:



- INJECT KNOWN CURRENT ( $I_m$ ) THROUGH DEVICE UNDER TEST ( $R_{DUT}$ )
- MEASURE VOLTAGE
- CALCULATE  $R = \frac{V}{I_m}$

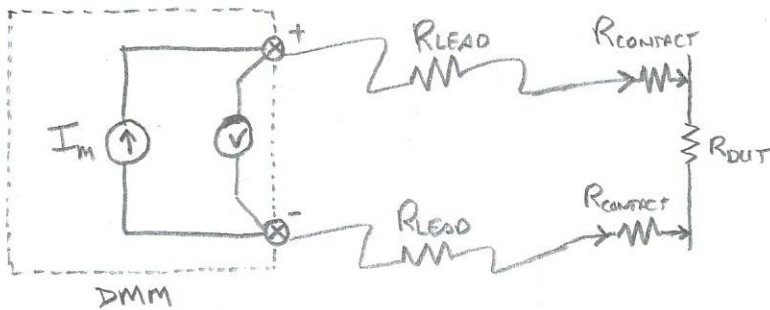- ERRORS / IN-ACCURACIES WHEN MEASURING LOW VALUES...  
( $< \text{FEW } \Omega$ )



- MEASURED RESISTANCE IS SUM  $R_{DUT} + 2 \times R_{LEAD} + 2 \times R_{CONTACT}$
- $R_{LEAD}$  CAN BE  $\approx 1 \Omega$  OR SO
- $R_{CONTACT}$  CAN BE FEW HUNDRED  $m\Omega$  AND CAN VARY WITH PRESSURE, CLEANLINESS, ETC.


- USING DELTA / ZERO / NULL...

- CAN SUBTRACT  $R_{LEAD} + R_{CONTACT}$  FROM MEASUREMENT...
- ... BUT  $R_{CONTACT}$  CAN VARY
- ACCURACY IS WORSE! HERE'S WHY...

GIVEN:  $R_{LEAD} = 0.7 \Omega$   
 $R_{CONTACT} = 0.2 \Omega$   
 $R_{DUT} = 0.3 \Omega$   
 DMM Accuracy  $\pm 0.1\%$

$R_{MEAS} = 2.1 \Omega \pm 0.0021 \Omega$   
 $R_{DUT} = 0.3 \Omega \pm 0.0021 \Omega$   
 $\pm 0.7\%$   
 7x WORSE!
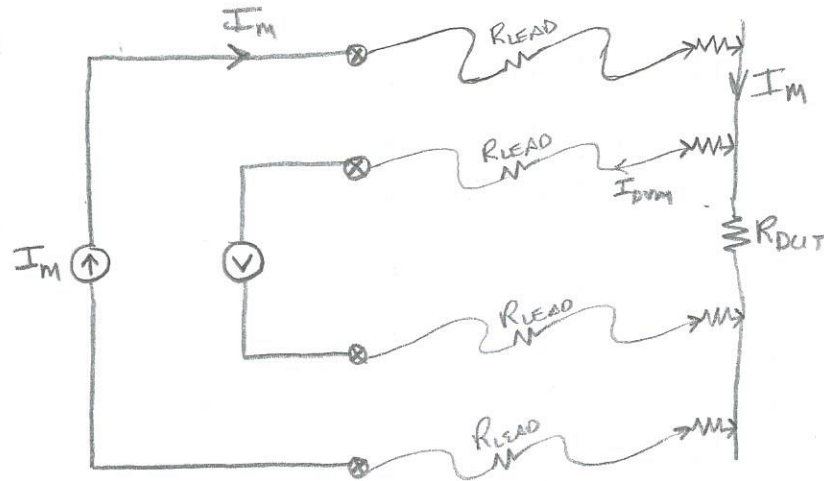
## 4-WIRE / KELVIN CONNECTION ELIMINATES LEAD &amp; CONTACT R



- FOR LOW RESISTANCE,  $I_m$  IS TYPICALLY  $1mA$ ,  $5mA$ ,  $10mA$ , ETC.
- $I_m \gg I_{DVM}$ , THUS LEAD & CONTACT VOLTAGE DROPS ARE VERY SMALL

EXAMPLE:  $I_m = 1mA$ ,  $R_{out} = 0.3\Omega$

$$V_{R_{out}} = 0.3mV$$

$$I_{DVM} \cong \frac{0.3mV}{10M\Omega} = 30pA$$

$\therefore$  VOLTAGE DROP ON DVM LEADS IS VERY SMALL ...  $< 1nV$