


BACK TO BASICS

555 BASED "ONE-SHOT"

MONOSTABLE MULTIVIBRATOR

- OUTPUTS A SINGLE PULSE IN RESPONSE TO A TRIGGER


R/C DETERMINE PULSE WIDTH OUTPUT

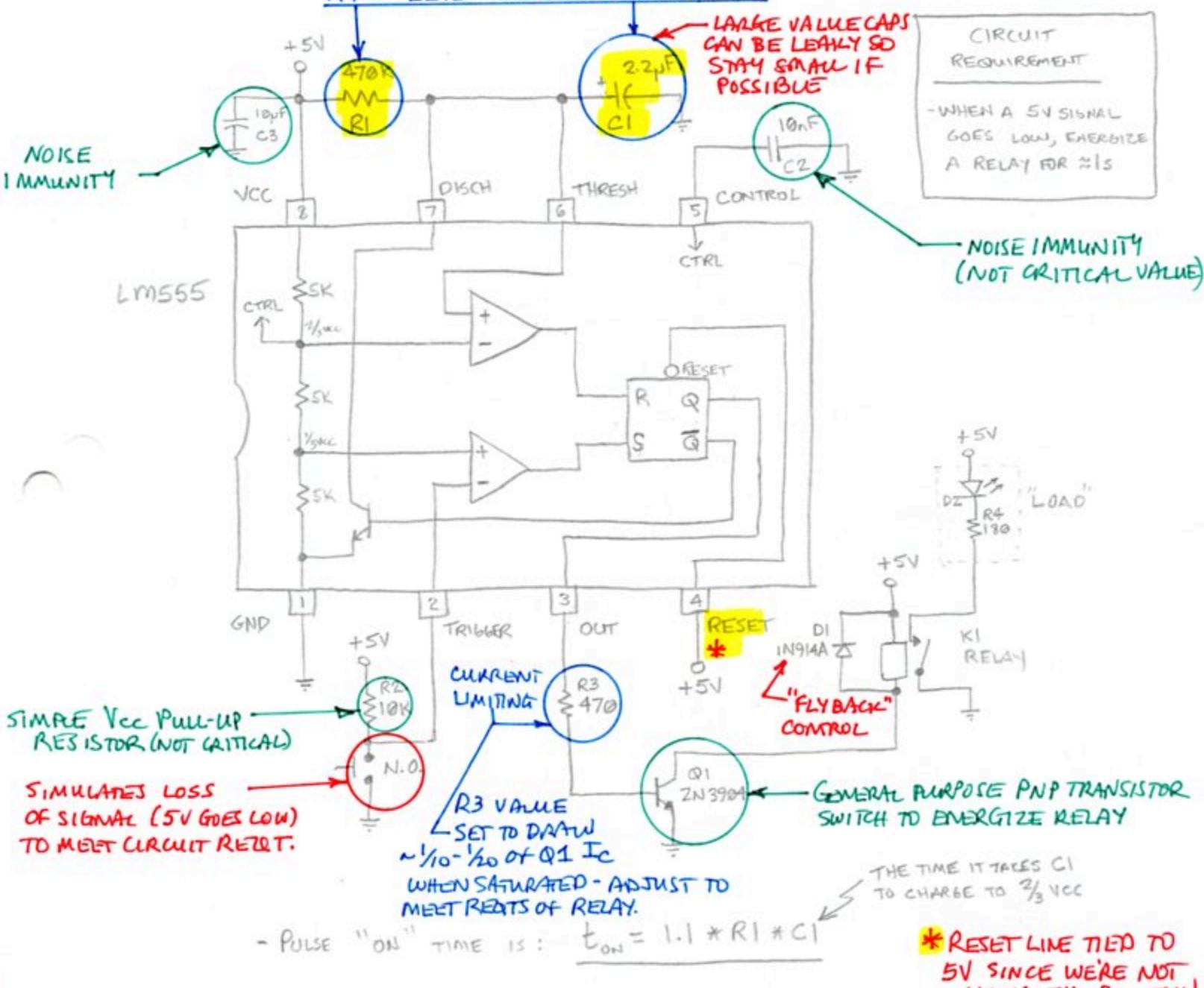

REMEMBER, A SIMPLE RC CIRCUIT CHARGES TO 63% IN ONE RC TIME CONSTANT. HERE, WE WANT 66.7%, SO IT MAKES SENSE THAT THE TIME IS JUST OVER 1 RC

BACK TO BASICS

W2AEW

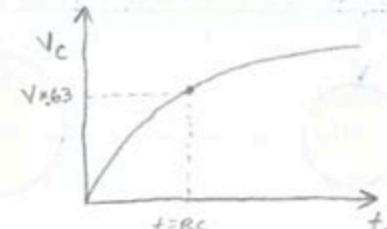555 ONE-SHOT MATH- WHY IS THE TIME = $1.1 \times RC$ FOR RC CIRCUIT
(CHARGING)

$$V_c(t) = V * (1 - e^{-t/RC})$$

RE-ARRANGE TO SOLVE FOR t

DIVIDE BY V :

$$\frac{V_c(t)}{V} = 1 - e^{-t/RC}$$

SUBTRACT/SWAP:

$$e^{-t/RC} = 1 - \frac{V_c}{V}$$

NATURAL LOG:

$$\frac{-t}{RC} = \ln\left(1 - \frac{V_c}{V}\right)$$

MULTIPLY BY $-RC$:


$$t = -RC \times \ln\left(1 - \frac{V_c}{V}\right)$$

IN OUR CASE, $\frac{V_c}{V} = 2/3$

THUS $t = -RC \times \ln\left(1 - \frac{2}{3}\right)$

$$t = -RC \times \ln\left(\frac{1}{3}\right)$$

$t = 1.1 \times RC$

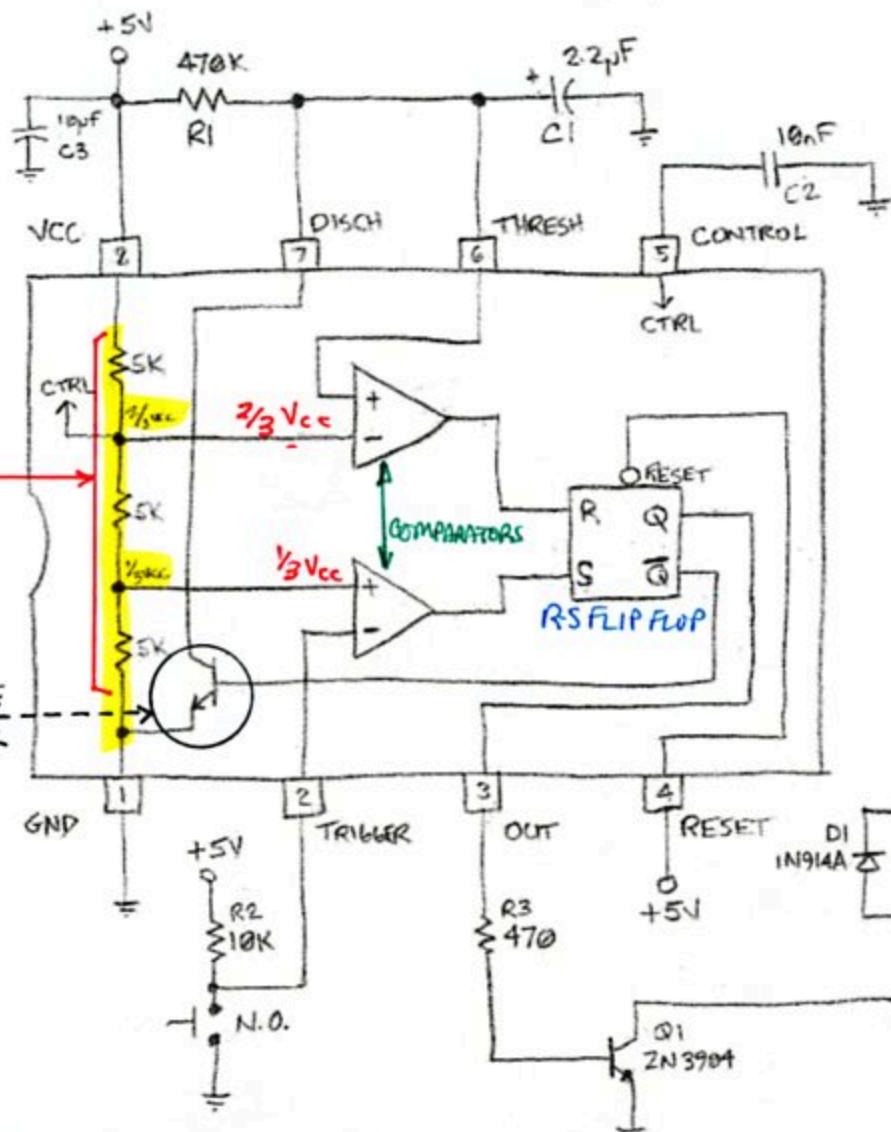

CIRCUIT REQUIREMENT

- WHEN A 5V SIGNAL GOES LOW, ENERGIZE A RELAY FOR $\approx 1s$

- * RESISTOR STRING SETS UP A VOLTAGE DIVIDER PRESENTING $\frac{2}{3} V_{cc}$ AND $\frac{1}{3} V_{cc}$ AT THE INPUTS OF THE TWO COMPARATORS
- * AT POWER UP THE RS FLIP FLOP IS IN A RESET CONDITION
 - * "Q" OUTPUT IS LOW $\therefore Q_1$ IS OFF AND LOAD (RELAY) IS NOT ENERGIZED
 - * " \bar{Q} " OUTPUT IS HIGH \therefore THE TRANSISTOR AT THE BOTTOM OF THE RESISTOR STRING IS TURNED ON AND IS PULLING CURRENT DOWN THRU R1 VIA THE "DISCH" PIN #7 PIN WHICH SATURATES THE TRANSISTOR AND PREVENTING C1 FROM CHARGING UP. THIS MEANS THE VOLTAGE AT PIN #6 "THRESH" REMAINS LOW (NEAR GND) \rightarrow THIS MEANS THE OUTPUT OF THE TOP COMPARATOR IS LOW AND WE'RE NOT GOING TO RESET THE FLIP FLOP ("R").
- * WITH 5V APPLIED TO THE TRIGGER (PIN #2) INPUT THE OUTPUT OF THE LOWER COMPARATOR IS ALSO LOW \therefore THE FLIP FLOP WILL NOT CHANGE STATE.
- * IF THE TRIGGER VOLTAGE (PIN #2) IS BROUGHT BELOW $\frac{1}{3} V_{cc}$ THE OUTPUT OF THE LOWER COMPARATOR GOES HIGH \rightarrow DO THIS BY PRESSING THE SWITCH (N.O.) TO BRING PIN #2 TO GND (AND $< \frac{1}{3} V_{cc}$).
- * THE FLIP FLOP OUTPUT THEN GOES HIGH, IN TURN CAUSING Q_1 TO TURN ON AND THE RELAY AS WELL.
- * AT THE SAME TIME " \bar{Q} " GOES LOW TURNING OFF THE DISCHARGE TRANSISTOR AT THE BOTTOM OF RESISTOR STRING BRINGING THE "DISCH" PIN (PIN #7) TO ESSENTIALLY OPEN CIRCUIT NOW ALLOWING C1 TO CHARGE UP THRU R1; IT CHARGES EXPONENTIALLY.

- ▲ C1 CHARGES EXPONENTIALLY UNTIL IT REACHES $\frac{2}{3} V_{cc}$ AT WHICH POINT THE TOP COMPARATOR GOES HIGH AND RESETS THE FLIP FLOP.
- ▲ AS SOON AS THE FLIP FLOP RESETS "Q" OUTPUT GOES LOW THUS TURNING Q1 OFF AGAIN WHICH TURNS OFF THE RELAY AGAIN.
- ▲ " \bar{Q} " GOES HIGH AT THE SAME TIME THUS TURNING ON THE DISCHARGE TRANSISTOR AND QUICKLY TAKES THE CHARGE OFF C1 BRINGING THAT POINT BACK TO THE SATURATION VOLTAGE OF THE TRANSISTOR.
- ▲ WE'RE NOW READY FOR THE NEXT TRIGGER EVENT.
- ▲ NOTE THAT t_{on} IS A LITTLE BIGGER THAN THE PRODUCT OF $R1 \times C1$ SINCE THE R-C CIRCUIT ONLY CHARGES TO 63% IN ONE TIME CONSTANT SO WE'RE MAKING SURE IT'S ON LONG ENOUGH TO BRING THE $\frac{2}{3} V_{cc}$ POINT ON THE TOP COMPARATOR'S INPUT TO ITS FULL VALUE; SO WE USE A MULTIPLICATION FACTOR OF $\times 1.1$ TO ENSURE IT DOES.

*NOTE: ONCE THE CIRCUIT IS TRIGGERED IT WON'T BE AVAILABLE TO RE-TRIGGER UNTIL IT RESETS. DEMONSTRATE THIS BY TRIGGERING QUICKLY THE TRIGGER PIN → (COULD BE SWITCH BOUNCE)

