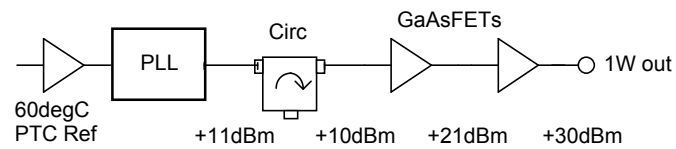


10GHz Beacon Transmitter

WA3JUF 1999



Beacon CW Keying

The FET amps are cut-off at key up, biased on at key down. Both were 1W devices and reasonable bias points were found with one pot. Otherwise, the circuit could be duplicated for each stage.

