

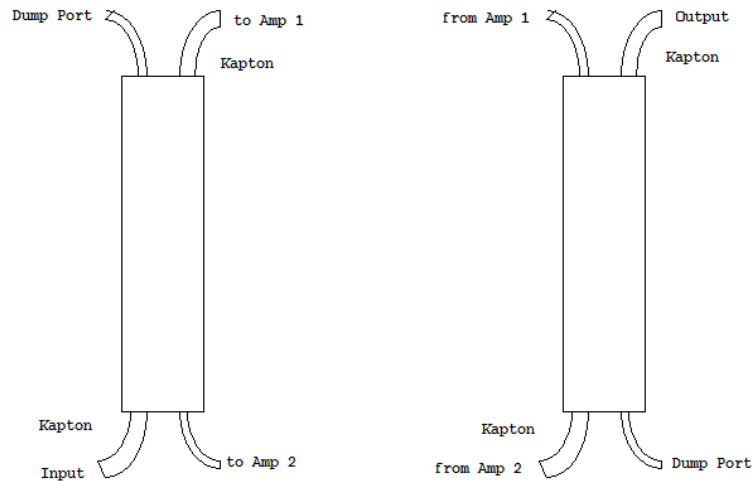


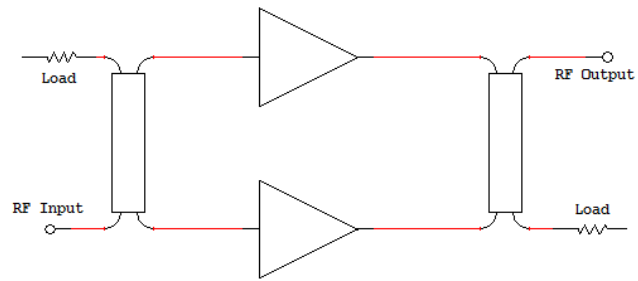Combining 2 RF amplifiers with Sage wireline
1981



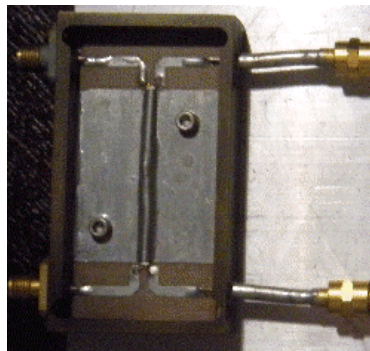The wires of the Sage coupler are crossed as show above when connected to combine 2 amplifiers of the same design.



1296 MHz Sage coupler