



**Figure 4.25** Circuit diagram of an appliqué box for an HP 8558B spectrum analyser, providing a 0–1500 MHz tracking generator output. (Reproduced with permission from Electronic Product Design, July 1994, p. 17) (Note: for 10μ read 10n)