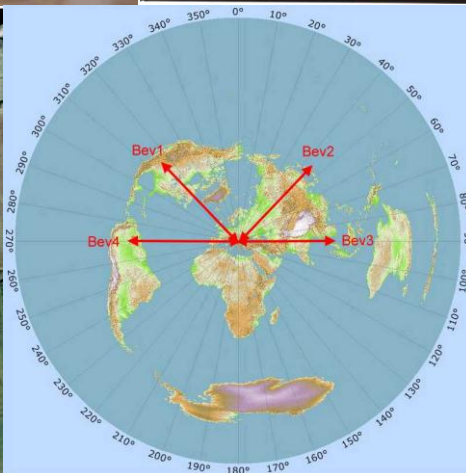


# YU5R Beverage Box

by Goran Stankovic dipl.ing.el. – YT2FSG – Date: 12.03.2014.

email: [goranstank@gmail.com](mailto:goranstank@gmail.com)

In Resava Valley Contest Club YU5R in Multi-two contest we used two SACX, six-pack and High Power Band Pass Filters products from 4O3A <http://www.4o3a.com/>. For the 1.8MHz High Power Band Pass Filter we used the product from <http://www.dual.rs/>.



For Rx antenna we made 3 two-directional beverage antennas from a pair of twisted wires from a military telephone cable (176m long and 2m high) and a Beverage Box.

Beverage Box includes relay switch for 6 Rx antennas and 3 radios, output for each radio have Low Band Pass Filters 1.8MHz, 3.5MHz, 7MHz and a preamplifier. For rig as Yaesu FT857 and FT950 we made an additional relay for switching the antenna.

The transmission line impedance of the twisted wires should be about 150 ohms and the Beverage antenna impedance should be about 450 ohms. We used the transformers of binoculars ferite Amidon BN73-202 and a galvanized water pipe as a ground connection at each termination. We used 4 of the 6 directions, two directions closed with 50 ohm terminator. Terminator is made of the connector PL239 and two parallel resistors of 100 ohm.





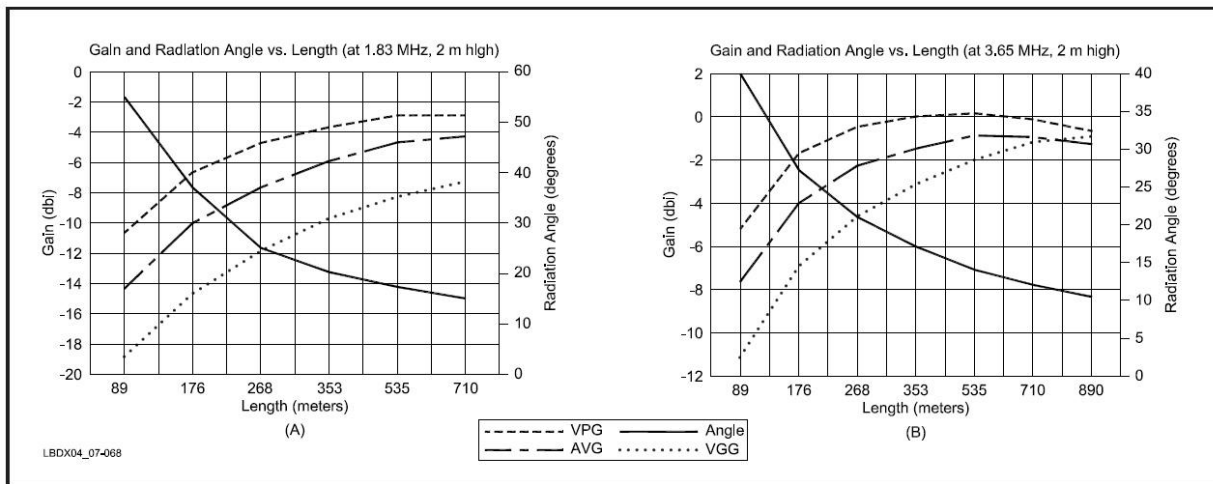


Fig 7-68—Gain and elevation angle for a 2-meter high Beverage antenna for 160 and 80 meters, as a function of the antenna length. Three curves are shown: over Very Poor Ground (VPG), over Average Ground (AVG), and over Very Good Ground (VGG). The radiation angle is computed for Average Ground. This angle only changes marginally between Very Poor and Very Good ground.

#### REFERENCE:


Book: Low-Band DXing - ON4UN

[http://www.w0btu.com/Beverage\\_antennas.html](http://www.w0btu.com/Beverage_antennas.html)

[http://www.iv3prk.it/user/image/site2-rxant.prk\\_two-wire-beverage.pdf](http://www.iv3prk.it/user/image/site2-rxant.prk_two-wire-beverage.pdf)

[http://www.g3xrxj.com/RxArray\\_files/2wire\\_bev/2wire\\_bev.htm](http://www.g3xrxj.com/RxArray_files/2wire_bev/2wire_bev.htm)


<http://www.bavarian-contest-club.de/projects/BCC-Projekte;art31,1082>

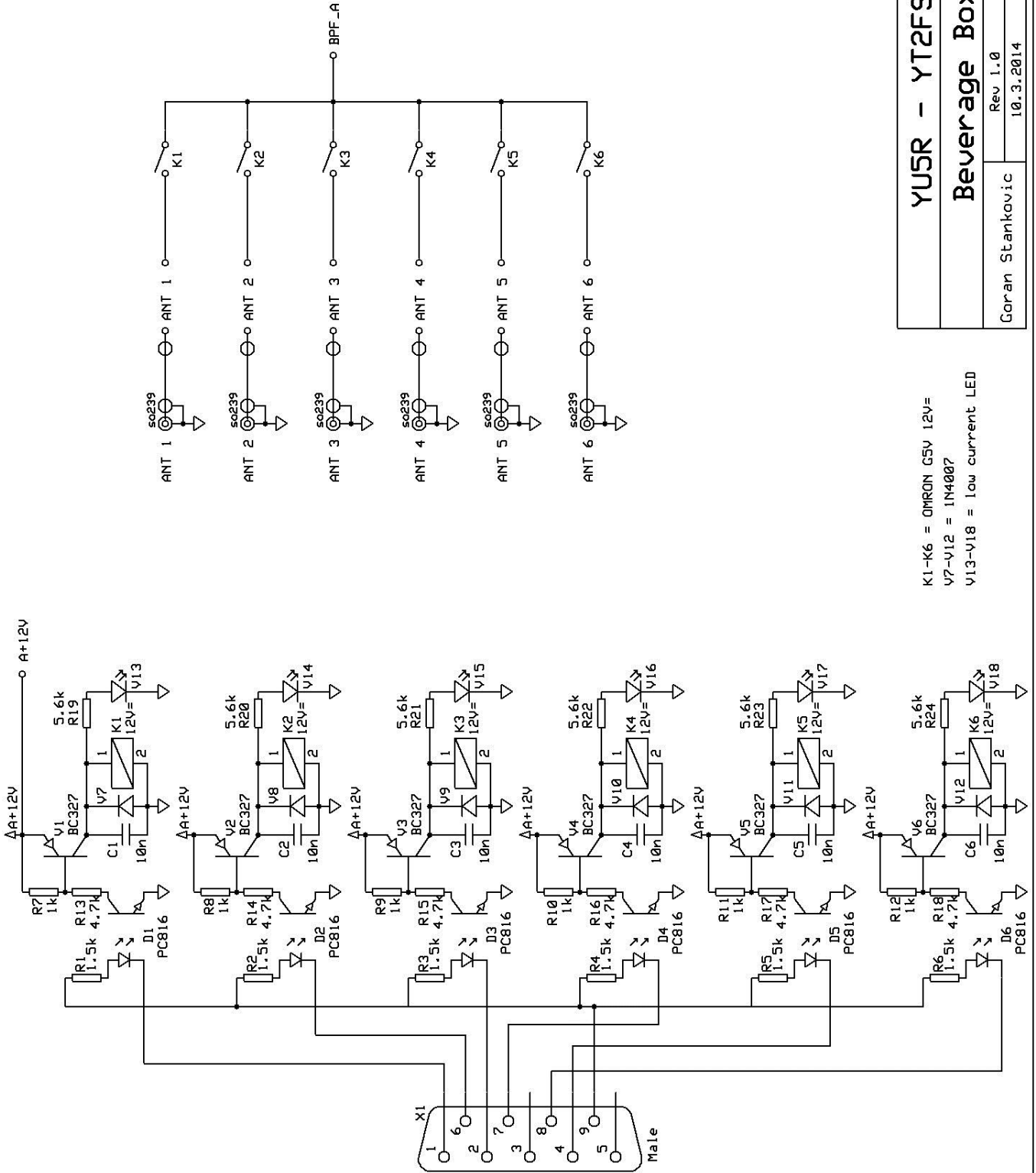

**YU5R - YT2FSG  
Beverage Box**


Coran Stankovic Rev 1.0 Page 1/8  
10.3.2014

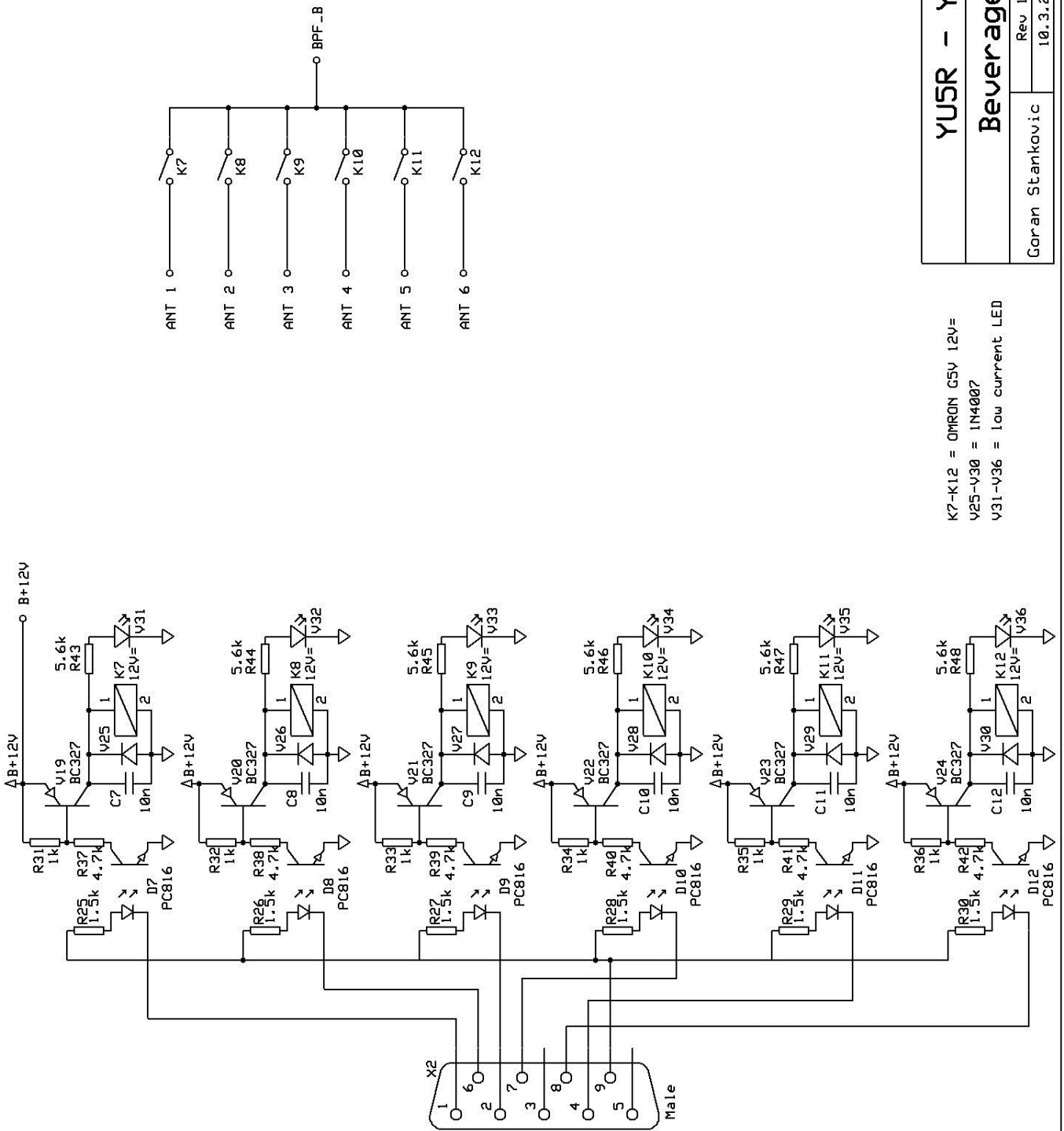K1-K6 = OMRON G5V 12V=  
V7-V12 = 1N4007  
V13-V18 = Low current LED




K7-K12 = OMRON G5V 12V=  
 V25-V30 = 1N4007  
 V31-V36 = 1w current LED

**YU5R - YT2FSG  
 Beverage Box**

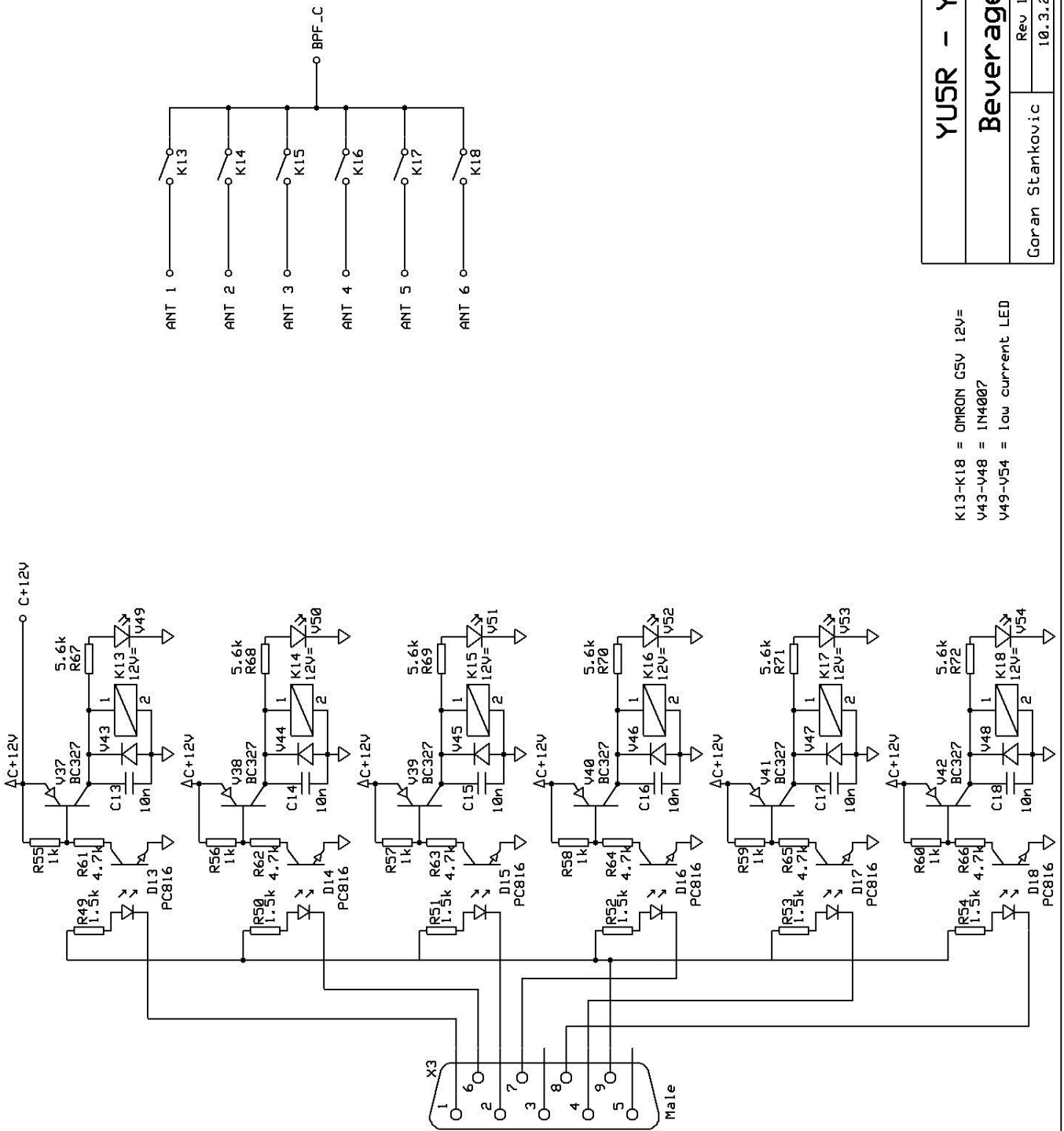


K13-K18 = OMRON G5V 12V=  
 V43-V48 = 1N4007  
 V49-V54 = Low current LED

<b>YU5R - YT2FSG</b>	
<b>Beverage Box</b>	
Coran Stankovic	Rev 1.0 10.3.2014
Page 3/8	

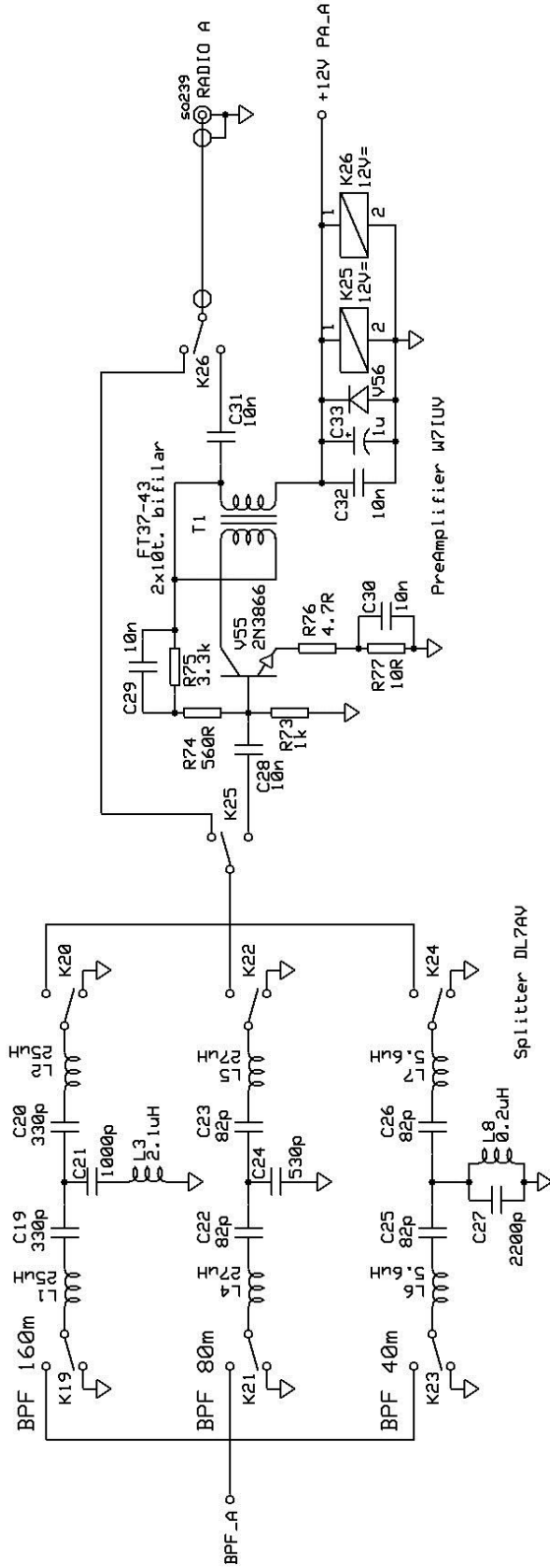


- L1, L2 = 25uH, AMIDON T68-2, 66t., CuL 0.4mm
- L3 = 2.1uH, AMIDON T68-6, 21t., CuL 1mm
- L4, L5 = 27uH, AMIDON T68-2, 69t., CuL 0.4mm
- L6, L7 = 5.6uH, AMIDON T68-6, 35t., CuL 0.7mm
- L8 = 0.2uH, Air D=7mm, L=7mm, 6.5t., CuL 1mm

- K19-K26 = OMRON GSV 12V=
- V56-V59 = 1N4007
- V60-V62 = low current LED

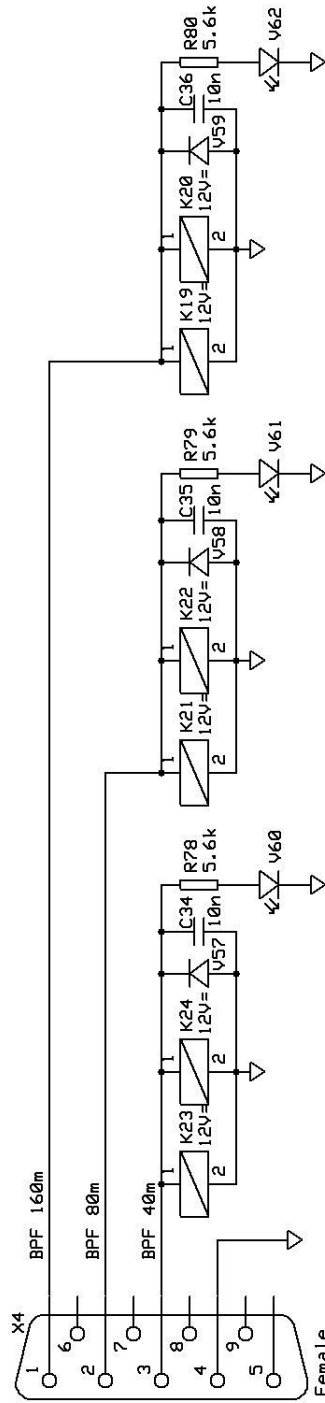


YU5R - YT2FSG	
Beverage Box	
Coran Stankovic	Rev 1.0
	10.3.2014
	Page 4/8



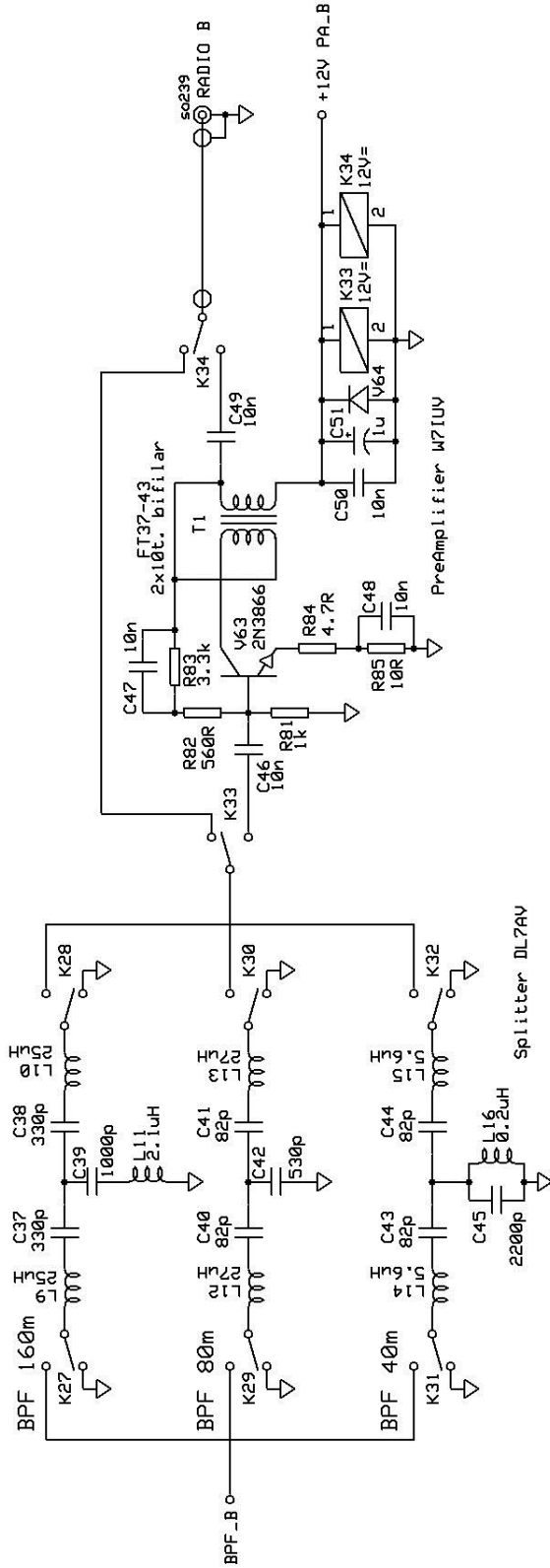


- L9, L10 = 25uH, AMIDON T68-2, 66t., CuL 0.4mm
- L11 = 2.1uH, AMIDON T68-6, 21t., CuL 1mm
- L12, L13 = 27uH, AMIDON T68-2, 69t., CuL 0.4mm
- L14, L15 = 5.6uH, AMIDON T68-6, 35t., CuL 0.7mm
- L16 = 0.2uH, Air D=7mm, L=7mm, 6.5t., CuL 1mm

K19-K26 = OMRON GSV 12V=  
 V7-V12 = 1N4007  
 V13-V18 = low current LED

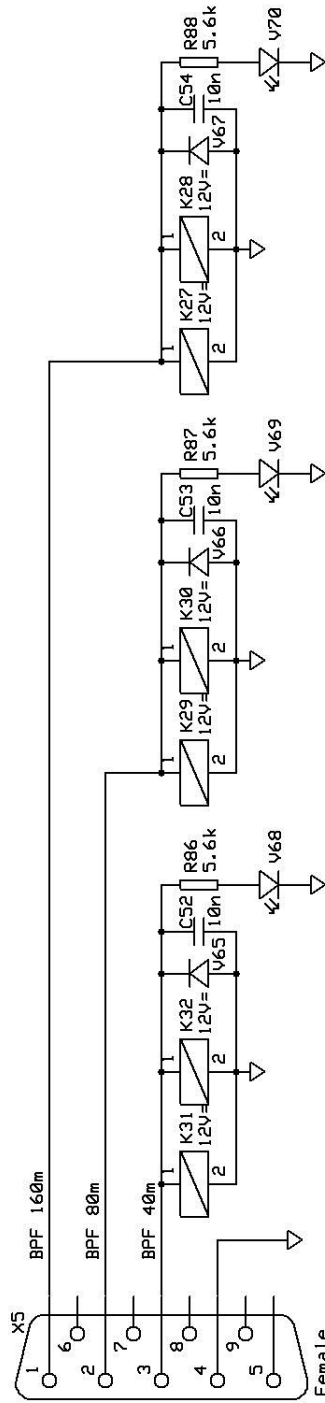


YU5R - YT2FSG	
Beverage Box	
Coran Stankovic	Rev 1.0
	10.3.2014
	Page 5/8



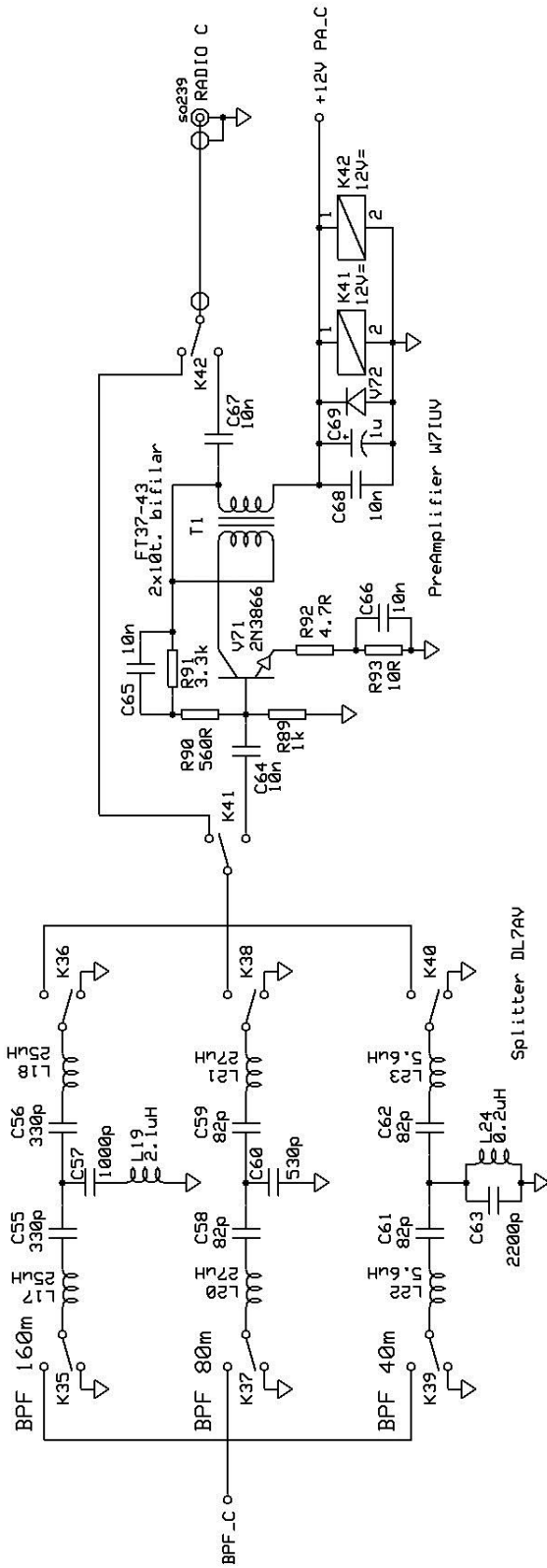


- L17, L18 = 25uH, AMIDON T68-2, 66t., CuL 0.4mm
- L19 = 2.1uH, AMIDON T68-6, 21t., CuL 1mm
- L20, L21 = 27uH, AMIDON T68-2, 69t., CuL 0.4mm
- L22, L23 = 5.6uH, AMIDON T68-6, 35t., CuL 0.7mm
- L24 = 0.2uH, Air D=7mm, L=7mm, 6.5t., CuL 1mm

- K35-K42 = OMRON GSV 12V=
- V72-V75 = 1N4007
- V76-V78 = low current LED

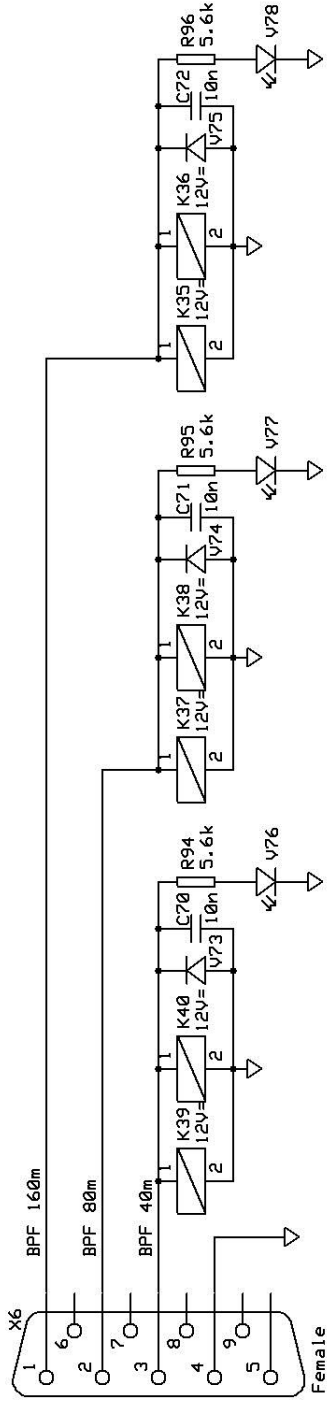


YU5R - YT2FSG	
Beverage Box	
Coran Stankovic	Rev 1.0
	10.3.2014
	Page 6/8

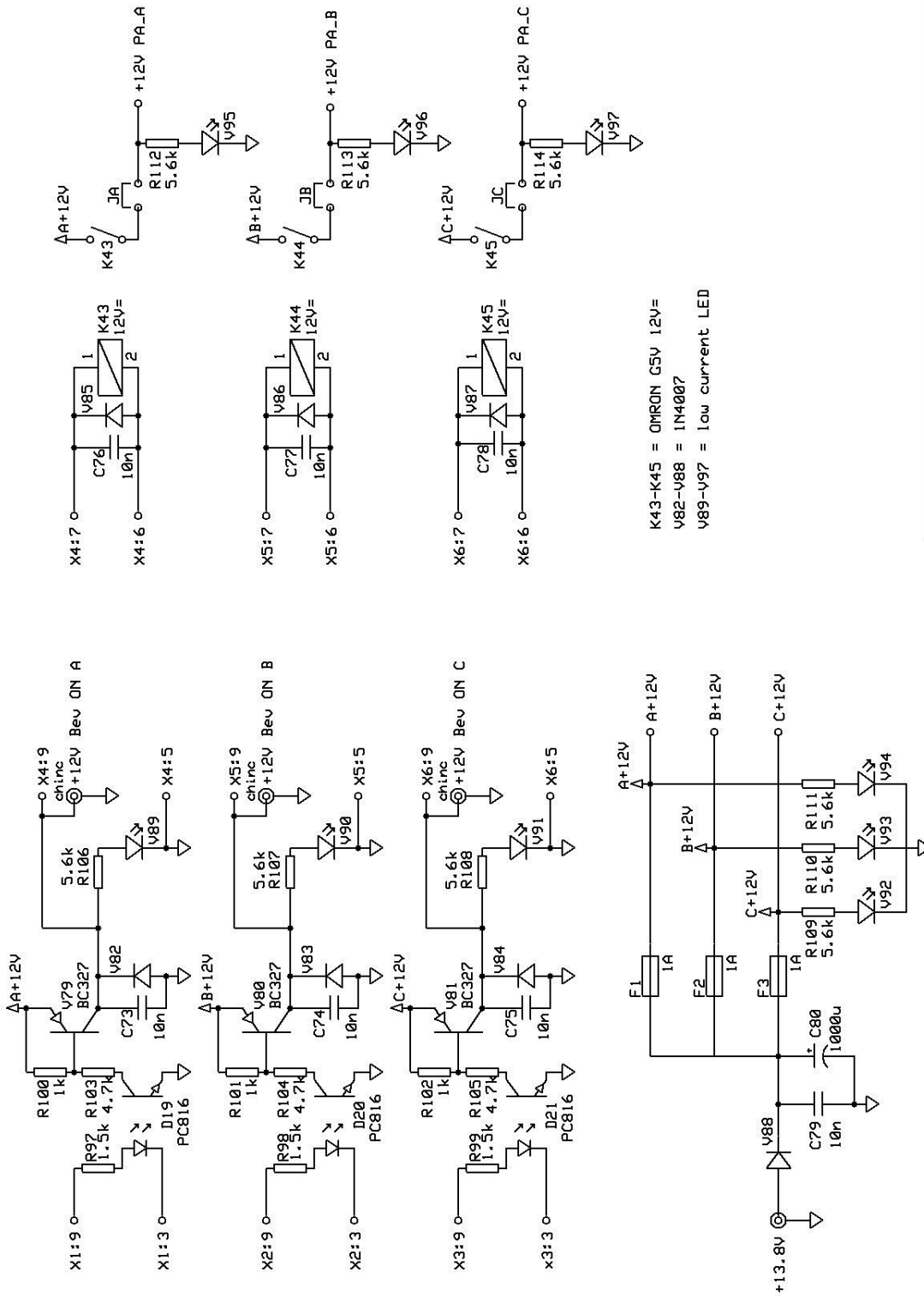

<b>YU5R - YT2FSG</b>	
<b>Beverage Box</b>	
Coran Stankovic	Rev 1.0 10.3.2014
Page 7/8	

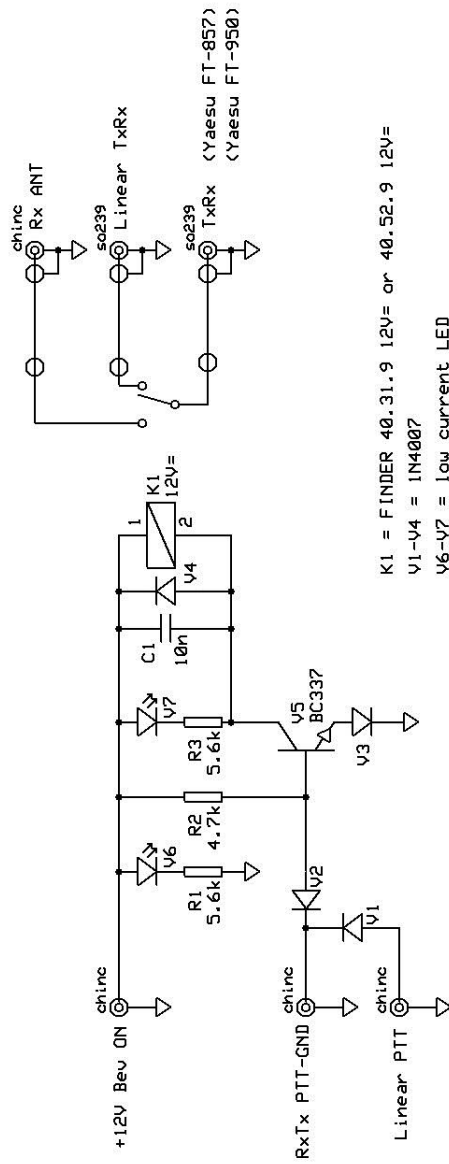
Add-on rigs that do not have input Rx antenna




K1 = FINDER 40.31.9 12V= or 40.52.9 12V=  
 V1-V4 = 1N4007  
 V6-V7 = low current LED

YU5R - YT2FSG	
Beverage Box	
Coran Stankovic	Rev 1.0 10.3.2014
	Page 8/8

Twisted pair two directional beverage

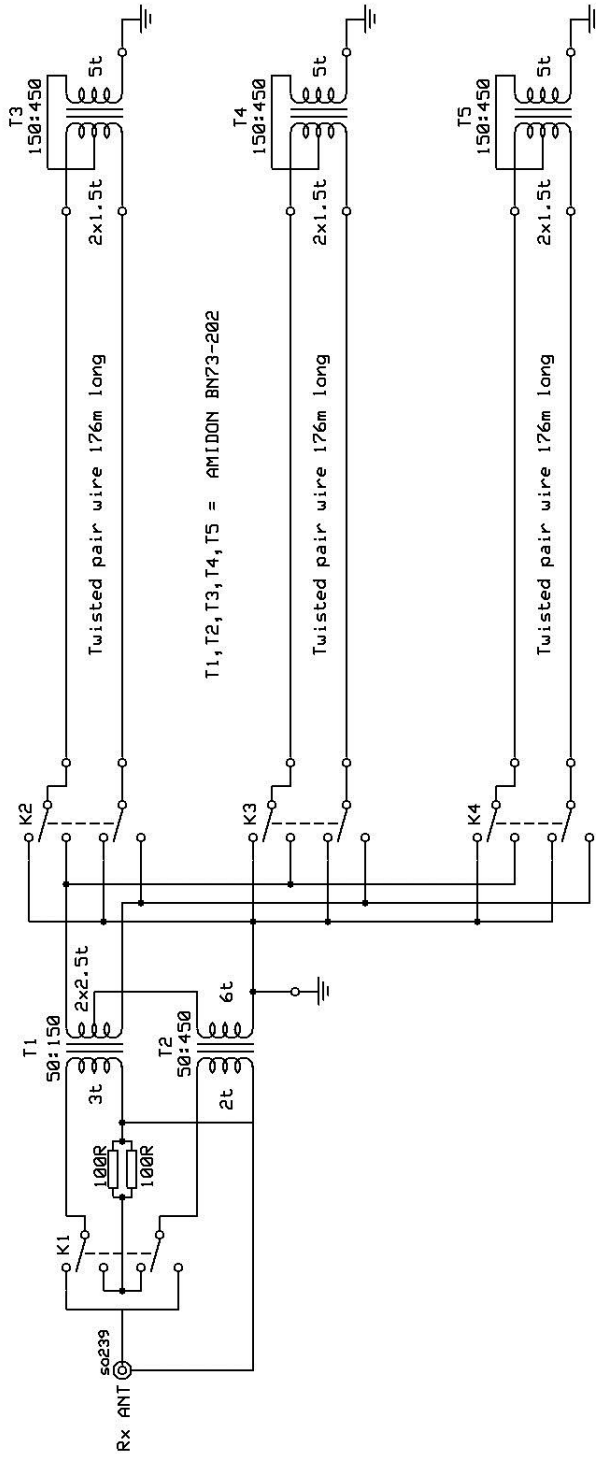

T1, T2, T3, T4, T5 = AMIDON BN73-202

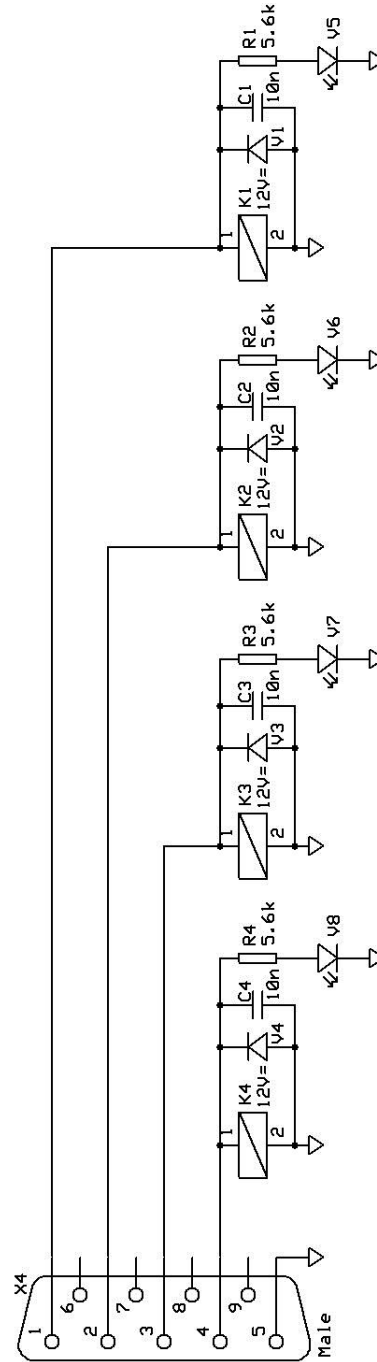

K1-K4 = FINDER 30.22.9 12V=  
 V1-V4 = 1N4007  
 V5-V8 = low current LED

<b>YU5R - YT2FSG</b>	
<b>Single Rig Beverage Box</b>	
Coran Stankovic	Rev 1.0
10.3.2014	
Page 10	