

My Circuit Collections

I started to write a book on the 29th of Oct 1968, with very useful electrical & electronics circuits. It is updating in my life time. Some are copied from various books and web pages some are designed by me and tested. I started to write in the computer on 1st March 2011.

J.T.Wijeratne (4S7VJ)

Contents


	page
1. Earth Leakage circuit breaker (ELCB)	3
2. Residual current circuit breaker (RCCB).....	4
3. Two way and three way system.....	5
4. Multi-way switching system.....	6
5. Code practice oscillator-1.....	7
6. Code practice oscillator-2 (improved version)	7
7. Code practice oscillator-3 and 4	7
8. Automatic Morse keyer with PCB layout.....	8
9. Electronic hand key for CW TX	9
10. LDR circuits (1. dark activated, 2. Light activated).....	9
11. Light switch	9
12. Light activated switch.....	10
13. QRP transmitter 80m (2 – 20 W).....	10
14. Linear Amplifier for 2m 7W	11
15. Linear Amplifier for 2m 20W	11
16. FM mic (Low power FM transmitter)	12
17. Simple QRP transmitter	12
18. VFO (1.75 – 7.5 MHz).....	13
19. VFO (40/80m high output).....	14
20. VHF Amplifier (11dB)	14
21. VHF Amplifier (12.5 dB)	15
22. VHF preamplifier (2m RX front end).....	15
23. Antenna coupler (ATU)	15
24. VHF RX (Regenerative)	16
25. Air band receiver (suitable for any VHF frequency).....	16
26. Voltage Indicator	16
27. Musical Door bell (6 melodies)	17
28. Musical Door bell with PCB layout	18
29. Dip meter-1	19
30. Dip meter-2	19
31. Dip meter-3 (1.5MHz – 250 MHz)	20
32. Field Strength meter (VHF 20 – 200 MHz)	20
33. Field Strength meter (HF 7 – 29 MHz)	21

34. FET voltmeter	21
35. FET voltmeter	21
36. RF power meter (15W and 100W)	22
37. SWR and RF power meter.....	22
38. Signal Generator AF, RF, IF	23
39. Signal Generator (AF).....	23
40. Voltage multiplier circuits	24
41. High power Regulator	24
42. Variable Voltage regulator	24
43. 1750Hz Tone burst for repeater activation	25
44. Stable tone burst for 1750Hz	25
45. Tone operated switch (Tone detector)	26
46. Tone Decoder (NE567)	26
47. Microphone preamplifier (2 circuits)	27
48. AF Amplifier (1W and 5W 2 circuits)	27
49. AF Amplifier (2W)	28
50. Tone oscillator for car signal light buzzer	28
51. Dicky Light circuit for Micro Panda car.....	28
52. Touch plate relay, Sensitive Relay.....	29
53. Timer for DF contest transmitter (HF)	29
54. Controller for DF contest transmitter (VHF)	30
55. Burglar Alarm	30
56. Invertor change-over circuit for power failure.....	31

House wiring


ELCB – Earth leakage circuit breaker:-

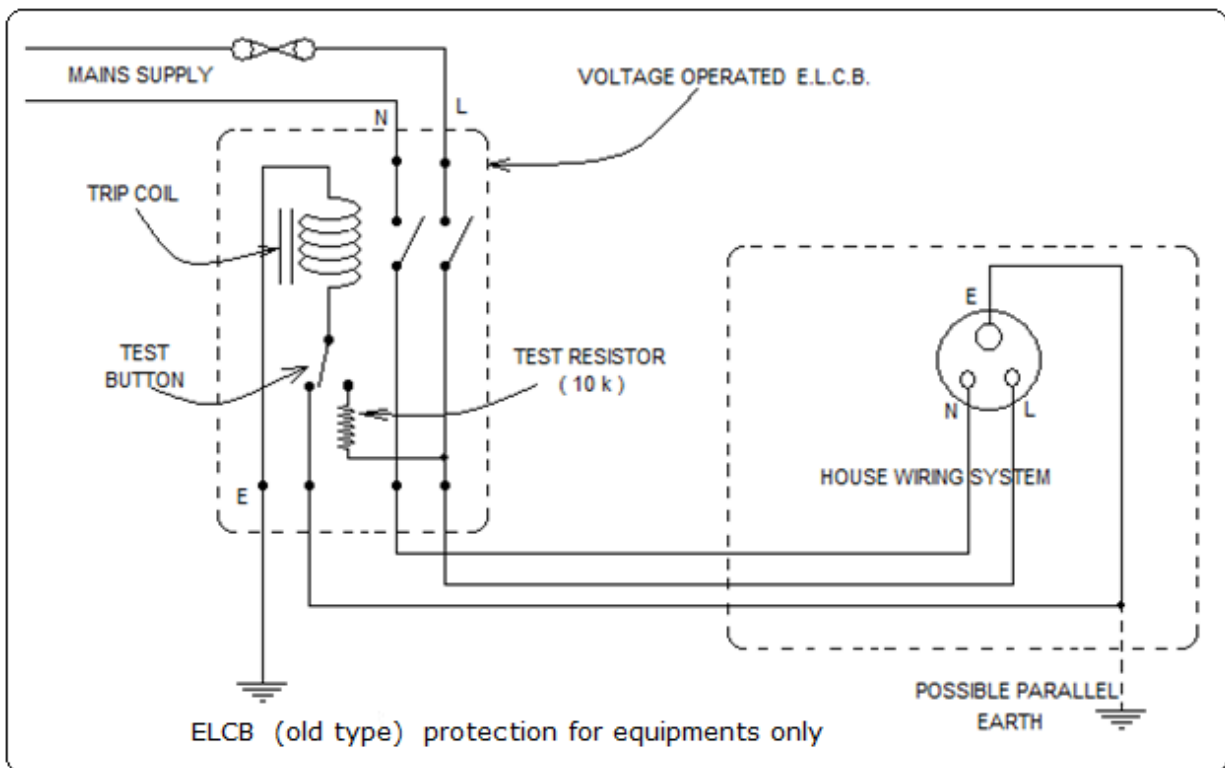
This was hardly used in Sri Lanka, before comes RCCB. This will be trip-off, while a current leakage in an equipment connected to the house wiring circuit, but it will never trip-off for a current leakage through human body to the earth.



Residual Current Circuit Breaker (R.C.C.B.) (Current operated Trip switch)

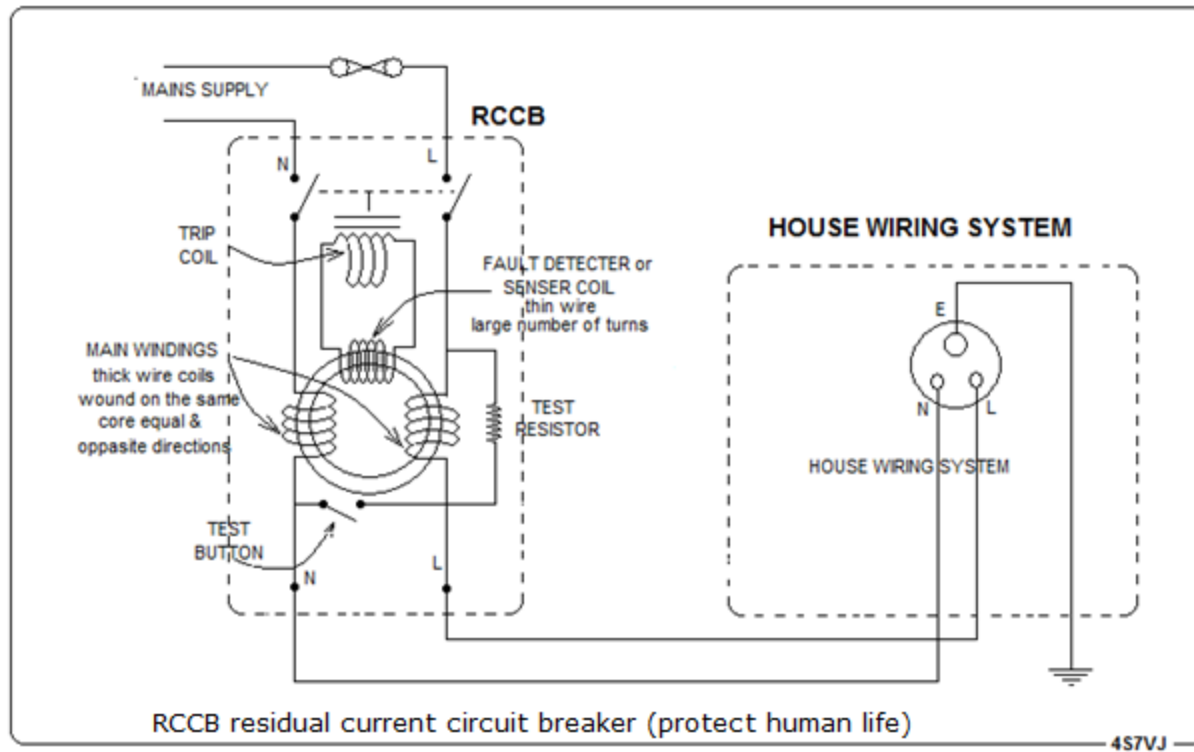I copied this from "REGULATIONS FOR THE ELECTRICAL EQUIPMENTS OF BUILDINGS" book borrowed from British Council Library (621.3282/37132) in 1973 and this is not to be seen in Sri Lanka at that time. Around 1985 this RCCB trip switch came to the market. The main purpose of this is the safety of the human life.




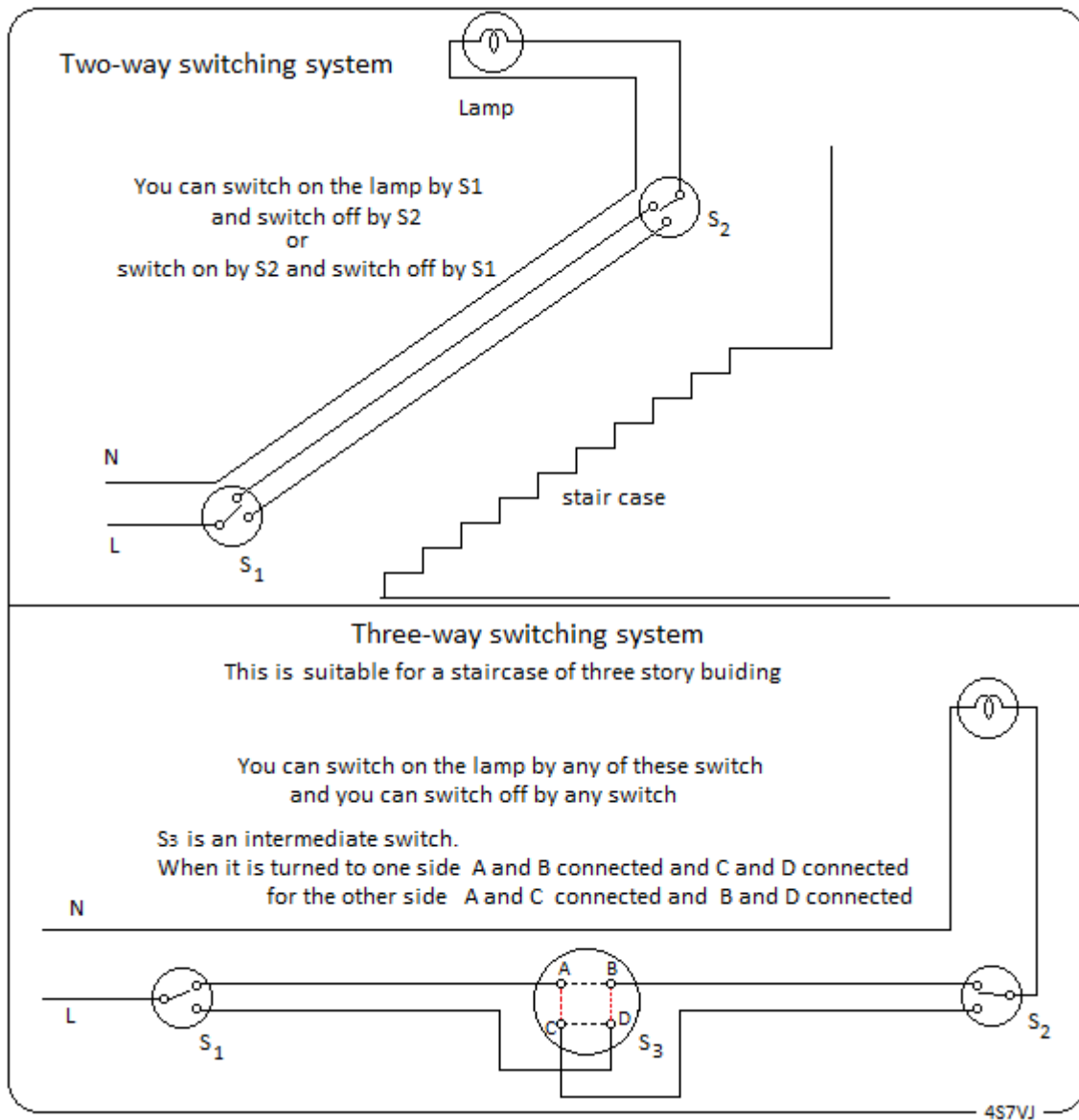

Multi-way switching system

suitable for a currydoor lights or staircase lights of a multi-storey building
 You can switch-on or switch-off the light with any of these switches
 You can extend with any number of intermediate switches

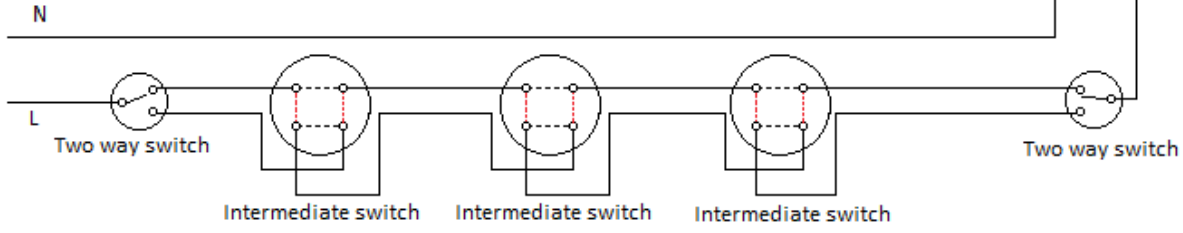
බහු මහල් ගොඩනැගිල්ලක පඩි පෙලකටද,
 දිග කොරිඩෝවකටද සුදුසු ලාම්පු පද්ධතියක්
 දැල්වීම හෝ නිවා දැමීම ඔනෑම සුවිචයකින් කළහැකිය




Multi-way switching system for security lights

You can install any number of security lights
 around the house and each switch in each
 room. Then you can switch on all lights with
 any switch and switch off by any switch.


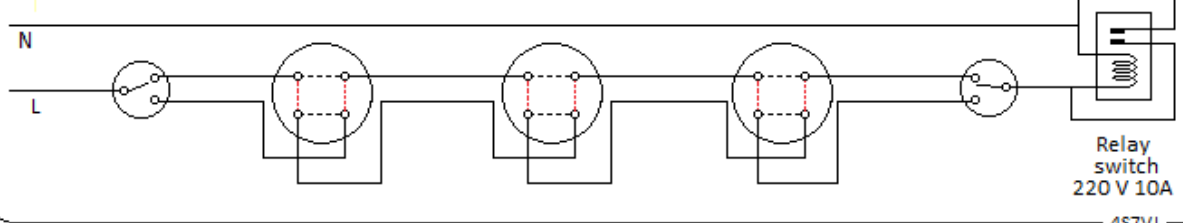
මෙහි ඇති ලාම්පු සියල්ලම, ඔනෑම සුවිචයකින්
 එකවර දැල්විය හැකිය. ඔනෑම සුවිචයකින් එකවර
 නිවාදැමිය හැකිය.




4S7VJ

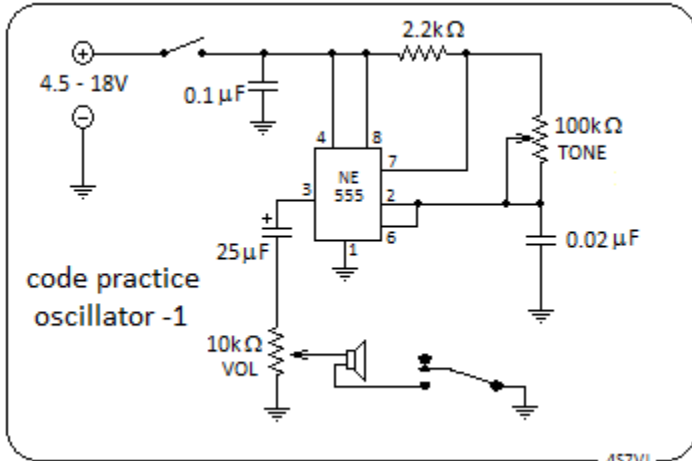

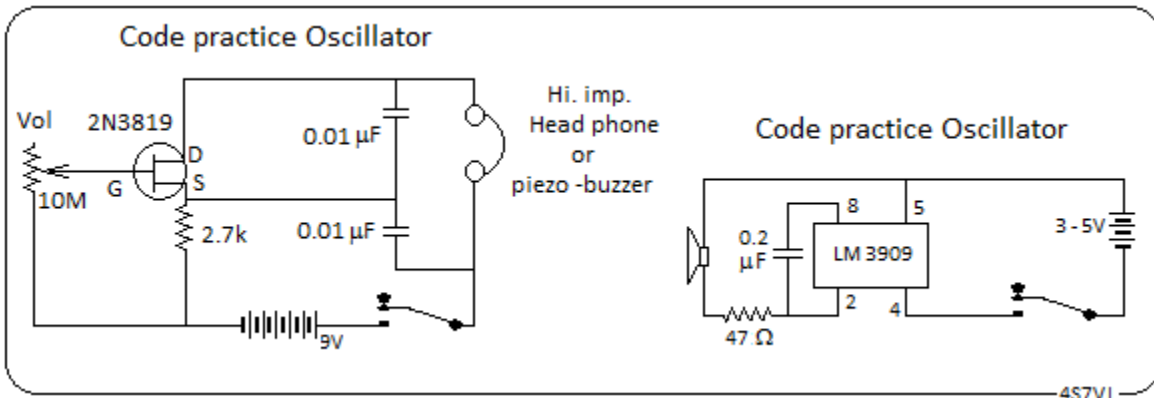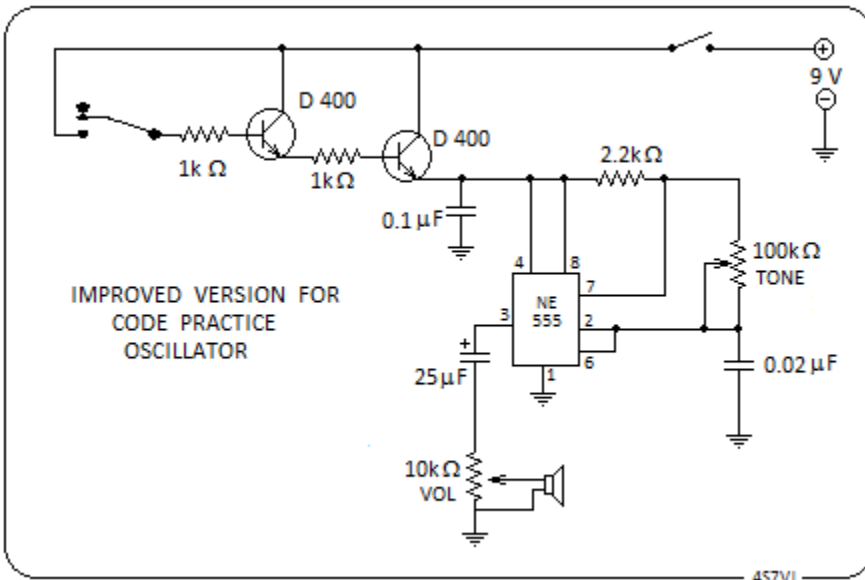These circuits are very useful for practice of Morse code sending




Automatic Morse key




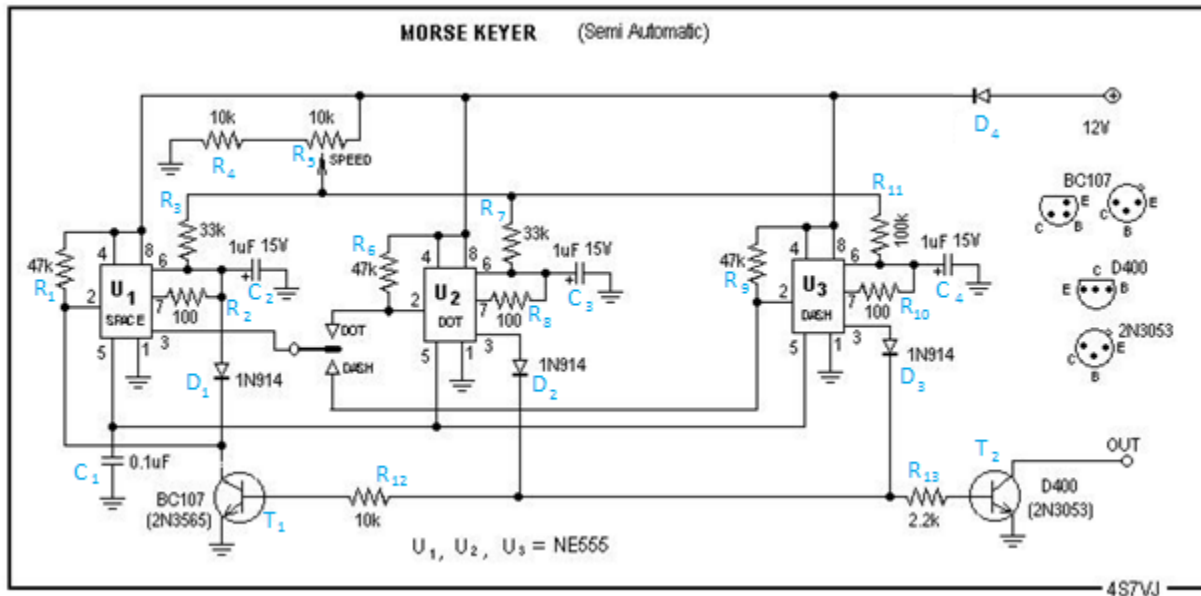




I received this Semi-Automatic Key circuit from 4S7GW, Wickey (expired on the 2nd July-2012) at about 1987. This is received through 145.625MHz – Yatiyantota repeater.


Since then I use this (made by me) with my HF TRX without any problem, it is working very well. Speed range is 5 W.P.M to 25 W.P.M.

PCB layout for Morse keyer

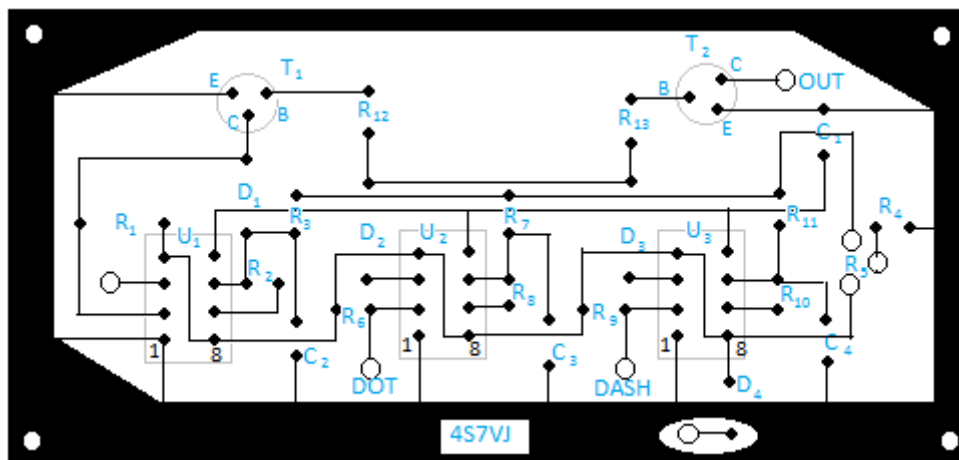


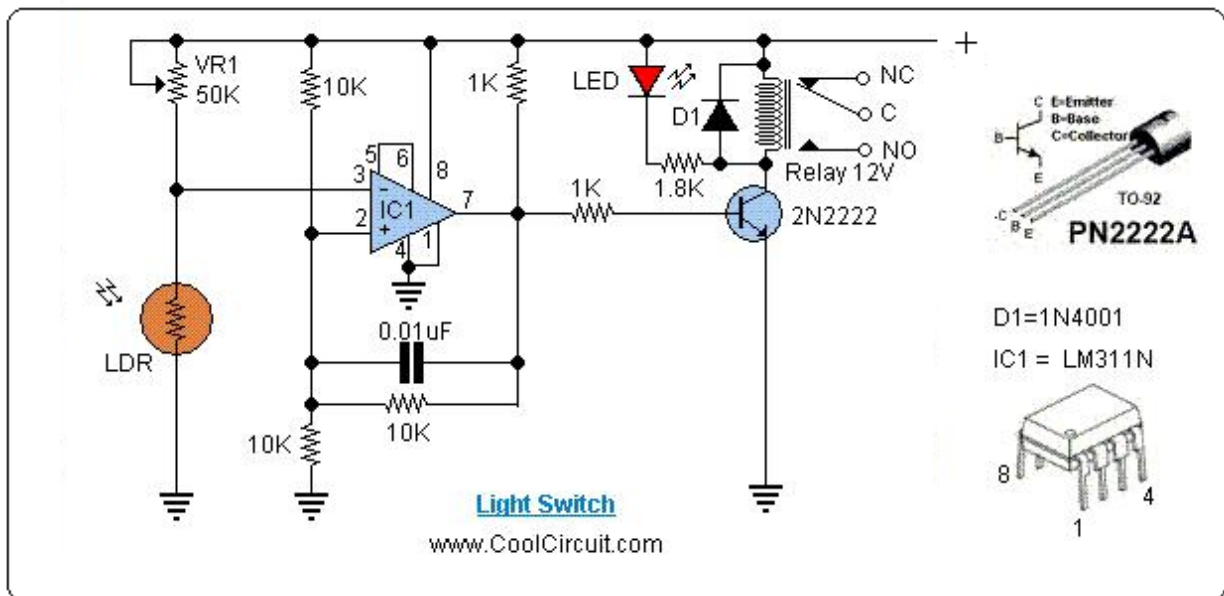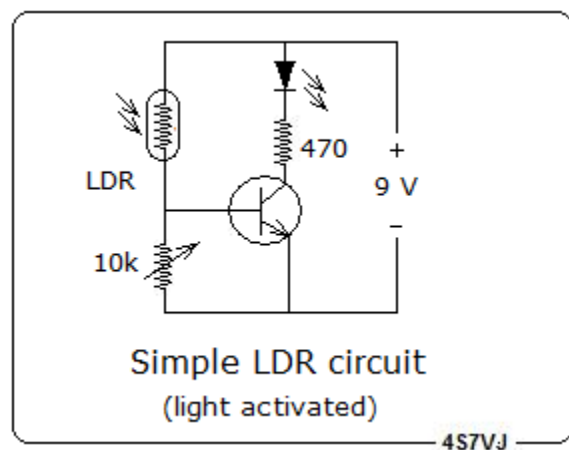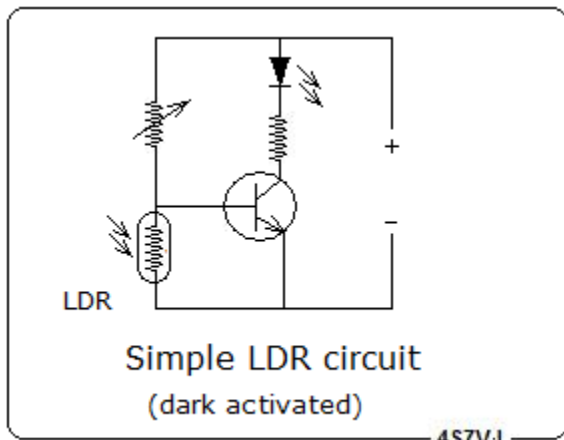
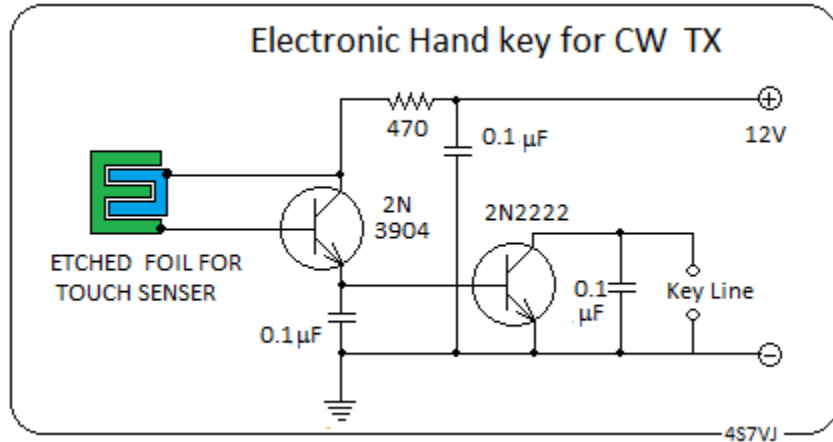


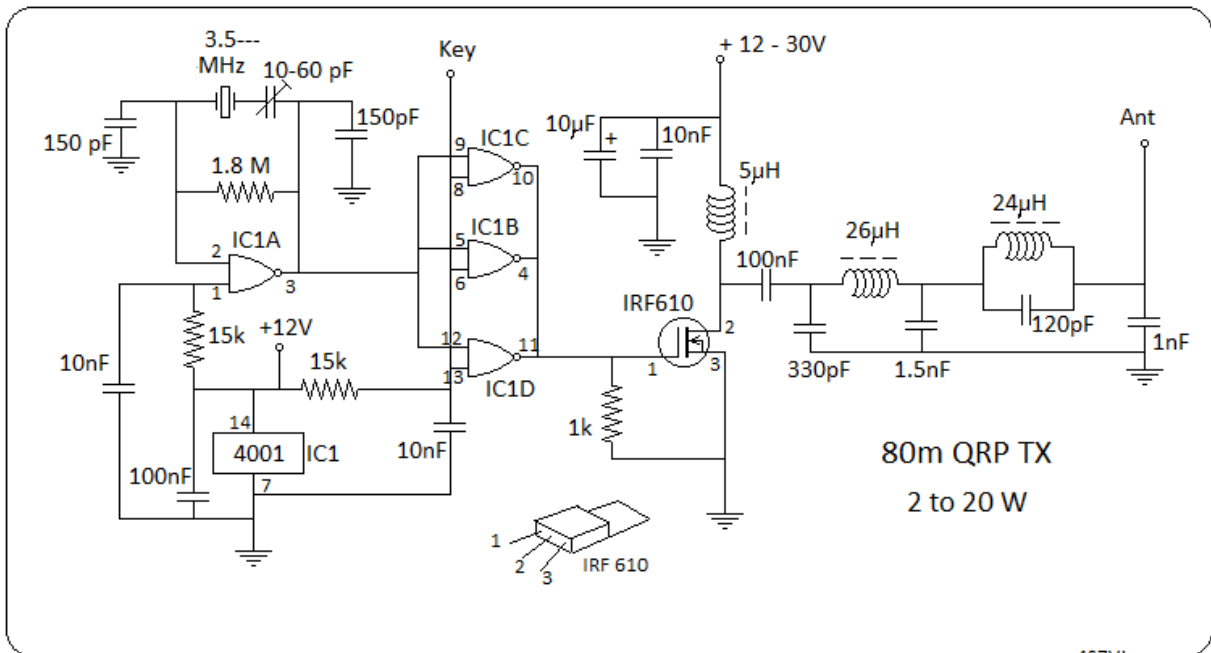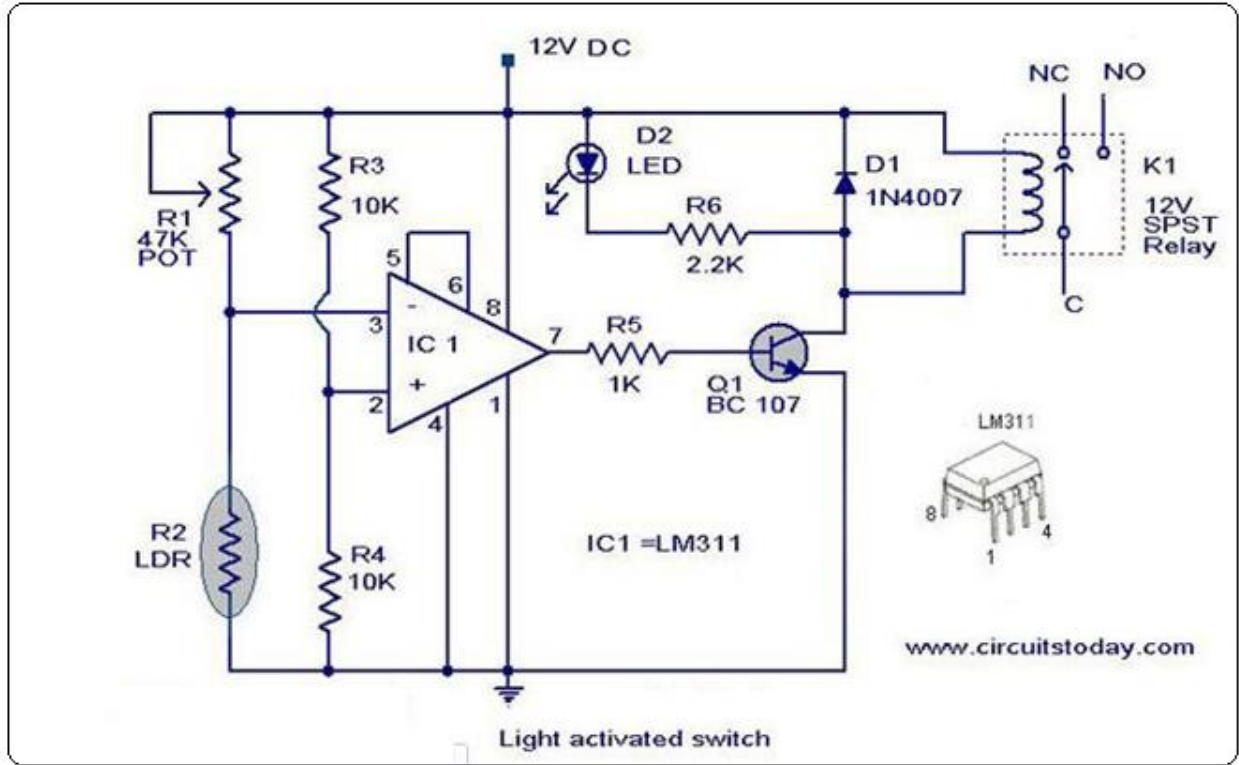


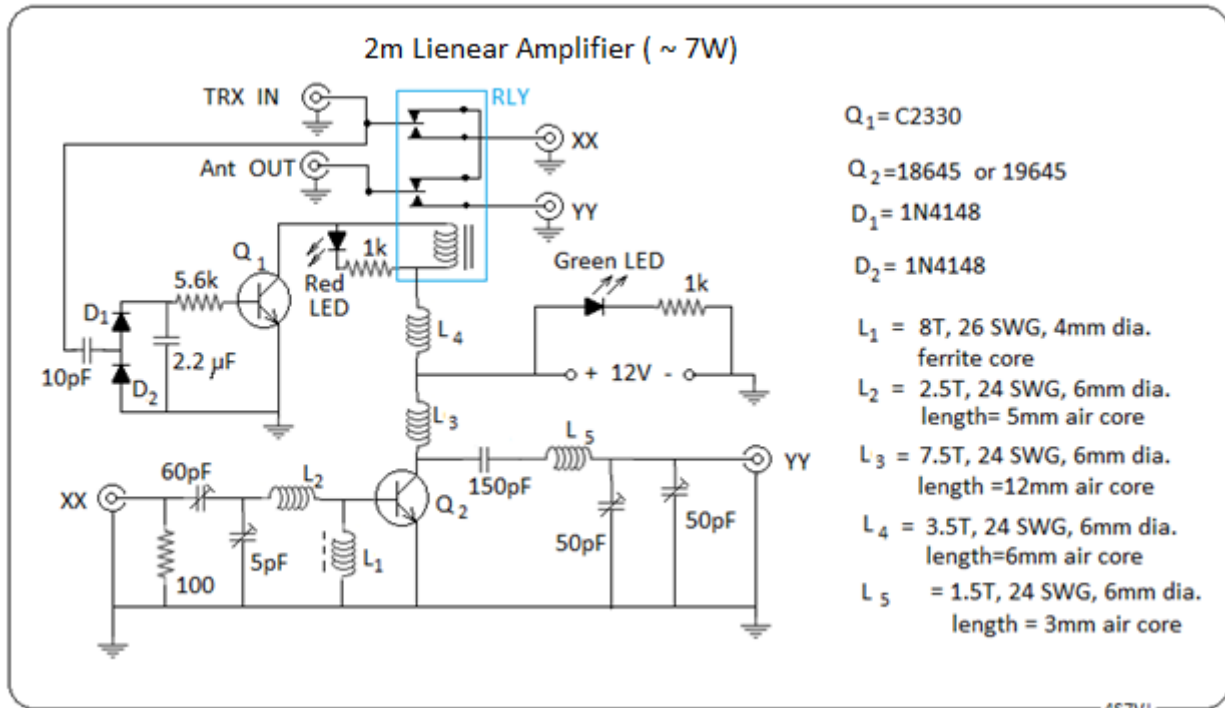

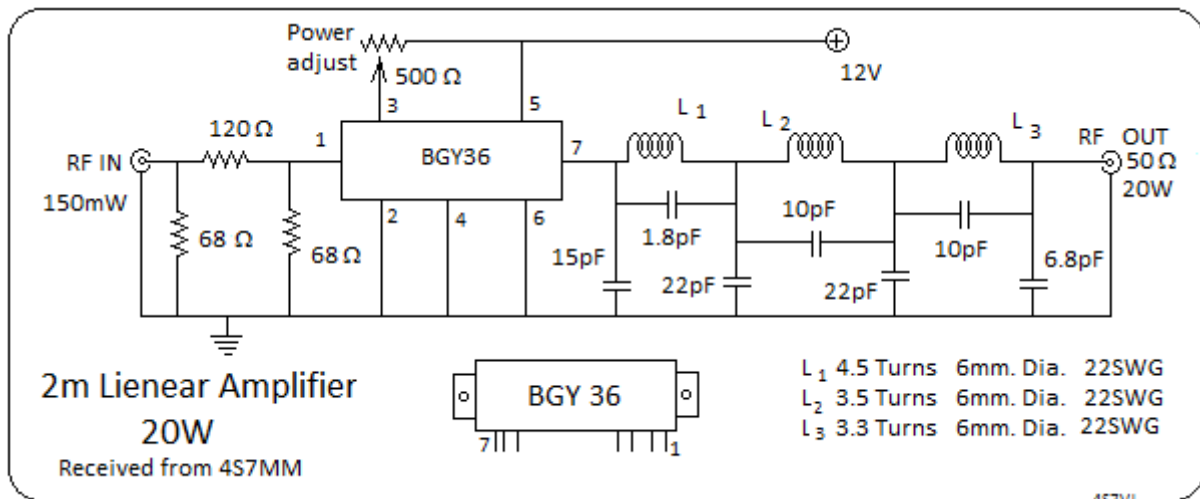I constructed for 4570V and he used more than 15 years






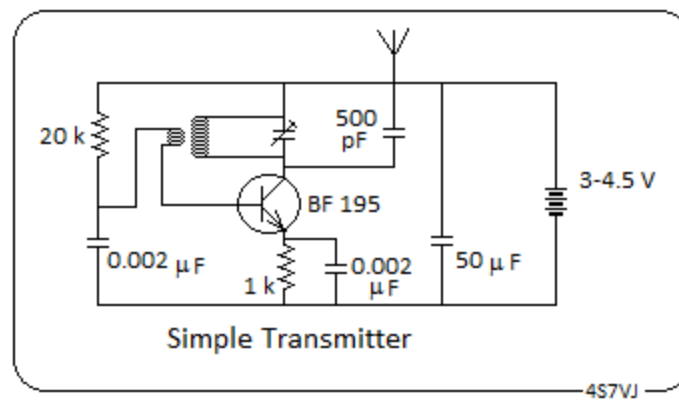
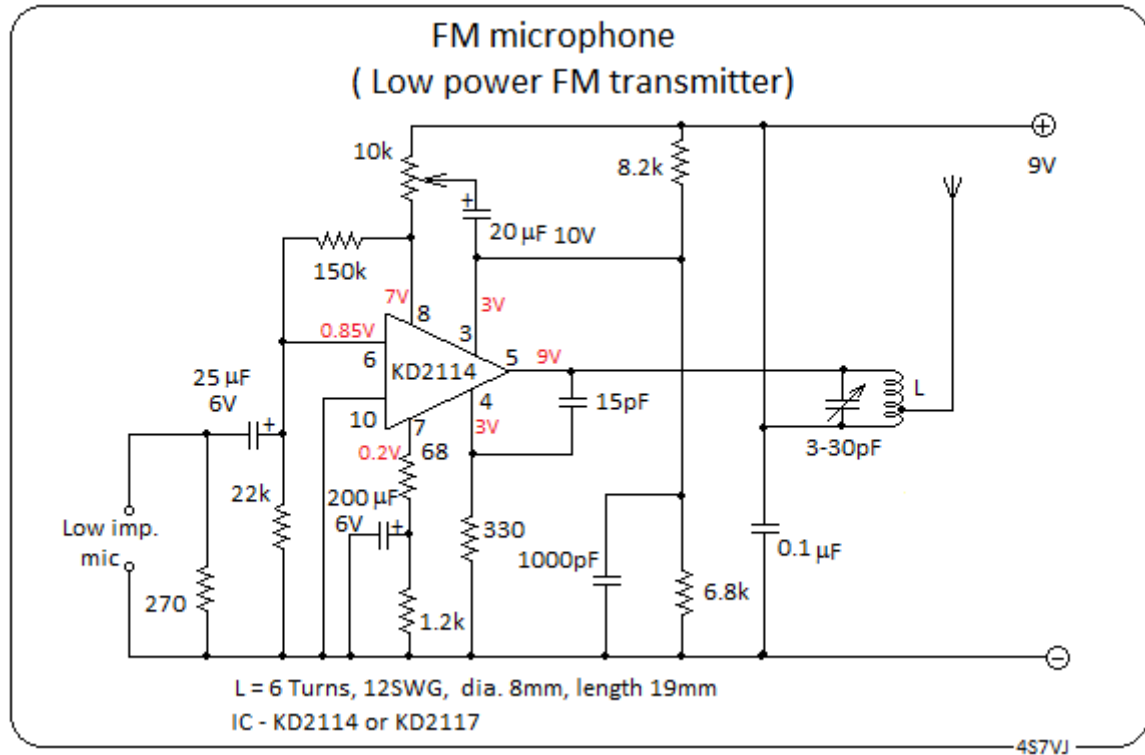




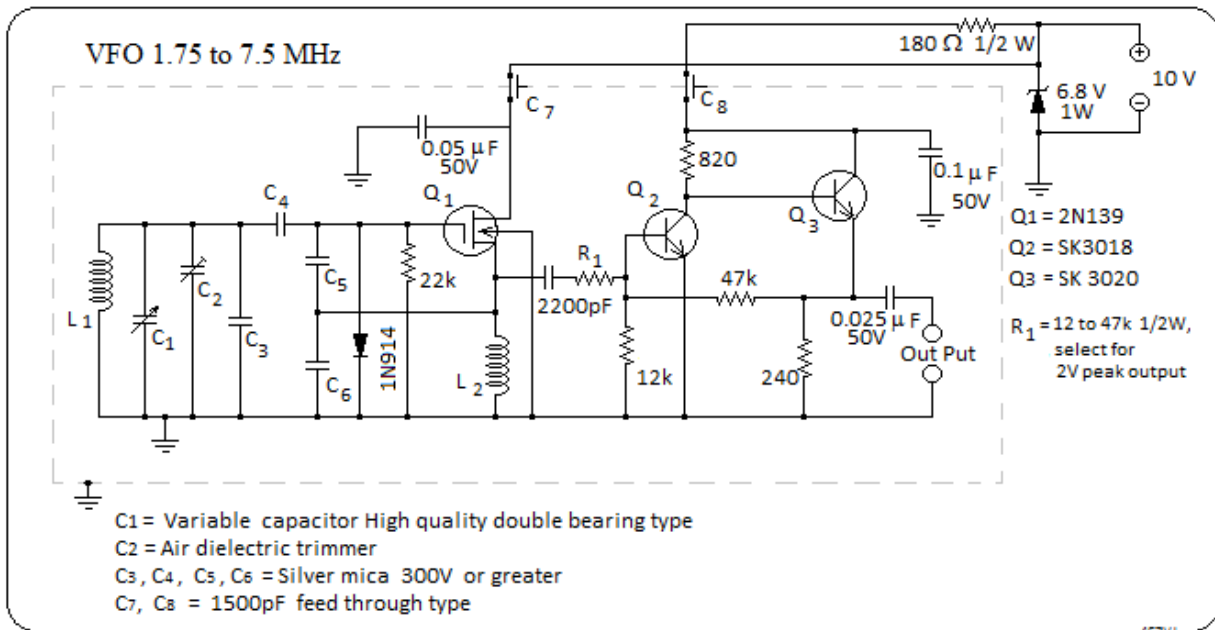
Tuned circuit data for L₁, and C₁ to C₆ (VFO 1.75 to 7.5 MHz)


Frequency range(MHz)	1.75 -1.9	2.5 – 2.7	3.5 – 4.0	5.0 – 5.5		7.0 – 7.5
Inductance (μH)	18.3	9.6	5.4	4.4	2.2	1.4
No of turns	32	19	17	14.75	11.5	8
S.W.G	24	24	20	20	18	18
Turns /inch	32	32	16	16	8	8
Dia. (inch)	1	1	1	1	1	1
B & W No.	3016	3016	3015	3015	3014	3014
C ₁ (pF)	75	75	100	100	50	50
C ₂ (pF)	50	50	25	25	25	25
C ₃ (pF)	100	120	100	None	None	120
C ₄ (pF)	470	470	390	390	270	390
C ₅ (pF)	1000	1000	680	680	560	680
C ₆ (pF)	1000	1000	680	680	560	680

(Copied from RCA hobby circuit manual)

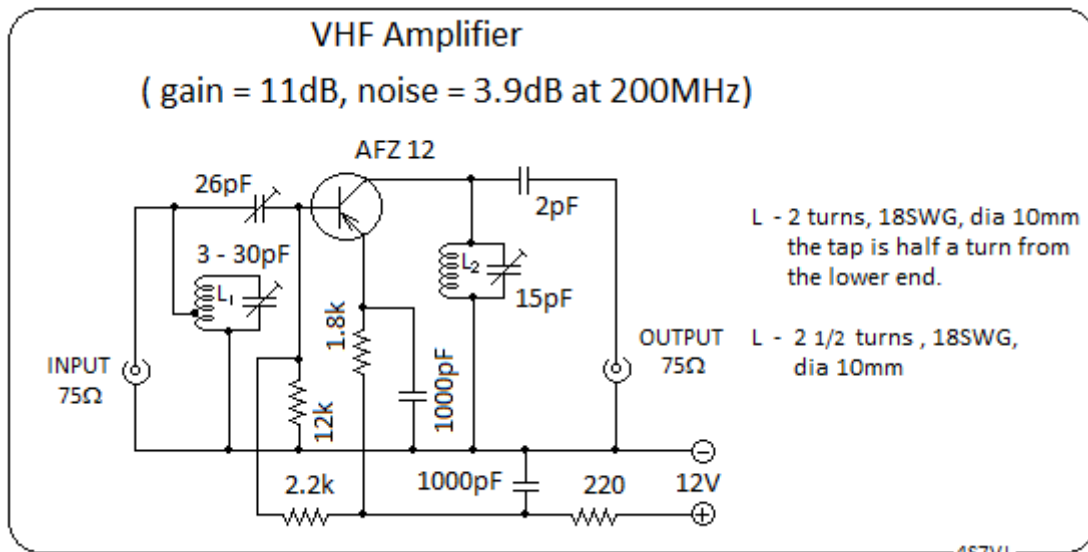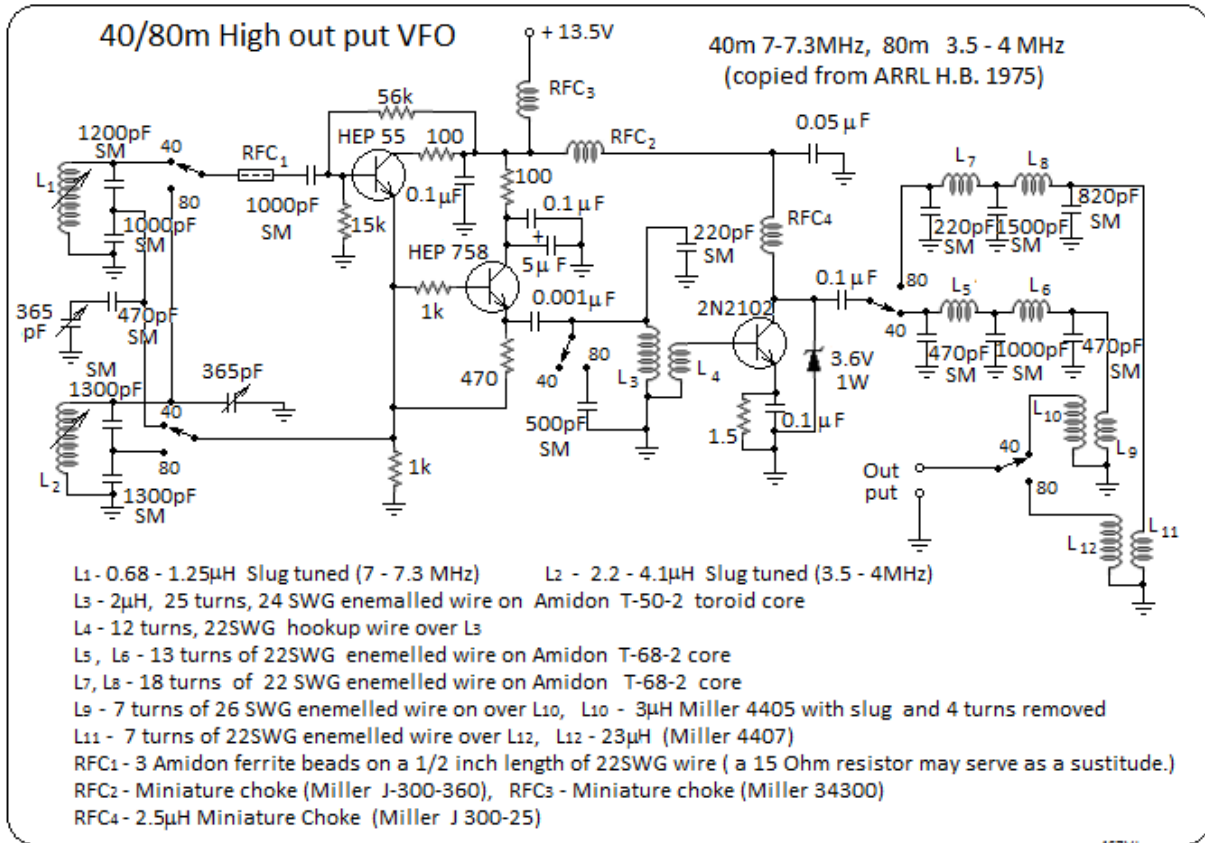


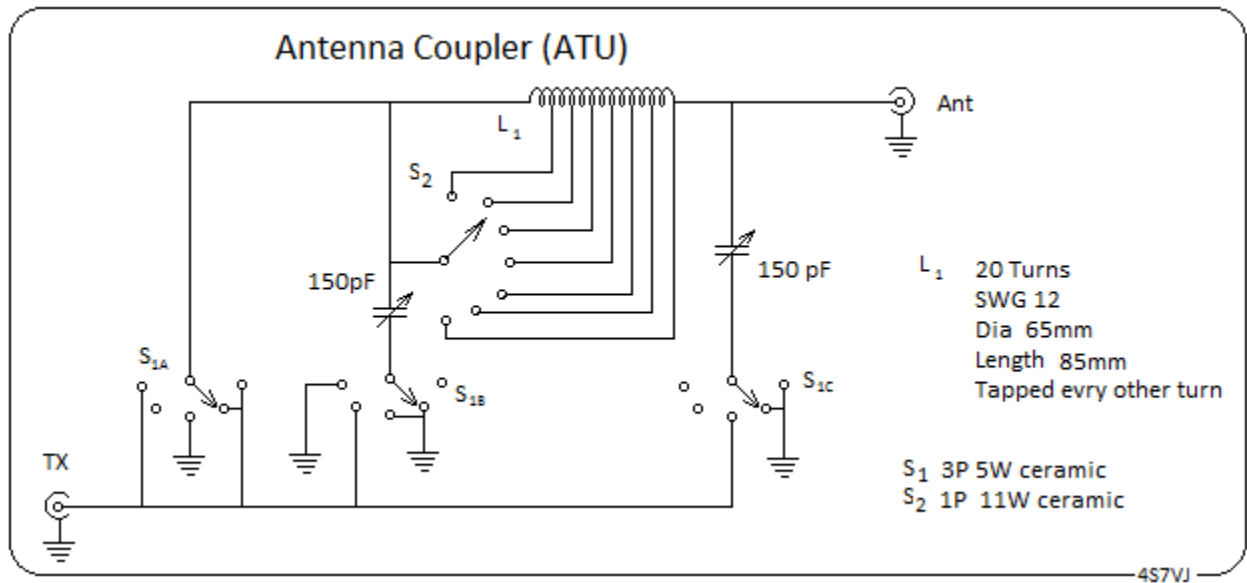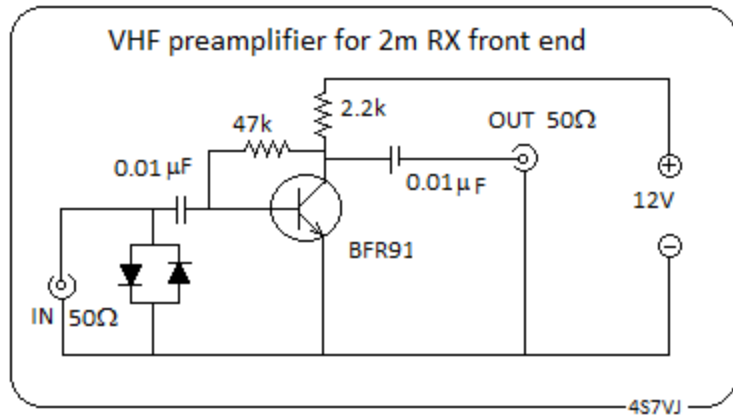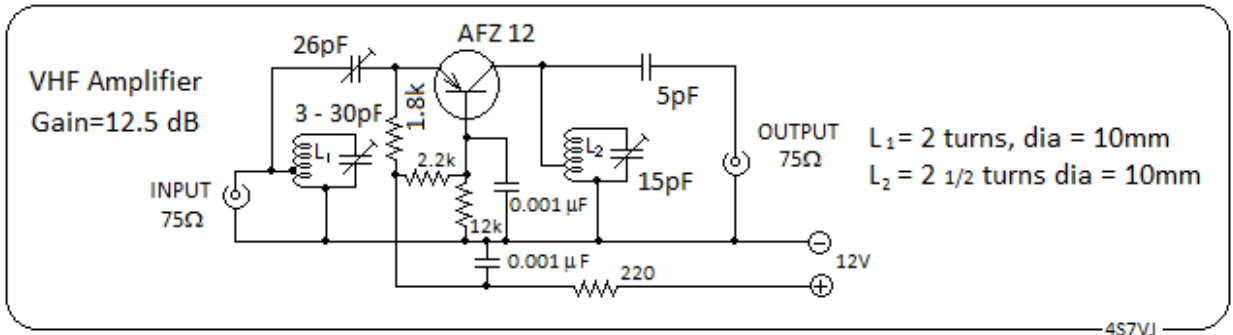


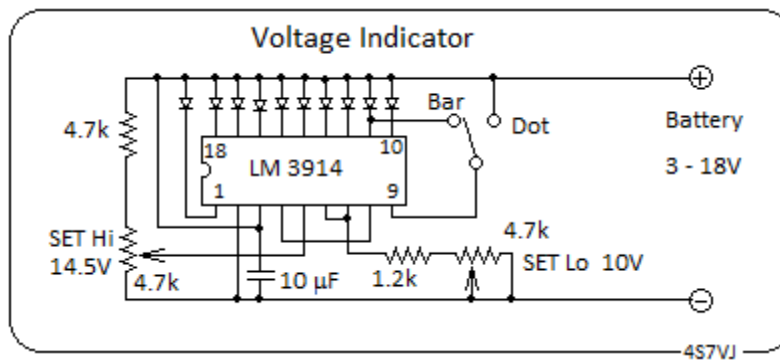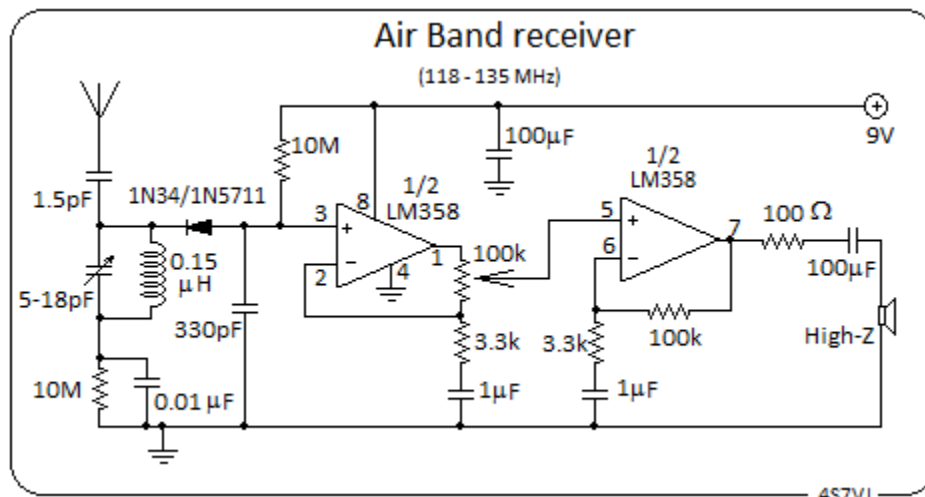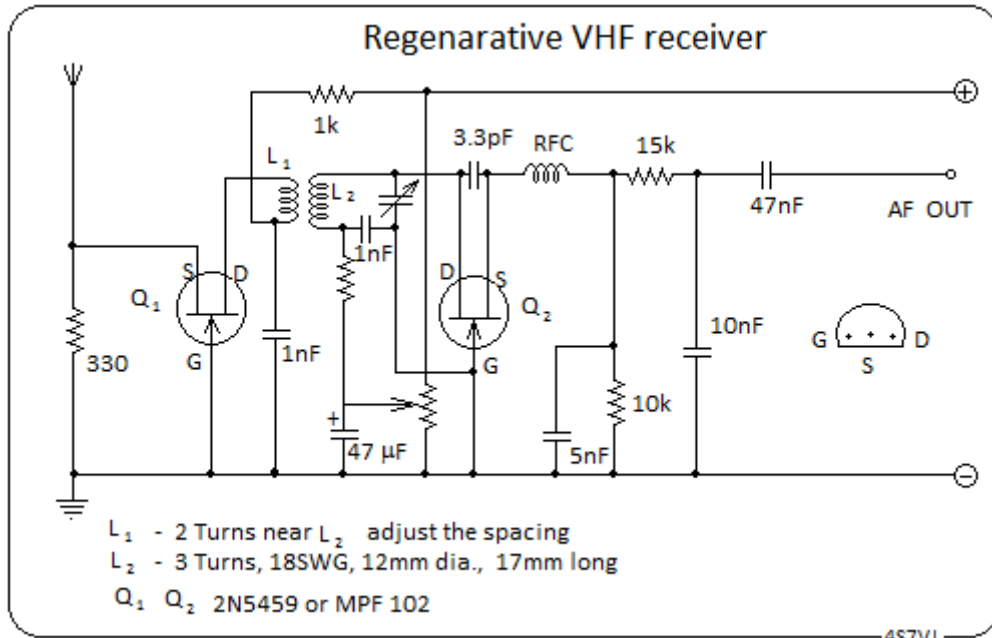

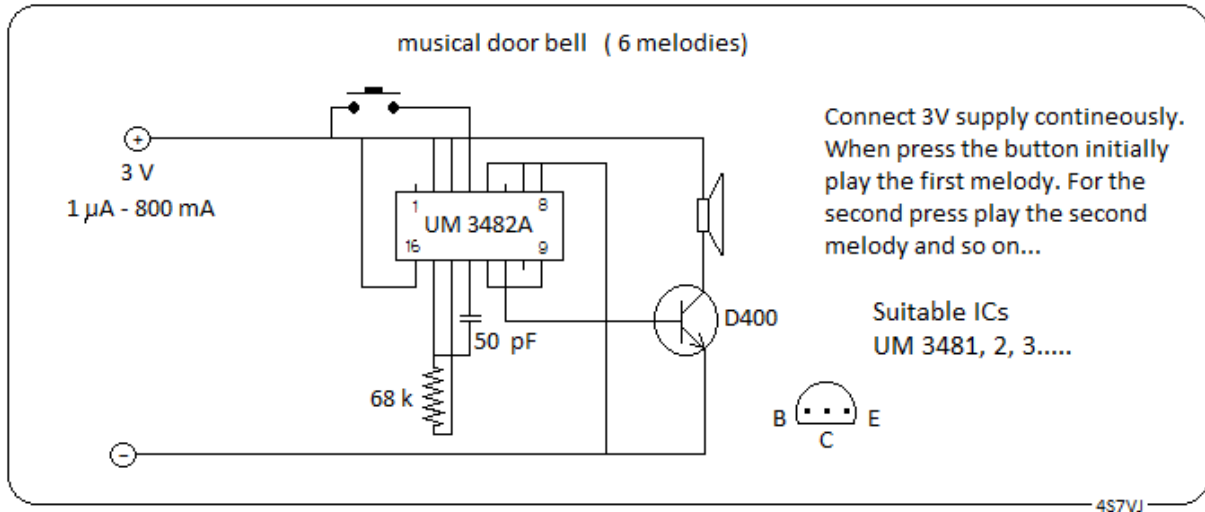


Vero board layout for the above circuit

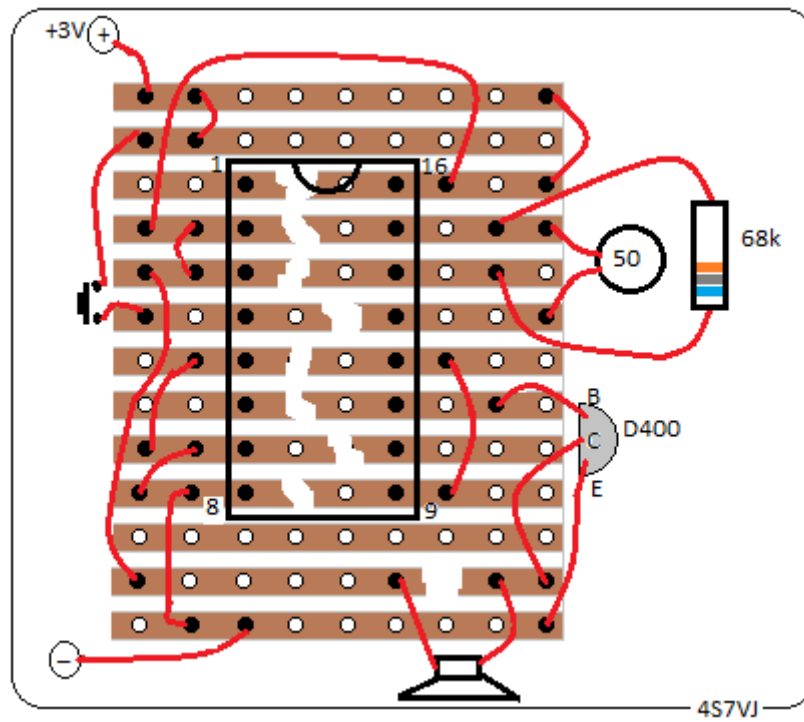

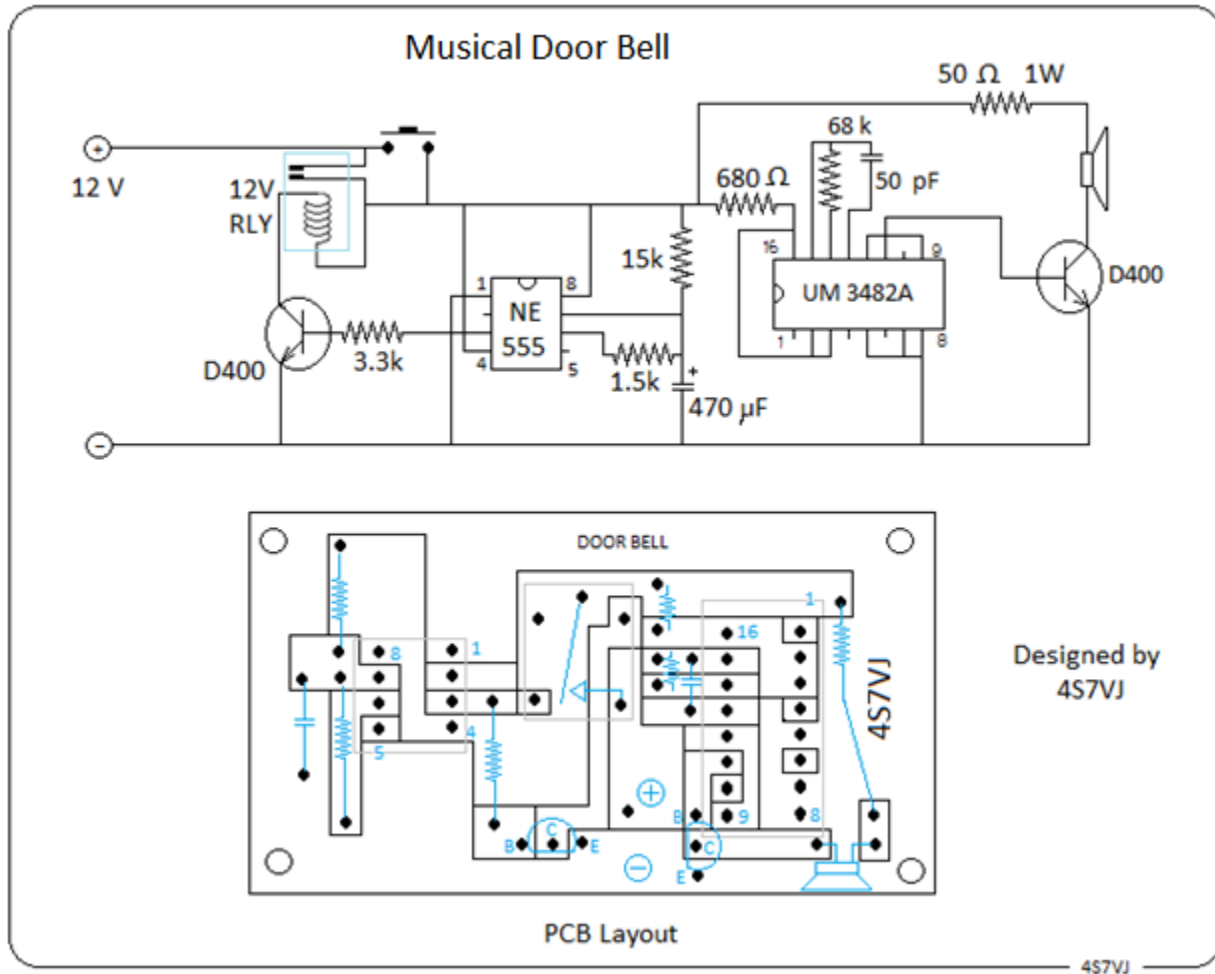


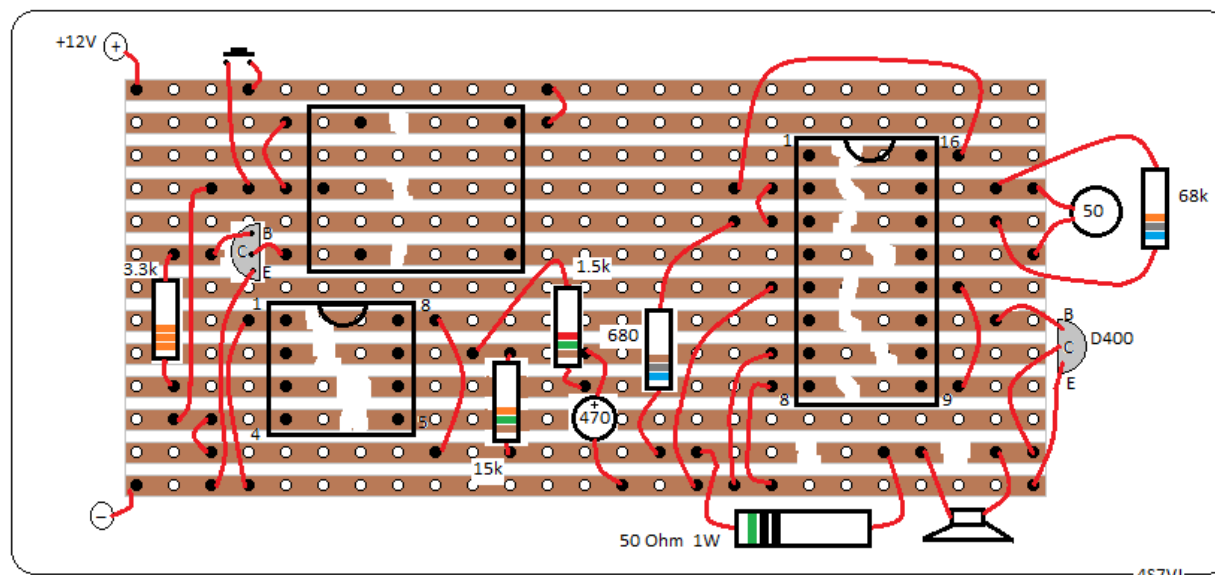Once you press the push button Door bell activated for one melody and automatically switched off after about 10 seconds. For different melodies use UM3481A3489 ICs.




Vero board layout for the above circuit



DIP meter-1

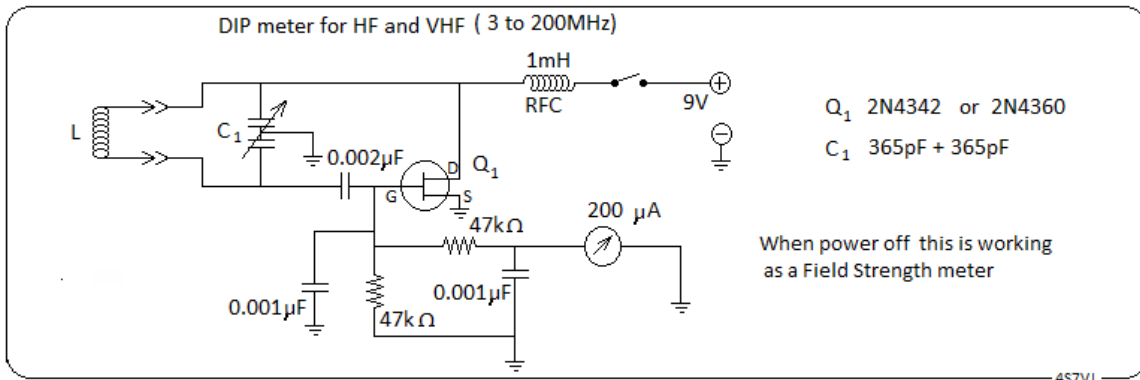


DIP meter-2

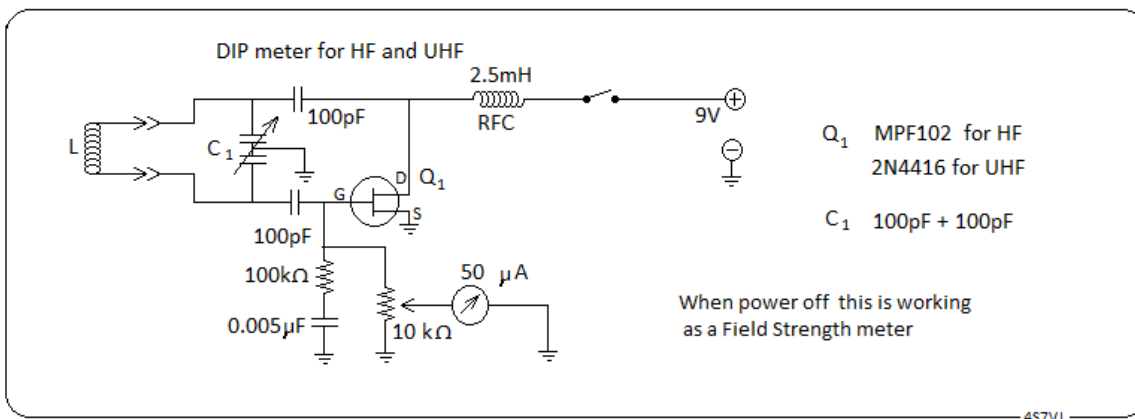


DIP Meter - 3

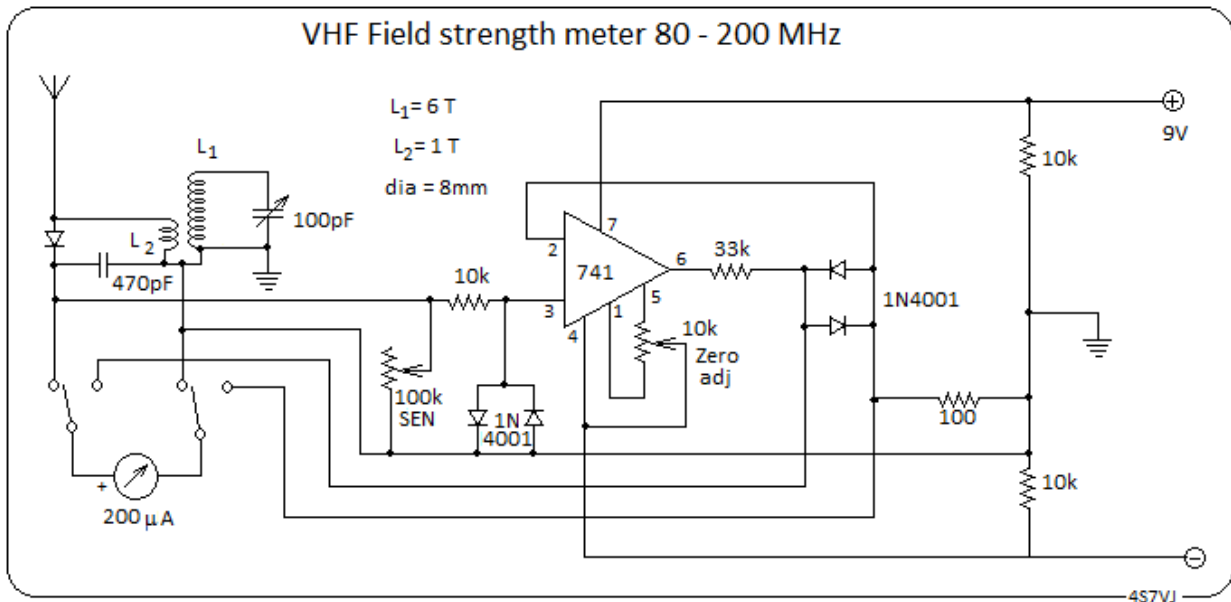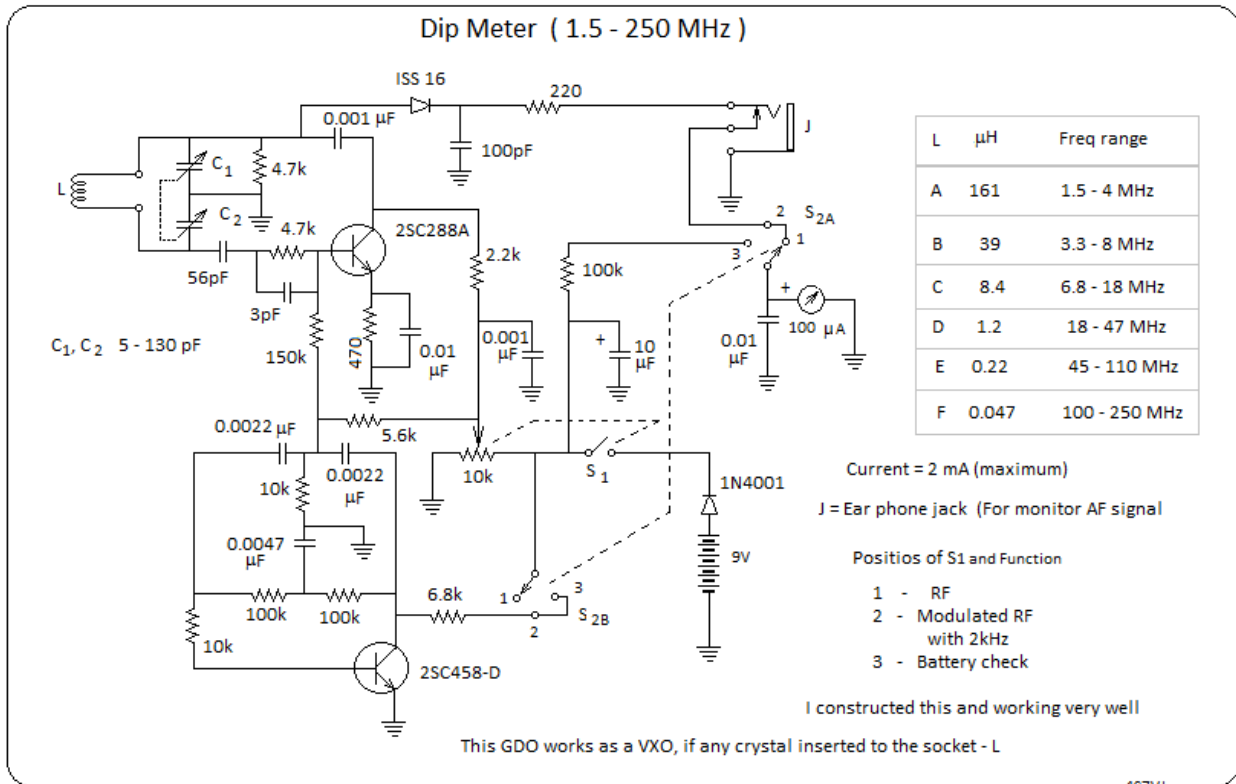


I constructed this, working very well.


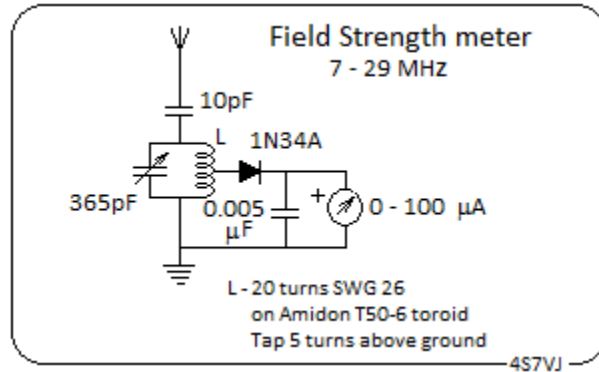




High impedance voltmeter



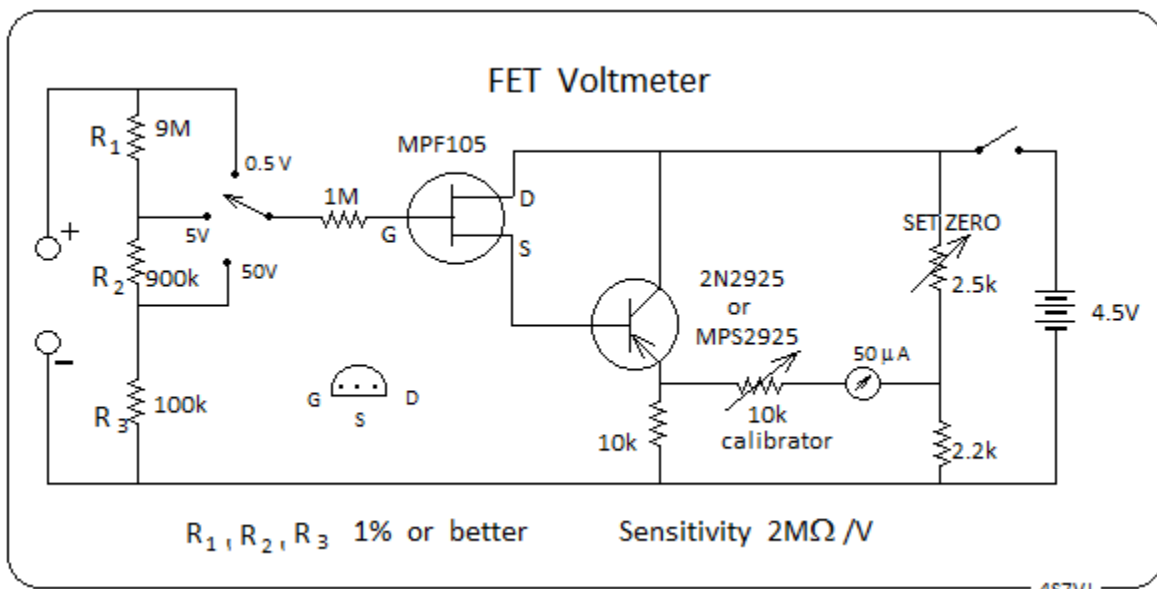




High impedance voltmeter

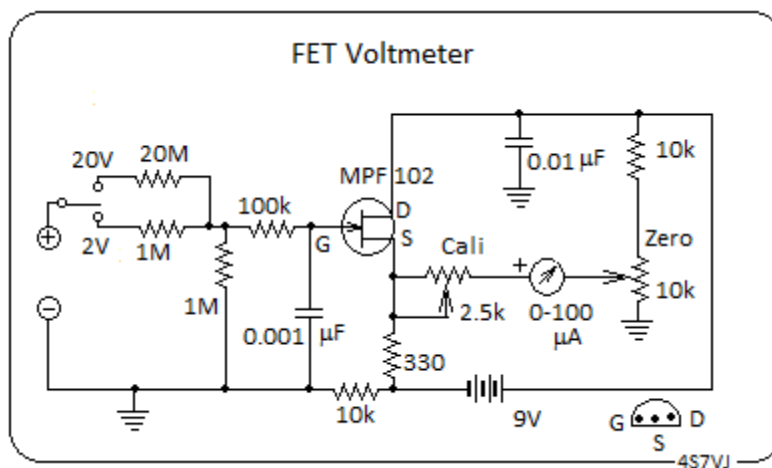

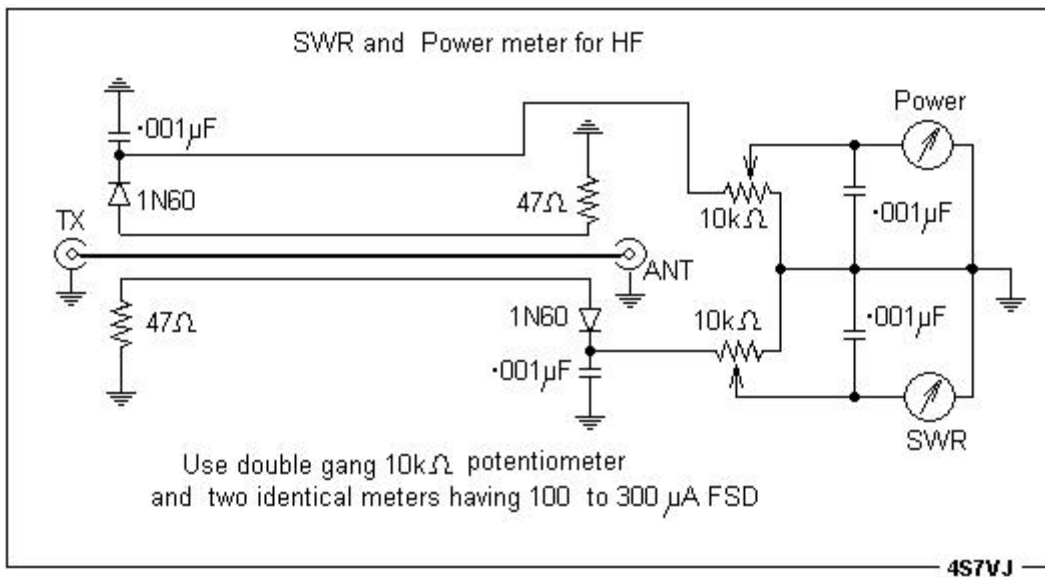
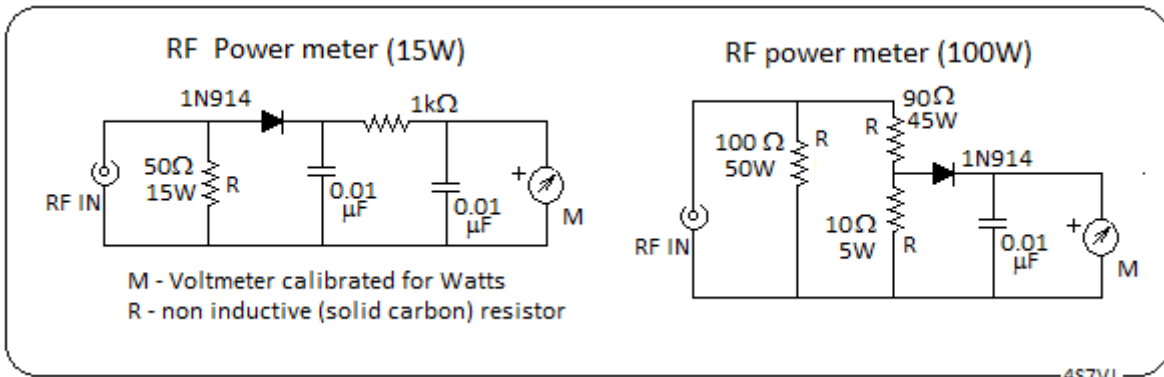


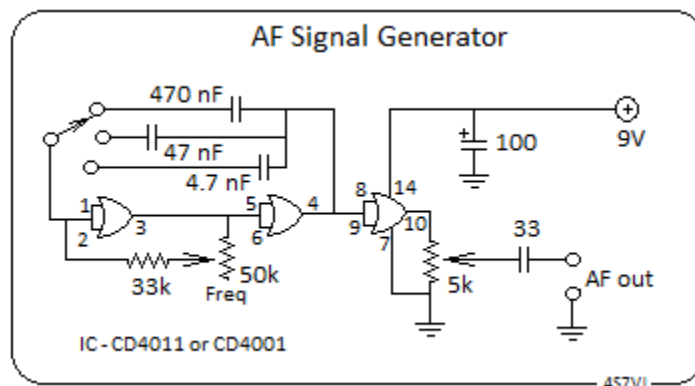
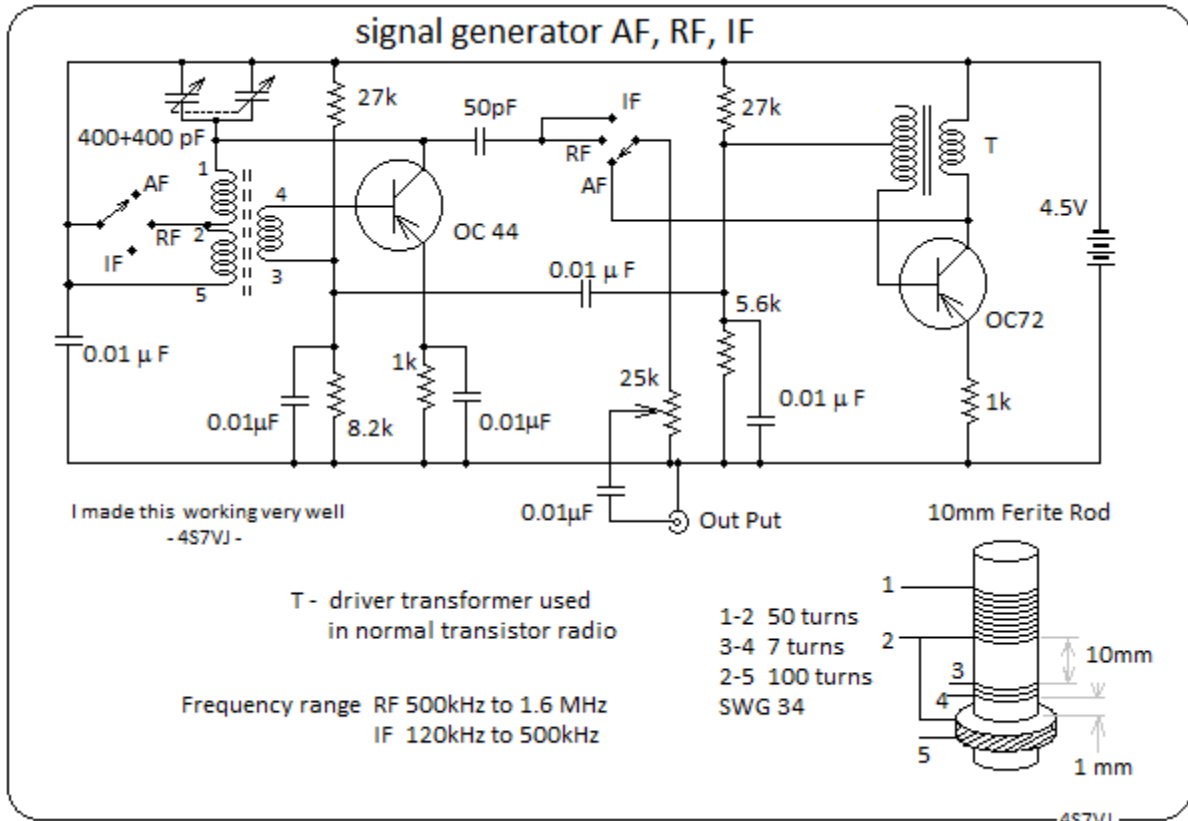


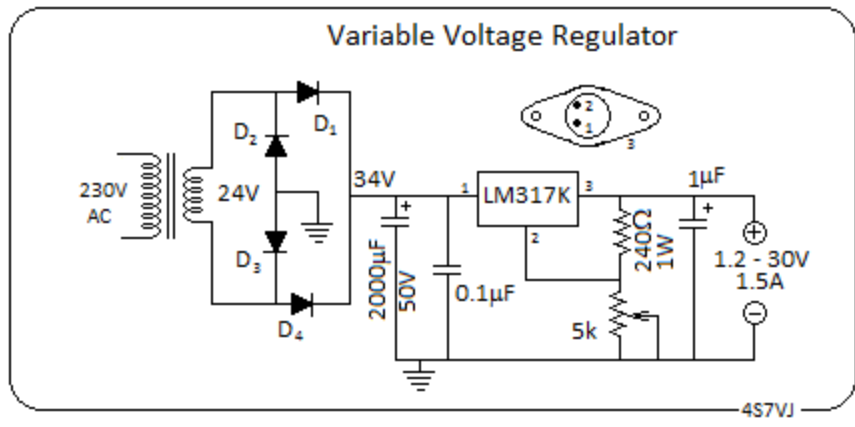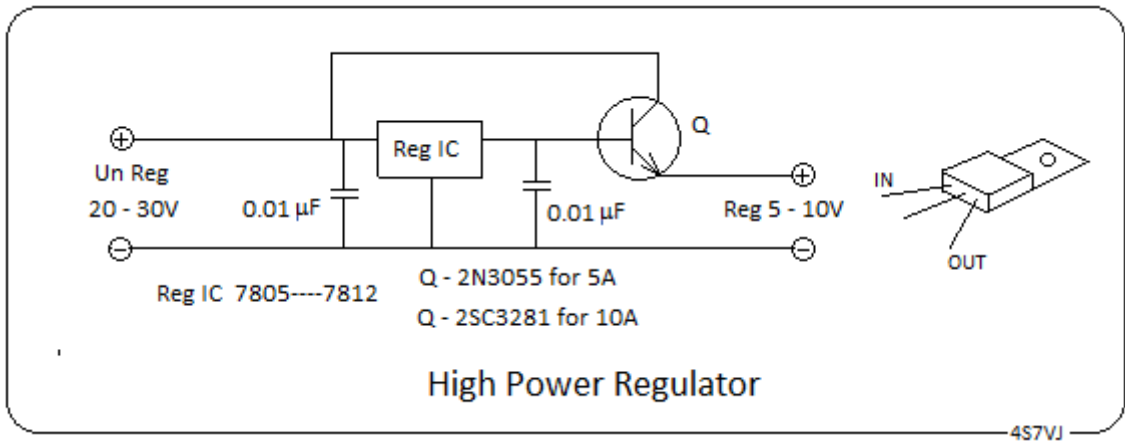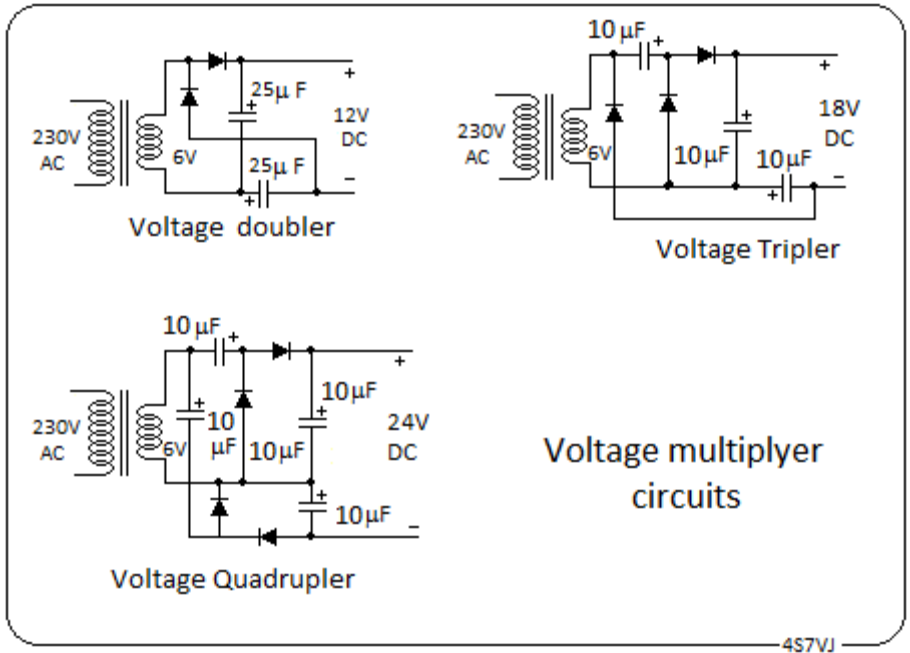


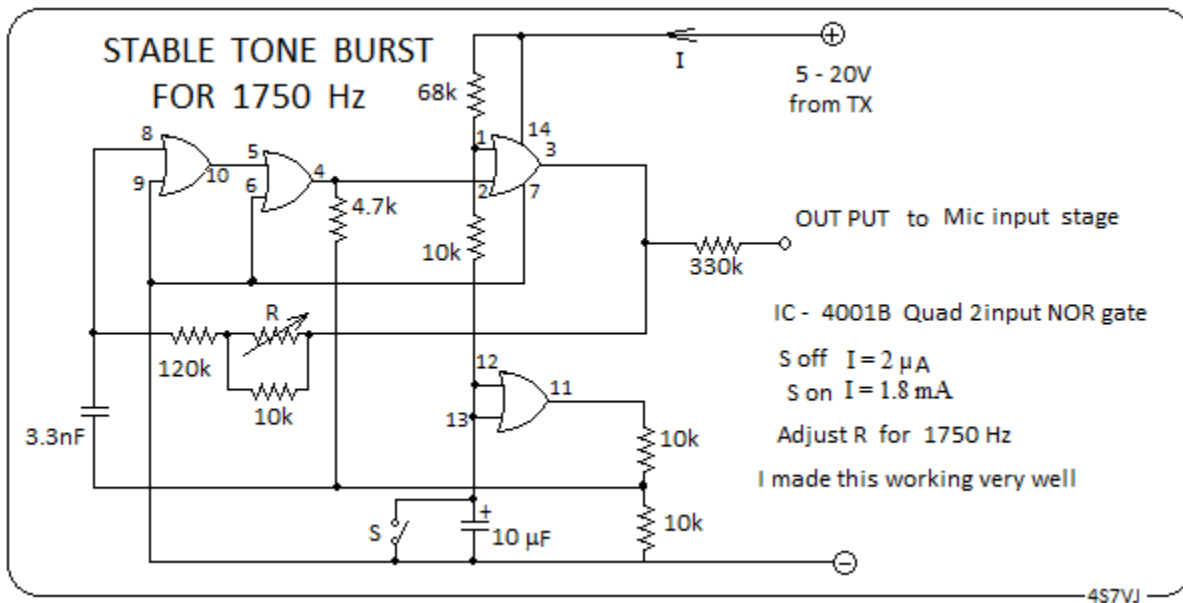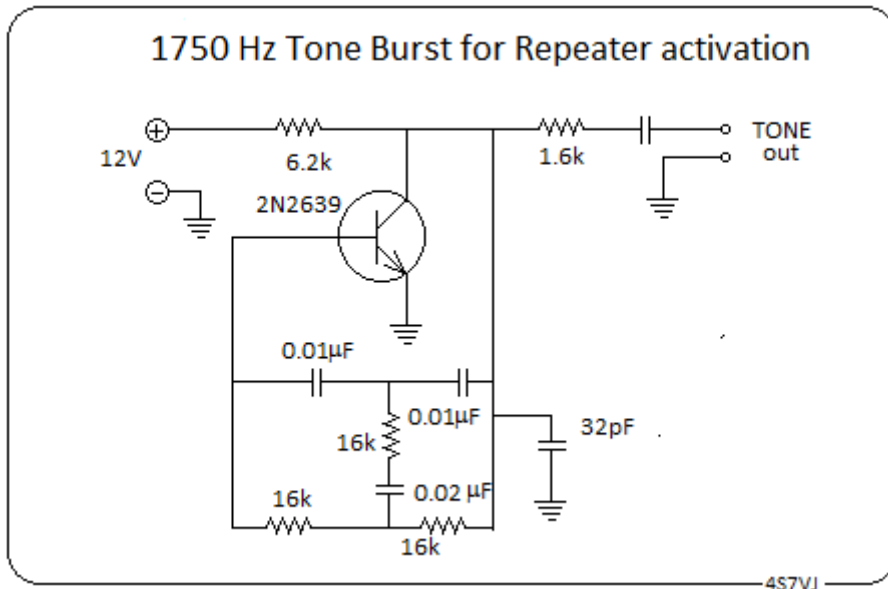

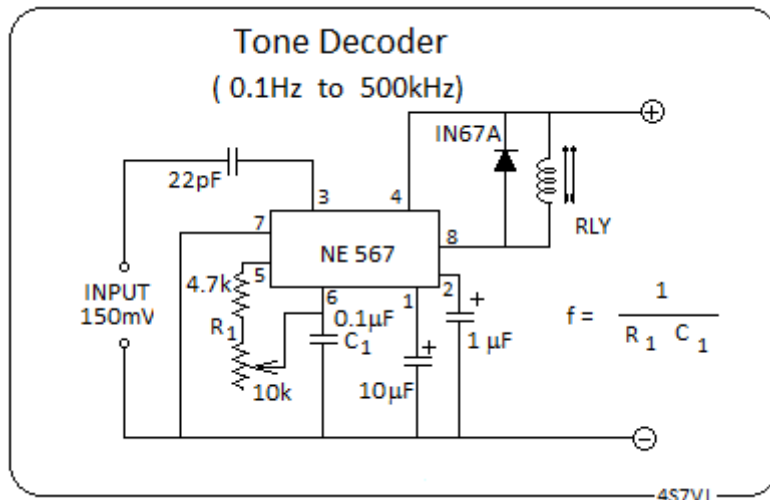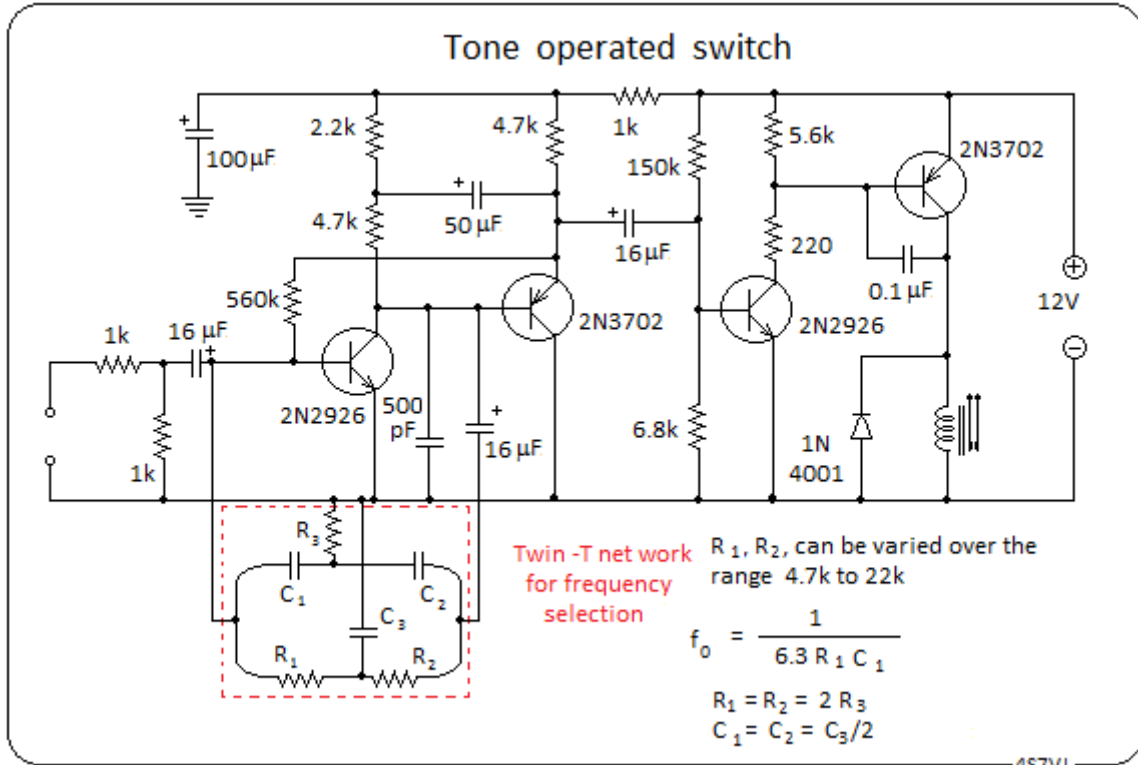
IC - 4001B Quad 2input NOR gate
 S off I = 2 µA
 S on I = 1.8 mA
 Adjust R for 1750 Hz
 I made this working very well



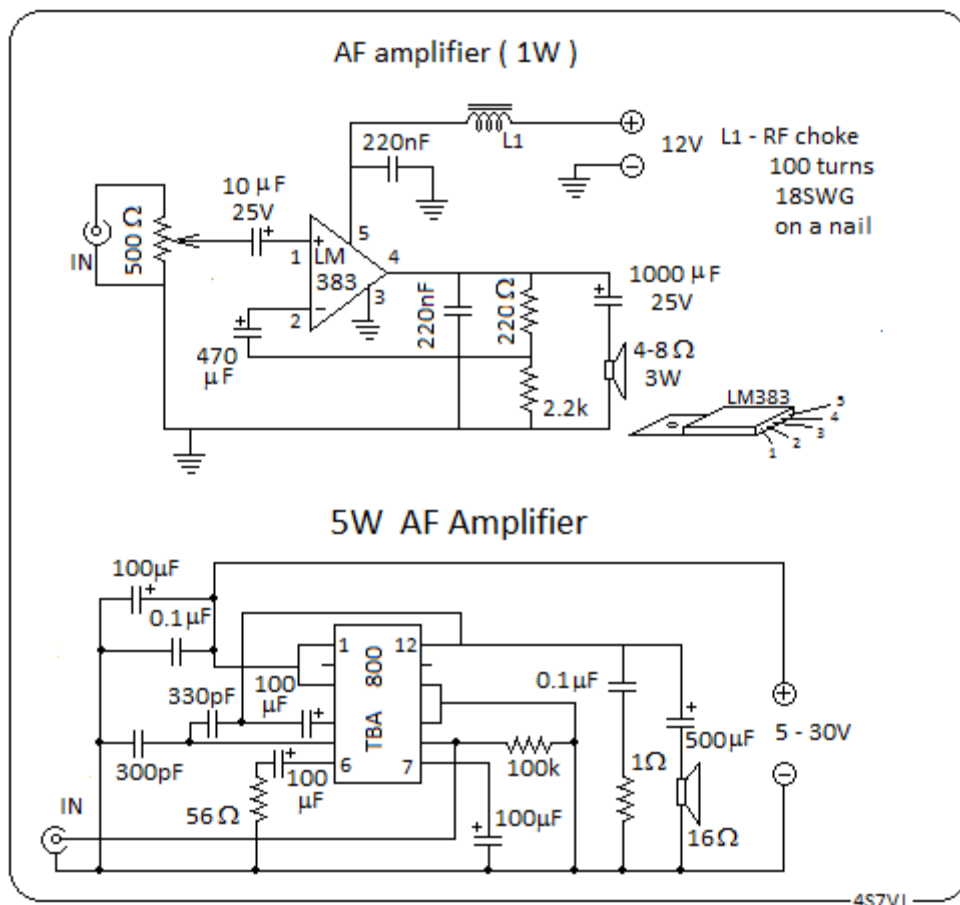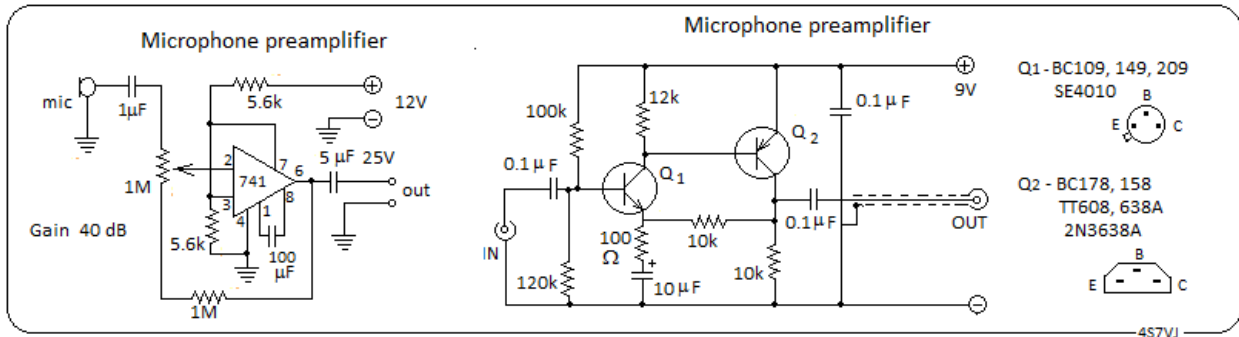


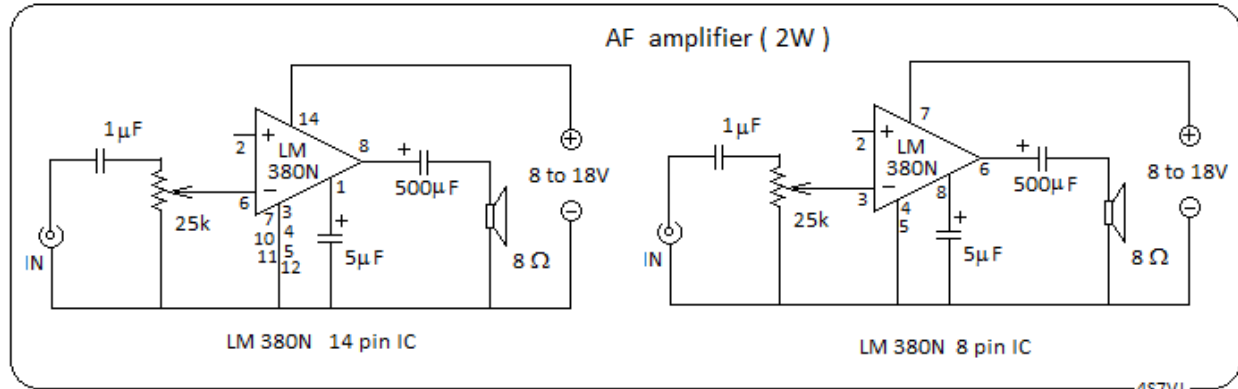




457VJ


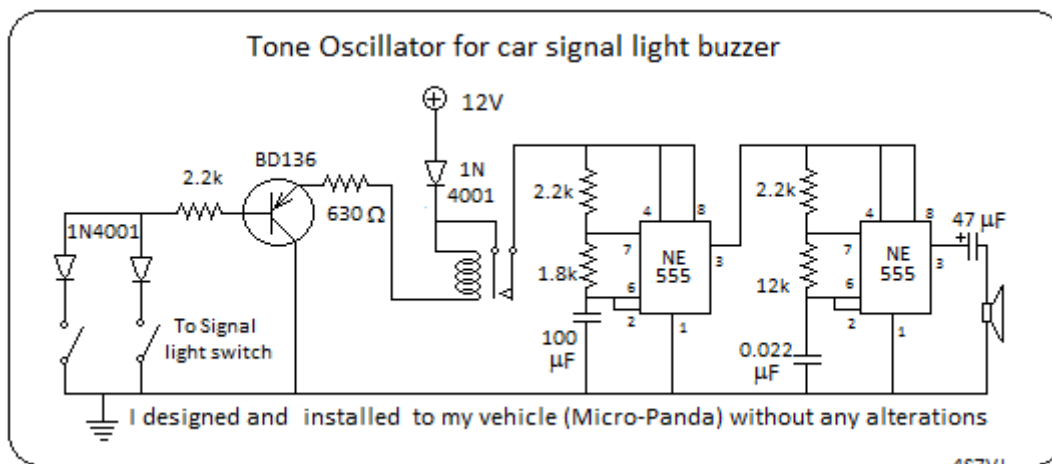



457VJ

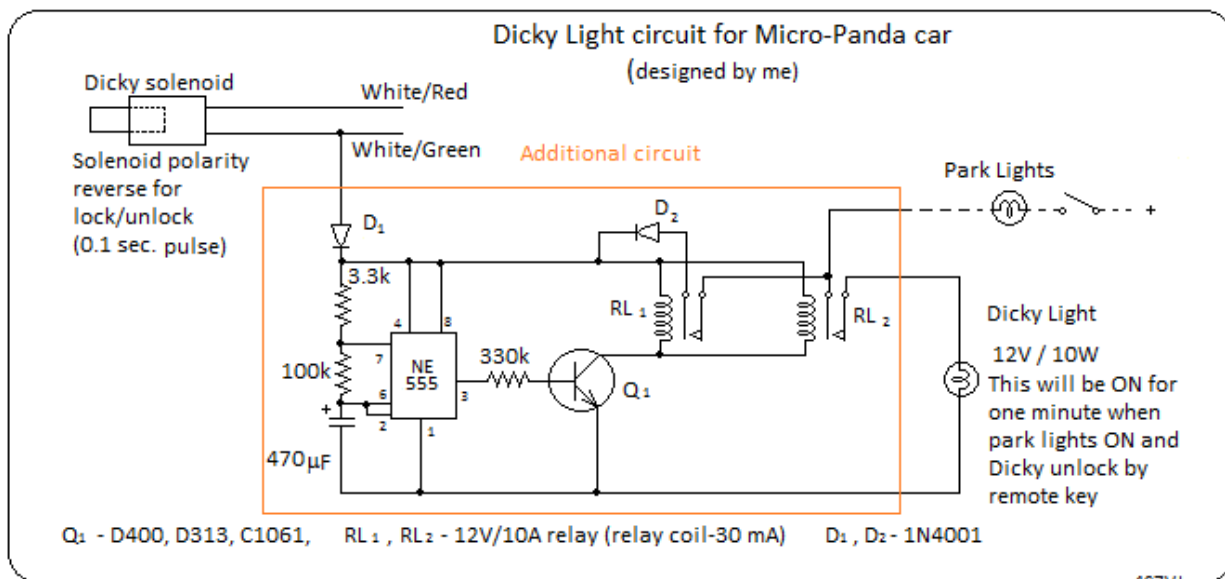

457VJ

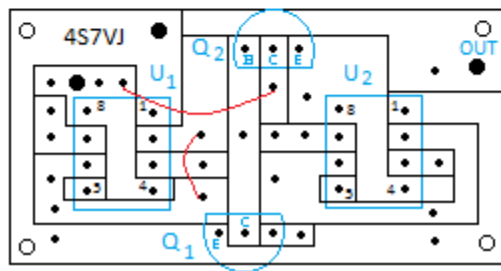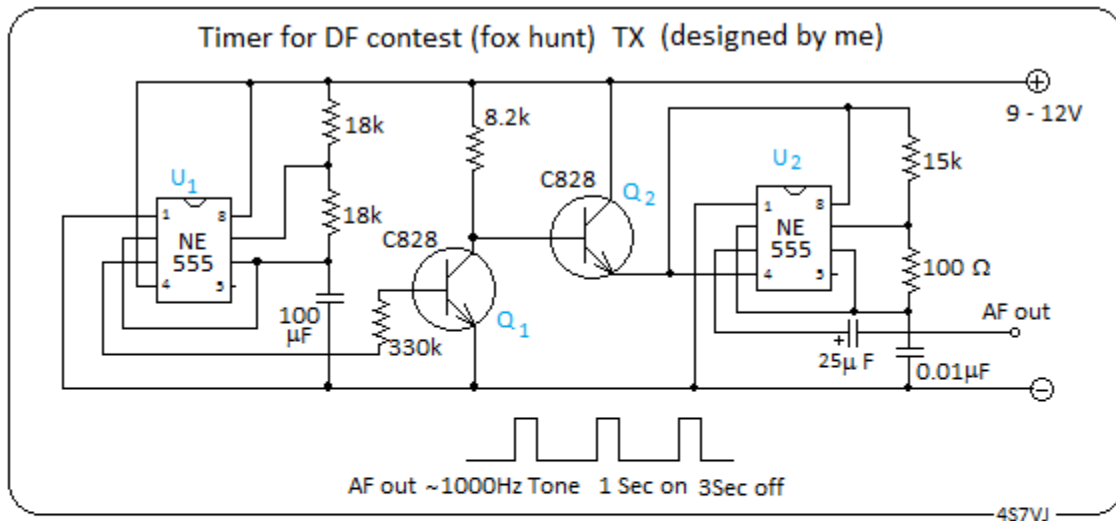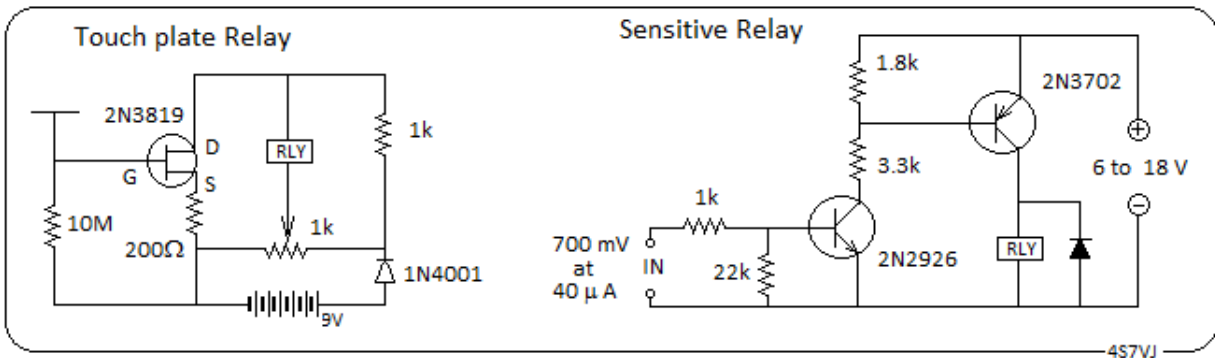

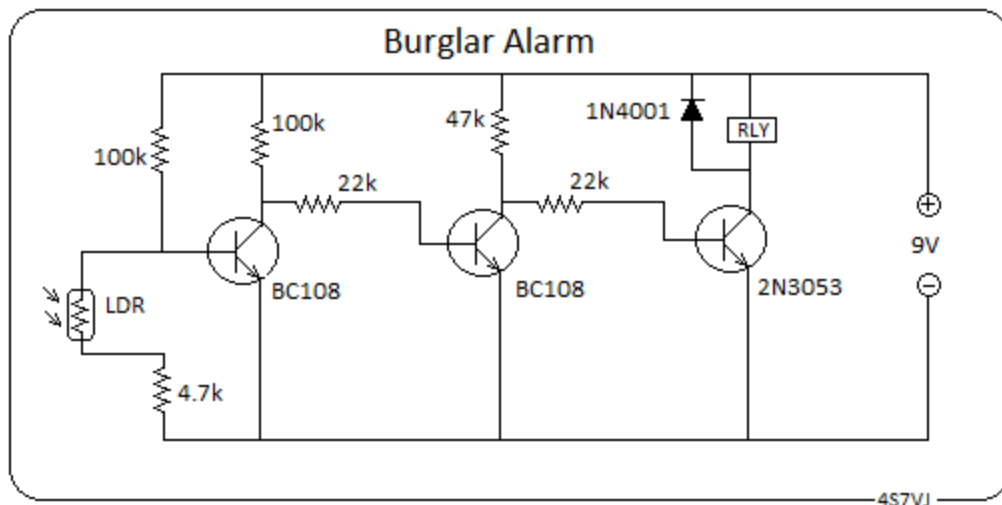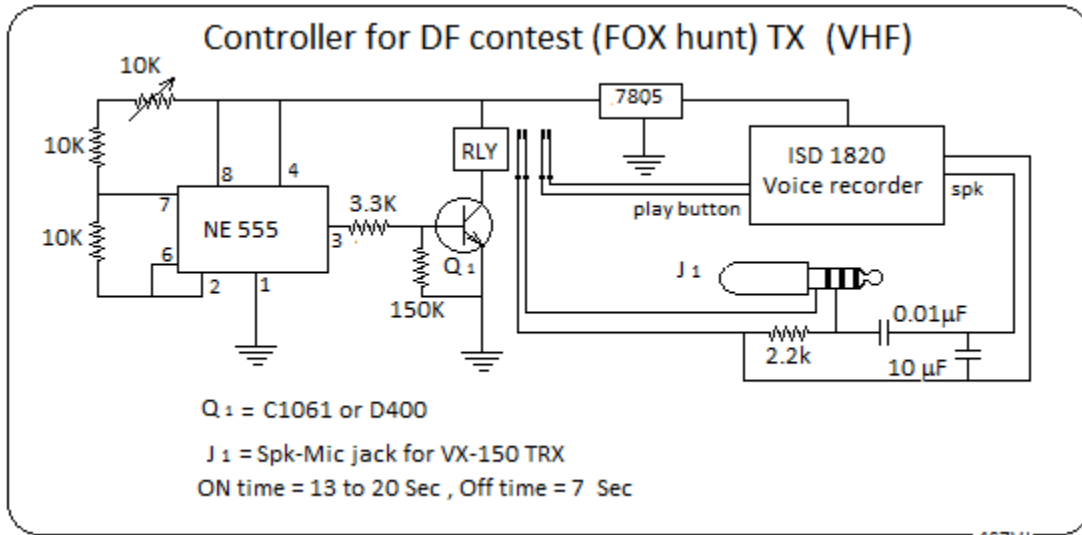

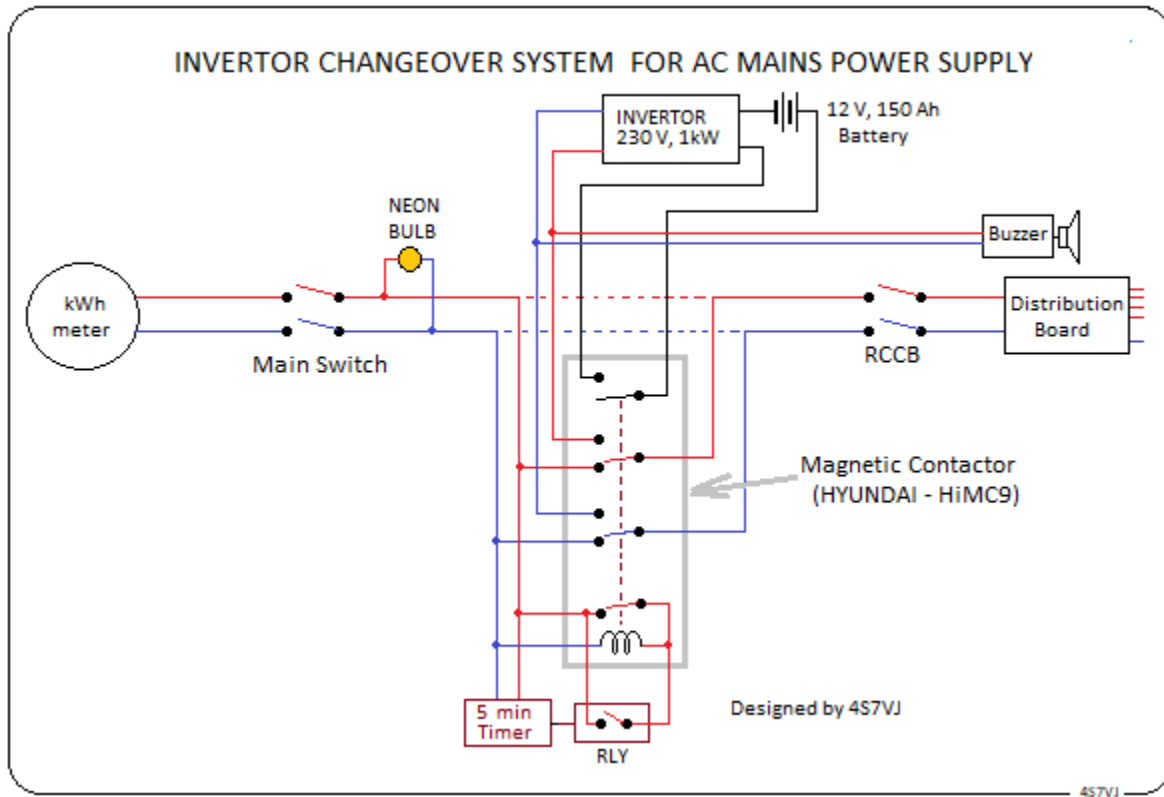

Last updated on 13th July 2020