

**RADIO AMATEUR EXAM**  
**GENERAL CLASS**

By 4S7VJ

**CHAPTER- 3****3.1            REACTANCE (X)**

When a.c. voltage applied to a capacitor or an inductor the current (r.m.s.) is proportional to the voltage (r.m.s.). For d.c. circuits, resistance is the ratio between voltage and the current. There is a similar quantity called reactance for a.c. circuits. Unit is Ohm.

**3.1.1            CAPACITIVE REACTANCE (X<sub>c</sub>)**

The reactance of a pure capacitor in an a.c. circuit is called capacitive reactance and it is inversely proportional with the capacitance and the frequency of ac. supply. The relationship between them is

$$X_c = 1 / (2\pi fC)$$

X<sub>c</sub> = Capacitive Reactance (Ohm - Ω )

f = Frequency ( Hertz - Hz )

C = Capacitance ( Farad - F )

π = 3.14 (mathematical constant, 22/7 )

Although the unit of reactance is Ohm, there is no power dissipation in reactance. The energy stored in the capacitor in one quarter of the cycle is simply returned to the circuit in the next. For the above formula, if f in MHz and C in μF, then X<sub>c</sub> will be in Ohms. It is more convenient.

Example:-

What is the capacitive reactance of a 500 pF capacitor at a frequency of 7060 kHz.

$$f = 7060 \text{ kHz} = 7.060 \text{ MHz}$$

$$C = 500 \text{ pF} = 0.0005 \text{ } \mu\text{F}$$

$$\begin{aligned} X_c &= 1 / (2 \times 3.14 \times 7.060 \times 0.0005 ) \\ &= \underline{\underline{45.08 \text{ Ohm}}} \end{aligned}$$

### 3.1.2 INDUCTIVE REACTANCE ( $X_L$ )

The reactance of a pure inductor (one with no resistance but practically all inductors have resistance) in an ac circuit is called inductive reactance, and it is directly proportional with the inductance and the frequency of the a.c. current through the inductor. The formula for it is:-

$$X_L = 2 \pi fL$$

$X_L$  = Inductive Reactance ( $\Omega$  )

$f$  = Frequency ( Hz )

$L$  = Inductance ( H )

$\pi$  = 3.14 (mathematical constant, 22/7 )

(If  $L$  in  $\mu\text{H}$  and  $f$  in MHz then  $X_L$  is in Ohms)

Example:-

What is the reactance of a 20  $\mu\text{H}$  inductor for 14200 kHz? If the resistance is negligible and current through the inductor is 10  $\mu\text{A}$ , what is the voltage across the inductor?

$$f = 14200 \text{ kHz} = 14.2 \text{ MHz}$$

$$L = 20 \mu\text{H}$$

apply the formula

$$X_L = 2\pi fL$$

$$= 2 \times 3.14 \times 14.2 \times 20$$

$$= \underline{\underline{1784 \text{ Ohms}}}$$

apply the Ohm's law for the inductor

$$I = 10 \mu\text{A} = 1/100000 \text{ A}$$

$$R = 1784 \Omega$$

$$V = I \times R$$

$$= (1/100000) \times 1784 \text{ V}$$

$$= (1/100000) \times 1784 \times 1000 \text{ mV}$$

$$= \underline{\underline{17.84 \text{ mV}}}$$

### 3.1.3 REACTANCES IN SERIES & PARALLEL

When reactance of the same kind (**with out combine capacitors and inductors** ) connected in series or parallel the resultant is as same as resistances.

For series reactance:-

$$X = X_1 + X_2 + X_3$$

For parallel reactances:-

$$1/X = 1/X_1 + 1/X_2 + 1/X_3$$

### 3.2 PHASE & PHASE ANGLE

If a magnet rotates with a uniform speed near a coil (like a bicycle dynamo) the graph between the generated e.m.f. vs angle of rotation (Fig. 3.1) is a sine wave. One wavelength is represents 360 degrees or one complete turn. Any instance defined as the PHASE of the sine wave. The angle of rotation ( $\alpha$  in Fig-3.1) is called as the **phase angle**.

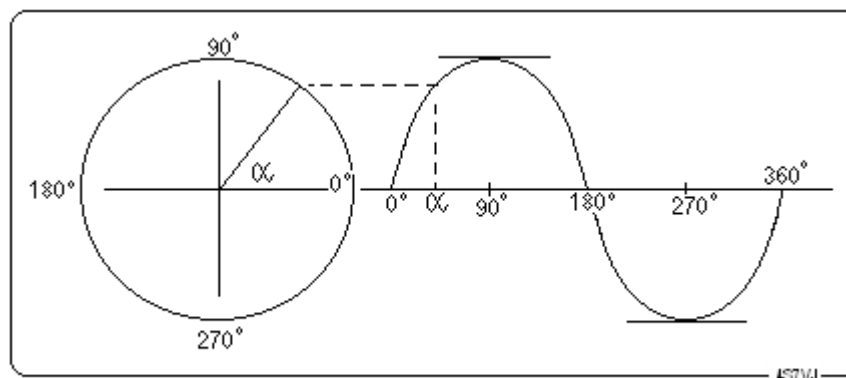


Fig. 3.1

#### 3.2.1 PHASE DIFFERENCE FOR RESISTORS

When a resistor connected to an a.c. supply, while the voltage across the resistor reaches maximum value, the current also reaches the maximum. In other word voltage and current are in phase; no phase difference.

#### 3.2.2 PHASE DIFFERENCE FOR CAPACITOR

When a capacitor connected to an a.c. supply, while the voltage across the capacitor reaches maximum value, the current will be zero. If you draw both graphs in the same diagram we can realize the phase angle of the voltage is  $90^\circ$  and for the current is  $180^\circ$ , for the above instant.

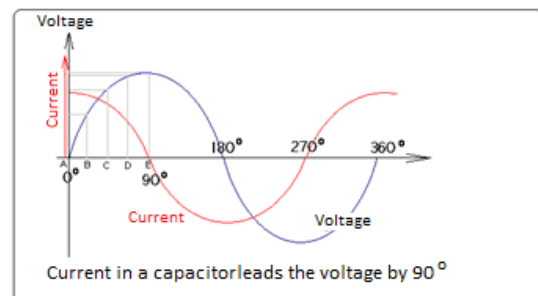


Fig 3.2

That means the current in the capacitor leads the applied voltage by  $90^\circ$ , or in other words the phase difference between the current and voltage is  $90^\circ$ .

### 3.2.3 PHASE DIFFERENCE FOR INDUCTANCE

When an inductor connected with an a.c. supply, the current is always lagging behind by  $90^\circ$  with the applied voltage, because of the induced back e.m.f.

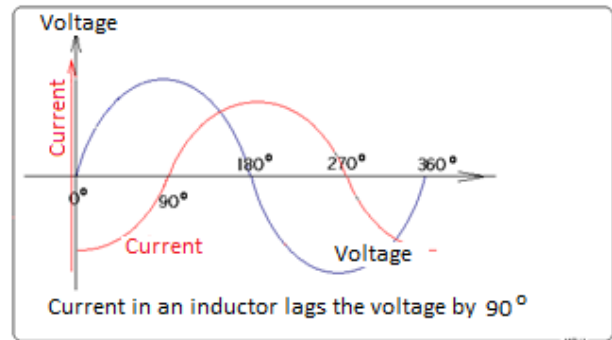


Fig 3.3

### 3.2.4 PHASE DIFFERENCE BETWEEN INDUCTANCE AND CAPACITANCE

If a pure inductor (L) and capacitor (C) are connected in series with a.c. supply, the current through the L and C are completely out of phase, or phase difference is  $180^\circ$ . The equivalent reactance of this series combination is

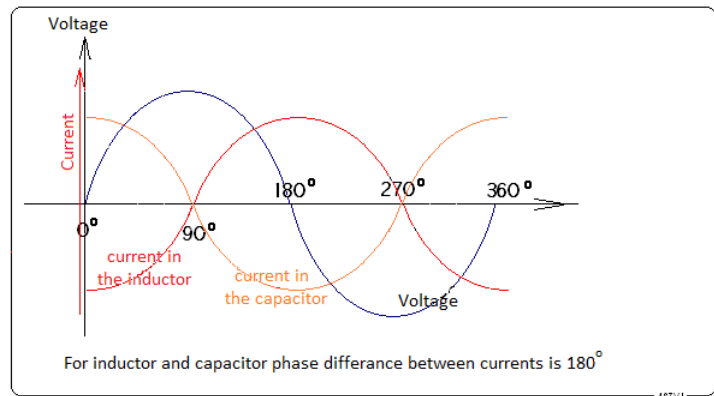


Fig 3.4

$$\mathbf{X = X_L - X_C} \quad \text{or} \quad \mathbf{X = X_C - X_L}$$

### 3.3 IMPEDANCE (Z)

When a circuit contains resistance, capacitance and inductance ( $X_C$  or  $X_L$  or both and  $R$ ) the combined effect of the three is called **IMPEDANCE** ( $Z$ ). Impedance is thus a more general term than either resistance or reactance. The unit is "Ohm". The relationship between them is as follows:-

$$\mathbf{Z^2 = X^2 + R^2}$$

or

$$\mathbf{Z = \sqrt{R^2 + X^2}}$$

Eg:- Resistance of an inductor is  $3 \Omega$  and the reactance for a given a.c. supply is  $4 \Omega$ . What is the impedance for this moment?

$$\begin{aligned} \text{apply } Z^2 &= R^2 + X^2, \quad R = 3, \quad X = 4 \\ \text{Therefore } Z^2 &= 3^2 + 4^2 = 9 + 16 = 25 \\ Z &= \sqrt{25} = \underline{\underline{5 \Omega}} \end{aligned}$$

### 3.3.1 OHM'S LAW FOR IMPEDANCE

Ohm's law can be applied to circuits containing impedance just as readily as to circuits having resistance or reactance only. The formula is

$$V = I Z$$

Where,  $Z$  = impedance

$V$  = voltage across the inductor

$I$  = Current through the inductor

#### **Example:-**

An inductor having a resistance of  $50 \Omega$  and a reactance of  $120 \Omega$  is connected to a  $130 \text{ V}$  a.c. supply. Find the current through the inductor and the power dissipation.

apply the formula

$$Z^2 = R^2 + X^2, R = 50 \Omega, X = 120 \Omega$$

$$\begin{aligned} \text{therefore } Z^2 &= 50^2 + 120^2 \\ &= 2500 + 14400 \\ &= 16900 \\ Z &= \sqrt{16900} \\ &= 130 \Omega \end{aligned}$$

for calculate the current, apply Ohm's law

$$V = I Z$$

$$\text{Therefore } I = V/Z$$

$$\text{Where } V = 130 \text{ volts, } Z = 130 \Omega$$

$$\begin{aligned} \text{then } I &= 130 / 130 \\ &= \underline{\underline{1 \text{ A}}} \end{aligned}$$

Power is dissipating through the resistance ( $50 \Omega$ ) only.

therefore apply,  $W = I^2 R$ ,  $I = 1\text{A}$ ,  $R = 50 \text{ Ohms}$

$$\begin{aligned} W &= 1 \times 1 \times 50 \\ &= \underline{\underline{50 \text{ Watts}}} \end{aligned}$$

## 3.4 RESONANCE

### 3.4.1 SERIES RESONANCE CIRCUIT

Suppose a capacitor is connected in series with an inductor and a source of a.c., (Fig. 3.5) the frequency of which can be varied over a wide range.

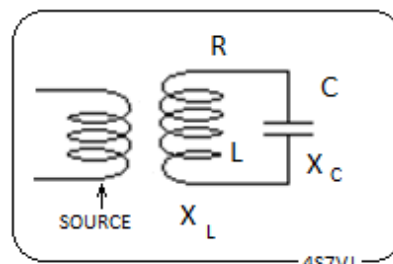


Fig 3.5

At some low frequency, the capacitive reactance ( $X_c$ ) will be much larger and the inductive reactance ( $X_L$ ) will be smaller. The resistance of the circuit ( $R$ ) is a constant, at any frequency ( $f$ ). On the other hand, at high frequencies  $X_L$  is a higher value and  $X_c$  is a smaller value. At one particular frequency  $X_L$  and  $X_c$  will be equal and the resultant inductance,

$$X = X_L - X_c = 0$$

Therefore the impedance is equal to the resistance. At this stage the current in the circuit will be **maximum**. This frequency is called "**RESONANCE FREQUENCY**" of the circuit.

### 3.4.1.1 RESONANCE FREQUENCY

The formula for the resonance frequency of tuned circuit is as follows:-

$$f = \frac{1}{2\pi\sqrt{LC}}$$

where,  $f$  = resonance frequency (Hz)

$L$  = inductance (H)

$C$  = capacitance (F)

$\pi$  =  $22/7 = 3.14$

Example:-

A  $5\mu\text{H}$  inductor and  $20\text{ pF}$  capacitor connected as a series resonance circuit. Calculate the resonance frequency.

apply the formula,

$$f = 1 / 2\pi\sqrt{LC}$$

$$L = 5\ \mu\text{H} = 5 \times 10^{-6}\ \text{H}$$

$$C = 20\ \text{pF} = 20 \times 10^{-12}\ \text{F}$$

$$\begin{aligned} \text{therefore } f &= 1 / [2 \times 3.14 \times \sqrt{(5 \times 10^{-6} \times 20 \times 10^{-12})}] \\ &= 1 / [6.28 \times \sqrt{100 \times (10^{-18})}] \\ &= 1 / [6.28 \times (10 \times 10^{-9})] \\ &= 0.1592 \times 10^8 \\ &= 15.92 \times 10^2\ \text{Hz} \\ &= \underline{\underline{15.92\ \text{MHz}}} \end{aligned}$$

### 3.4.1.2 RESONANCE CURVE

If a plot is drawn of the current flowing in the series resonance circuit vs the frequency is varied, it would look like the curve in the diagram. (Fig. 3.6)

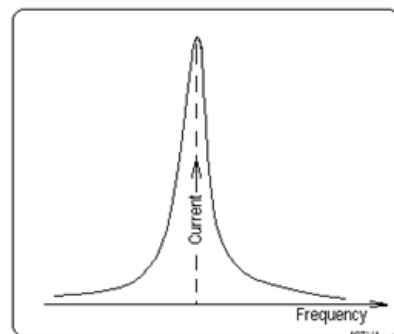


Fig-3.6

The shape of the resonance curve at frequencies near resonance is very sharp the sharpness of the curve is depend on the ratio of X/R of the circuit.

### 3.4.1.3 Q-FACTOR (quality factor)for series resonance circuits

X/R ratio of a **series resonance circuit** is defined as the quality factor. (Q-FACTOR)

$$Q = X / R$$

Q = Quality factor

X = Reactance of either coil or capacitor

R = Resistance of the coil

There is no unit for the Q-factor because it is only a ratio. If the reactance of the series resonance circuit is of the same order of magnitude as the resistance, that means low Q circuit, the current is varying rather slowly as the frequency is moved in either direction away from the resonance. Such a curve is said to be **broad**.

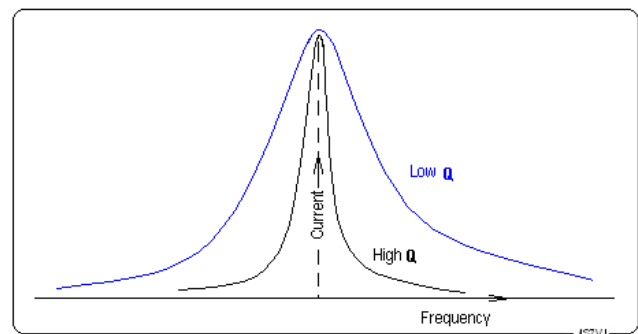


Fig 3.7

On the other hand if the reactance is considerably larger than the resistance, that means high Q circuit, the current is varying rapidly as the frequency moves away from the resonance and the circuit is said to be **sharp**. A sharp circuit will respond a great deal more readily to the resonant frequency than frequencies quite close to the resonance. Low-Q or broad circuit will respond almost equally for the band of frequencies centering around the resonant frequency.

#### 3.4.1.3.1 Another formula for Q-factor

$X_L = 2\pi fL$  (for coil) or  $X_C = 1/(2\pi fC)$ , (for capacitor)

Therefore  $Q = 2\pi fL/R$  or  $Q = 1/(2\pi fCR)$

Normally we represent  $2\pi f$  by Greek letter  $\omega$

Therefore  $\omega = 2\pi f$ ,  $Q = \omega L/R$  or  $Q = 1/\omega CR$

#### 3.4.1.4 SELECTIVITY

Selectivity is the ability to respond strongly at one desired frequency and discriminate against others. High-Q resonance circuits are essential to get more selectivity for

receivers, especially for communication receivers. But the low-Q circuits are useful for amplify a desired frequency band for the same receiver.

### 3.4.1.5 VOLTAGE RISE AT RESONANCE

When an a.c. voltage applied (induced signal voltage from the antenna for receivers Fig-3.8) to L-C circuit, if it is resonance the voltage appears across either the inductor or capacitor is considerably higher than the applied voltage. The ratio of the reactive voltage to the applied voltage is also equal to the Q-factor. That means:-

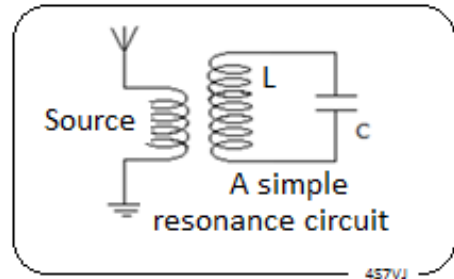


Fig 3.8

$$\text{the reactive voltage} = Q \times \text{applied voltage}$$

#### **Example:-**

For a series resonance circuit, the resultant of inductive and capacitive reactance is 300 Ohms, the resistance is 0.2 Ohms. What is the Q-factor?

If the applied voltage is 0.1V, What is the voltage across the capacitor or inductor?

$$\begin{aligned} \text{Q-factor} &= X / R, \quad X = 300, \quad R = 0.2 \\ \text{Therefore } Q &= 300/0.2 \\ &= \underline{\underline{1500}} \end{aligned}$$

$$\begin{aligned} \text{applied voltage} &= 0.1 \text{ volts} \\ \text{voltage across capacitor or inductor} &= 1500 \times 0.1 \\ &= \underline{\underline{150 \text{ v}}} \end{aligned}$$

### 3.4.2 PARALLEL RESONANCE CIRCUITS

When a variable frequency source of constant voltage applied to a parallel resonance circuit, there is a resonance effect similar to that in a series circuit. In this case the current drawn by the source is minimum at the maximum impedance of the circuit. Obviously that is the resonance frequency. At resonance frequency,  $X_L$  and  $X_C$  are equal but the current through the inductor and capacitor is completely out of phase and they are canceling each other.

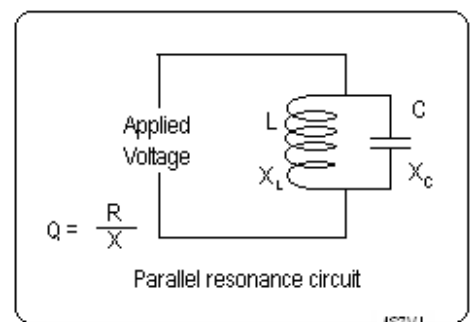


Fig 3.9



At frequencies below resonance, the current through L is larger than that through C, because  $X_L$  is smaller than  $X_C$ . There is only partially cancellation of the two reactive currents, and therefore the line current is larger than the current taken by R alone. At frequencies above resonance the situation is reversed and more current flows through C than L, so the line current again increases. At resonance the current is totally depend on the resistance of the coil. **Finally we can say for the parallel resonance circuit shows maximum impedance at the resonance.**

Practical applications for parallel resonance circuit are traps for multiband antennas and notch filters.

### 3.4.2.1 Q-FACTOR FOR PARALLEL RESONANCE CIRCUITS

For parallel resonance circuits, quality-factor is the reciprocal of that of a series

$$Q = R / X$$

$X = 2\pi fL$  (for coil) or  $X = 1/(2\pi fC)$ , (for capacitor)  
Therefore  $Q = R/2\pi fL$  or  $Q = 2\pi fCR$

Normally we represent  $2\pi f$  by Greek letter  $\omega$   
Therefore  $\omega = 2\pi f$ ,  $Q = R/\omega L$  or  $Q = \omega CR$

### 3.4.3 APPLICATIONS OF RESONANCE CIRCUITS

#### 3.4.3.1 SERIES RESONANCE CIRCUITS

These are very useful for various tuning stages of receivers and transmitters. For receivers high-Q series resonance circuits are useful for good selectivity. Low-Q circuits are useful for RF amplifier stage for amplify whole frequency band.

#### 3.4.3.2 PARALLEL RESONANCE CIRCUITS

Parallel resonance circuits are useful for traps of multi band antenna systems. Normally these are low-Q circuits because those are acting like rejecter circuit for a particular frequency band.

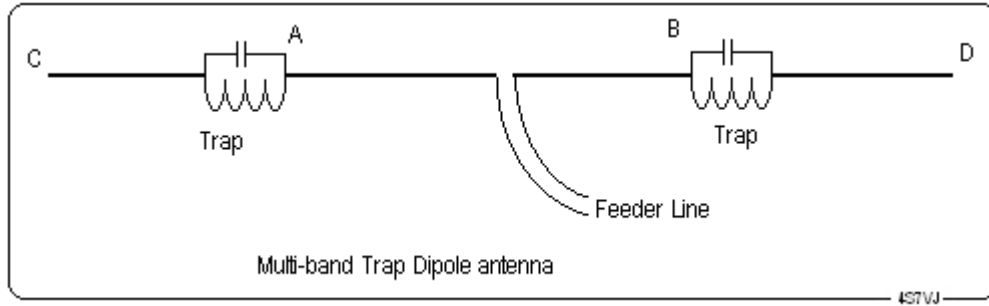


Fig 3.10

Fig. 3.10 shows a multi band dipole antenna. For example if it is designed for 15m (21 - 21.450 MHz) and 20m (14 - 14.350) bands, both traps (identical LC resonance circuits) must be tuned for 15m band. If any signal (TX or RX) reaches within 15m band both traps are resonating and acting as high impedance. Then the active part of the antenna is limited to "AB" portion; for 20m band signals both traps having very low (about 0.1 Ohm or less) impedance. Then whole "CD" portion is acting as the antenna.

### 3.5 TRANSFORMERS

Two coils having mutual inductance constitute a transformer. The coil connected to the source of energy is called primary coil and the other one is the secondary coil. A transformer can be used only with a.c., because for d.c., no voltage will be induced in the secondary coil since the magnetic field is not varying.

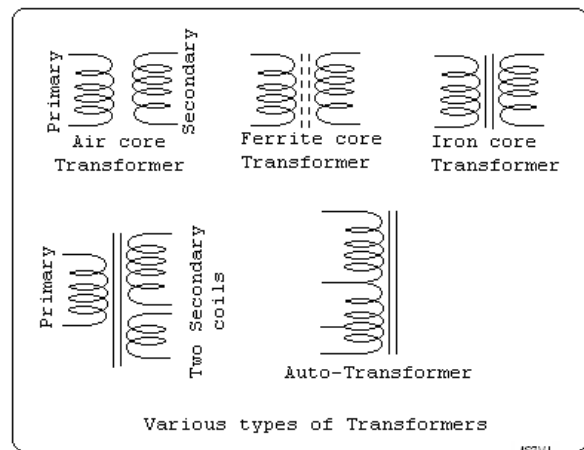


Fig 3.11

The main purpose of the transformer is changing voltage according to the requirements. Step-up transformer will be increasing the voltage and step-down will be decreasing the voltage.

### **3.5.1 VARIES TYPES OF TRANSFORMERS**

Symbols for a few numbers of transformers are shown in Fig-3.11. Soft iron core transformers are used for a.c. having low frequencies. Ferrite core transformers are used for HF work and air core used for VHF and higher frequencies.

#### **3.5.1.1 AUTOTRANSFORMER**

The principle of the transformer can be utilized with only one winding instead of two; the principles just discussed apply equally well to the earlier transformers as well.

A single winding transformer is called an autotransformer (Fig. 3.11). The current in the common section of the winding is difference between the line (primary) and the load (secondary) , since these currents are out of phase. Hence if the line and load currents are nearly equal the common section of the winding may be wound with a thinner wire. The autotransformer is used chiefly for boosting or reducing the power line voltage by relatively small amounts.

Continuously variable auto transformers are used for automatic a.c. voltage stabilizers.

#### **3.5.2 VOLTAGE, CURRENT & TURNS RATIO**

For a sine wave a.c. supply, the voltage is proportional to the number of turns. Therefore the ratio of the voltages of primary and secondary coils is equals to the ratio of number of turns.

$$V_s/V_p = N_s/N_p$$

Where,

$V_p$  = primary applied voltage

$V_s$  = secondary induced voltage

$N_p$  = number of turns on primary

$N_s$  = number of turns on secondary

#### **CURRENT & TURNS RATIO**

If we assumed that the efficiency = 100% then the current is inversely proportional to the number of turns.

$$I_s/I_p = N_p/N_s$$

Where,

$I_s$  = secondary current

$I_p$  = primary current

$N_s$  = no. of turns on secondary

$N_p$  = no. of turns on primary

The actual current in the secondary winding is always slightly less than the theoretical value of secondary current because the efficiency slightly less than 100%.

**Example:-**

A transformer has a primary of 920 turns and applied voltage is 230 volts. There are two secondary coils. Voltages will be 1200 volts and 12 volts.

What is the voltage per turn and what will be the number of turns for both secondary coils.

$$\begin{aligned} \text{voltage for 920 turns} &= 230\text{V} \\ \text{voltage per turn} &= 230/920 \\ &= \underline{\underline{0.25 \text{ volts/turn}}} \end{aligned}$$

1st method:-

for 1200 v. secondary:-

$$\begin{aligned} N_s/N_p &= V_s/V_p \\ V_p &= 230, \quad V_s = 1200, \quad N_p = 920 \\ N_s &= N_p \times V_s / V_p \\ &= 920 \times 1200 / 230 \\ &= 4 \times 1200 \\ &= \underline{\underline{4800 \text{ turns}}} \end{aligned}$$

for 12 v. secondary:-

$$\begin{aligned} V_p &= 230, \quad V_s = 12, \quad N_p = 920 \\ N_s &= N_p \times V_s / V_p \\ &= 920 \times 12 / 230 \\ &= 4 \times 12 \\ &= \underline{\underline{48 \text{ turns}}} \end{aligned}$$

2nd method:-

$$\begin{aligned} \text{Volts per turn} &= 0.25 \\ \text{Therefore turns per volt} &= 1/0.25 = 4 \\ \text{no. of turns for 1 volt} &= 4 \\ \text{no. of turns for 1200 v} &= 4 \times 1200 \\ &= \underline{\underline{4800 \text{ turns}}} \\ \\ \text{no. of turns for 12 v} &= 4 \times 12 \\ &= \underline{\underline{48 \text{ turns}}} \end{aligned}$$

**3.5.3 EFFICIENCY & POWER**

A transformer can only transfer power with different e.m.f. Hence, the power taken from the secondary cannot exceed that taken by the primary from the source. There is always some power loss in the resistance of the coils and the core material so practically the power output is slightly less than the power input.

$$\text{efficiency} = \text{power output}/\text{power input}, \text{ (less than 1)}$$

OR

$$\text{efficiency} = 100 \times (\text{power output}/\text{power input}) \%$$

Normally efficiency is represented by a percentage.

The efficiency is always slightly less than 100%. Construction of a transformer is shown in Fig 3.12. It is a low frequency transformer made by using soft iron core and copper wires. There are three types of power losses in these transformers. The first loss is the heat generated in windings due to the resistance ( $I^2R$ ). But this is a negligible amount. The other two are hysteresis loss and eddy current loss.

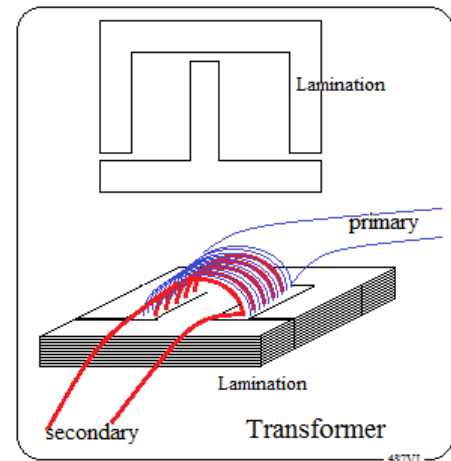


Fig-3.12

### **3.5.3.1 HYSTERISIS LOSS**

Due to the current flow of the primary coil, the soft iron core becomes a temporary magnet because almost all the molecules turn to one direction due to the magnetic field generated by that current. The next moment the direction of the current turns to the reverse. According to this all the molecules turn in the opposite direction. This creates heat and it is a loss of energy. This loss is called as hysteresis loss. This is minimum for soft iron.

### **3.5.3.2 EDDY CURRENT LOSS**

When the a.c. current flows through the primary coil, a current is induced through any conductors nearby. These currents in the core are called eddy currents. The heat generates due to eddy current is called **eddy current loss**. In order to minimize this eddy current losses soft iron core laminates are used.

### **3.5.4 MAGNETIZING CURRENT**

The current that flows in the primary when no power is taken from the secondary (secondary is open) is called the magnetizing current of the transformer. In the normal operations the magnetizing current should be very small in comparison with the primary load - current at the rated power output.

### **3.5.5 IMPEDENCE OF TRANSFORMER**

For transformers  $V_s/V_p = N_s/N_p$  and  $I_s/I_p = N_p/N_s$  (paragraph 3.5.2)

$V_p$  = Applied voltage at the primary coil (input)

$V_s$  = voltage at the secondary coil (output)

$N_p$  = Number of turns at the primary coil

$N_s$  = Number of turns at the secondary coil

$I_p$  = current at the primary coil,

$I_s$  = current at the secondary coil

Let the impedance of the primary coil is  $Z_p$  and the load impedance at the secondary is  $Z_s$

According to the Ohm's law  $V_p = I_p Z_p$  and  $V_s = I_s Z_s$   
Substitute this to first equation.

$$I_s Z_s / I_p Z_p = N_s / N_p$$

$$\text{Therefore } (I_s / I_p) \times (Z_s / Z_p) = N_s / N_p$$

$$\text{But } I_s / I_p = N_p / N_s$$

$$\text{Therefore } (N_p / N_s) \times (Z_s / Z_p) = N_s / N_p$$

$$\text{Therefore } Z_s / Z_p = (N_s / N_p) \times (N_p / N_s) = (N_s / N_p)^2$$

$$\mathbf{Z_s / Z_p = (N_s / N_p)^2 \text{ or } N_s / N_p = \sqrt{(Z_s / Z_p)}}$$

are very useful formulae.

Example :-

A transistor AF amplifier requires a load of 100 Ohms for optimum performance, and is to be connected a loudspeaker having an impedance of 8 Ohms. What is the turns ratio of the suitable transformer?

We can use the formula of  $N_s / N_p = \sqrt{(Z_s / Z_p)}$

$$Z_s = 8\Omega, \quad Z_p = 100\Omega$$

$$\text{Therefore } N_s / N_p = \sqrt{(8/100)} = \underline{0.282} \text{ or } N_p / N_s = \underline{3.55}$$

### 3.6 THE DECIBEL

#### 3.6.1 Comparison of Power Ratios

It is useful to appraise signal strength in terms of relative loudness as registered by the ear. For example, if a person estimates that a signal is twice as loud when the transmitter power is increased from 10 to 100 watts. He or she will also estimate that a 1000w signal is twice as loud as a 100w signal. The human ear has a logarithmic response. This fact is a basis for the use of the relative power unit called the decibel (dB). A decibel is one-tenth of a Bel. The number of decibels corresponding to a given power levels of P1 and P2 is given by,

$$\mathbf{dB = 10 \text{ Log}(P2/P1)}$$

It is convenient to memorize the decibel values for few of the common power ratios. A change of 1 dB in power level is just detectable as a change in loudness under ideal conditions. Double the power is 3 dB gain, 4 times is 6dB, 10 times is 10 dB, 100 times is 20dB, 1000 times is 30 dB, million times is 60 dB.

If P2 is smaller than P1,  $(P2/P1) < 1$  (decimal value) and there is no gain, it is a power loss or attenuation. For example input power = 1mW and output is 0.01mW, then  $P2/P1 = 0.01/1 = 0.01$ ,  $dB = 10\text{Log}(0.01) = -20$  Therefore power gain is -20dB. In another word power loss or attenuation is 20dB.

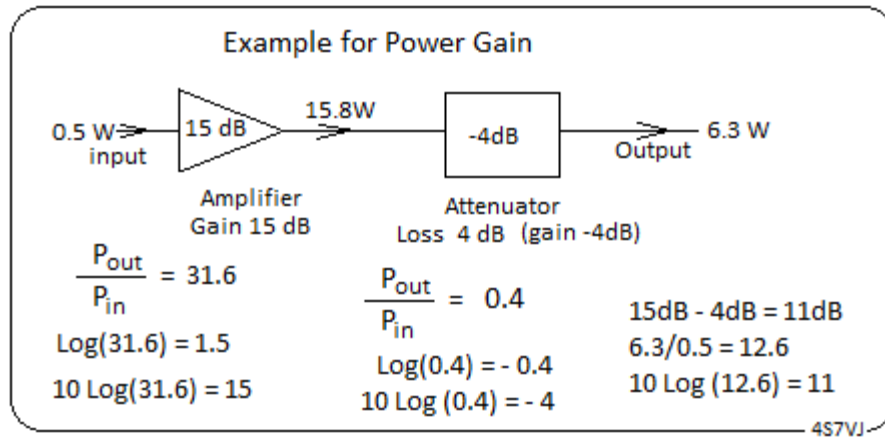


Fig 3.13

### 3.6.2 Comparison of Voltage and Current ratios

The decibel is based on power ratios. Voltage or current ratios can be used, but only when the impedance is the same (input and output) for both value voltage or current.

If the given power levels are  $P_1$ ,  $P_2$  and respective voltages are  $V_1$ ,  $V_2$  (for the same impedance of  $Z$ )

Then  $P_1/P_2 = (V_1/V_2)^2$  because  $P_1=V_1^2/Z$ ,  $P_2=V_2^2/Z$

Then  $\text{dB} = 10\text{Log}(P_1/P_2) = 10\text{Log}(V_1/V_2)^2 = 20\text{Log}(V_1/V_2)$

Therefore  $\text{dB} = 20 \text{Log}(V_2/V_1)$

$\text{dB} = 20 \text{Log}(I_2/I_1)$

### 3.6.3 Absolute value for decibel

#### 3.6.3.1 Absolute value for acoustic

The decibel is a relative unit. When using decibels to specify an absolute power, voltage or current level, the decibel value must be qualified by a reference level. For example, in a discussion of sound intensity, a reference level of 1 dB corresponds to an acoustical field strength of  $10^{-16} \text{ W/cm}^2$ , the normal human hearing threshold at 600 Hz and the threshold of pain occurs at 130 dB.

#### 3.6.3.2 Absolute value for power gain (dBW and dBm)

In radio work power is often rendered in dBW, when the reference level taken as 1 watt and dBm for 1mW reference level.

Few examples with this notation:-

- (i) 1kW is equivalent to 30dBW or 60dBm.
- (ii) 500W is equivalent to 26.9dBW or 57dBm
- (iii) 100W is equivalent to 20dBW or 50dBm
- (iv) 1W is equivalent to 0dBW or 30dBm
- (v) 100mW is equivalent to -10dBW or 20dBm
- (vi) 50 $\mu$ W is equivalent to -43dBW or -13dBm

### 3.6.3.3 Absolute value for voltage gain (dBV and dB $\mu$ V)

Voltages are some times given as decibel values with respect to 1 volt or 1 micro-volt.

Few examples:-

- (i) 5V is equivalent to 14dBV or 134dB $\mu$ V
- (ii) 100mV is equivalent to -20dBV or 100dB $\mu$ V
- (iii) 1 $\mu$ V is equivalent to -120dBV or 0dB $\mu$ V

### 3.7 Power Factor

I used the primary winding of a small power transformer as a choke coil and connected to AC mains supply in series with a capacitor of 2 $\mu$ F/300V (Fig 3.14) and these are the observations:

Resistance of the choke coil,  $R = 2140$  Ohms

Inductance of the choke coil,  $L = 15$  H (measured with DMM) and following readings were taken from clip-on ammeter and Digital Multimeter.

Applied voltage,  $V = 215$  volts

Current through the circuit,  $I = 23.3\text{mA} = 0.0233$  A

Voltage across the choke,  $V_L = 242$  volts (greater than the applied voltage)

Voltage across the capacitor,  $V_C = 35$  volts

Apparent power in the whole circuit =  $215 \times 0.0233$   
= 5 VA, (or 5watts)

Normally we use the unit as "VA" (Volt Ampere) instead of watts because this is an apparent power, not the actual power.

Actual power or the power loss in the inductor (choke coil),  
 $I^2R = 0.0233^2 \times 2140 = 1.16$  Watts

**The ratio of the power consumed to the apparent power is called the "Power Factor" of the circuit.,** and in this example the power factor would be  $1.16/5 = 0.23 = 23\%$

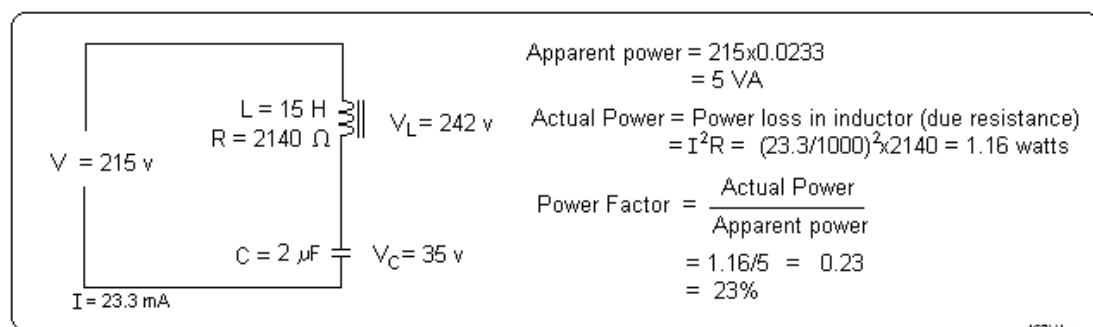


Fig. 3.14



### **3.7.1 Power Factor for Resistor and Inductor**

The power factor of a purely resistive circuit is 1 or 100%, while the power factor of a pure reactance is zero.

### **3.7.2 Cos $\phi$**

If the phase difference between the current and the voltage is  $\phi$  then the power factor is equal to  $\cos\phi$

### **3.7.3 Practical Importance of the Power Factor**

If we connected a suitable capacitor with any electrical equipment having an inductance, (motor, fluorescent light transformer, choke coil etc.) the power factor will be increase and we can get two advantages.

1. The efficiency of the equipment will be increase.
2. The consumption of electrical energy will be reduced, that means reduce the electricity bill.

\*\*\*\*\*

**EXERCISE**

**3.1** What is the reactance of a capacitor having  $1.5 \mu\text{F}$  for 50 Hz, 230 V ac-supply. What is the current flow.

(ans:-  $2.1 \text{ k}\Omega$ , 0.1 A)

**3.2** An inductor of 2 H. is connected to a 240 V 50 Hz supply What is the inductive reactance ? If the resistance is negligible, what is the current flow?

(ans:-  $628 \Omega$ , 366 mA)

**3.3** An inductor having  $4 \mu\text{H}$  is connected with a capacitor of  $100 \text{ pF}$  connected as a series resonance circuit. calculate the resonance frequency.

(ans:-7.96 MHz or 7960 kHz)

**3.4** In a series resonance circuit, the inductor and capacitor each have a reactance of 200 Ohms at the resonant frequency. The resistance is 0.1 Ohms. What is the Q-factor of the circuit? If 10 mV applied to the circuit, What is the voltage across the capacitor or inductor at resonance?

( ans:- 2000, 20 Volts )

**3.5** A transformer has a primary of 1100 turns and applied voltage is 220 volts. Centre tapped secondary voltages will be 12+12 V. What is the voltage per turn and what will be the number of turns for both secondary coils.

(ans:- 0.2 V/turn, 60+60 turns)

**3.6** The secondary coil of a step-down transformer is 6V 2A and 50 turns. What is the number of turns and current consumption of the primary for 240 V ac supply?

(ans:- 2000 turns, 50mA)

**3.7** If the input power of an amplifier is 10 watts, the power output will be 400 watts. What is the power gain ?

( ans:- 16 dB )

**3.8** Power gain of a pre-amplifier is 50dB. It is coupled with a power amplifier having 20dB gain. What is the total power gain of the system?

If the input power is  $1 \mu\text{W}$ , what is the power output of the pre-amplifier and the final power output?

( ans:-70dB, 100mW, 10W )

**3.9** The antenna gain is 6dB for a directional antenna. What is the dBi value for this antenna?

(ans:- 8.14 dBi)

**3.10** A choke coil having an inductance of 10H and a resistance of  $3k\Omega$ , connected with a capacitor having  $4.7\mu\text{F}$  and connected in series with 230V, 50Hz ac mains supply. What is the power factor of the system?

(Ans:- 0.76 or 76%)