



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Sep 1963

Title: New Approach to Receiver Front-End Design, A

Author: William Squires, W2PUL

[Click Here to Report a Problem with this File](#)



2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001

Only \$24.95*

*plus shipping and handling

Additional sets available:


2009 Ed., ARRL Order No. 1486, \$24.95
 2008 Ed., ARRL Order No. 9406, \$24.95
 2007 Ed., ARRL Order No. 1204, \$19.95
 2006 Ed., ARRL Order No. 9841, \$19.95
 2005 Ed., ARRL Order No. 9574, \$19.95
 2004 Ed., ARRL Order No. 9396, \$19.95
 2003 Ed., ARRL Order No. 9124, \$19.95
 2002 Ed., ARRL Order No. 8802, \$19.95
 2001 Ed., ARRL Order No. 8632, \$19.95



ARRL The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.
 ONLINE WWW.ARRL.ORG/SHOP
 ORDER TOLL-FREE 888/277-5289 (US)

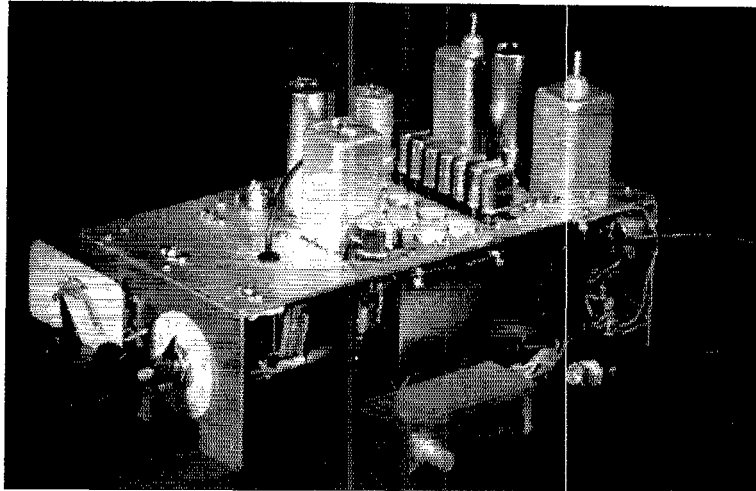Improved Performance with a Beam-Deflection Mixer



An experimental receiver front end using two beam-deflection mixers.

A New Approach to Receiver Front-End Design

BY WILLIAM K. SQUIRES,* W2PUL

Six years ago some of the principal weaknesses of contemporary communications receivers were outlined and a technique for alleviating at least some of the ills was described¹. At that time it was pointed out that overload and cross modulation were serious offenders and that "modern" multiple-conversion receivers behaved extremely badly in this respect. Six years later, most still do.

CURRENT receivers, having two or three stages of conversion plus one (or two) r.f. stages before any appreciable selectivity, perform very poorly under exactly those conditions that are most important, when the desired signal is weak and the undesired signal is strong. Even though the receiver's stated selectivity is superb and should be capable of rejecting the unwanted strong signal, cross modulation and overload result in the strong signal "riding through", often in the form of key clicks, "monkey chatter," squeaks and apparent noise. Often the operator is unaware of his receiver's misbehavior; he assumes

*% Squires-Sanders, Inc., 475 Watchung Av., Watchung, N. J.

¹ Goodman, "What's Wrong with our Present Receivers?", *QST*, January, 1957.

the band is that crowded and noisy. But some of those commercial radioteletype stations, foreign phones, and big military signals are not even in the amateur bands!

While *cross modulation* and *overload* are not the only deficiencies (spurious responses, tweets, and inadequate i.f. and image rejections are frequent offenders), the major attention in this article will be toward describing techniques for reducing both of these deficiencies while simultaneously offering a number of performance advantages.

General Principles


First, the principles outlined by Goodman² are still very valid:

- 1) As little gain as possible before taking full selectivity.
- 2) Superb linearity in any stage preceding selectivity.

To achieve (1), the ideal receiver should have *no r.f. stage* and have as few conversions as possible. Then what about sensitivity? Image and i.f. rejection? Oscillator radiation? We have been taught over the years that the more r.f. stages — and the more conversions — the better the receiver. But r.f. stages are simply an apology for poor mixer performance and inadequate image re-

² Op. cit.

Fig. 2—Image rejection circuits. (A) Local oscillator below signal. (B) Local oscillator above signal.

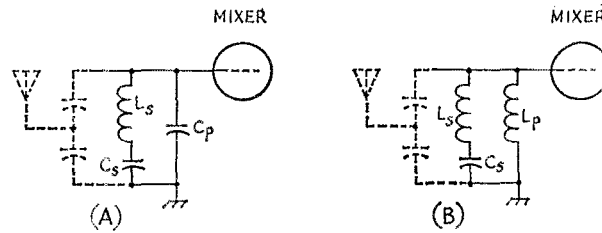

behavior is superb. With this circuit, followed immediately with a steep-skirted crystal bandpass filter, the following measurements were made.

Two signal generators (properly isolated and matched to the antenna input impedance) were used. One, the *signal*, was set at 2 μv .; the other, the *unwanted*, was set to 100,000 μv . The front end was tuned, of course, to the weaker signal. Then the unwanted was tuned as closely as possible to the signal frequency until interference was just barely discernable. Both generators were 30 per cent modulated at 400 c.p.s. With two different bandpass filters, the following results were obtained:

Signal = 2 μv . Unwanted = 100,000 μv .
 (+ 94 db. above signal)

Filter Bandwidth	Unwanted (Frequency from Signal)	
	- 6 db. (s.s.b.)	- 60 db. (c.w.)
2.5 kc.	5.0 kc.	14 kc.
.35 kc.	1.7 kc.	9 kc.

This means that when receiving a weak (2- μv .) s.s.b. signal, an unwanted signal only 14 kc. away must be 94 db. stronger — to be just noticeable. (That's about S9 + 60 db. on an honest S meter).

Placing the unwanted signal 100 kc. away (to simulate a big local, or an out-of-band commercial) and increasing the level of the unwanted until a just noticeable reduction in signal level occurred (using the same filters) required 400,000 μv . to just affect a 1- μv . signal. When the unwanted signal was increased still further, it required 1,500,000 microvolts (yes, 1.5 volts), to produce a 3-db. reduction in wanted-signal output.

With cross modulation and overload well in hand, the next question is what kind of sensitivity, or noise figure, can be obtained.

Sensitivity

Although limited by outside (high antenna noise temperature) noise on the h.f. bands, low noise is still of some importance — and of course increasingly so as we go above 20 Mc. Theoretical analysis of the 7360 tube indicated excellent noise characteristics below 30 Mc. before the onset of transit time loading. The calculated value of the equivalent shot-noise resistance was 1500 ohms, leading to a calculated 5.3-db. noise figure (with 20-db. conversion gain) at 30 Mc. Measured noise figures are listed below:

Req. Mc.	Noise figure, db.
29.5	5.5
21.25	4.4
14.25	4.3

This results in about 0.4 μv . for 10-db. (S + N)/N sensitivity in typical s.s.b. bandwidths on 10 meters, which is more than adequate (goodbye r.f. stage!).

Image Rejection

With single conversion and no r.f. stage the problem of obtaining good image rejection remains. Either a comfortably high i.f. can be used (*à la* Goodman), or something must be done in the input circuit of the mixer. An extremely useful technique, particularly for our relatively narrow amateur bands is to employ an "image-rejection circuit" of the types shown in Fig. 2.

When the local oscillator frequency is below the signal, 2A is used and L_s and C_s are made series-resonant (and low impedance) at the image frequency. For any h.f. band except 10 meters they may be set at the center of the band minus twice i.f. and left alone. Then at the signal frequency, L_s and C_s look inductive and are parallel-resonated with C_p .

When the local oscillator is above the signal, 2B is used, and L_s and C_s are set at the image as before. At signal frequency they look capacitive and are resonated by L_p .

As a result, a curve of impedance versus frequency as shown in Fig. 3 results, using circuit 2A. The degree of image rejection is simply the ratio of the two impedances Z_s/Z_i (ignoring antenna-coupling effects). With coil Q_s of 200 and good shielding and grounding, measured rejection on 10 meters, with a 1.0-Mc. i.f., was greater than 90 db. With Q_s of 150, a 1.0-Mc. i.f., and normal care, 60 db. can be readily obtained on any h.f. amateur band. The "rejection notch" remains relatively broad and need not be tuned over an amateur band, except in covering 10 meters at one bite. The signal peak must be tuned for best sensitivity, but this is done with the usual antenna trimmer.

Summary

To obtain really good cross modulation and

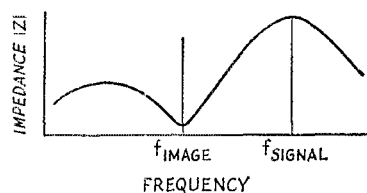


Fig. 3—Impedance curve of the image-rejection circuit of Fig. 2-A.

overload behavior, the r.f. stage must be eliminated and as few highly linear mixers used as possible, so that full selectivity is taken promptly after mixing. Using a beam-deflection tube as a balanced low-level mixer, high conversion gain, good i.f. rejection, and low noise can be obtained together with extremely linear operation—and consequent freedom from cross modulation. However, with no r.f.-stage selectivity, either a very high i.f., or unconventional image-rejection circuits must be used to obtain adequate attenuation of image frequencies. For amateur band use such circuits are comparatively simple, need not be tuned once set, and provide from 60 to 90 db. of rejection.

The resulting "front-end", followed by a steep-skirted crystal bandpass filter, produces the expected results. On-the-air use shows a remarkable ability to "dig out the weak ones", particularly when the band is crowded with big signals. The bands appear refreshingly cleaner and many of those "foreign phones" are gone. There is no wilting, collapse or distortion on big locals (in a really tough location, *delayed* a.g.c. can be applied to the 7360). Since the front end does not overload or "hang-up" on noise pulses the suggestion of protecting the *i.f.* with a *pre-i.f. silencer* appears attractive. This has been done with genuinely amazing results, as will be described in a subsequent article. QST

Strays

When W9CN and K6KP got together recently on s.s.b., it was their first meeting in thirty-seven years. They had met in April, 1926, when Art was W9CN and Lee was signing 3JK in Maple Shade, New Jersey.

Speaking of the old days, WA4LIG tells us this one. Seems that an amateur friend, using a carbon mike coupled to the plate coil of his transmitter, started to say "hello" into the microphone when it exploded, blackening his face and filling his mouth with mica and smoke. He later found that his young brother, curious tyke, had taken the microphone apart, spilled the carbon granules, and replaced the carbon with shotgun powder.

K1YMY was first licensed thirty years ago while he was a high school student. His first QSO was with W1AAJ. Followed 25 years' inactivity as a ham until last summer, when Dick was assigned his present call. His first contact? Sure — W1AAJ!

To the ARRL's new Newington, Connecticut address has been added the "Zip" number 06111. Use it when you write League Headquarters. The Zip code number should be placed two spaces to the right of the state.

The Tower ARC is appropriately named: their beam antenna is 465 feet above New York's Madison Avenue, on the roof of the Metropolitan Life Insurance Building. Tower members are Metropolitan employees.

Passengers in the same jet flight to England recently, and in adjacent seats, were four hams: WA2WQA, K2MHH, W3HZP, and K7LTT.

Calling all dental hams: Doctor Matt Eisenman, K3LEC, will speak on amateur radio at the American Dental Association Convention in Atlantic City, New Jersey, October 16. Dentist-hams are invited to join a Dental Ham Net. For information, write Matt at 907 Jefferson Street, Wilmington, Del.

FEEDBACK

In the circuit for the Two-Tone Test Oscillator (page 20, July QST), the resistor labeled 68K

should have been 6800 ohms — the same as the resistor to its right.

In the circuit diagram of the "High Quality Speech Compressor," page 21 of the February, 1963 issue, the 470-pf. capacitor *C*₃ has been labeled twice, possibly causing some uncertainty as to the value of the adjacent cathode resistor. The cathode resistor is 10K, and the grid resistor 2.2 megohms.

In the circuit diagram of W4KCW's d.s.b. transmitter on page 26 of the April, 1963 issue, the No. 1 and No. 2 grids of the lower 6BQ6GTB have been interposed. The pin numbering is, however, correct as shown.



September 1938

... J. A. Pierce, W1JFO, summarized 1938's exciting experiments in five-meter DX. The big news of the month was the announcement of the first "trans-con" QSO on 56 Mc. W6DNS and W1EYM did it.

... Clinton B. deSoto reported on "Ham Radio and Model Airplane Control," an aspect of hamming then only two years old. (For model control a quarter-century later, see the cover of this issue and page 11).

... The winners of the 1938 W/VE contest were announced. First place went to VE2EE. The U.S. winner was W6MVK.

... W3EMM and W3BEK detailed the efforts of Norfolk, Virginia amateurs to establish a city-sponsored emergency communications system, one of the country's first.

... And technical features included a W1CC five-band 807 exciter with crystal or e.c. oscillator control; a deluxe rotary beam support by W9TMP; portable equipment used by the Norfolk emergency communicators; and a W1TS auxiliary transmitter for 160 and 80 meters. QST