



Care and
Feeding of
Power Grid
Tubes

CARE AND FEEDING OF POWER GRID TUBES

Copy right © 1967 by Varian. All right reserved. Printed in the United States of America. This book, or parts thereof may not be reproduced in any form without permission of the publisher.

LIBRARY OF CONGRESS NO. 67-30070

Table of Contents

SECTION I **1**

INTRODUCTION **1**

SECTION 2 **3**

WHAT IS A POWER GRID TUBE? **3**

2.1 TRIODES **3**

2.2 BEAM TETRODE **8**

2.3 PENTODES **13**

2.4 INDUCTIVE OUTPUT TUBE (IOT) **14**

2.5 MULTISTAGE DEPRESSED COLLECTOR IOT (MSDC IOT) **21**

2.6 CATHODE EMITTERS **23**

SECTION 3 **28**

ELECTRICAL DESIGN CONSIDERATIONS **28**

3.1 CLASS OF OPERATION **28**

3.2 TUBE PERFORMANCE COMPUTER FOR R-F AMPLIFIERS **30**

3.3 TYPICAL R-F AMPLIFIER CIRCUIT DESIGNS **44**

3.4	COMPONENT PARTS	50
3.5	LEAD LENGTHS	51
3.6	FILAMENT BY-PASSING	51
3.7	SCREEN AND SUPPRESSOR GRID BY-PASSING AND SCREEN TUNING	52
3.8	GROUND-GRID CIRCUITS	53
3.9	PROTECTION	53
3.10	KEYING	56
3.11	AMPLITUDE MODULATION	57
3.12	POWER SUPPLY CONSIDERATION	59
3.13	STABILIZING THE AMPLIFIER	61

SECTION 4 66

LINEAR AMPLIFIER AND SINGLE SIDEBAND SERVICE 66

4.1	WHY SINGLE SIDEBAND	66
4.2	RATING TUBES FOR LINEAR AMPLIFIER SERVICE	67
4.3	SELECTION OF TUBES FOR SINGLE SIDEBAND SERVICE	75
4.4	LINEAR AMPLIFIER DESIGN	83
4.5	ADJUSTING AND MONITORING THE LINEAR AMPLIFIER	87

SECTION 5 **90**

NEUTRALIZATION **90**

- 5.1 NEUTRALIZATION BELOW VHF 90**
- 5.2 PUSH-PULL NEUTRALIZATION 92**
- 5.3 SINGLE-ENDED NEUTRALIZATION 92**
- 5.4 NEUTRALIZING GROUNDED-GRID AMPLIFIERS 94**
- 5.5 NEUTRALIZATION PROCEDURE 98**
- 5.6 SELF-NEUTRALIZING FREQUENCIES OF TETRODES AND PENTODES 101**

SECTION 6 **106**

VARIOUS APPLICATIONS **106**

- 6.1 ADJUSTMENT OF LOADING AND EXCITATION 106**
- 6.2 OPERATING VOLTAGES AND CURRENTS 107**
- 6.3 EFFECT OF DIFFERENT SCREEN VOLTAGES 108**
- 6.4 THE THREE HALVES POWER LAW 108**
- 6.5 BALANCE OF AMPLIFIERS 110**
- 6.6 HARMONIC AMPLIFIER AND CONTROL OF HARMONICS 111**
- 6.7 SHIELDING 113**
- 6.8 DRIVE POWER REQUIREMENTS 115**

- 6.9 VHF AND UHF OPERATING CONDITIONS FOR
SATISFACTORY PLATE EFFICIENCY AND
MINIMUM DRIVE 117**
- 6.10 COOLING TECHNIQUES 119**
- 6.11 TUBE LIFE 151**

Illustrations

Figure 1:	Constant current characteristics of a triode with a μ of 12.	5
Figure 2:	Constant current characteristics of a triode with a μ of 20.	5
Figure 3:	A typical set of grounded-grid constant current curves for a zero-bias triode with a μ of 200.	6
Figure 4:	Internal configuration of a planar triode.	7
Figure 5:	Incorrect screen circuit for tube requiring low impedance screen supply.	10
Figure 6:	A correct screen circuit for tube requiring low impedance screen supply.	11
Figure 7:	Another approach to swamping the screen circuit.	11
Figure 8:	Typical curve of grid current as a function of control grid voltage for a high power thoriated tungsten filament tetrode.	12
Figure 9:	Secondary-emission characteristics of the metals under ordinary conditions. The curve shows the ratio of the number of secondary to primary electrons for various primary-electron impact velocities expressed in volts. (After Harries.).....	13
Figure 10:	Eimac K2 IOT Amplifier	17
Figure 11:	Eimac K2 Inductive Output Tube	18
Figure 12:	Typical tuning curves for UHF TV IOT. The lower curve is the reflected drive signal. The upper curve shows the output tuning.	20
Figure 13:	Equipotential Lines in a three stage collector. The potentials are determined by collector geometry and collector voltages.	22
Figure 14:	Electron trajectories at near to ideal power. The tube gap is at the left side of the image, which is only half the collector. The right collector element is at cathode to anode potential. The middle section is approximately half the cathode	22
Figure 15:	Electron trajectories at higher than ideal power. Less power is recovered in the middle, depressed collector segment.	23
Figure 16:	Typical MSDC IOT power supply schematic	23
Figure 17:	Typical oxide cathode.	24
Figure 18:	Typical spiral tungsten filament.	25
Figure 19:	Typical bar tungsten filament.....	26
Figure 20:	Typical mesh tungsten filament.	27
Figure 21:	Plate efficiency vs. conduction angle for an amplifier with tuned load. (From Thomas L. Martin, Jr., "Electronic Circuits," p. 452, Prentice-Hall, Inc., Englewood Cliffs, N.J., 1955).	29
Figure 22:	Variation of plate and grid voltage	31
Figure 23:	Plate voltage and grid voltage scales	31
Figure 24:	Instantaneous values of plate and grid current.	32
Figure 25:	Constant current characteristics for 4CX20,000E/8990 tetrode.	33
Figure 26:	Constant current characteristics for 4CW100,000D tetrode.	43
Figure 27:	A typical circuit for an R-F amplifier.	45
Figure 28:	Relative harmonic output vs. resonant circuit Q.	46
Figure 29:	Determination of input capacitor C1.	46
Figure 30:	Determination of Loading Capacitor C2	47
Figure 31A:	Determination of Inductor L	48
Figure 31B:	Reactance of an r-f choke vs. frequency.	49
Figure 32:	A typical circuit using "zero-bias" triodes showing	metering

	circuits and method of grounding the grid to r-f. The grid current is measured in the return lead from ground to filament.	53
Figure 33.	A typical circuit using "Zero-bias" triodes showing metering circuits. The grid is grounded to r-f with a by-pass capacitor. The grid is raised 1Ω above d-c ground to allow the grid current to be measured.	53
Figure 34.	Tetrode and pentode protection chart.	54
Figure 35.	Triode protection chart.	55
Figure 36A.	Screen voltage control circuit for exciter keying or protection against loss of excitation when supplying screen from high voltage source.	56
Figure 36B.	A typical method of keying a tetrode or pentode amplifier.	57
Figure 37.	Basic screen and plate modulation circuits.	58
Figure 38.	Usual circuit supporting VHF parasitic oscillation in HF r-f amplifiers.	63
Figure 39.	Placement of parasitic suppressors to eliminate VHF parasitic oscillations in HF r-f amplifiers.	64
Figure 40.	Relative spectrum space occupied by AM signal and SSB signal modulated by frequencies of 200 to 3000 Hz.	67
Figure 41.	R-F output of SSB transmitter with single-tone modulation. (a) Oscilloscope pattern (b) Spectrum for 1000-Hz tone.	68
Figure 42.	Spectrum of SSB transmitter modulated by two-tone test signal containing 400- and 2500-Hz tones and transmitting upper sideband.	69
Figure 43.	Spectrum of SSB transmitter modulated by 1500-Hz tone and injecting carrier to obtain second r-f signal equal in amplitude to tone.	69
Figure 44.	R-f output of SSB transmitter modulated by two-tone test signal as seen on the oscilloscope.	70
Figure 45.	Single-tone condition.	72
Figure 46.	Two-tone condition.	74
Figure 47.	Three-tone condition.	74
Figure 48.	Spectrum at the output of a non-linear device with an input of two equal amplitude sine waves of $f_1 = 2.001$ MHz and $f_2 = 2.003$ MHz.	78
Figure 49.	Ideal grid-plate transfer curve for Class AB operation.	80
Figure 50.	Block diagram of Intermodulation Distortion Analyzer. A low-distortion two-tone r-f signal is generated at 2 MHz and applied to the test amplifier. The output of the amplifier is dissipated in a dummy load and a portion of the output signal is examined on the screen of a high-resolution panoramic analyzer or tunable voltmeter. Distortion products as low as - 75 decibels below one tone of a 81	81
Figure 51.	Intermodulation distortion products may be predicted mathematically. This universal family of IMD curves applies to all perfect tubes obeying the 3/2-power law. (See Section 6.4.) The curves are plots of IMD level (Y axis) referred to the drivibias. As the drive is increased, the various IMD products pass through maxima and minima. Misleading conclusions of amplifier performance may be drawn if the equipment happens to be tested near a cusp on the IMD curve, where a particular product	

	drops to an extremely low level. The whole operating range of the equipment must be examined to draw a true picture of IMD per 83	
Figure 52.	IM Distortion Test Data for EIMAC 4CX1500B (EC2 = 225V)	85
Figure 53.	IM Distortion Test Data for E1MAC 4CX1500B (EC2 = 250V) ..	86
Figure 54.	Wire neutralizing system.	91
Figure 55.	Push-pull grid neutralization, basic circuit.	92
Figure 56.	Single-ended grid neutralization described by Bruene, basic circuit.	92
Figure 57.	Single-ended plate neutralization, basic circuit.	93
Figure 58.	Single-ended plate neutralization showing capacitance bridge circuit present.	94
Figure 59.	Neutralization of a symmetrical grid-excited amplifier by cross-connected capacitors.	96
Figure 60.	Neutralization by cross-connected capacitors of a symmetrical cathode-excited amplifier with grounded grids.	96
Figure 61.	Neutralization by cross-connected capacitors of a symmetrical cathode-excited amplifier with compensation of lead inductance.	97
Figure 62.	Circuit of grounded-grid amplifier having grid impedance and neutralized for reactive currents.	98
Figure 63.	Tetrode characteristics involved in feedback circuit.	100
Figure 64.	Graphical presentation of components of output circuit voltages in tetrode when self neutralized.	100
Figure 65.	Components of output voltage of a tetrode when neutralized by added series screenlead capacitance.	103
Figure 65A.	Components of output voltage of a tetrode when neutralized by added external grid-to-plate capacitance.	104
Figure 66.	Components of output voltage of a tetrode neutralized by adding inductance common to screen and cathode return.	104
Figure 67.	Three-halves power of commonly-used factors.	109
Figure 68.	Plate-Current Pulse Length and Power Output of Harmonic Amplifiers.	112
Figure 69.	4.125A mounting providing cooling, shielding and isolation of output and input compartments.	121
Figure 70.	4CX250B chassis mounting providing cooling, shielding and isolation of output and input compartments.	121
Figure 71.	Incorrectly mounted tube. Submounted metal base shell tube prevents effective cooling and does not contribute to shielding.	122
Figure 72.	Measuring back-pressure.	123
Figure 73.	Cooling Airflow Requirements.	125
Figure 74.	Combined correction factors for land-based installations.	128
Figure 75.	Conversion of mass airflow rate to volumetric airflow rate.	129
Figure 76.	Typical vapor-phase cooling system.	134
Figure 77.	4CV35,000A tetrode mounted in BR-200 boiler.	135
Figure 78.	EIMAC vapor-cooled tubes for mounting in EIMAC Boilers.	135
Figure 79.	CB-202 control box.	137
Figure 80.	Cutaway of "classic" boiler and tube combination (BR-101 boiler and 4CV8000A tetrode).	138
Figure 81.	Cutaway view of EIMAC Control Box showing position of float switches and overflow pipe.	138
Figure 82.	Typical 4-tube vapor cooling system with common water .. supply.	139

Figure 83. Cutaway of pressure equalizer fitting. 140

Figure 84. Typical 4-tube system using “steam-out-the-bottom” boilers.... 141

Figure 85. Cutaway view of “steam-out-the-bottom” boilers..... 143

Figure 86. Nukiyama heat transfer curves..... 145

Figure 87. Useful conversion factors. 148

Figure 88. Different conduction cooled tubes manufactured by EIMAC. 149

Figure 89. Variation in properties due to changes in temperature. 150

Figure 90. Relative thermal conductivity of BeO. 150