## Construction Manual for the

## K2DI v.III, Digital Interface

and

K2DI-PCI, Computer's Interface



by Paulí Núñez, EA3BLQ

Revision June, 2005

This page is left blank on purpose

## INDEX

Foreword	3
K2DI v.III Digital Interface	4
Picking the received AF signal up from P2 at the KAF2 or	
KDSP2 boards	. 9
K2DI-PCI Computer Interface	10
Pictures and Schematics	15
How to install the separators	25
Schematics	29

## FOREWORD:

This document could be considered as the 4<sup>th</sup> and last installment of my Digital Interface Saga. The other three installments or episodes being: "K2 Digital Interface v.I", "K2 Digital Interface v.II.2" and "DI v.II.2 installed into the K2/100".

For those of you who do not know it; let me succinctly explain this part of the story. If you already know it and think I am being too repetitive, please accept my apologies and thanks for your bearing with me.

It was back in summer 2002, when Elecraft launched the KAF2 option, -latter on they launched the KDSP2 as a DSP filter alternative to the KAF2-, when I discovered that my DI v.II.2, Digital Interface, could not be installed into a Complete Basic K2, featuring all the options: KDSP2 or KAF2, KAT2, KIO2 and KBT2, nor into the Integrated K2/100, because in neither of the two set-ups there was any free space available for my PCB. At the time it could only be installed in a NO KAF2 or NO KBT2 configuration of the K2 as explained in the K2 Digital Interfacev.II.2 PDF file.

From that moment on I promised myself I had to find a way out of this "cul-de-sac". It was a personal defy I had to overcome. From time to time I gave a thought to the challenging problem and it was by mid November 2003 that I was suddenly struck with new ideas that gave rise to a new design of my Digital Interface, the K2DI v.III. When I tested the prototype board, a new idea gave birth to the design of the K2DI-PCI, Computer Interface, as an optional daughter board of the DI.

The boards are silk-screened and double sided with plated-through holes, as usual.

The main features of both circuits are explained in the forthcoming pages of this document.

## K2DI v.III Digital Interface

## Main features:

- The circuit is the very same as the one used in v. II.2 but for an outlet of 5VDC that has been added to supply voltage to the K2DI-PCI. The board has been redrawn to a much smaller size: 59 mm (2 5/16") x 35 mm. (1 3/8").
- Its features include the Microphone Configuration Extender as well as a buffered, fixed audio output and the cutting of the Front Panel microphone connector's AF and PTT lines when transmitting data, so as to avoid the unwanted transmission of shack noise through a live microphone.
- This board may be used as a stand alone Digital Interface by connecting J3 to a Mini Din connector at the rear K2 panel, or as a mother board for the K2DI-PCI.

### How it works:

#### Microphone Configuration Header Extender

All pins of J1 and J2 are connected in parallel except for the AF and PTT lines, which are connected in parallel only while the K2 is in standby or reception mode but are cut while transmitting digital data, as explained further on.

Through the ribbon cable, J1 receives and sends signals from and to the Microphone Configuration Header at the Front Panel board and because of the parallel connection of J1 and J2, J2 becomes an extension of the aforementioned Configuration Header. Thus J2 is the header where you are to configure the Front Panel Mic Connector in accordance with your microphone's wiring and needs.

#### Buffered, fixed audio output:

The received audio is fed to J4 either from Aux Audio J5 at the K2's RF Board or from pins 1 and 2 at P2 on the KAF2 or KDSP2 board.

Although I don't see any inconvenience to feed the AF signal by taping P2 at the KAF2 or KDSP2, instead of J5 at the RF board, so as to take advantage of the filters, this is the user's choice. In any case, care must be taken not to tape and connect the wrong pins to J4 at K2DI board. P2 at the KAF2 and KDSP2 has the GND signal at pin 3, while J4 at K2DI and J5 at the K2's RF board have the GND signal at pin 2. An error when identifying the pins would produce a short. To prevent this I have modified the P2 three pins male header so that when installed, I get the normal 3 pins male header on the bottom side of the board while I also get a 2 pin male header on the top side (pins 1 and 2). Further on this document you'll find pictures showing this mod.

For consistency sake, I decided to copy the Elecraft's original K2 Audio Amplifier circuit to feed U2, the AF amplifier (LM386N) and to control its audio level. The use of a couple of J310 FET (Q1 and Q2), biased through a 3.3 MOhm resistor, as in the K2, is very useful as it allows the disconnection of the AF amplifier from the product detector when on data transmission.

## Cutting the Front Panel mike connector's AF and PTT lines and muting the AF amplifier, when transmitting data:

Due to its low current drain and its switching features, I've chosen the use of a CD4053BE CMOS Analogue Multiplexer to cut and commute the AF and PTT lines from the Front Panel Microphone Connector, through J1, to the Rear Digital Connector when transmitting data, and to disconnect U2, the audio amplifier LM386, from the product detector by grounding the gates of Q1 and Q2, following Elecraft's design.

### K2DI STANDBY (Receive) POSITION

The K2DI circuit schematic (see page 29) shows the device in its standby (receive) position, by default, the multiplexer mosfets are biased high due to pins 9, 10 and 11 of U1, CD4053BE CMOS, being fed with 5V DC through R3 (a 10K resistor). In this way we have:

- a) The ground connected at pin 14 of U1 (a) goes nowhere as pin 13 has no connection.
- b) The outgoing microphone signal from the AF pin at J2 goes to the AF pin in J1 through pins 15 and 1 of U1 (b), as both AF pins are contacted in parallel, and
- c) The signal from the PTT pin at J1 goes to the PTT pin at J2 through pins 4 and 3 of U1 (c), connecting the PTT pins in parallel too and thus enabling the Front Panel AF and PTT lines.

Because of the DC component (2.5 V fed through R1 and R2) present in the U1 (b), three 10  $\mu$ F electrolytic capacitors (one inlet and two outlets of U1) are needed to decouple the DC from the signal.

#### K2DI DIGITAL TRANSMIT POSITION

When, because of data transmission, the PTT is keyed through the Rear Data Connector or by means of the K2DI-PCI Serial or Tone (VOX) circuits, pins 9, 10 and 11 of U1, CD4053BE, are grounded through pin 3 at J3. Then the voltage at those pins drops to 0 V., setting the multiplexer mosfets low and thus three switching operations are activated:

- 1) U1 (a) Switches pin 14 from pin 13 to pin 12 and grounds the gates of Q1 and Q2, setting them low and thus disconnecting the AF amplifier.
- 2) U1 (b) Switches pin 15 from pin 1 to pin 2, connecting the outgoing digital signal received from the computer's soundcard through pin 1 of J3, and coming from pin 1 of the MiniDIN connector or from pin 1 of P1 at the K2DI-PCI board, to the AF pin at J1 and thus to the K2 TX circuitry. The unwanted mic signal coming from the AF pin at J2 (if any) is cut and has no way out.
- 3) U1 (c) Switches pin 4 from pin 3 to pin 5, keying the rig by grounding the PTT pin at J1 and disconnecting the microphone PTT line at J2

## CAUTION:

• Avoid triggering the K2 PTT through the KI/O2 by means of a program's CAT facility. If you do, the K2DI v.III WILL NOT be activated and the Digital transmission WILL NOT take place.

# Read K2DI v.III Parts List

DESIGNATORS	VALUE	DESCRIPTION	QTY
C1, C2, C3, C4, C10	10μF 16/25v	Electrolytic or tantalum capacitor	5
C5	220µF 16/25v	Electrolytic capacitor	
C8	.01	Capacitor "103"	
C10	.022	Capacitor "223"	1
C6	.047	Capacitor "473"	1
C7, C9	.1	Capacitor "104"	2
J1	Right angle dual row header	16 pin male	1
J1 and Microphone.	IDC Female connector for flat	FC-16P (16 pin female dual row)	2
Configuration Header at	cable.		
Front Panel board			
J2	Dual-row header	16 pin male	1
J4	Connector with locking tab	3 pin male	1
J5 at the RF board	Male header	3 pin male	1
J4 & J5 at RF board	Housing	3 pin female	2
J4 and J5 at RF board	Hardware	Female crimp pins for the housings	6
Q1, Q2	J310	FET TO-92	2
R4	2.7 Ω	Resistor (red-violet-gold)	1
R3	10K	Resistor (brown-black-orange)	1
R1, R2	100K	Resistor (brown-black-yellow)	2
R5	3.3 MOhm	Resistor (orange-orange-green)	1
R6	2K POT 3329H202 or T7YB	Trimmer pot for audio level adjustment	1
R7 <sup>(*)</sup>	220 Ω	Resistor (red-red-brown)	1
		See text for comments on R7 (*)	
U1	CD4053BE or HEF4053BP	CMOS (16 pins)	1
U2	LM386N	Low Voltage Audio Amplifier (8 pins)	1
J2	Hardware	Mic Conf. Header Extender Jumpers	8
Separators	Hardware	Male-female hexagonal 1.8cm.	2
Separator	Hardware	Male-female hexagonal 1.5cm.	
Separator	Hardware	Female-female hexagonal 1.5cm.	
Separators	Hardware <sup>(1)</sup>	ardware <sup>(1)</sup> Male-female hexagonal 7mm	
Screws	Hardware	M3 pan head screws 4mm.	4
Screws	Hardware	M3 pan head screws 6mm.	4
Nuts	Hardware	M3 nuts	4
Washers	Hardware	Split Lock washer	4
J1 at K2DI and Mic.	Miscellaneous	15.5 cm. flat ribbon cable 16 wires	1
Configuration Header at			
the K2's Front Panel Brd.			
Dig. Interface v.III	Miscellaneous	Printed Circuit Board	1

#### PCB used as a stand alone Digital Interface

J3	Male Connector with locking tab	4 pin male	1
J3	Housing	4 pin female	1
J3	Hardware	Female crimp pins for the housing	4
MiniDIN Connector	Miscellaneous	4 pin panel MiniDIN connector	1

#### PCB used as mother board for the K2DI-PCI board

J3	Male header	4 pin male	1
J5	Male header	2 pin male	1

### Picking the AF up from P2 at the KAF2 or KDSP2 boards

P2 at KAF2 or KDSP2	Special Male-male header	3 and 2 pin	1
P2 at KAF2 or KDSP2	Housing	2 pin female	1
P2 at KAF2 or KDSP2	Locking tab	2 pin male	1
P2 at KAF2 or KDSP2	Hardware	Female crimp pins for the housing	2

 $^{(1)}$  To be used only in case the KBT2 option is installed. (See pictures section)

## ASSEMBLY INSTRUCTIONS:

Please note that all the soldering rules, warnings and tips you have learned and used when assembling your K2, are to be applied in the assembly of this circuit too.

### Install and solder components in the following order:

- a) \_R1, \_R2: 100K resistors (brown-black-yellow)
- b) \_R3: 10K resistor (brown-black-orange)
- c) \_R4: 2.7Ω resistor (red-violet-gold)
- d) \_R5: 3.3 MOhm resistor (orange-orange-green)

e) \_R6: 2K trimmer pot (3329H202 or T7YB). By factory default, the trimmer pot is usually set to its midpoint [+/- 1 Kohm]

Once installed, setting R6 clockwise (CW) will increase the resistance and thus the volume level of the signal fed to U2 (LM386 audio amplifier). Obviously, to decrease the volume, R6 is to be set counterclockwise (CCW).

f) \_R7: 220 $\Omega$  resistor (red-red-brown) \* See text bellow for notes on this resistor.

- g) \_C6: 0.047µF (473) capacitor
- h) \_C7, \_C9: 0.1µF (104) capacitors
- i) \_C8: 0.01µF (103) capacitor
- j) \_C10: 0.022µF (223) capacitor
- k) \_Q1, \_Q2: J310 FET
- I) \_J1: Dual row right angle header (16 pin male)
- m) \_J2: Dual row header (16 pin male)

n) \_J3: Connector w/locking tab (4 pin male), if K2DI v.III. is used as a stand alone board. A 4 pin male header when K2DI is used as a motherboard in conjunction with the K2DI-PCI

- o) \_J4: Connector w/locking tab (3 pin male)
- p) \_C1, \_C2, \_C3, \_C4, \_C11: 10µF 16/25v electrolytic capacitors

q) \_C5: 220 $\mu$ F 16/25v electrolytic capacitor. If the K2DI-PCI board is to be installed, please bend the leads so that the capacitor is installed resting on its side on the PCB.

- r) \_U1: CD4053BE or HEF4053BP CMOS (16 pins)
- s) \_U2: LM386 low voltage audio amplifier (8pins)

#### (\*) NOTES ON THE R7 RESISTOR'S VALUE TO CONTROL LM386'S GAIN.

The manufacturer's General Description of the LM386 reads: "...The gain is internally set to 20 to keep external part count low, but the addition of an external resistor and a capacitor between pins 1 and 8 will increase the gain to any value up to 200."

The factory default gain of  $\pm 20$ , attained through the inner 1.35Kohm resistor allocated between pins 1 and 8 is too low for our needs.

On the other way if we externally bypass that resistor by inserting a  $10\mu$ F electrolytic capacitor between those pins (+ lead to pin 1) the gain is increased to 200. Good enough to drive a  $4\Omega$  speaker but too high for the sound card, as it gets overdriven.

On this account and by inserting one external resistor in parallel with the inner resistor and in series with the electrolytic capacitor, between pin 8 of the IC and the (-) lead of the capacitor, we may set that gain to the level that meets with our needs, within the range of 20-200.

As a result of some computing, I've got the following options for R7's resistor value:

1) One 1.2Kohm resistor (brown-red-red) will render a gain of about 50 (perhaps a bit on the low side)

2) One 330 $\Omega$  resistor (orange-orange-brown) will render a gain of about 75

3) One 220 $\Omega$  resistor (red-red-brown) will render a gain of about 90.

4) One 180 $\Omega$  resistor (brown-grey-brown) will render a gain of about 100 and

5) One 100 $\Omega$  resistor (brown-black-brown) will render a gain of about 125

I have chosen option #3, but the builder may choose the option he/she thinks most suitable for his/her needs and/or preferences.

## CAUTION:

- Please, remember to configure J2 header (the microphone configuration header extender) in accordance with your mic needs, as per Table 2 on the Elecraft's "Assembly and Operating Instructions" for the KSB2 SSB Adapter: "P1 Wiring for Selected Microphones", as you would do on the Microphone Configuration Header at the Front Panel board itself.
- If your intention is to construct the K2DI-PCI board too, then it is most convenient to set up the mic configuration at this step, before constructing and assembling the K2DI-PCI daughter board to the K2DI v.III board. If you fail to do so you may forget this step and be compelled to undo the K2DI v.III / K2DI-PCI assemblage so that you can reach the J2 header at the K2DI.

# Picking the received AF signal up from P2 at the KAF2 or KDSP2 boards

**Caution:** If you, to take advantage of the filtering provided by either circuitry of the KAF2 or KDSP2 devices and/or because the connection for the K2DI v III.2 is handier, decide to pick the received AF signal up from the P2 connection at the KAF2 or KDSP2 boards, instead of picking it up from the auxiliary AF connection provided at J5 on the RF board, please bear in mind the following facts:

a.- In both cases the K2's audio circuit is the very same balanced one, but

b.- On the RF board, the 3 pin distribution at J5 correspond to pins 1 and 3 for the audio lines and GND is connected to pin 2.

c.- On the KAF2 or KDSP2 boards, the 3 pin distribution at P2 correspond to pins 1 and 2 for the audio lines while the GND connection is located at pin 3.

Obviously the 3 pin female connector you may prepare to connect J4 at the K2DI to J5 on the RF board <u>cannot</u> be used for connection to P2 on the KAF2/KDSP2 boards. It would produce a short.

To avoid this risk I have prepared the special male-male header shown on the image at the right, which is to substitute the one provided by Elecraft with either of their devices.

Should you have the original P2 header already installed you are to desolder it taking outmost care in the process so as not to damage the soldering pads.

The square soldering pad, near the down board's edge, corresponds to pin 1.

The special header is to be introduced for installation into the KAF2 or KDSP2 through the bottom side of the board, taking care to position its pin 1 through the square soldering pad. Check before soldering. The 3 equal pins with the plastic holder go on the bottom side. (See pictures below)

Soldering is done on the top side of the board. Before soldering check the header's positioning once again and, if it is ok, solder only pin 3. Check the positioning once again and see that the plastic holder is flush with the board and that the pins are perpendicular to the board and parallel to those of P1. If

any correction is necessary please do so by reheating the pin 3 solder. If it is ok please go on soldering pins 1 and 2, but taking care to use a minimum amount of solder, just the necessary to secure a good contact between the board and the pin. Use a magnifying glass to check the joints.

Once finished soldering please prepare the locking tab by cutting out the borders of the indents at its bottom to allow more contact field for the pins and perhaps you will have to shorten its base by a couple millimeters to allow it to sit flush on the board when installed in the two pins.



Special header installed w/o locking tab.

Locking tab installed.

Showing tab and pin 3 (GND) solder.

This pick up set-up also applies for the KAF2 audio filter board.



## K2DI-PCI Computer Interface

## Main features:

- The board measures 73 mm (2 7/8") x 35 mm (1 3/8").
- Its circuitry (see the schematics on page 29) features a Serial Port (RTS and DTR) PTT or a VOX (Tone) PTT, to be chosen by the user when setting the J3 and J4 jumpers in accordance with his/her needs and/or preferences.
- The Serial Port is isolated by an optocoupler.
- The Line In/Mic or Line Out/Spkr soundcard connection is isolated by two  $600:600\Omega$  coupling transformers (Atech ATS-075), which feature a very flat response and an Insertion Loss of 1.0 dB Max at 1 Khz 1 Vrms.
- One 10K POT controls the AF In audio volume level.
- A connection for an optional PTT ON Led is provided, to be installed in case this board is used as an external stand alone computer interface.
- This board has been designed to be the K2DI's daughterboard but, as I have pointed out, it also can be used as a stand alone external Computer's interface.

## How it works:

### PTT SWITCHING

The PTT circuit provides the possibility of using any of two modes of PTT switching: either Serial (RS232) PTT or VOX (Tone) PTT, depending on the user's choice or needs.

Many a program for digital communications (PSK31, SSTV, etc.), when setting-up the PTT switching option, allows the user to choose either Serial COM port or Soundcard/VOX and, when choosing the former, you can even choose the use of the RTS, DTR or both RTS & DTR signals.

### Serial (RS232) PTT

This mode features the use of an Optically Coupled Isolator, the 4N32, to achieve the switching of the PTT while maintaining a very good isolation between the rig and the computer. This Optocoupler (U1 on the schematic) is driven when any or both pins RTS and/or DTR of a Computer's Serial (RS232) connector (pins 4 and 7 on a DB9 and pins 4 and 20 on a DB25) are biased high ( $\pm$ 5 vDC). When this happens the 4N32's inner infrared LED (pin 1 anode and pin 2 cathode) biases the photo sensor base so that the collector (pin 5) and the emitter (pin 4) become conductive and grounds the PTT line on pin 3 at P1, thus switching the PTT circuit on.

Pins 1 and 2 at J4 must be jumpered. J3 must be open.

### VOX (Tone) PTT

This circuit uses a Low Power Dual J-FET Operational Amplifier, the TL062 (U2 on the schematic), and consists of two sections with different functionality:

In the first section (U2 a) a square wave signal is obtained from the AF signal coming from the TR1 secondary and fed to pin 2. When the tension level on pin 2 is higher that that on pin 3, the output on pin 1 will be at 0 (zero) volts level, and vice versa, when the tension level on pin 2 is lower than that on pin 3, the output level on pin 1 will be that of  $\pm 5$  vDC.

In this way pin 1 will render a square wave signal whenever there is an AF signal fed to pin 2. In the absence of such an AF signal the output will be 0 (zero) volts.

Because of this, whenever there is an AF signal fed to pin 2, the 1N4148 (D3) diode rectifies the square wave signal present at pin 1 and charges the C5 capacitor at 5 vDC. The values of the conjunct R7 and C5 determine the time constant, when the capacitor will remain charged.

While C5 is charged, the second section (U2 b) will render 5 vDC on its outlet at pin 7. When, because there is no AF signal at pin 2, C5 gets discharged, there will be 0 (zero) volts present at pin 7.

The tension present at pin 7, through R5 biases Q1 which emitter and collector become conductive and drive the PTT switch by grounding pin 3 at P1.

Pins 2 and 3 at J4 as well as those of J3 must be jumpered.

#### Soundcard isolation

The soundcard's Line In/Mic and Line Out/Spk are isolated from the circuit by a couple of 600:600  $\Omega$  audio coupling transformers by Atech Technology Co. Ltd., the ATS-075, which offers a very flat response and a very low profile.

#### AF In level

So as not to overdrive the transmitter and to prevent IMD, the level of the audio fed to the K2 for transmission may be set by means of the 10K trimmer potentiometer R2.



- If and when using the VOX (Tone) PTT option, care must be taken to mute, at your OS, all the sounds and chimes scheduled to announce Windows' and other program's events or happenings (Start -> Configuration -> Control Panel -> Sound, Audio and Voice Devices -> Change Sound Scheme -> Properties -> Sound). It is MOST IMPORTANT that no unwanted sound is produced. Otherwise, those sounds will inadvertently trigger the PTT and, to our own despair and annoyance or what is more embarrassing, to that of the contacted remote station or the listeners, the unwanted sound will be transmitted.
- If your Sound Card has the full duplex feature, when setting the Sound Card Mixer, remember to mute the Line In or Microphone In at the Sound Level Control, so that the received audio or noise is not echoed to the Line Out outlet and thus get the PTT switched On continuously.

Page	1	2
------	---	---

## **K2DI-PCI** Parts List

DESIGNATORS	VALUE	DESCRIPTION	QTY	MOUSER
C1	.1µF	Capacitor "104"	1	
C5	.47µF	Capacitor "474"	1	
C3, C4	4.7μF	Electrolytic or tantalum capacitor	2	
C2	10µF	Electrolytic or tantalum capacitor	1	
D1, D2, D3	1N4148	High speed diode	3	
J1	Connector with locking tab	3 pin male	1	
J1b	Housing	3 pin female	1	
J2	Connector with locking tab	4 pin male	1	
J2b	Housing	4 pin female	1	
J3	Male header	2 pin male (PTT jumper)	1	
J4	Male header	3 pin male (PTT jumper)	1	
LED1	LED	red LED	1	
P1	Female Header	4 pin female	1	
P2	Female Header	2 pin female	1	
Q1	PN2222A or MPS2222A	NPN General purpose transistor	1	
R1, R3	470 Ohm	Resistor (yellow-violet-brown)	2	
R5	10K	Resistor (brown-black-orange)	1	
R2	10K POT (Miniature)	Trimmer pot for audio level adjustment	1	652-3329H-1-103
R4, R7	100K	Resistor (brown-black-yellow)	2	
R6	3.3M	Resistor (orange-orange-green)	1	
R8	1K	Resistor (brown-black-red)	1	
TR1,TR2	Transformer	Coupling transformer Atech ATS-079B	2	421-ATS079B
U1	4N32	Optocoupler	1	
U2	TL062	Dual operational amplifier	1	
J1b & J2b	Hardware	Female crimp pins for the housings	7	
J3, J4	Hardware	PTT Jumpers	2	
Separators	Hardware	Female-female hexagonal 1cm. separators	3	
Lock Washers	Hardware	Split Lock Washers	3	
MiniDin Conn.	Hardware	4 pin Chassis MT MiniDin to Sound Card	1	161.2104
MiniDin Conn.	Hardware	3 pin Chassis MT Mini Din to RS232	1	161,2103
K2DI-PCI	Miscellaneous	Printed Circuit Board	1	

## ASSEMBLY INSTRUCTIONS:

Please note that all the soldering rules, warnings and tips you have learned and used when assembling your K2, are to be applied in the assembly of this circuit too.

### Install and solder components in the following order:

- a) \_R1 \_R3: 470 Ω resistors (yellow-violet-brown)
- b) \_R8: 1K resistor (brown-black-red)
- c) \_R5: 10K resistor (brown-black-orange)
- d) \_R4, \_R7: 100K resistors (brown-black-yellow)
- e) \_R6: 3M3 resistor (orange-orange-green)
- f) \_D1, \_D2, \_D3: 1N4148 High speed diode
- g) \_C1: .1µF capacitor (104)
- h) \_C5: .47µF capacitor (474)
- i) \_C3, \_C4: 4.7µF electrolytic or tantalum capacitor
- j) \_C2: 10µF electrolytic or tantalum capacitor
- k) \_P1: 4 pin female header (to be installed on the bottom side of the board and soldered on the top) (\*)
- \_P2: 2 pin female header (to be installed on the bottom side of the board and soldered on the top) (\*)
- m) \_R2: 10K POT trimmer
- n) \_Q1: NPN General purpose transistor (PN2222A)
- o) \_U1: Optocoupler (4N32)
- p) \_U2: Dual operational amplifier (TL062)
- **q)** \_LED1: Optional PTT on LED (red). Useful if the board is installed as a stand alone External Computer Interface.
- r) \_TR1, \_TR2: 600:600 $\Omega$  Coupling transformer (Atech ATS-075). Mouser's catalogue part # 421-ATS075 (page 542)
- s) \_J1: Connector with locking tab (3 pin male)
- t) \_J2: Connector with locking tab (4 pin male)
- u) \_J3: Header (2 pin male)
- v) \_J4: Header (3 pin male)

(\*) Should the board be used as a stand alone External Computer Interface, these two female headers ought to be substituted by a 4 and 2pin male connectors installed on the top face of the board and soldered on the bottom.

This page is left blank on purpose

## **Pictures**





K2DI v.III XRay image



K2DI V.III Parts Placement



K2DI V.III Constructed and ready to be installed



K2DI v.III installed on the top cover of the K2



K2DI-PCI PCB's x-ray image



**K2DI-PCI** Parts Placement



Constructed K2DI-PCI ready to be installed



K2DI-PCI fitted on top of its motherboard, the K2DI v.III

Construction Manual for the K2DI v.III and K2DI-PCI boards © EA3BLQ - Revision June 2005



Side view of the installed PCBs



KF2 with modified 3 pin male header





KDSP2 Board. Mind the 2 pin header on the top



K2DI-PCI board showing the female headers placed on the bottom



Ribbon cable connected to the Front Panel Mic Configuration Header



Side view of the K2, showing the ribbon cable coming out between the Control and Front Panel boards, the KDSP2 option and the installed K2DI v.III & K2DI-PCI boards. Mind the J1 and J2 straight connectors at the K2DI-PCI board. Right angled connectors collided with the Side Panel.



The ribbon cable connected to the K2DI v.III Digital Interface



How the Serial PTT and Soundcard cables are fixed to the top cover



I have used a Minijack stereo for the Serial PTT rear connection and have isolated the PC signal GND with one bakelite washer. The jack is centered in the former OUT XVTR hole.



## How to install the separators

The separators as well as the screws and nuts I provide are Metric 3 and because of that and for esthetic consistency sake, I suggest that, when installing the board(s) on the top cover of the K2, the constructor uses them instead of using the hardware supplied by Elecraft (screws and bolts for the loudspeaker and male-female separators for the KBT2)

KBT2 Internal battery setup



Substitute the screws, bolts and KBT2 Battery Bracket's separators for the ones supplied with the K2DI v.III kit.

## NO Internal battery setup





This page is left blank on purpose

## SCHEMATICS

## K2DI v. III

K2 Digital Interface featuring a Mic. Configuration Header Extender and Rear Panel Data Connector (It Includes a buffered, fixed audio output and the cutting of Front Panel mic. connector's AF and PTT lines, when transmitting data). © Paulí Núñez, EA3BLQ - November 2003



Construction Manual for the K2DI v.III and K2DI-PCI boards © EA3BLQ - Revision June 2005

#### Page 31 K2DI-PCI

#### Sound card interface for the K2's K2DI by EA3BLQ

Circuit for a daughter PC board of the K2DI v.III PCB, designed to interface the K2's DI with a computer. It features Opto isolation for the RS232 PTT circuit, as well as isolation for the sound card connections. Another remarkable feature is the possibility to choose the PTT mode between RS232 or VOX, according to user preferences.



Construction Manual for the K2DI v.III and K2DI-PCI boards © EA3BLQ - Revision June 2005