

CRYSTAL SETS TO SIDEBAND

A Guide to Building an Amateur Radio Station

By Frank W. Harris, KØIYE

© Frank W. Harris 2022, Rev 16

(Note: This book is in PDF format. If schematics and drawings appear to have insufficient resolution, increase the display magnification.)

Table of Contents

Chapter 1

THE FASCINATION OF RADIO

Exploring the shortwave bands

Growing up in the Morse code era

The joy of building it yourself

A brief history of radio communication

Henry, Maxwell, Hertz, Tesla and Marconi.

Fessenden, Edison, Fleming, DeForest and Armstrong

The sinking of the RMS Republic and the birth of ham radio

Ham radio since 1910

Becoming a radio amateur

Chapter 2

HOMEBUILDING AMATEUR RADIO EQUIPMENT

What qualifies as homebuilding?

When homebrewing is not appropriate

Barriers to modern homebuilding –

Time, frequency stability and lead inductance

Basic electrical knowledge

Magnets and static electricity

Voltage, current, resistance, energy and power

(Illustrated with drawings of water and mechanical analogies)

Conductors, Insulators and semiconductors

Capacitors, inductors, transformers and alternators

Home power distribution, transformers at low and high frequencies

Chapter 3A

SETTING UP AN ELECTRONICS WORKSHOP

Research and Development as Recreation

R&D as recreation

How to build radios (or anything else) in your basement

Persistence, read books, keep a notebook and work in small increments

Tools needed for kit assembly & simple projects.

A bright light over the work area

Soldering iron and small tools

hand magnifier or jeweler's loupe

Tools needed for scratch-building ham receivers and transmitters

The ARRL Amateur Radio Handbook

Parts catalogs - (usually on-line these days)

Wood carving gouges for making PC boards

(or other means of making circuit boards)

Quality multimeter

>50 MHz Oscilloscope

(I can't work without one, but maybe you can.)

Frequency counter or precisely calibrated receiver

Calculator

Simulation "Spice" software for experimenters

Freeze spray

Lab notebook

Nice-to-have tools

A collection of electronic junk

Lab power supply

RF frequency generator

Capacitance meter

Test leads and socket boards

Chapter 3B

SETTING UP AN AMATEUR WORKSHOP

Techniques for building and trouble-shooting circuits

Trouble shooting with minimal equipment

Basic troubleshooting strategies

Basic trouble-shooting strategies

The necessity of oscilloscopes and frequency counters

Constructing transistorized circuits

Bread-board prototype first

Hook-up wire

Magnet wire

Wire connections and soldering

Tinning connections before soldering

Using a hemostat

Tweezers for surface mount components

Printed circuit boards are essential

Single-sided printed circuit boards

Double-sided circuit boards

Two-sided boards can become shielded enclosures

Trouble-shooting a receiver

"Shooting a board"
 Trouble-shooting a transmitter
 "Tuning" a transmitter
 Light bulbs are simple antenna substitutes
 Mismatched antennas may cause the transmitter to overheat.
 Heat sinks
 The limits of plug-in boards
 Failure is the mother of success

Chapter 4A

HERTZIAN WAVES IN THE BASEMENT

The nature of radio waves
 Mechanical and LC electrical oscillators
 Antenna and transmission line theory
 Crystal set components

- LC tuner
- PN junction diode detectors
- P-type and N-type semiconductors
- Detection of AM signals

 Homebuilding the parts for a crystal set

- The Jamestown diode
- The Caribou headphone

 Revisiting Crystal Sets in 2006

- Learning to troubleshoot
- Selective tuning

Chapter 4B

HERTZIAN WAVES IN THE BASEMENT

(Continued)

Recreating Hertz's radio equipment

- Transmitting and receiving as simply as possible
- The 1880 ten-meter communicator

 Proving that radio waves exist and aren't just capacitive or magnetic coupling
 Demonstrating standing waves to measure frequency
 Resonant Spark Gap Transmitters

- Neon light bulb relaxation oscillators
- "Negative resistance"

 Building homebrew transistors

- Bipolar transistors, PNP and NPN
- Demonstrating power gain
- The Boulder Rock Radio

 The first transistorized ham transmitter

Chapter 5

GETTING ON THE AIR

- DECIDING WHAT TO DO FIRST

How to earn a license

The rules of the homebuilding game – Whatever makes you happy!

Picking an HF band

Getting acquainted with the HF ham bands, 160 to 10 meters + 6 meters

Instant high quality HF communications

VHF/ UHF handheld transceivers

Morse code abbreviations and Q-codes

Building an antenna

Dipoles

Multi-band dipoles

80 meters when you don't have room for a dipole

The curtain rod vertical

A multi-band vertical antenna

Lightning protection

Chapter 6A

BUILDING A QRP HOMEBREW

A single-band, crystal-controlled QRP module

The transmitter mainframe

HF construction methods

Making your own PC boards

“Dead Bug” and “Gouged Board” construction

Superglue “Island Boards”

Coax jumpers

Shielded boxes

The complete QRP crystal-controlled transmitter

Transistor amplifiers and oscillators

How an amplifier becomes an oscillator

Class A and Class C amplifiers

Stabilizing the operating point, bypass caps and emitter resistors

Quartz crystals – the key to frequency stability

The 40 meter QRP circuit

Oscillator and buffer

Inductors, RF transformers and impedance matching

Tapped toroid inductors

How to wind them (and mistakes you might make)

The final amplifier stages for the QRP

Tuned versus broadband - Use both for best results

Bifilar wound, broadband transformers

How to wind them (and how you might screw up)

Ferrite bead RF chokes, expensive RF power transistors, heat sinks & output connectors

Conquering inductors

- Calculating resonance

- Calibrating trimmer capacitors

- Calculating turns on powdered iron and ferrite toroids

- Chebyshev output low pass filters

Chapter 6B

BUILDING A QRP HOMEBREW (Continued)

Using your QRP in the real world

Keying your QRP

- MOSFET power transistors

A “spot switch” for the QRP

An audio tone for sending Morse code

Troubleshooting your QRP

- Eliminating chirp

How to get a full 5 watts out of your QRP

Calculating bias resistors

Retuning your QRP for other ham bands

Chapter 7A

BUILDING A **Direct-conversion** CODE PRACTICE RECEIVER

A simple, direct-conversion receiver

- A great first project for a new ham

- Excellent sensitivity and good stability

- Poor selectivity

Adding 700 Hz audio filtering

- High pass and low pass filters

- Cascaded bandpass filters increase selectivity

- Operational amplifiers

Building with integrated circuits

AM broadcast filter

Getting rid of the image

Chapter 7B

BUILDING A **Regenerative** CODE PRACTICE RECEIVER

A simple regenerative code practice receiver.

- Receiving CW, SSB and AM on multiple bands.

- Demonstrating AM reception on the broadcast band, 550 KHz to 1700 KHz.

Regen receivers that didn't work - cautionary examples.

Chapter 7C

BUILDING A Superheterodyne CODE PRACTICE RECEIVER

A simplified superheterodyne code practice receiver.

Receiving CW, SSB and AM over the entire HF spectrum.

The superheterodyne principle

Preselector and RF amplifier

A wide range HF VFO

Mixers - MOSFET and JFET

IF amplifier for 6 MHz

Suppressing unwanted signals on the IF frequency

BFO for 6 MHz

AM detector

Audio amplifier

Discrete transistor worked better than LM386 chip

Power supplies

Muting the supply for use with a transmitter

Chapter 8

POWER SUPPLIES

Line powered power supplies

Power supply safety features

Isolation, 3-conductor cords, fuses, switches and ratings

Supply performance and regulation

Rectification, ripple, chokes, capacitors and bleeders

Zeners, linear and switching regulators

A QRP regulated power supply

A variable voltage version for lab bench

Cheapskates and old batteries

Using supposedly dead alkaline batteries

A 200 watt QRO regulated power supply

A battery power supply for the radio shack

Solar cell charging, low drop-out regulators

Buck-type switching power supply

Battery powered shack lighting

A 15,000 volt power supply for lab experiments

Chapter 9

ACCESSORIES FOR THE TRANSMITTER

A straight key

An electronic bug

Building dummy loads

A QRP tuning indicator

A band-resonant antenna coupler

- “T” type antenna coupler
- The "Fri-match" antenna tuner
- A low pass filter
- How to stay legal with a homebrew transmitter
- Antenna and power relays
- MOSFET power relay replacement
- Homebrew QSL cards

Chapter 10

VARIABLE FREQUENCY OSCILLATORS

- Drift is a big deal today
- Low frequency VFOs drift less than high frequency VFOs
- JFET transistors
- The oscillator circuit
- The buffer, final amplifier and output filter
- The 50 secrets of avoiding drift
 - JFETs, single-sided PC boards, cast metal box, multiple NPO caps, small variable caps, precision voltage regulation and more
- Vernier tuning
- Varactor tuning elements – advantages and disadvantages
- A precision power supply
- A voltage doubler power supply for battery use
 - Square wave generator with a multivibrator
 - Squaring up the square wave
 - Charge pump, diode/ capacitor voltage doubler
 - Schottky diodes for efficiency
- Temperature compensation methods
 - Positive coefficient capacitive trimmer compensation
 - How to adjust the compensator
 - Thermistor/ varactor temperature compensation

Chapter 11

Building a VFO for the higher bands (PMOs)

- Old approaches that no longer work
 - Frequency multiplication
 - High frequency oscillators
- Pre-Mix Oscillator method of frequency translation
- A VFO-controlled QRP module
- Crystal oscillators are stable, aren't they?
 - Crystal oscillator circuits
 - Butler oscillators and big crystals - then measure the drift!
 - Precisely regulate the power supply
- Mixers, bipolar transistor and dual-gate MOSFET
 - Optimum drive requirements

- Direction of tuning, drift error cancellation
- Multistage filters and filter/amplifiers
- The QRP final amplifier stages
- Spot switches for PMO QRPs

Chapter 12

SIMPLIFIED QRO AMPLIFIER DESIGNS

- The basic features of a modern linear power amplifier
- It looked easier in the Handbook
 - Linear “noise mode” operation
- A tuned 50 watt class B amplifier
 - Ferrite balun transformers
- An untuned, sort-of-linear, class B, amplifier
 - Keying the 50 watt transmitter
- A linear Class AB amplifier, this time for sure
 - Single Sideband (SSB) needs a linear
 - Biasing without thermal runaway
 - Clamp diodes prevent runaway
 - Mechanical construction

Chapter 13A

BUILDING AN ALL-BAND HF RECEIVER

Constructing the 80 meter core receiver

- Building a receiver - an unusual adventure
- What’s a reasonable goal?
- An “adequate performance” HF communication receiver
- Does it have to be so complicated?
- Planning your receiver
 - Direct conversion versus superheterodyne
 - Why not single conversion?
 - Start with a single-band, single-conversion superheterodyne
 - How do modern digital receivers do it?
- Receiver construction – build with shielded modules connected by thin coax.
- The 80 meter preselector
 - Reception on 80 meter and 160 meters is aided by a tuned transmatch
- The Variable Frequency Oscillator
- Mixer magic
 - Mixers will give you lots of static – and howls and squeals
 - A practical homebrew mixer made from discrete parts – it’s harder than it looks
 - Dual gate MOSFET mixers
 - Not all MOSFETS work equally well
 - A JFET alternative mixer
- Crystal ladder filters – essential for CW
 - All 9.000 MHz crystals aren’t equal

- Using the BFO oscillator to match crystals
- Switch in filters with a rotary switch
- The IF amplifier
 - Lessons learned from a dual-gate IF amplifier
 - The cascode amplifier strip - variable gain with constant Q
- Automatic Gain Control (AGC) - not a luxury
- The product detector
 - Nearly anything works at least a little
- The AF amplifier – a vital part of the signal dynamic range
 - Protecting your ears from strong signals
 - How Hi-Fi should it be?

Chapter 13B (continued)

BUILDING AN ALL-BAND HF RECEIVER

Building HF converters and extra features for the 80 meter receiver

- HF converters for the other ham bands
 - Converter mixers - tuned or untuned?
 - Filtering 80 meter signals out of other bands
 - Crystal oscillators
 - Band switching
- An LED digital band annunciator
- Driving a speaker
- AM and FM detectors
- Receiver power supplies
 - Use a linear regulator, not a switching regulator
 - Receiver muting while transmitting
- Tuning in CW and SSB signals

Chapter 14

OLD-TECH VACUUM TUBE RADIO

- How old can radio technology be and still be used on the air today?
- Why bother with vacuum tubes?
 - Glowing filaments, colored plasmas and Jules Verne glass envelopes
- Power supplies for tubes
 - High voltage power supply safety
- The old-tech QRP transmitter
 - Vacuum tube amplifiers
 - The three roles of the triode filament
 - RF sinewave oscillator
 - Quartz crystals
 - Triode and pentode oscillators
- Old-tech voltage regulation – big, crude and expensive - but beautiful!
- The travails of triode tubes
 - The oscillator and buffer

The final amplifier – triodes chirp
 The transmitter power supply
 An inadequate supply from a 1935 radio
 A good power supply made from cheap, modern, boring parts
 How to check out junk power transformers
 A complex but adequate supply made from ancient parts
 It works! It's a success on today's 40 meter band and no one suspects it's old.
 An old-tech receiver
 A super regenerative receiver made from ancient tubes
 The power supply
 Super-regen on the modern hambands
 Lots of fun, but not up to modern QRM & QRPs - back to the drawing board!

Chapter 15

THE NOBEL PRIZE FOR SIDEBAND

It can't be that hard! Want to bet?
 The sideband generator – how it works
 The 9 MHz oscillator / amplifier
 The audio amplifier
 The balanced modulator
 Building your own crystal ladder filter
 Decoupling the power supply leads
 Getting rid of RF feedback - RF filtering for all inputs
 Tuning and testing
 Using the generator for AM modulation and CW
 Moving the 9 MHz SSB signal to a hamband
 Move the SSB only once!
 No wonder most ham rigs are transceivers
 Moving the 9 MHz signal to the difficult HF hambands
 Move the VFO first, then mix it with the SSB 9 MHz.
 Pick your oscillator and VFO frequencies carefully
 Hearing your own VFO in the receiver
 The hardest band – 17 meters
 40 meters and 12 meters
 Covering the widest band – 10 meters
 A linear sideband QRP, VFO-tuned module
 All stages must be linear and low distortion
 All gain stages should be broadband to prevent oscillation
 Sometimes high pass filter output is needed and not the usual low pass
 Checking out the generator
 Driving a 50 watt linear amplifier

Chapter 16A

HOMEBUILDING VHF HAM RADIOS

VHF amplifiers & frequency generation

Introduction

VHF lessons learned by trial and error

Available 2 meter homebrew designs

A 2 meter FM modulated signal generator

 An FM modulator

 Raising the 18 MHz signal up to 2 meters

The great VHF amplifier mystery

 How do commercial handhelds generate 5 watts?

VHF driver designs

 A regenerative VHF amplifier

The "200 mV phenomenon"

 How the professionals do it - with ICs

A one watt to 3 watt 2 meter bipolar amplifier

Experimenting with various VHF bipolar transistors

 How to test a transistor

Lesson from FM radios

Success using extra forward bias

Success using an emitter follower to match impedance

Desperation - a VHF vacuum tube amplifier

One watt output? Not so hard after all

 How to measure VHF power and voltage

Commercial VHF power meters

Getting serious about VHF amplifier design - impedance matching

 Available transistors with VHF power parameter specs

 Matching dummy loads is easy

 Calculating L and C values

Chapter 16B**BUILDING VHF 2 METER TRANSMITTERS**

A repeater-activating code generator

Sometimes VHF milliwatts are enough

An microphone amplifier for the FM transmitter

60 Hz hum is hard to eliminate with FM

How to test a phone transmitter on the air when there's no one to listen

A one watt transmitter design

Antenna coupler

Rotary crystal switch

Power supply for the transmitter

 Reducing 60 Hz hum

 Static-like noise when releasing PTT button

Volume meter design

Optical couplers

Harsh noise on the modulation

A dream come true

One watt to 5 watt 2 meter MOSFET amplifiers

2SK3075 MOSFET
MRF137 MOSFET
MRF148A MOSFET
MRF136 MOSFET

Coax balun transformers

60 Hz hum - again

Push To Talk implementation

Antenna switching

Status of the VHF project

Chapter 16C

BUILDING VHF 2 AND 6 METER RECEIVERS

An overview of VHF receiver designs

Building a **2 meter** to 15 meter receiver/converter

Receiving **2 meter** hams on an ordinary commercial FM radio

Building a **6 meter** to 15 meter receiver/converter

Building a **6 meter** Direct Coupled receiver

A proposed **6 meter** ssb transceiver

A Foster-Seeley wideband FM detector

60 Hz hum filter in a receiver

A ratio detector for FM

The simplest wideband FM detector

An FM "crystal set"

Chapter 16D

BUILDING VHF 6 METER TRANSMITTERS

R&D - Developing a 6 meter CW QRP driver

A 6 meter AM transmitter driver

A 5 watt 6 meter CW and SSB QRP final

Building and testing a 6 meter SSB QRP driver

An improved VFO with 1.2 MHz range

A 6 meter QRP linear amplifier for CW, AM and SSB

A 6 meter QRP driver for SSB

A 6 meter SSB QRP transceiver

Chapter 17A

ANCIENT MODULATION & RELATED TOPICS

Defining amplitude modulation

AM modulation for vacuum tube final amplifiers

Plate, screen and cathode modulation

A "collector modulator"

Building a nostalgic 10 meter AM hand-held transmitter

A crystal-controlled regenerative 10 meter receiver
 Converting a MOSFET keyer into an AM modulator
 The Maunder Minimum
 Using the 10 meter walkie-talkie as an RF generator
 Generating AM with an SSB balanced modulator
 Compensating for non-linearity
 Compression by accident
 You probably don't need to build a voice compressor
 A 40 meter pulse width modulator
 Transmitting voice with a CW transmitter
 Narrowband AM voice modulation

Chapter 17B

MISCELLANEOUS RADIO PROJECTS

Ham TV - The old way.
 Getting on 60 meters – lots of work, little reward
 Building an avalanche practice beacon
 building a whistler receiver
 Ultra, ultra high frequency - talking on a light beam
 The highest frequency - Homebrew Geiger counters
 The simplest Geiger counter
 A more modern Geiger counter
 Homebrewing with PIC microcomputers

Chapter 17C

MISCELLANEOUS ELECTRONIC PROJECTS & TOPICS

Class D pulse width modulated audio amplifiers
 Homebrew Electrolytic Capacitors
 An entertaining, educational project, but not practical
 A butterfly hatching alert - CMOS oscillators
 Electrocardiograms for Hams - build your own ECG
 Solder Smoke - a solution for a problem I hope you never have
 Developing patentable inventions in the basement
 A thrilling experience, but rarely lucrative

In conclusion,

Homebrew ham radio is never complete. When it works perfectly and has all the latest innovations, the hobby is over. Not likely. Long live homebuilding!