

# 100 Watt RF Power Amplifier for 2 GHz

## Overview


Old cellular phone base station modules operating in the 1.9 GHz band are starting to show up at ham fests. These devices are ripe for experimental applications of high-power (+100 watts) microwave energy in the 2 GHz band. With a fairly reduced output power (10 watts or so), the stock power amplifier modules will cover the 2.3 GHz and 2.4 GHz amateur radio bands. All that they require is some minor tweaking and a decent +28 VDC power supply.

The RF power amplifier section of the cellular phone base station module which will be covered here is based around a Philips BLF4G20LS-110B LDMOS RF power transistor. This LDMOS RF power transistor will do an easy 100 watts at frequencies from 1.8–2.0 GHz. The BLF4G20LS-110B does require a clean +28 volt power supply and will draw at least 10 amps when run near its maximum output power. Since the BLF4G20LS-110B has around 13 dB of in-band gain, to reach the 100 watt (+50 dBm) limit will require around 5 watts (+37 dBm) of RF drive power. Because of the nature of the narrowband impedance matching sections in the stock amplifier's pre-driver circuits, we will be driving the BLF4G20LS-110B externally.

The stock base station amplifier module has a very nice 1.9 GHz-band isolator (M/A-Com MAFRIN0336) on the RF output. We'll be keeping this isolator, as they protect the amplifier in case of a high SWR situation, but when run out-of-band, they loose isolation and are not as effective. They can even increase the insertion loss, further reducing the output RF power.


This is all still very experimental right now, but should be a good starting point.

## Pictures & Construction Notes

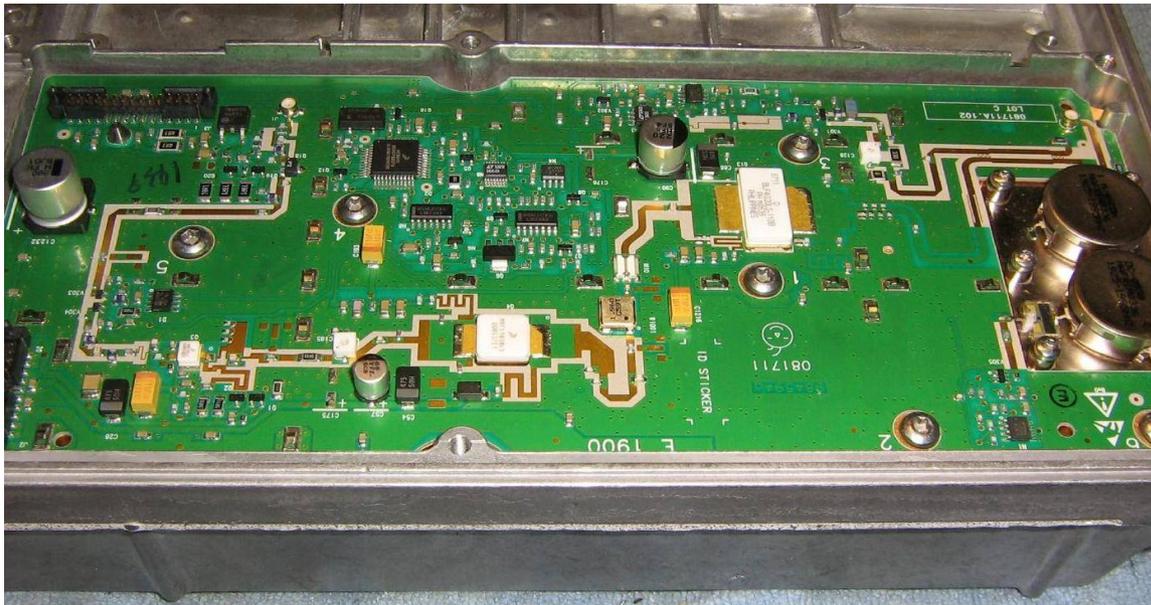

Stock RF power amplifier section of a 1.9 GHz cellular phone base station module. FCC ID: L7KTSPB-01.

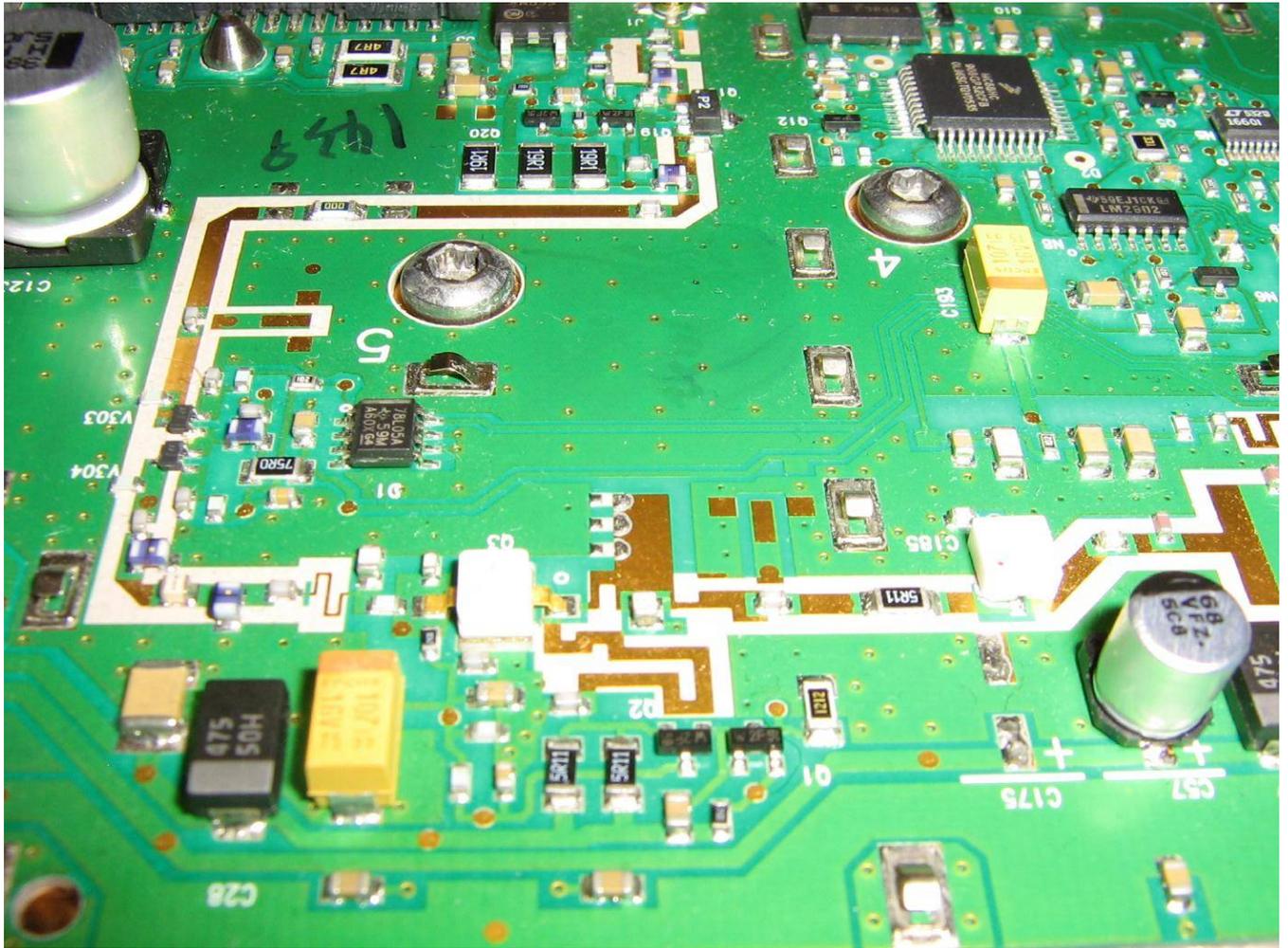
The RF input circuitry is on the left-side, RF output is on the right. The silver circular part is the output RF isolator.



Close up of the RF input circuitry.

The smaller white transistor on the left is a MRF281Z, which feeds a MRF1903LS.

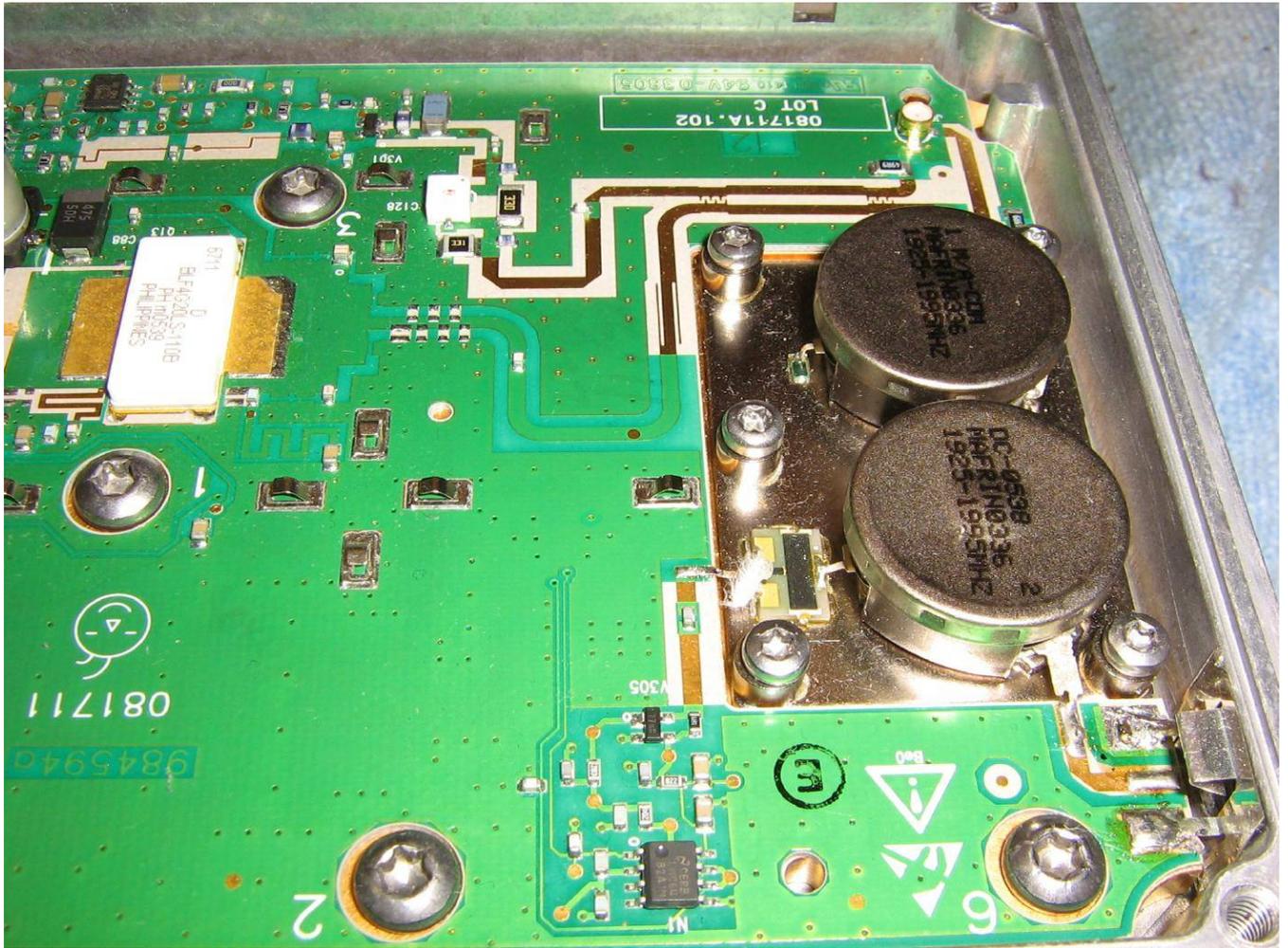
We won't be using the pre-amplifier transistors in this amplifier, but they may be documented in an upcoming project.



Close up of the RF output circuitry and isolator.

The SMA RF output connector is on the lower-right.

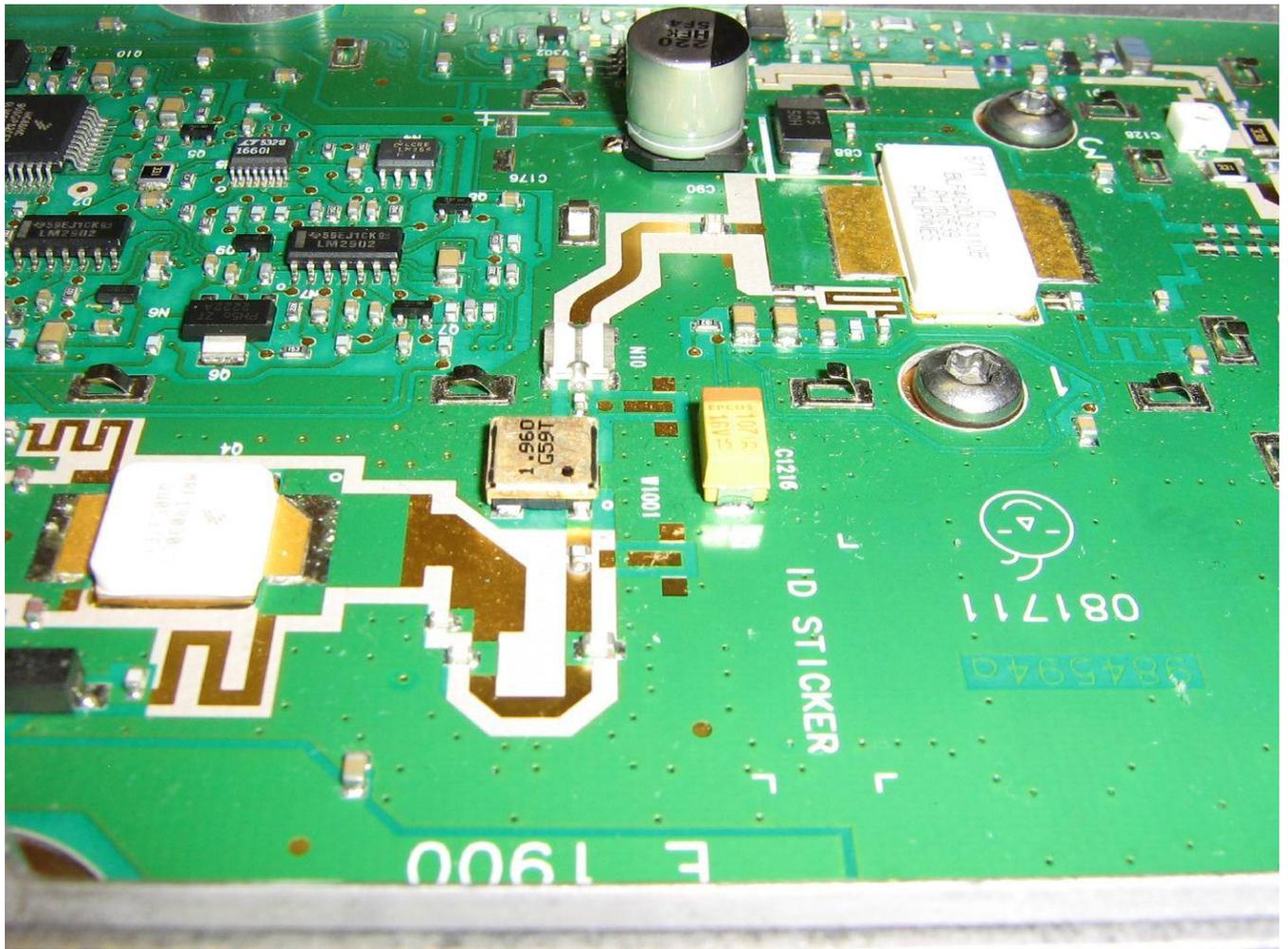The top PC board traces form a directional coupler to monitor the BLF4G20LS-110B's RF output.



Input circuitry and impedance matching section for the Philips BLF4G20LS-110B. The MRF19030LS is on the lower-left. The silver box in the middle is a 1.96 GHz bandpass filter.



The front-panel to the rack-mounting system we'll be using for this amplifier.

The panel was salvaged from an old rack-mounted power supply and some of the holes were filled with Bondo. A fresh coat of paint, labels, and clear coat help to finish it off.


The RF output will be via a panel-mounted female N connector.

The +28 VDC input will be protected with a 15 amp fuse.




Modifying and cutting down the module's original aluminum case so it can be mounted to the front-panel.

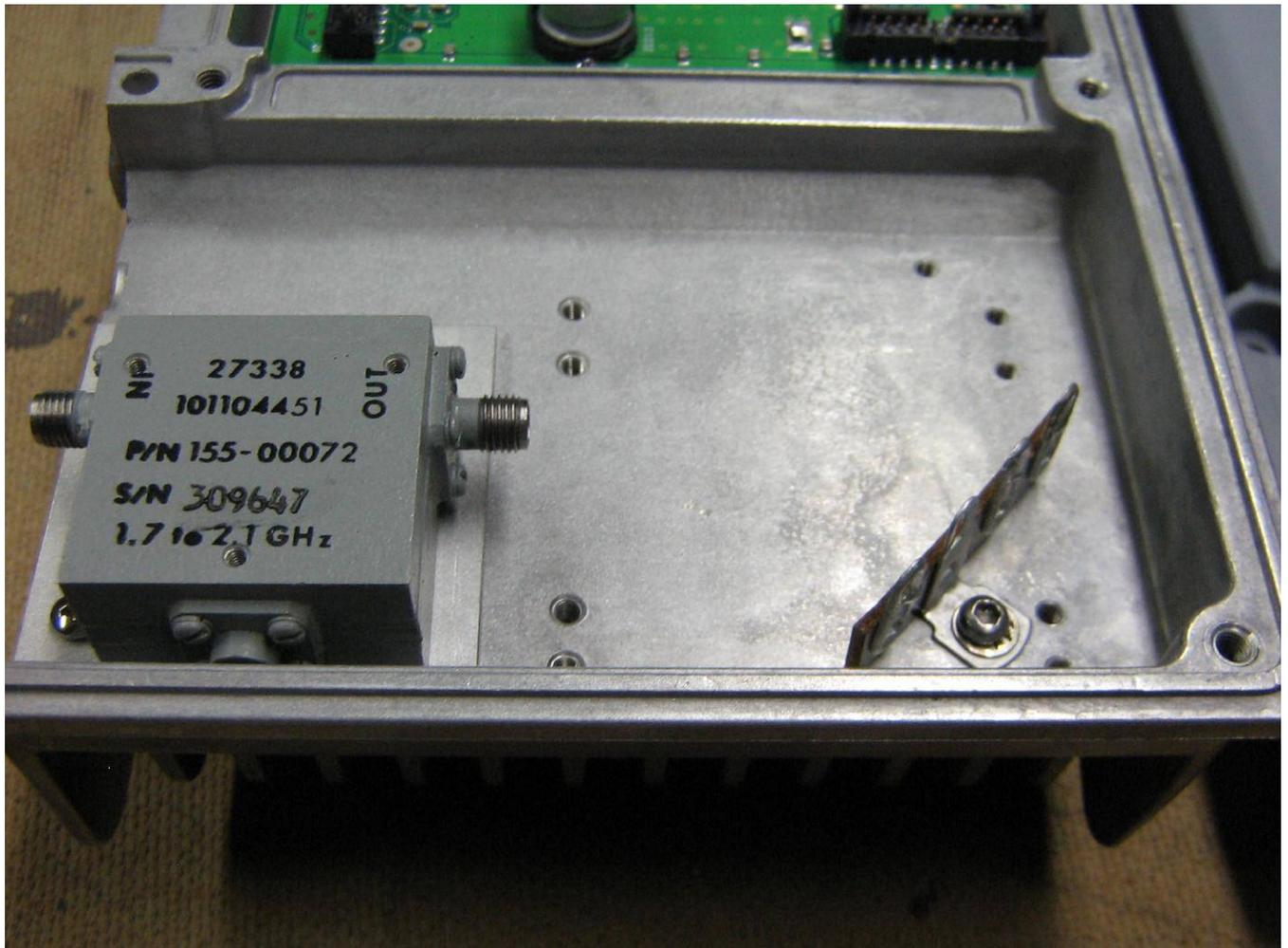The amplifier case will be attached to the front-panel with four 1/4-inch bolts and hardware protruding through its cover.




A salvaged 1.9 GHz-band isolator was added to the input of BLF4G20LS-110B. This is to help solve any stability problems, but may restrict the amplifier's overall frequency range. This input isolator is optional.

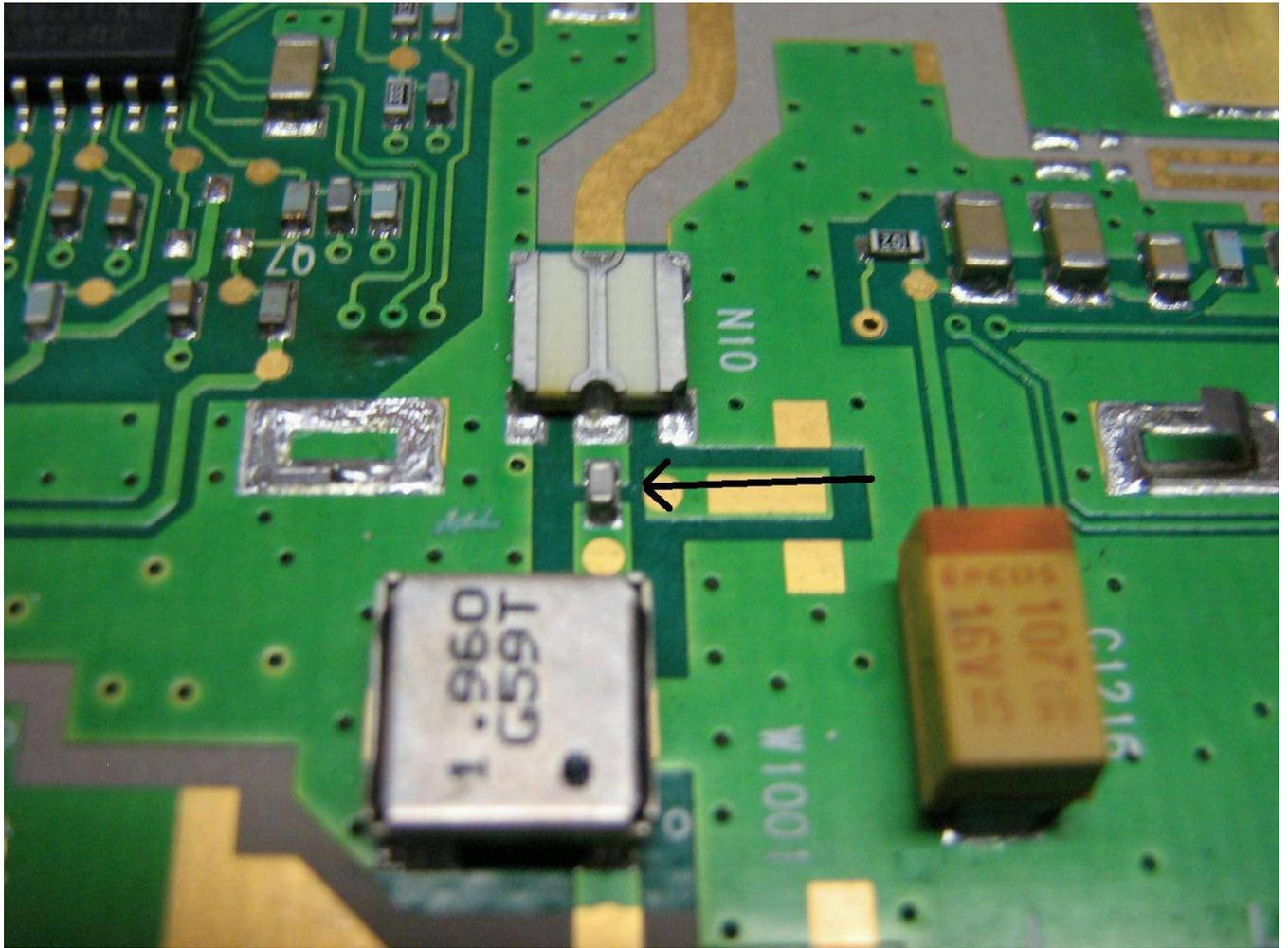A solder terminal strip was added on the lower-right for centralizing the DC input power connections.




Arrow points to a series capacitor which will need to be removed to isolate the input to the BLF4G20LS-110B.

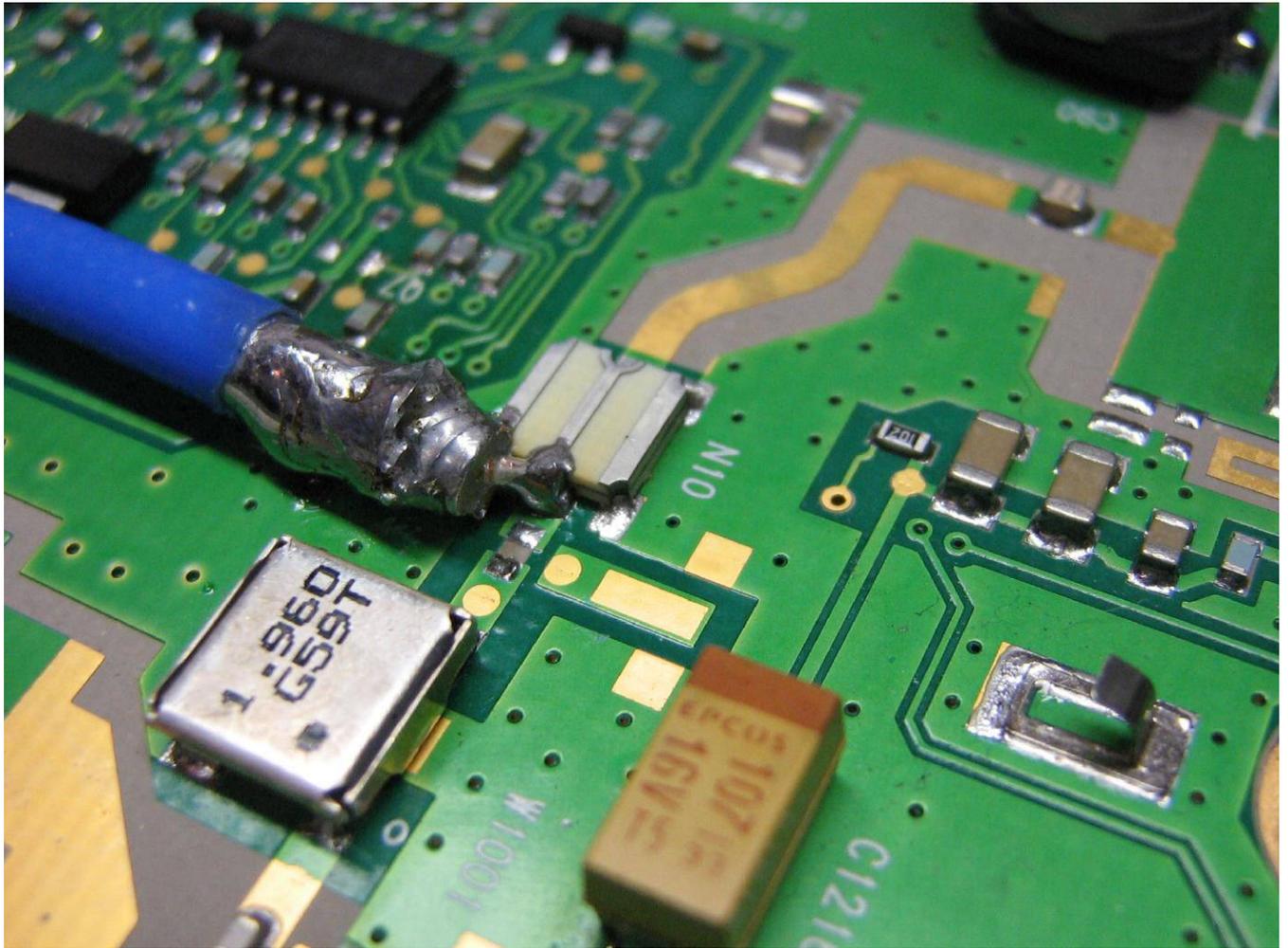This is first of several modifications which will need to be done in order to use the amplifier.




After that capacitor is removed, solder a piece of 50 ohm coax for the RF input to the BLF4G20LS-110B.

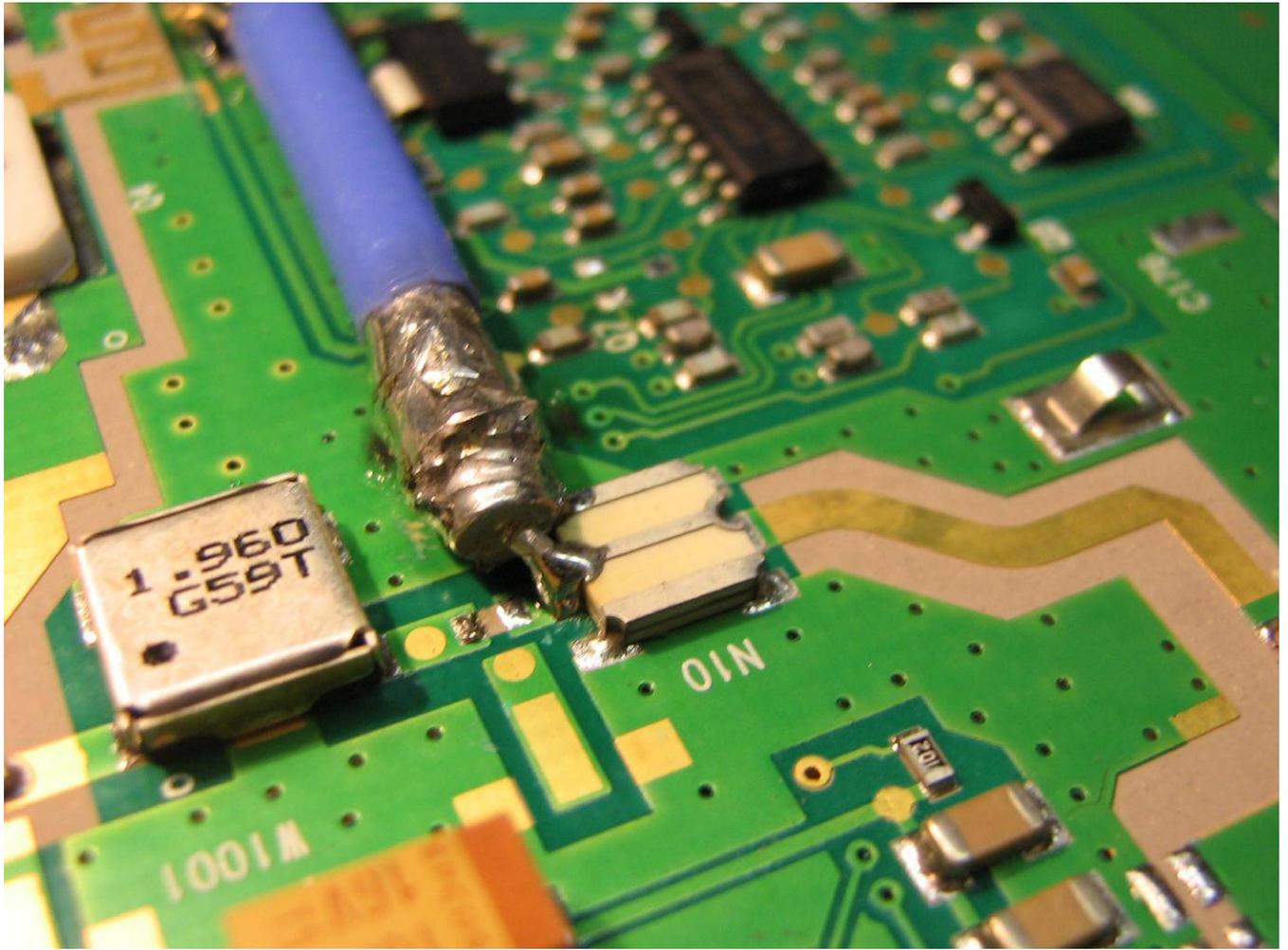Solder the center of the coax to the surface-mount jumper device labeled "N10" on the PC board. Scrape away some of the amplifier PC board's top coating and solder the shield of the coax to the ground plane.



Alternate view.

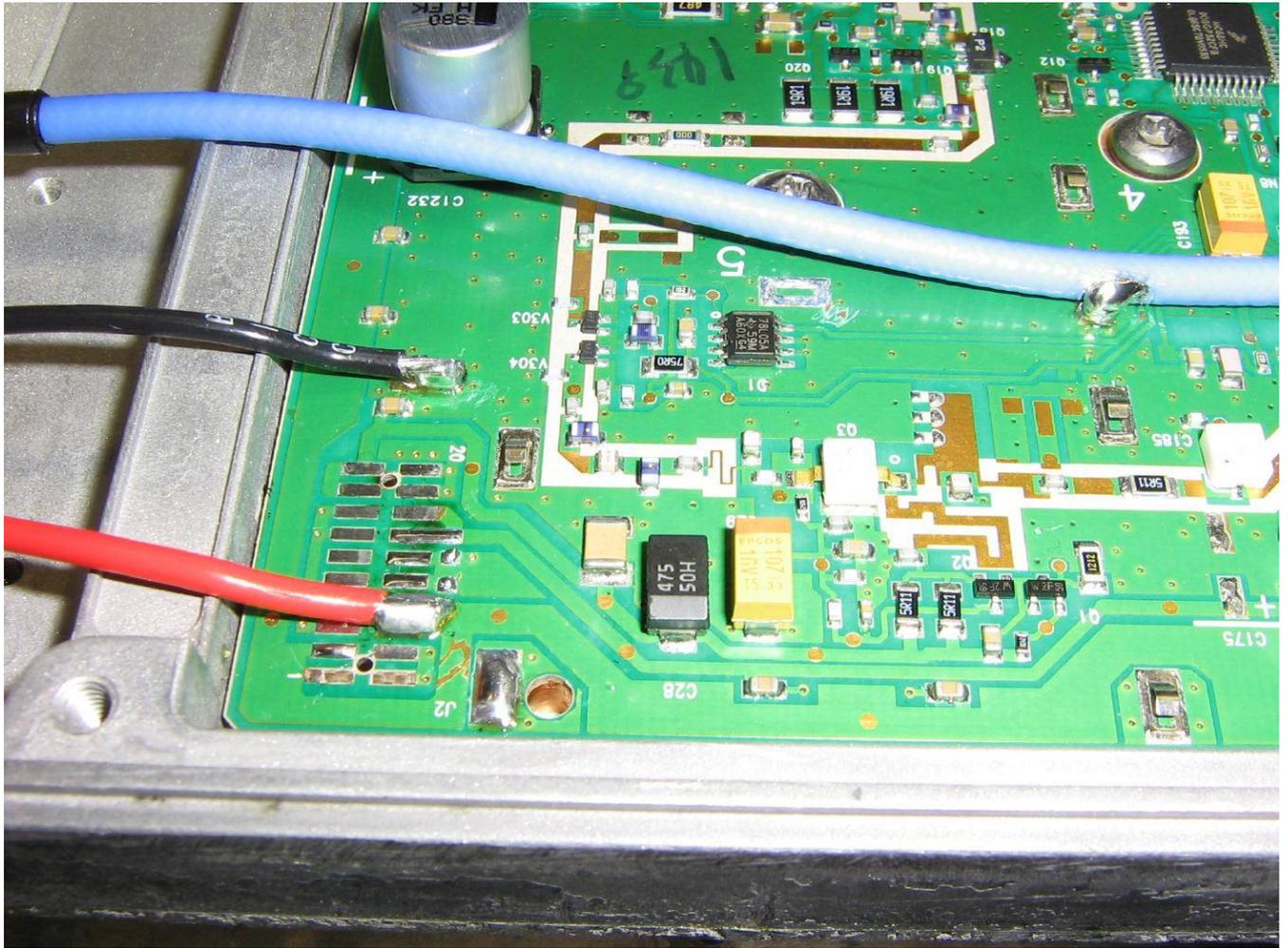Try to use Teflon dielectric coax to avoid any melting and to ease soldering.




+28 VDC power input connections.

The **BLACK** wire is **NEGATIVE**.

The **RED** wire is **POSITIVE**.

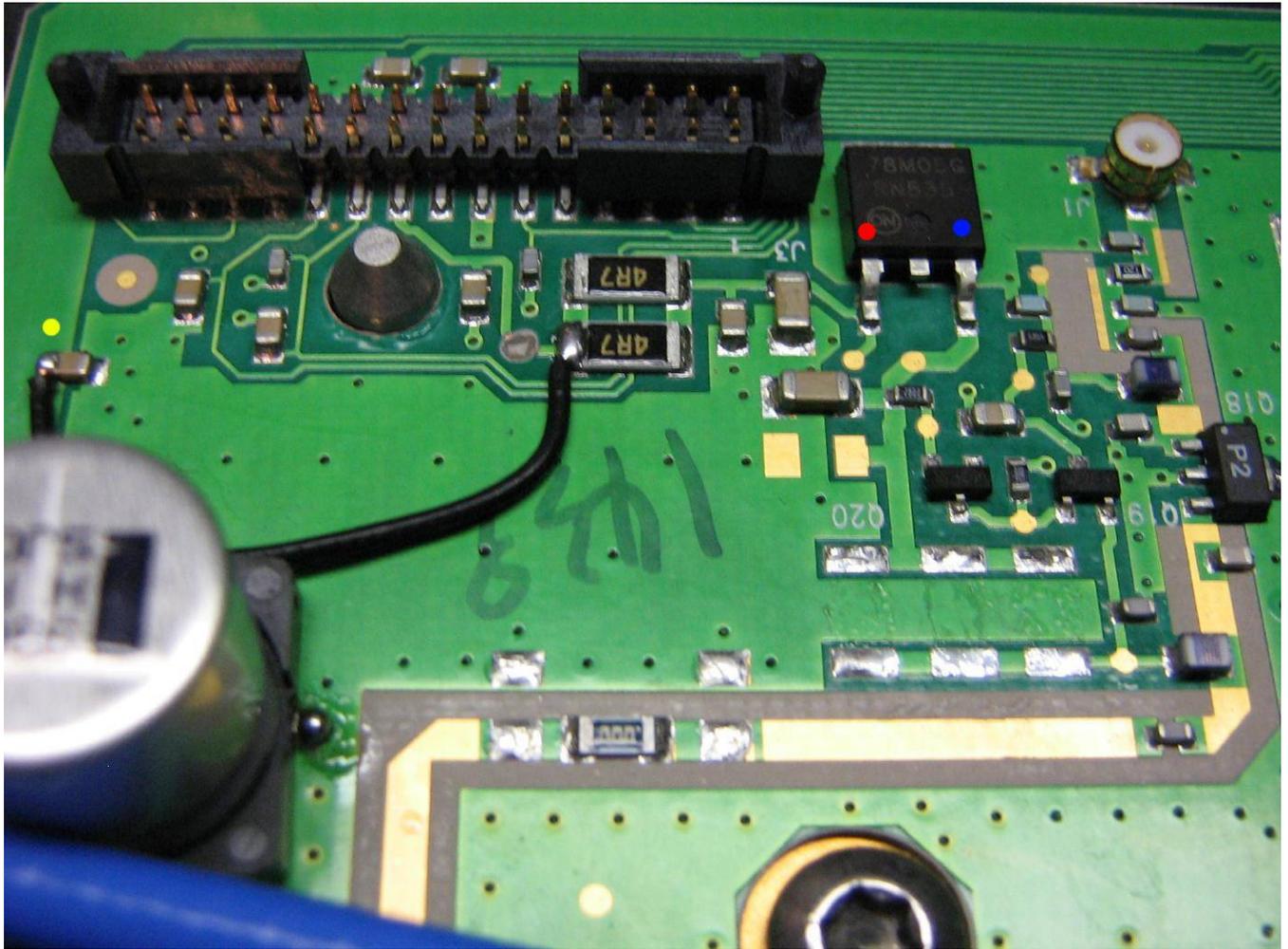Unsolder the amplifier's original power input terminal strip and solder the power connection wires like so. The negative wire is actually going to an unused solder pad on the amplifier's ground plane.




The BLF4G20LS-110B requires an approximate 3.2 VDC bias voltage on its gate for proper class-AB operation.

To generate this voltage, we'll isolate and use a 78M05 voltage regulator on the amplifier circuit board.

In the above picture, the **YELLOW** dot is the +28 VDC input for the 78M05. The **RED** dot is the input pin for the 78M05 and the **BLUE** dot is the 78M05's output.


Note that you'll need to follow the traces on the output of the 78M05 and remove three series resistors, as shown above.

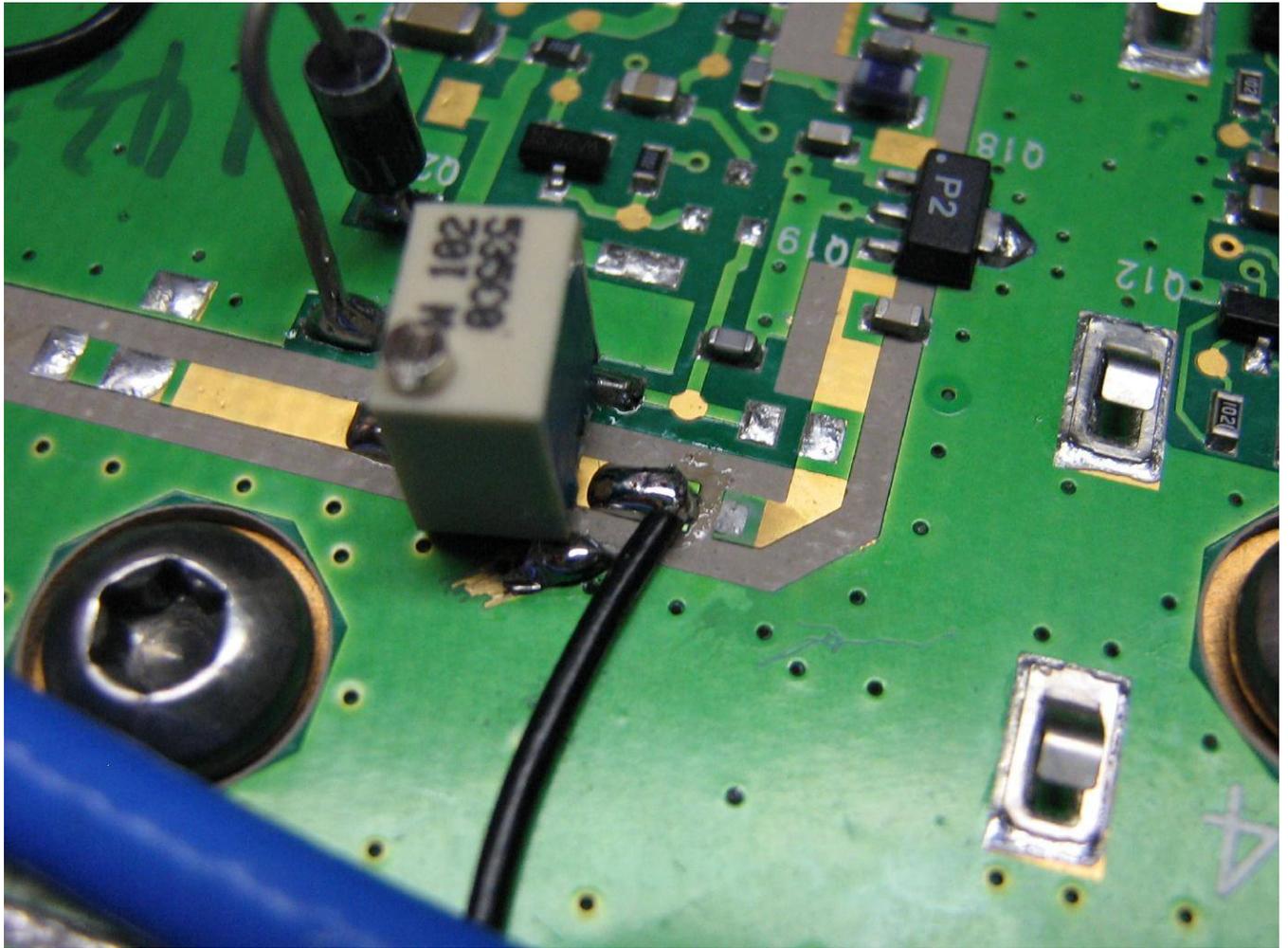Solder a jumper wire from the **YELLOW** dot (+28 VDC) to the two parallel 4.7 ohm resistors on the input of the 78M05.



After removing several unnecessary components on the output of the 78M05 voltage regulator to isolate the solder pads, you'll need to add a series 1N4001 diode and a surface-mount multiterm 1 kohm potentiometer. The series diode is optional, but helps to protect the BLF4G20LS-110B from exceeding its maximum gate voltage.

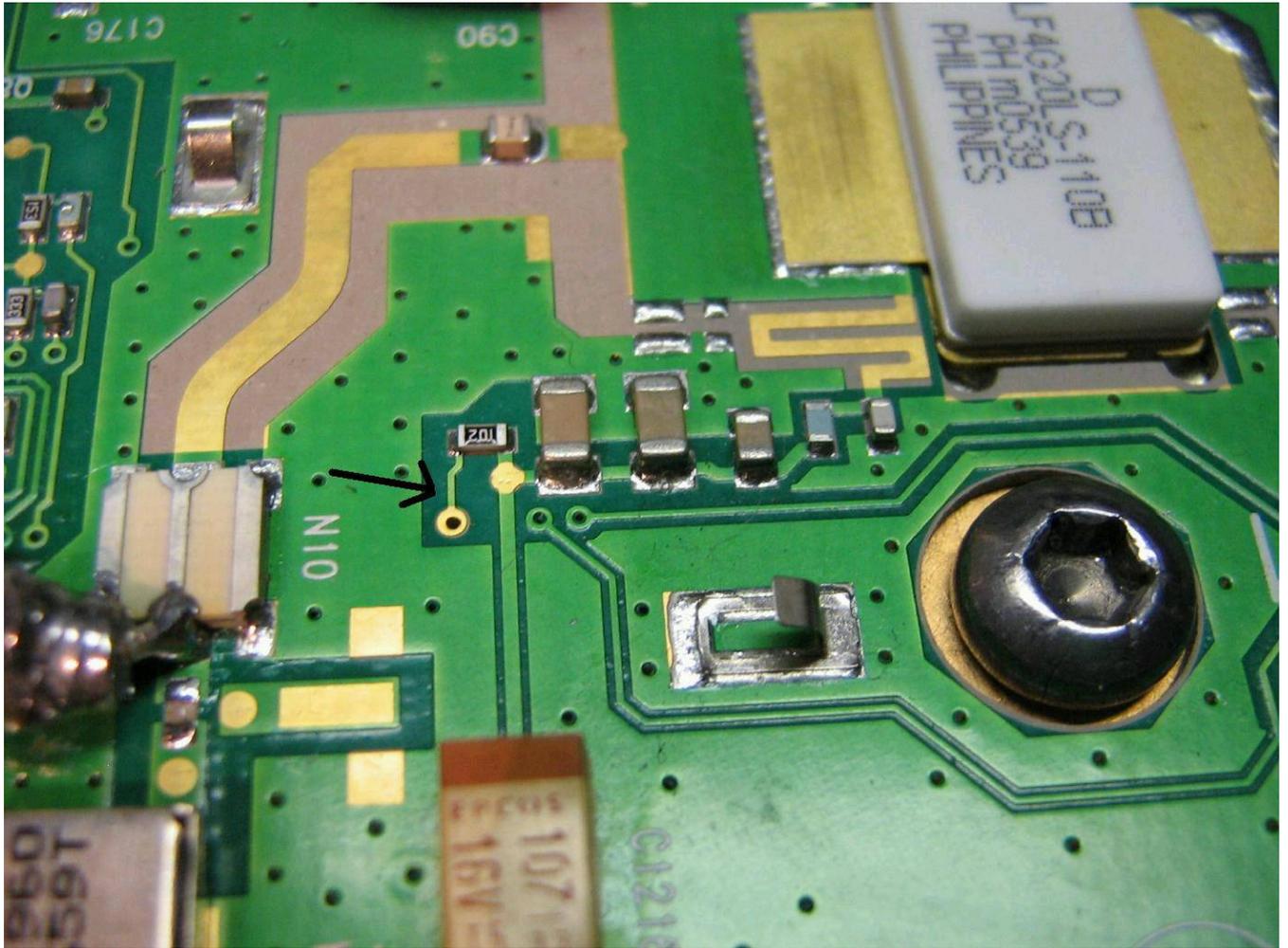
One side of the 1 kohm potentiometer will go to the +5 VDC and the other to ground. The wiper output will go to the gate bias circuitry near the BLF4G20LS-110B.




BLF4G20LS-110B gate bias components.

You'll need to cut the trace where the arrow is pointing to isolate it from that feed-through via.

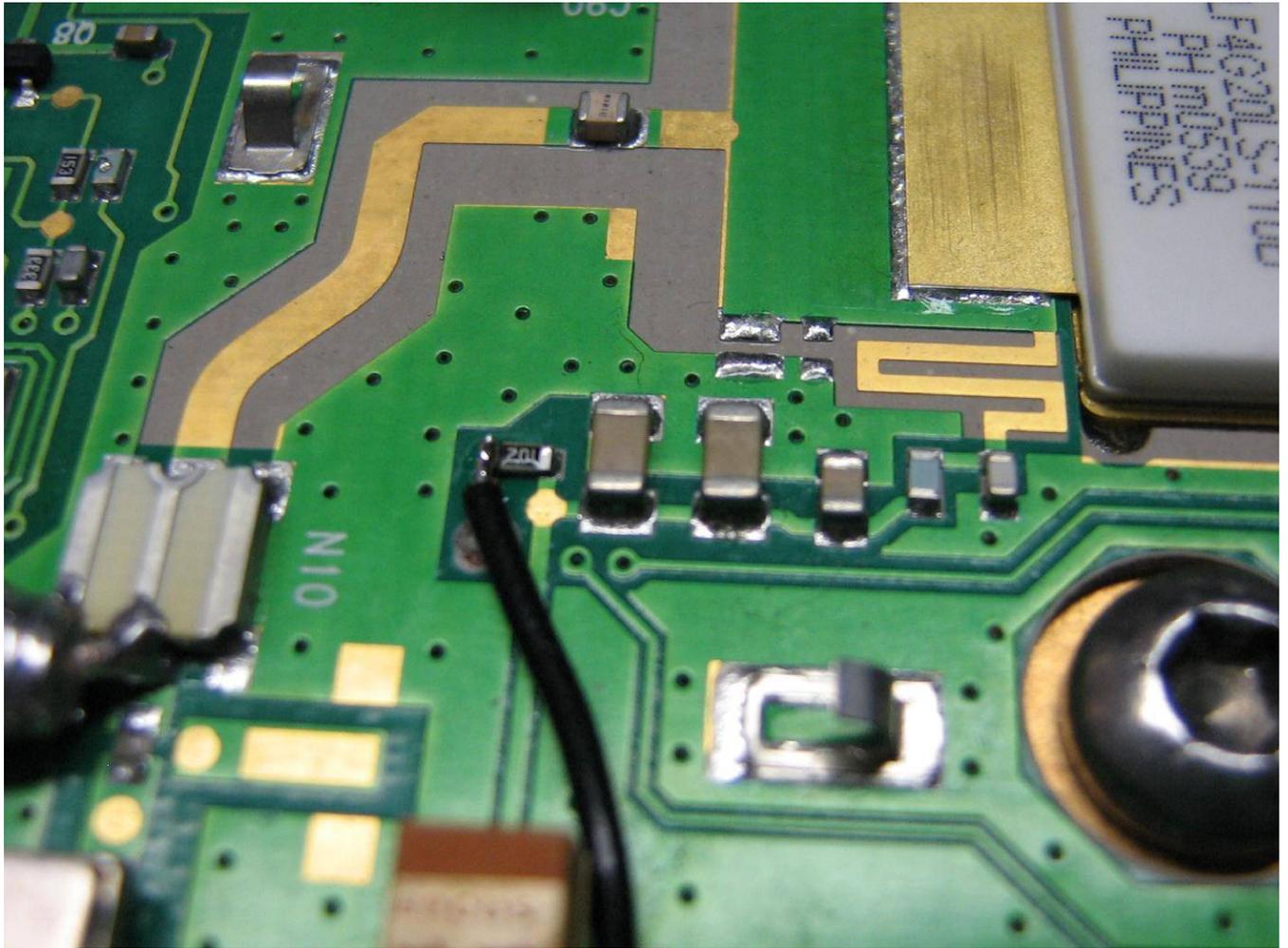
We'll be isolating this bias line and adding our own gate bias voltage.



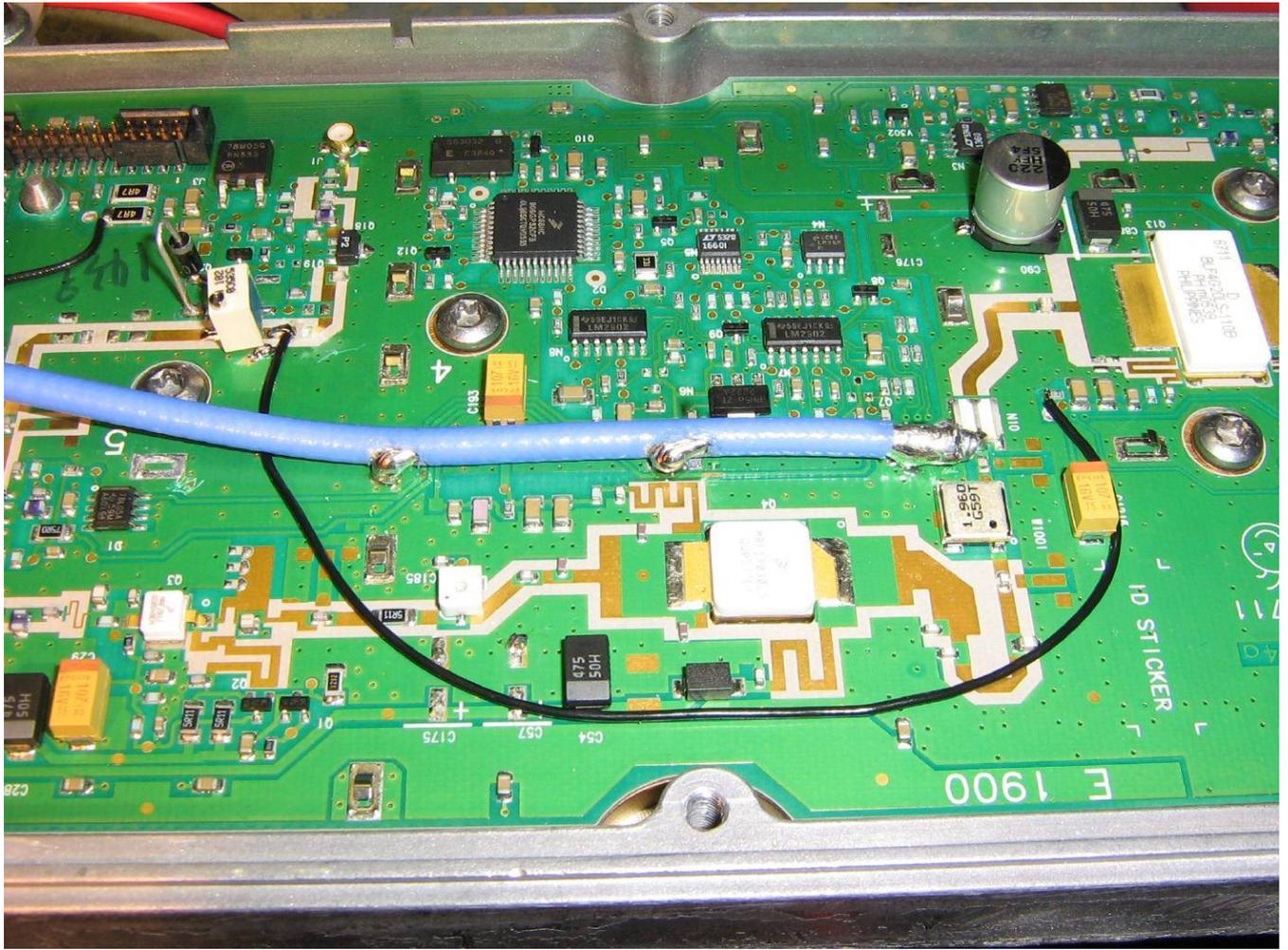Solder a wire from the wiper of the 1 kohm potentiometer on the output of the 78M05 to the 1 kohm resistor in the BLF4G20LS-110B gate bias input, as shown above.



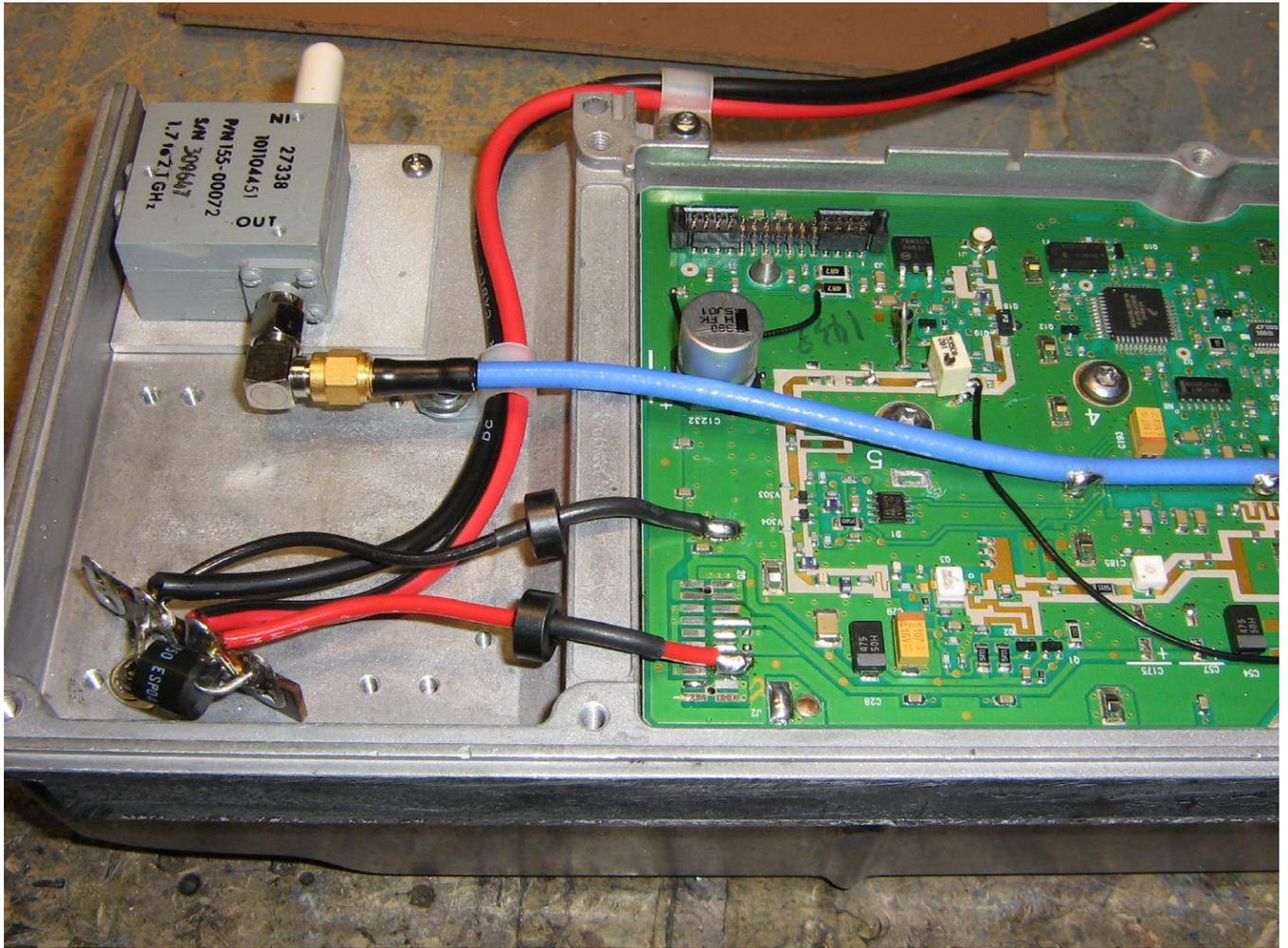
Overview of the modifications performed so far.



Finishing and connecting the DC power input connections and RF input.

Optional ferrite beads were slipped over the DC power wires.

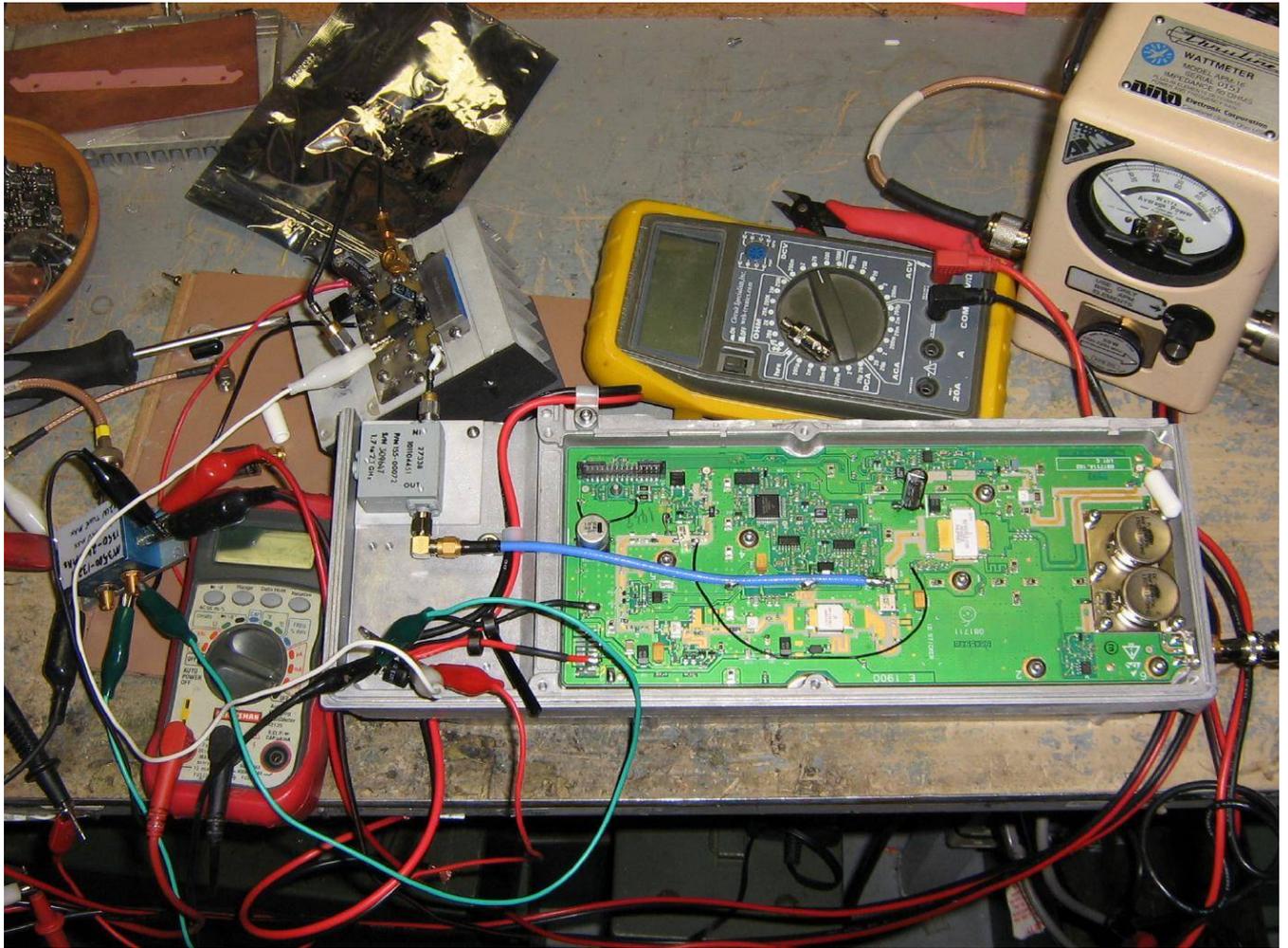There is also an optional DC polarity protection diode on the solder terminal strip.




Setting the quiescent drain current on the BLF4G20LS-110B.


Connect good 50 ohm loads to the input and output of the amplifier and apply a clean source of +28 VDC power through an accurate current meter.

Slowly adjust the 1k ohm gate bias potentiometer until the amplifier is drawing around 650 mA of current with **NO** RF power applied. This should be equal to around 3.2 volts DC on the BLF4G20LS-110B's gate.

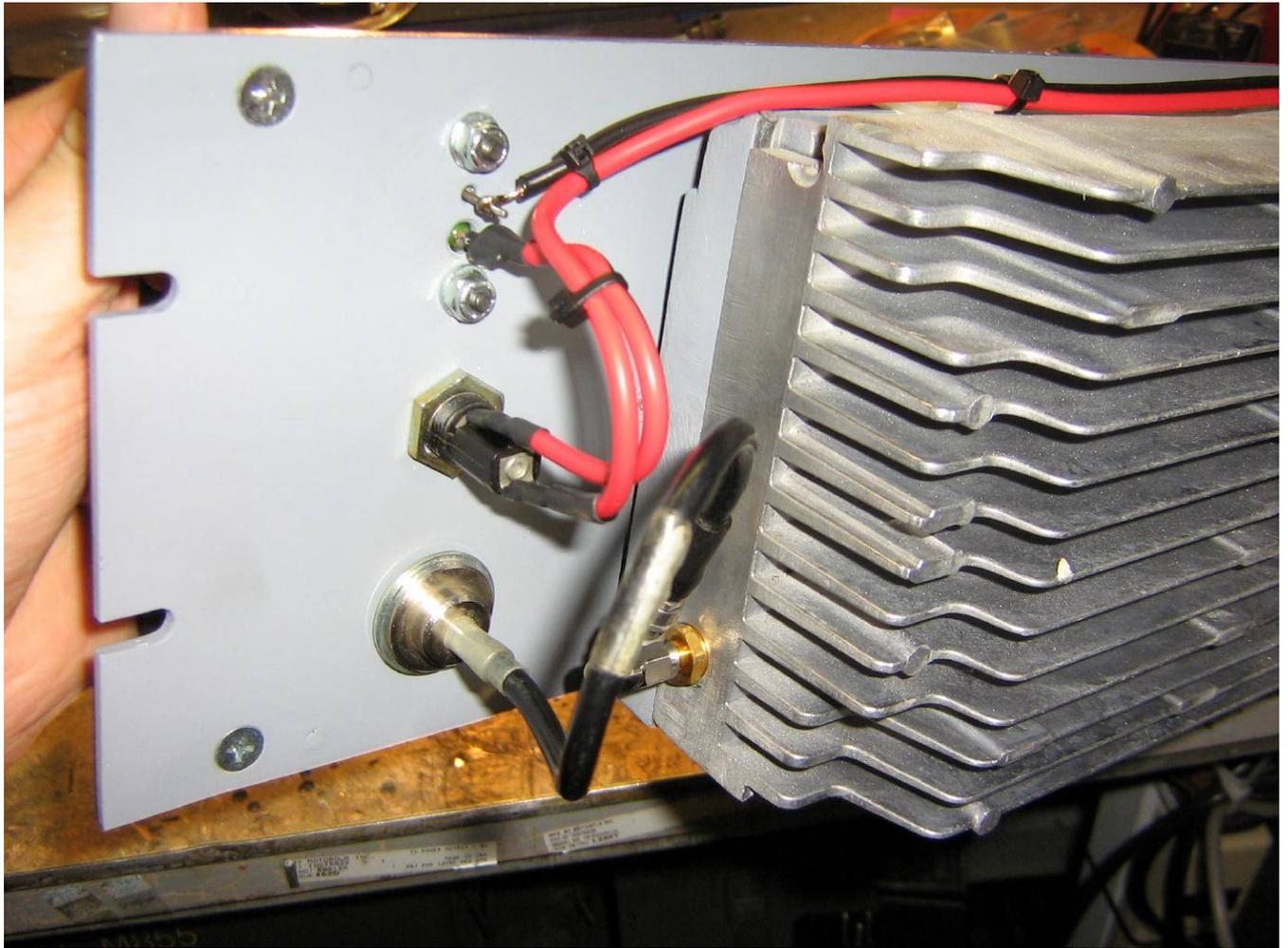Let everything "warm up" for a bit and see if the quiescent drain current varies at all over time. It should be fairly stable when set.



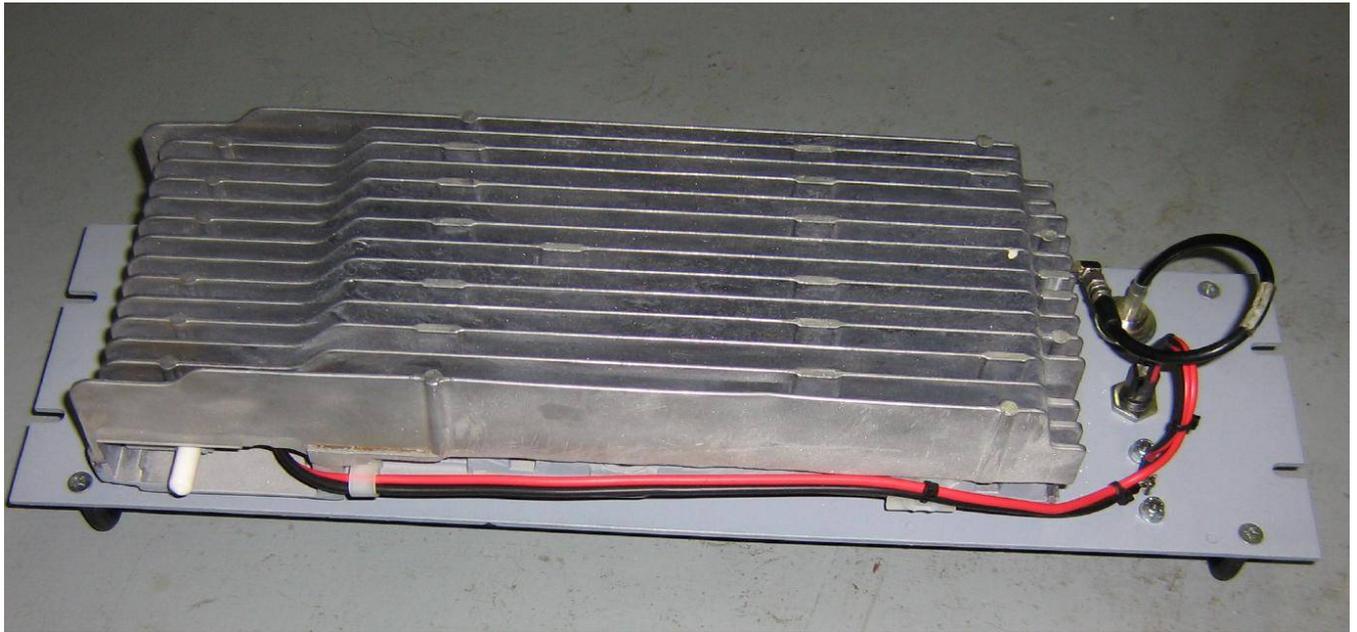Rear view of the front-panel showing the DC input wiring and fuse, and the panel-mounted N connector for the RF output.



Rear view of the amplifier showing the DC power and RF connections.


The white cap protects the SMA connector on the input RF isolator.



Finished amplifier front-panel overview.

5 watts in gives around 100 watts output at 2 GHz. I'll keep fiddling with it to try and get more RF power out at 2.3–2.4 GHz.

## BLF4G20LS-110B Application Note Schematic

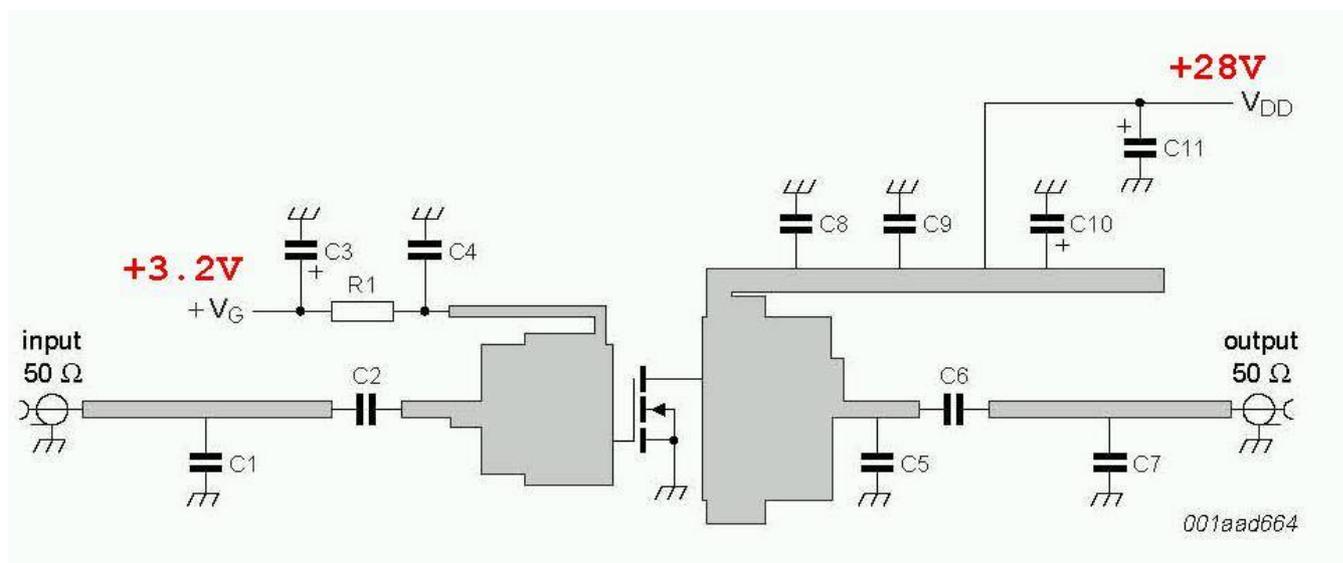

**Table 8: List of components (see [Figure 10](#)).**

Component	Description	Value	Dimensions	Catalogue number
C1	multilayer ceramic chip capacitor	[1] 0.1 pF		
C2, C4, C8	multilayer ceramic chip capacitor	[1] 11 pF		
C3, C10	tantalum capacitor	10 $\mu$ F		
C5	multilayer ceramic chip capacitor	[1] 0.5 pF		
C6	multilayer ceramic chip capacitor	[1] 8.2 pF		
C7	multilayer ceramic chip capacitor	[1] 0.2 pF		
C9	multilayer ceramic chip capacitor	1 $\mu$ F		1812X7R105KL2AB
C11	Philips electrolytic capacitor	220 $\mu$ F; 35 V		
R1	Philips chip resistor	5.6 $\Omega$	0603	
W1	hand made wire		5 mm	

[1] American Technical Ceramics type 100B or capacitor of same quality.