

"CAN I HAVE MY BATTERY BACK NOW, DAD ? ...

SEQUENTIAL TR CONTROL - 2 METRE TRANSMITTER - SINGLE SIGNAL HW7
HW 9 CONVERSIONS - CAR BOOT SPECIAL - SHD TRANSMITTER - L.P. FILTERS
AF FILTER/CLIPPER - 10MHz TRANSMITTER - ARGOSY MODIFICATION - TTL TX
10 METRE RECEIVER - 2 METRE CAR ANTENNA - V.H.F./H.F. POWER METER
GOOD OPERATING - COMMUNICATION FORUM - V.H.F./S.S.B. & MEMBER'S NEWS

JOURNAL OF THE G QRP CLUB





C G-QRP CLUB

St. Aidan's Vicarage, 498 Manchester Rd ROCHDALE, Lancs, OL11 3HE. Rochdale [0706]31812


Dear Hembers

Another summer brings the usual UK crop of RadioRallies and events. I hope to be at several local rallies and the club will be out in force at the RSGB National Convention in July.

We have a major stand at that event with 16 feet of frontage as part of the RSGB main exhibit. This year the RSGB theme will be "amateur radio and youth" and our contribution will be to display and encourage the QRP and Home Construction aspects of our hobby.

On the same theme, Gerald, G3MCK, has been serving as a club representative on the RSGB Study Group working on the proposed Student Licence. Gerald is clearly showing that our approach to amateur radio is ideal for the newcomer.

Hope to see you on the bands - 73

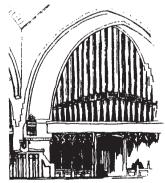

NEVER WORKED G3RJV?...Here's Your Chance!


On SATURDAY, JULY 30th, G3RJV/A will be active from St. Aidan's Church, Rochdale from 9am to 9pm (0800 - 2000 GMT) WHAT FOR ? This will be a SPONSORED QRP STATION as my meagre effort towards raising some funds to restore the St. Aidan's Church Organ. Thats it on the left. For the experts, its a Father Willis, 3 Manual, 44 stops and 2,565 pipes. Not QRP! About half a million pounds worth of whistles in need of several thousand pounds worth of restoration. I intend to work QRP for 12 hours and invite people to sponsor me for the number of contacts made. But - I will be making gentle QSOs not contest quickies, so the total could be quite modest.


The Station will be an Argonaut 509 (2w out) with a GSRV from the Church Tower. If you want to work G3R3V/A on that day, Try these bands/times on QRP Frequeies 0800:80m,0900:40m,1000:20/15/10,1200:80/40,1300:20/15/10,1700 & last hour on 80m I will be looking for members and two way QRP QSOs all day and US members from but 1500 on 20/15m. Please write to G3R3V for a SPONSOR FORM or, if you wish, send a fixed donation (Cheques:St.Aidan's PCC). Perhaps see you on that day?

SEQUENTIAL T/R CONTROL FOR D.C. TRANSCEIVERS

by G3MBN

I have been carrying out some mods to my d.c. rigs for 80 and 160. After a few reports of chirps, it became obvious that there was a timing probleam with the fully qsk design. This meant installing a bit of logic to achieue sequential timing during the c/o operations. ie the VFO was still busy changing frequency between TX and RX when the TX was still activated. I have enclosed my version of a suitable circuit for use with any d.c. transceiver. Originally found in ARRL Hand Book 1983. When set up correctly it is extremely effective and simple to install.

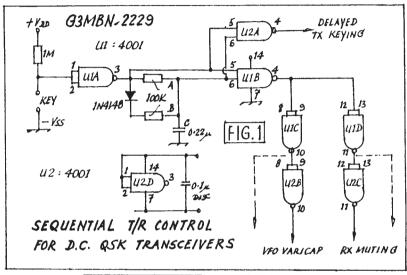

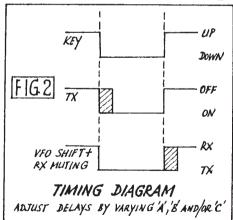

McSPRAT MEETING ON OCTOBER 15th AT STRATHCLYDE COUNTRY PARK WATERSPORT CENTRE, MOTHERWELL. ALL INTERESTED CONTACT GM3 MXN Phone 0698 887176.

ONE WATT VHF TRANSMITTER

By Gordon Pope G3ASV.


This is the circuit of the one watt 144mHz Tx in use at G3ASV, together with the PCB pattern and component positioning layout. The P.A. stage draws about 100mA in the key down position. I found it was also draws about 100mA in the key down position. necessary to key the driver stage Tr6. This was This was because of carrier breakthrough to the antenna occured during key-up and was annoying on local contacts.


R22 was added during circuit refinement and was not included in the original PCB layout. In my model, I have included it on the PCB pattern side.

The side tone oscillator is not critical and was built on a small piece of veroboard. R.F feed resistor R26 is connected close to the coaxial O/P lead with a short lead to the side tone generator.

I have not included the PCB layout of the modulator as here again it is not critical, although in my model BA102 diode D1 is arranged to have short leads to VC1 using a 16.669mHz crystal and covers about 15KHz on either side of the CW calling frequency.
Tuning up was done with an absorption wavemeter calibrated with a

commercial dip oscillator.

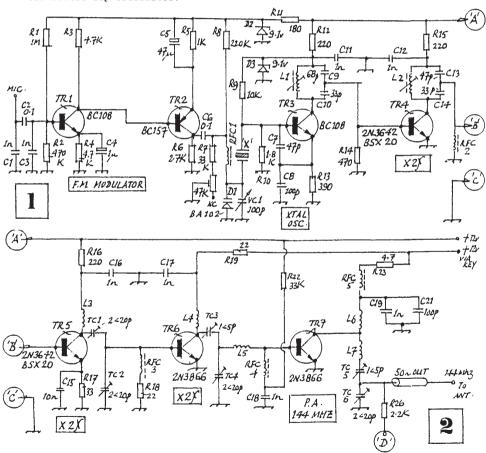

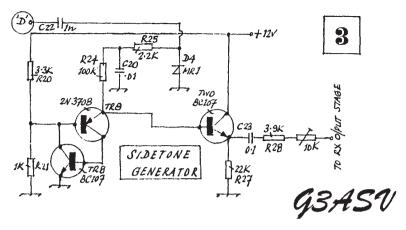


G3ASV TWO METRE TRANSMITTER

INDUCTOR SCHEDULE:

RFC 1:3 turns 24 swg through 2 holed ferrite core

RFC 2 : 4 turns 28swg through ferrite bead

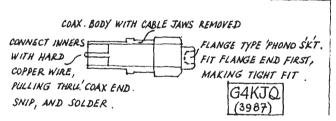RFC 3/4/5/ : 3 turns 28 swg through ferrite bead



PHONO TO COAX ADAPTOR

R. Crawford G4KJQ

A flange type phono socket whilest not much use for bulkhead fitting can be saved from the junk box and used with a coax plug to provide a useful adaptor.


"NOTES ON THE IMP" (see SPRAT 53)
GOEBQ


I am pleased that the rig seems to have gone down well and hope to talk to a few of your imps

The receiver audio section has more than enough gain; I had included the preamp after the mixer (from Georges mods to the Ju6:CQRP Handbook). Since my phones are rather insensitive and this could possibly be omitted. Alternatively observant readers will have noticed G3HKD's audio filter from the same issue which could well replace the preamp and provide some selectivity.

A useful mod is to connect a capacitor from the input to the audio gain control to earth (rather than from the track as in Ian's version), as this seems to cut out a lot of noise and hiss. I used 0.luf, but experiment to suit your phones and taste.

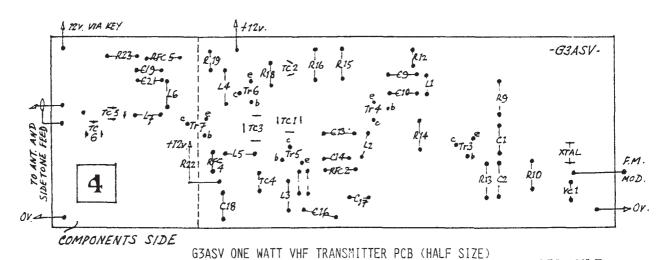Anyway I'm well pleased having worked 17 Dxcc with the 250 mw to a half size bent GSRV. Its much more fun than 3W!



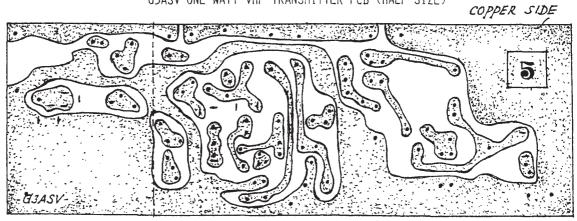

Here at LX1BK I started QRP'ing with the HW7 way back in '74. But even after many modifications I didn't like the direct conversion RX, so I changed to a superhet using an XF9B filter out of my junkbox. The oscillator frequencies are as follows:

Band	VFO Frequency	Remarks			
14	5 MHz				
10	6.3 MHz	tripling to 19			
21	6 MHz	doubling to 12			
28	6.3 MHz	tripling to 19			

Fig 1 shows the detailed circuit diagram of this modification. The MC1496 comes from a former mod given by DJ1ZB in the QRP circuit book p.71, a SO42 (G3WWS in SPRAT 38) could be used instead (or even the original Q1). It is mounted on the HW7 board near D1.

For the RF amplifier I use a T50-6 with 22 turns and a 6 turn link on the source side and in the drain a 6mm former with a slug tuned to the same inductance. Both circuits are tuned by the two sections of C1 which I made by sawing the stator of a conventional capacitor in two. The transistor and its associated components are mounted under the main circuit board.

TR offset is obtained using a RIT circuit in the VFO, markings on the front panel show the settings for the different bands. This is not very accurate and a neater solution is to adopt the DJ1ZB circuit given in the same article.

IC1 (130.55mm) is mounted horizontally in the rear left corner about 30mm from the upper edge of the back plate. There is enough room for a two stage audio filter and a LM386 audio stage, and even a simple AGC (e.g. Solid State Design P104).

PC2 (32.75mm) is mounted on two long screws immediately above the push switches to ensure short leads. Here I confess that the circuit is not the best; good filtering requires bandfilters not single tuned circuits. However, there are enough contacts to switch a bandpass circuit.

PC3 (30.90mm) is mounted parallel to the main circuit board over RFC1, C28 etc so as to clear the main tuning capacitor.


I make PC boards as follows:

First I make an approximate component layout (often this need only be a mental picture).

I then drill the mounting holes using bits of Veriboard as a template. I then mill away the copper between the leads using a high speed motor tool.

Components are mounted on both sides of the board to obtain a high packing density. I usually run the B+ line the whole length of one side of the board.

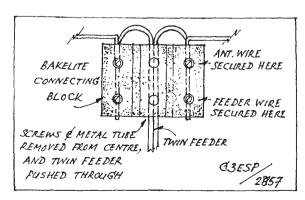
Once the TR offset had been trimmed correctly the modified rig worked very well and netted me quite a few contacts, especially on 10MHz.





CHEAP DIPOLE CENTRE PIECE


Walter Farrar G3FSP

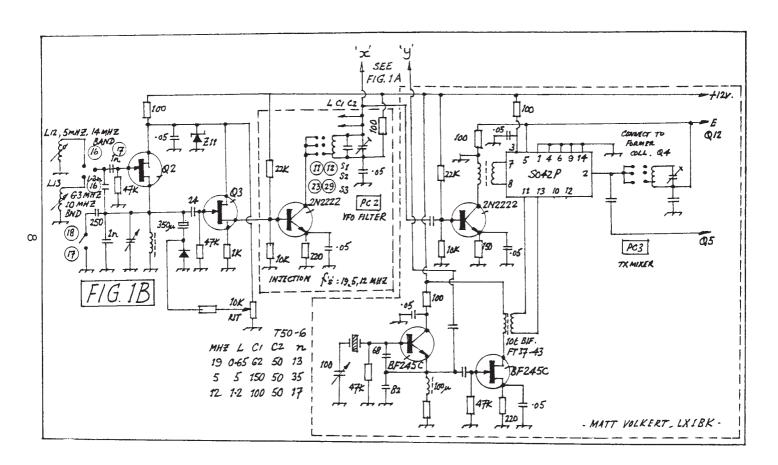Wanting to rig a 20 metre dipole in a hurry, I quickly found enough 16swg H/D copper wire and some twin feeder, but what about a centre piece? I found a Bakelite 3-Way electricians conencting block (a polythene one may not be strong enough) and the antenna was assembled as shown in the sketch.



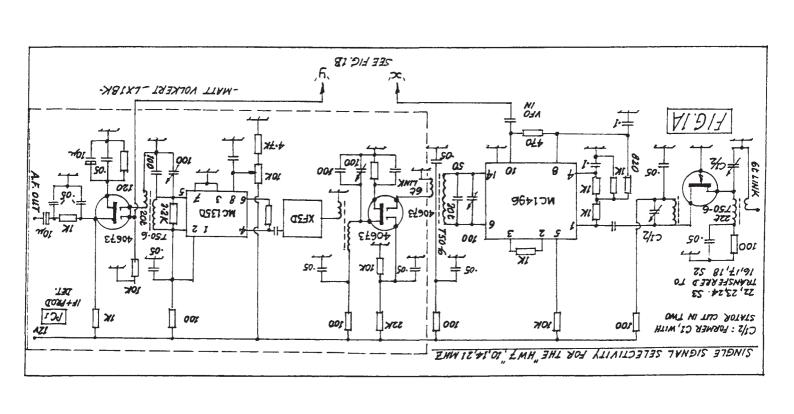

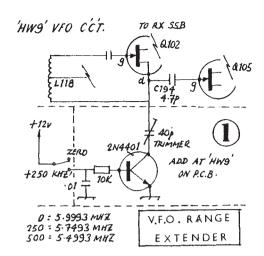

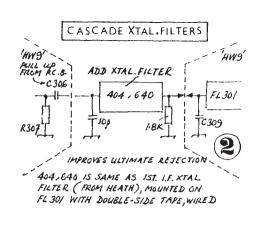

REQUIRED FOR RX SSB, ALSO
FOR CW, NO NOIST-FILL
BETWEEN 470

100 Ju
15v

ADD

RSII

D305

U302

COULD ADD SLOW/FAST SW.


SLOW A.G.C. MOD.


A SELECTION OF HW9 MODIFICATIONS

BY D.A. MICHAEL W3TS

A selection of modifications for the popular Heath ${\sf HW9}$.

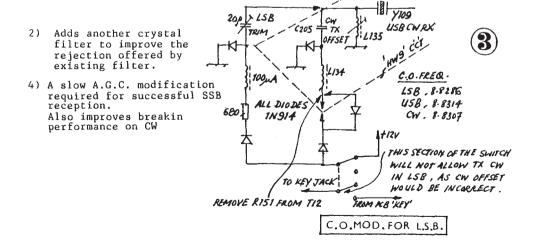- Extends the tuning range for the reception of SSB signals.
- Enables upper and lower sidebands to be received and includes a CW C.I.O Freq.



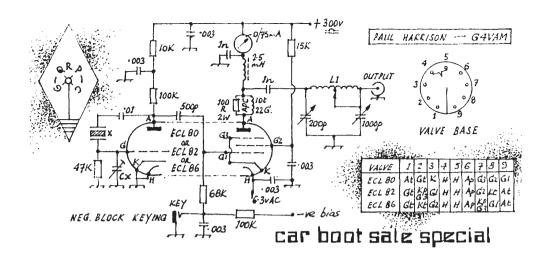

CAR BOOT SALE SPECIAL Paul Harrison G4VAM

The Valve, Transformer and Smoothing Capacitor were culled from an

old tape recorder bought at a Car Boot Sale for 50 pence.... a) Cx = 0-50pf (adjust for best drive)

b) No component values are critical

c) V1 could be ECL80, ECL82 or ECL86 base connections given for each

d) Use Fundamental Crystal.

Test results for ECL86 1.8MHz = 6 watts out

3.5MHz = 5w 7.0MHz = 5w

10.1MHz = 4w14.0MHz = 1.5w


e) Pentode section screen. Power variation circuit shown

f) L1 : Try 1 inch dia former, 65 turns of 26 swg taps at 5,10,15,20,25,35 & 55 or a T130-2 toroid for compactness (of size and field)

var. output

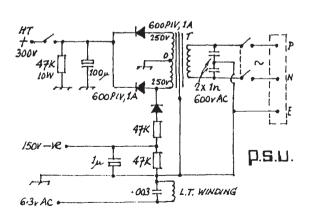
g) 100 ohm APC = 10 turns of 22 swg on 100ohm 2 watts carbon resistor

I prefer neg, block keying for crisp clean note. The PSU provides a suitable power line. Cathode keying of the PA is possible but remember to earth the grid bias resistor. Remember the key terminals are at high voltage albeit at high resistance. It: 250-0-250 volts D1/2/3: 600piv, 1 amp.



ECL 80 ECL 82

ECL BG

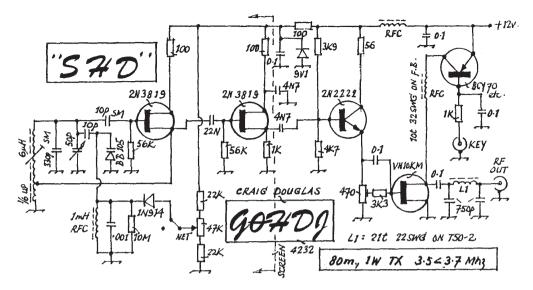


This circuit is the result of many happy hours reading through back issues of SPRAT. Many of the ideas are borrowed, so I hope the originators do not mind. I enjoy construction and everything from the power supply to antenna balun is homemade.

The circuit is simple. The VFO coil is 6uH, slug tuned : mine is 21 turns of 24 swg, tapped at 18 turns on a 9/16" ceramic former (car boot sale). Trial and error plus calculations and frequent checks with a dip oscillator got it working in the range 3.50 - 3.70 MHz. A BC108 could replace the 2N2222A but the latter gives more drive

As with the VOXNER - the 470 preset should be adjusted from the earthy end until 2.9 - 3.0 volts is attained. The RF output seems to peak at this point to about 1 watt.

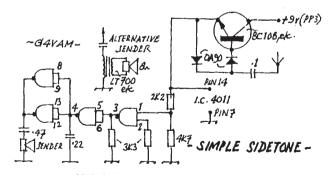No PCB layout is given - mine was rather large. The rig has been in use for some time and received pleasing reports from fellow QRPers and QRO stations. Thanks go to members of the Yeovil ARC for their interest and help with the SHD.



SIMPLE SIDETONE Paul Harrison G4VAM

The circuit was developed to avoid the requirement for a separate sidetone circuit in every rig I build. The oscillator is stolen from the "Hilltopper" by ${\sf GM4JMU}$ and values changed to suit.

TRI acts as an RF switch and no other switch was provided. The antenna is 18 feet of hookup wire draped near the ATU. The circuit is sensitive enough to be activated by the author's LW output 7MHz TX.


D1/2 are germanium diodes. The sounder was from an old pager but a crystal earpiece might serve or try the inser¶ gircuit shown.

W3NQN STANDARD CAPACITOR 7 ELEMENT LOW PASS FILTERS


Values calculated by G3RJV from the data supplied by W3NQN for Seven Element Low Pass Filters using standard capacitor values.

REFERENCE: SHORT WAVE MAGAZINE - December 1983 and January 1984.

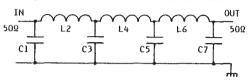W3NQN SEVEN ELEMENT LOWPASS FILTER CIRCUIT



BAND MHz :	C1/7 pF	C3/5 pF	L2/6	L4	W1RE swg	CORE		
3.5	470	1200	25 t	27t	28	T37-2		
7.0	270	680	21 t	24t	26	T37-6		
10.1	270	560	19t	20t	26	T37-6		
14.0	180	390	16t	17t	26	137-6		
21.0	82	220	12t	14t	22	T37-6		
28.0	56	150	10t	11t	20	T37-6		
	ADDITIO	ADDITIONAL BANDS :						
1.8	820	2200	30t	34t	26	T50-2		
18.0	110	270	14t	15t	24	T37-6		
24.5	82	200,	12t	13t	22	T37-6		

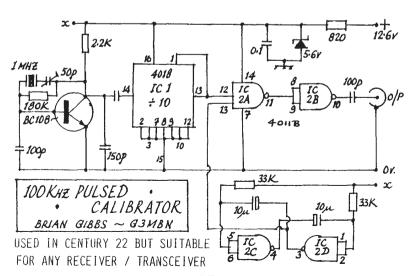

AUDIO FILTER AND CLIPPER FOR THE Ten Tec ARGOSY II and other receivers Bills Wright GOFAH

You don't have to look out the window to see when it's winter. Just listen to all the heating switches crashing about on your receiver! Well, I got a bit fed up with this so I devised this circuit to give my ears a rest and at the same time reduce the hiss that was noticeable on my Hi-Fi headphones.

Although it was specifically designed for my Argosy 2, based on the Corsair l circuit, it will work with any receiver that can provide about half a volt P/P of audio at the input. On the Argosy 2 only one soldered connection is made for the 8 volt supply, while the audio uses an existing plug and a short made-up lead; so the modification need not be permanent.


The circuit, Fig.1, is built around a dual FEI OP-AMP on a small board 3.3" long by 0.7" wide and is attached by two 6BA screws and spacers top the inside right-hand side panel near the audio gain control and above the audio CW filter. There are two holes here one of which was used to hold the mains power feed to the $\rm ON/OFF$ switch on the PSU only, and so keep hum inducing mains away from the rig.

Al functions as a soft clipper with a gain of unity. The maximum output is 1 volt P/P; that is 6 db above the normal signal levels provided by the ΛGC of the $\Lambda rqosy$. After the clipper the audio passes through a 3-pole low pass filter. This removes any harmonics that may be produced by the clipper and the HF hiss. The filter is flat to 2.7 kHz, 3 db down at 2.9Hz, -10 db at 4kHz and -20 db at 5.8kHz. The output coupling capacitor was chosen so that, with the $\Lambda rqosy$ audio CW filter switched OFF, the LF end is -6db at 100Hz. There is no DC isolating capacitor on the input as this is already provided by C27 on the IF-AF hoard. Λ LuF capaciator should be used here for other receivers.

Construction is by the usual printed circuit board and Dalo pen method. I mark the PC board through a piece of plain perforated board as a guide for the component lead holes. Rub-down transfers are used for the holes and a Dalo pen to join them up resulting in a very professional appearance. The Decon-Dalo 33 Blue PC pens are OK but other black ink versions are not so good. You may have to expand the layout in Fig.2 to accomodate larger capacitors. The board should he cut to size and the mounting holes marked out and drilled first; whenever I do it the other way round I end up making "adjustments" with a small file! After the board has been etched and drilled, tin it all over with a clean iron. This helps when the components are fitted and again gives it that professional for lee look.


The connections for the audio in and out use 0.1" PCB plugs (Cirkit cat. page 53). Take plug 26 from the filter switch board and plug it to the input. Hake up a short twin lead with PCB plugs and connect the output back on to 26 on the filter switch board. The PCB plug on this end of the lead may need cutting down with a sharp knife for a fit. The 8 volt supply is taken from one of the "REG" points on the control board.


The performance of the clipper is very good with no distortion on peaks while doing vy fb on the "crashes". The filter removes the hiss without reducing the speech quality. This means I can continue to use my Hi-Fi headphones which do not have the odd resonances of the cheaper ones. I once tried on a pair of well known Japanese communication headphones which had virtually no response at 750 Hz, OK for speech but lousy for proper radio!

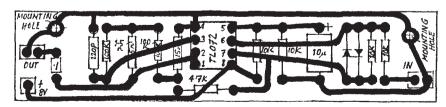

LAYOUT-COPPER SIDE

FIG. 2

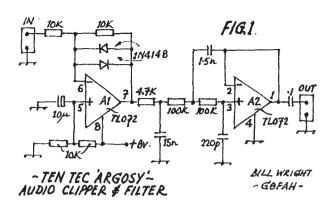

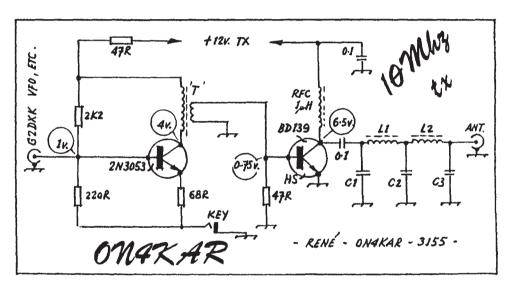

10 MHz, 1.5 wtt Output Transmitter ON4KAR

The VFO is from G2DXK's design in RAD COM for June 1984 retuned for 10.1MHz. The Driver is of W3TS (SPRAT 44) but the transformer is made from salvaged TV set shielded IF transformer: Prim. (4.5uH) 52 turns of 0.4mm enam wire on 5mm dia slug tuned former

Sec. 8 turns of 1mm enam wire on Prim. winding Tune for most power out.

PA transistor: BD139 (with heatsink) L1=L2: 4t 1mm wire on 4C6 core (Mullard) C1=C3: 270pF, C2 530pF (2 x 270pF in Par.), RFC: 1uH. Quoted voltages are RMS on TX measured with an Heath AM5218 VTVM.

SWITCHABLE RF AMP FOR THE TEN-TEC DIGITAL ARGOSY By D.A. Michael, W3TS

The ARGOSY II is a very good QRP/QRO transceiver, but when I use mine on 80 and 40 metres it seemed to be more sensitive than really needed causing the AGC to pop on attack and a higher than necessary background noise. Most siginals where way over S9 and my normal noise wa S4. I was looking for a way to reduce the ARGOSY II sensitivity by about 10dB.

At first I thought of adding an attenuator pad, but that does not help the dynamic range or reduce the internal noise from the RF amp stage. After looking at the schematic of the RF/MIXER BOARD 80784-D, I thought of turning off the RF AMP Q2 in RX only (it needs to be on for TX or no output results as it is a TX pre-driver stage). Turning off Q2 makes a great attenuator - it was too good - signals were very weak. Next thought was to reduce the amplification of Q2. So I clipped off one end of C12 (0.01) the emitter bypass in the Q2 emitter circuit. That worked very well, it reduced the gain about 16dB on RX and TX. I experimented a bit using my step attenuator and an external xtal calibrator as a signal generator and by putting a 100 ohm resistor (1/4 watt) in series with the best compromise between gain reduction and sensitivity loss.

Now for a way to have full gain on TX and switchable gain on RX. I don't have a noise blanker so I used the noise blanker switch as my RF GAIN reduction switch. I tried a diode and a transistor as a switching element. The diode showed a slight loss over the transistor in the TX mode, so I stayed with the transister (the transistor also requires less "on" current).


Figure 1 showes the final circuit. The noise blanker switch cable "24 is hooked up to the circuit. I didn't have a small mating connector so I used 18AWG solid copper wire as pins. I then soldered smaller 24AWG stranded hook-up wires on them to reach to the transistor circuit. This circuit is built ugly-style on top of the RF/MIXER board near Q2 and C12, with the grounded end of C12 pulled up out of the board and the control transistors emitter pushed into the C12 ground hole.

The result is very pleasing, with reduced internal noise from the RF AMP and an improved AGC action because not all signals are S9 and over. The antenna background noise is less than S1. Also improved was the DYNAMIC range and the crystal filter rejection because the mixer sees 10dB less signal.

A FEW OTHER DIGITAL ARGOSY INPROVEMENTS.

I have added a 220ohm 1/4watt resistor across the ANT. plug 33 on the RF/MIXER board. This cuts down the AM station BCI that I was having on 80m cw. I live 1 mile from a 1KW AM station; this helps. I believe because the RX ANT curcuit is not shunted with much resistance and a peak voltage from out of band high power TX'S can cause some intermod in D1 and D2. Mybe D1 and D2 should be PIN diodes - but I had good luck with the simple shunt resistor.

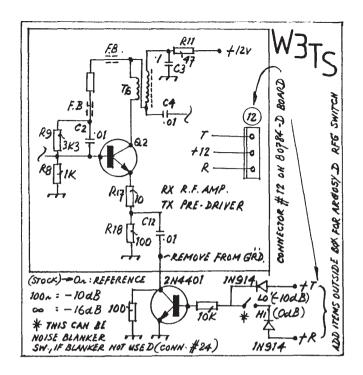
Also a hiss reduction can be had by shunting C17 (0.01) on the IF-AF board 80785-D with another 0.01 (or change C17 to a 0.02) and shunt R35 (100k) with a 470pf. This improves the high frequency roll off of the audio preamp stage.



TTL TRANSMITTER FOR 80 METRES

By Derek Scofield G4UOV

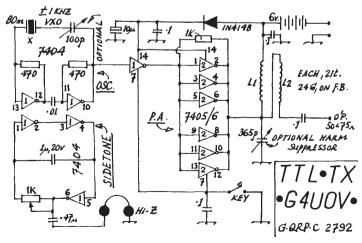The circuit is a TTL TXM for 80 metres with approximately 400mW output. It is designed around two TTL inverted chips. The first 7404, two gates used as a crystal controlled oscillator buffered by gate 3, fed to 7405 o/c invertors in parallel. The circuit works very well. I have only tried it so far locally, but had 599 from about ten miles on a long wire



A SIMPLE 29MHz DIRECT CONVERSION RECEIVER

By John Young BRS33339

(Re-printed from Oscar News)

The receiver described is a simple direct conversion set designed for the reception of the OSCAR satellite. It was built more than three years ago and the only change to the design since then has been the introduction of two tuned circuits at the input to eliminate interference from a local AM CB station. It has been used with simple dipoles, ground planes and beam antennas, both as a fixed and as a portable station.

The circuit comprises a cascade RF amplifier using 2N3819 or 2N3823 fets, (the 2N3823s will give the better noise figure), a diode harmonic mixer (1) driven by an oscillator/buffer (2), a low noise AF pre amplifier preceded by a simple low pass filter, an AF power amplifier. The output socket JI from the AF pre amplifier may be used to drive a tape recorder (Mic input), or may be connected to the domestic hi-fi (phone input). An LM380 IC amplifier is incorporated to drive an external loud speaker (8 to 35 ohm) or headphones.

The RF amplifier, mixer, LO/buffer, AF pre-amp. and AF power amp. were each constructed on separate boards such that future modifications may be made without rebuilding the whole receiver.


Although designed for the section of the 10 metre band allocated to amateur satellites, the receiver will operate over any 300KHz segment of the 10 metre band, (this being determined by the bandwidth of the RF amplifier). When setting up the receiver for the first time, it is recommended it be tuned to the SSB portion of the band, and when working satisfactorily be re-tuned to the satellite portion of the band. The setting up procedure is as follows:-

Set the oscillator tuning capacitor to full mesh and its associated 3-30pF band spread trimmer to half mesh. Tune the oscillator to 14.250MHz by adjusting the tuning slug in L2. The 1K pre-set pot (set LO) should be at 75% of maximum. The frequency of the LO may be checked against another receiver or by a frequency counter connected to the source of the buffer amplifier, (via a 1K and 0.1uF in series).

Connect an antenna and headphones. Turn up the AF gain until a hiss is heard in the headphones. Tune T2, followed by L1 and T1 for maximum increase in noise output. Tune the LO until an SSB station is heard and re-peak T1, L1 and T2 for maximum output. When the receiver is operating satisfactorily, retune the LO to 14.725MHz and peak up T2 followed by T1 and L1.

If you now disconnect the antenna there will be a noticeable drop in the output noise level, even if you live in a quiet rural area. Connect and disconnect the antenna while adjusting the LO drive for the highest ratio of antenna noise to receiver noise. Finally, by adjusting the bandspread capacitor and L2 alternatively, set the LO to cover the range 14.700 to 14.750MHz at the 10% and 90% points of the main tuning dial.

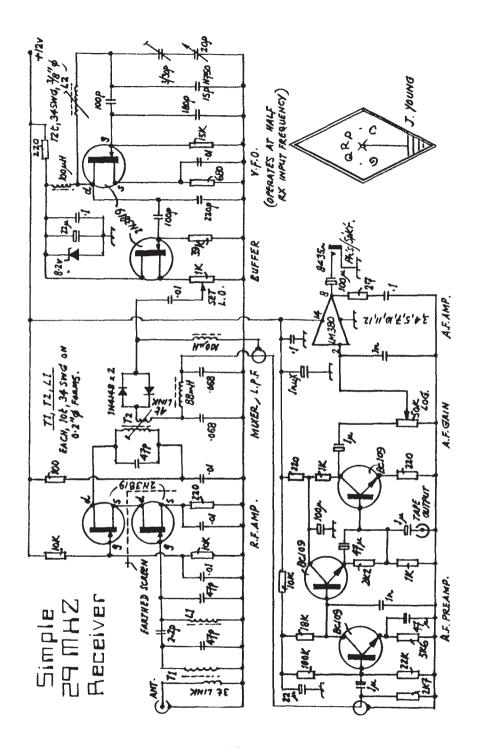- (1) Pat Hawker G3VA. Russian Direct Conversion Demodulator. "Technical Topics", Radio Communication, April 1977
- (2) J. Young BRS 33339. The Cadet DC Receiver for the Novice Radio Communication, October 1973




TWO METRE CAR ANTENNA Udo Velten DLIHCU from an idea by Fans, PAONO in CQ-DL

A simple low cost antenna which needs no holes in the chassis of the car.

FUNCTION: A radiator is fed via a pi filter and a serial C (C3) made from two brass sheets, mounted in rubber silicon on the inner and outer rear window. RADIATOR: a 50-53cm long brass rod, dia 3mm, Cut and try.

C1/C2: 30pF trimmer, add 20pF parallel if mismatched. SWR to 1:1 if possible.

L: 4 turns with dia of 10mm.

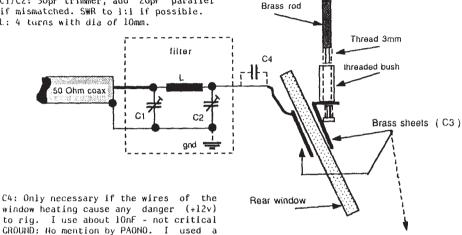

window heating cause any danger (+12v) to rig. I use about 10nF - not critical GROUND: No mention by PAONO. I used a handy and prefer clear and conditions. works with a rig thats grounded via the power supply.

Its no DX Antenna but its a fun idea. Cover the radiator with thermo shrinking tube if you wish. Do not forget to degrease the window before mounting the brass sheets.

from my experience the thin radiator produces flutter qsb driving. A stiffer material may help but thread cutting etc is more difficult on a steel rod.

30mm 30mm For easier mounting/dismounting of the

40mm

Rubber cap

radiator, solder a 3mm nut on the thread end of the rod at the upper end of the thread.

30mm

inner

Do not worry about heating wires in the window. According to Jan's and my own experience, there is no problem with resonating heating wires.

A SPRAT TIP VIC FLOWERS G8QM

A recent visit to WH Smith has solved the problem to find a suitable binder for my copies of SPRAT. They sell a very neat "9 x 7 ring Binder" at #1.20. Using a single hole punch, I make two holes at the ring spacing of 8cm apart, equidistant from top and bottom of each SPRAT and 1/4" from rear edge. clears the printing nicely. Each file holds twelve issues comfortably and of course they are easily removed if required. The contents of each binder may be displayed neatly on the spine by means of "Letraset" numbers and letters.

THE SUFFOLK TROPHY

Elegibility, any member of the G-ORP club. When Annually on Region 1 QRP Day, 17th June Any six hours during the day, taken in not more than two periods. Start/Finish times of periods to be shown in the log. Contacts Contacts with any station in IARU Region 1 count Form of Contact Normal OSOs, there are no special contest exchanges. Bands Any bands for which the operator is licensed. Power Not to exceed 3 watts RF output (CW) or 10 watts PEP (SSB). Scoring Each Region 1 country contacted on each band counts 1 The claimed score should be the total of IARU Region 1 Countries contacted on all bands used. For example 6 countries on 7MHz and 16 on 14MHz give a score of 23. Only 1 contact per country per band is allowed, irrespective of mode. Enries These should give name, address, call, power and mode used, brief equipment details, and the call sign, time and band of each contact claimed for scoring purposes. A summary giving the claimed score for

each band and the overall claimed score must be included.

Entries to A.D. Taylor, G8PG, 37 Pickerill Road, Greasby, Merseysude, L493ND to be received by 17th July. Any received after that date will be disallowed.

Awards At the discretion of the Committee the winner will receive a memento trophy and a book token for £15. Second and third will receive merit certificates.

THE G QRP CLUB YEARBOOK: A New Service to Members

Members have been enquiring about the Club Callsign/Number Membership List and we are pleased to announce that it will be part of a FREE booklet which will be issued to members with the Autumn SPRAT. The booklet will also contain a full range of information about club services and useful advice for QRP amateur radio

THE R.S.G.B. NATIONAL CONVENTION 1988 JULY 15th, 16th & 17th NATIONAL EXHIBITION CENTRE, BIRMINGHAM

The G QRP CLUB will be there with a Major Stand and Display
We invite all members to visit our stand
Please let G3RJV know if you can give some time on the stand
or simply report to the stand early on the day you attend

CLUB MEMBERS DELEGATES AT RADIO SCOUTING SEMINAR

Jennifer, G8WWO, member 4575, wife of our Membership Secretary, G4HYY, was a UK delegate for WAGGGS (World Association of Girl Guides and Girl Scouts) at the second European Seminar on Radio Scouting. At the seminar, held in Geneva, she met another club member Emilo, EAIMQ. Emilo went on to operate the ITU station with the special call 4U3ITU.

PLEASE NOTE THAT THE MEMBERSHIP SECRETARY, G4HYY, WILL BE AWAY FOR FOUR WEEKS FOLLOWING THE R.S.G.B. NATIONAL CONVENTION. This may mean some delay in membership services and the enrolling of new members.

PIRATED CALL: Watch out for G4FKD (Adrian is in the USA at present)

We regret to announce the death of Wally Yarwood, G6LKC, 2931. Wally served the club well as one of our SPRAT distributers and his cheerful help will be missed.

We regret to announce that the name of ${\sf G3BOV}$, whose death was announced in the last issue, was Edward, not Jack, as stated.

EUROPEAN CW ASSOCIATION Tony Smith G4FAI

New EUCW Chairman

From January 1, 1988, the Chairman of EUCW is Tony Smith, G4FAT, nominated by the G-QRP Club. He succeeds Edgar Schnell, DL6ML, who has been chairman for the last three years.

AGCW-DL YL-OM CW Party

To be held as part of ACCW-DL's "Year of CW YLs", this event will be held on Monday evening, 8th August, 1988, from 1630 to 1800 UTC on 3540-3560 kHz.

Reports from YL operators = RST + 88, eg 59988
Reports from OM operators = RST + age, eg 59935
Scoring:YL-OM and OM- YL QSOs = 5 points
:OM-OM and YL-YL QSOs = 1 point
:QSOs with DKOAG and DFOACW = 10 points

Logs to be sent by 10th September to:Mrs Gisels Rink, DL6ZAR, Rontgenstr. 36, D-6450 Hanau, west Germany

Worked Scandinavia on CW Award

There has been so much interest in this new Award with its beautiful Scandinavian landscape that SCAG. the Scandinavian CW Activity Group has revised its rules. The number of awards will no longer be limited, SWLs are welcome, and it is now a little easier to gain the award!

European stations need to work 75 CW stations from five of these countries, LA OH, OY, OZ, TF, and SM. At least five of these stations should be SCAG members whose membership number should be obtained during the qso. Only QSOs made after January 1st 1988 are valid for this award. Applicants should send a list, confirmed by two other amateurs, of the calls worked showing date, band, OTH, name and SCAG number where appropriate. No QSL card are required.

The fee for the award is US \$7, or DKK50 sent by postal giro to DK-7192185 or 17 IRCs. All applications to R.Meilstrup OZ5RM, Bavnestien 6, DK-2850 Haerum, Denmark.

SWLs should send a self-addressed envelope, plus one IRC, to obtain a copy of the SCAG membership list to assist in identifying SCAG members, SWL applications should be confirmed by two local amateurs or registered SWLs.

ORP BESIDE THE SEASIDE

Saturday September 10th GREAT YARMMOUTH YORK ROAD DRILL HALL, WEST DOOR Commence 1400hrs BST to 1900hrs Talk in on S22 from 1315 hours Call sign G3YRC

Provisional programme 1400 to 1420 Registration 1420 to 1430 Welcome by G30EP 1430 to 1500 Tape by G3R3V

1500 to 1600 Available 15 minute slote for guests to speak 1600 to 1630 "East Anglia The area/s contribution to two world wars with special reference to Charles Lamber alias AJ Alan.

1630 to 1730 Exhibition of Home brew equipment and judging 1730 to 1800 Prize giving and raffle 1800 to close down your chance to natter

Prizes for best piece of home brew and longest distance travelled. Mini flea market. Equipment testing: full size G5RV and 2 metre colinear antennae available terminated in PL259. Anyone staying overnight will be taken on a tour of the harbour which was once the World's leading herring port the following morning if desired. A small library of technical books will be available for reference purposes.

GOOD QRP OPERATING Gerald Stancey G3MCK

There's no doubt that operating standards today aren't like they were in the good old days; in fact they never were and never will be! However there is no doubt that a general improvement in operating standards would be to the benefit of all concerned. This is not meant to knock the recently licensed operator. In fact some of the worst examples of poor operating can be heard from holders of old calls; we all get careless and sloppy from time to time.

The following suggestions are not meant to be exhaustive and are based on my observations on 80m CW. However I believe that the basic principles apply to all bands and modes. Firstly, good CW operating has very little to do with speed; it is all about common sense. Now we all do this don't we? All the time?

Many QRP CW QSO's are conducted under marginal conditions. This means that your sending must be easy to read and error free. You can be sure that the only time the other operator correctly copies your call will be the one time you send it incorrectly. For example he may well only read G-MCK, or G--CK but you can bet your boots he will read G2MCK! The next thing is to get the basics of the QSO over quickly; RST, QTH, name, G-QRP number. Of these the most important, and most abused is the RST. Just go and look in the manual and see what the R numbers mean. "I am reading you with very little difficulty", this sounds like a reasonable way of describing many QSO's doesn't it? That is R4. How many times do you hear R5 being sent when it should be R4?

Giving a poor report often seems to be considered to be an insult so operators often shy away from telling the truth. However giving an honest poor report is most helpful to the other man because if he is a competent operator it will enable him to judge how to conduct his side of the QSO. For example, the answer to questions like should I rag-chew or should I rubber stamp will be obvious.

With marginal conditons only three things can happen. They can improve, they can remain the same, or they can get worse. There are no prizes for guessing what always seems to happen in practice. I find nothing more annoying than having given a guy a report of 339 to have him come back and repeat verbatim everything I have sent to him and then as an afterthought give me information. For example don't come back on your first over with a transmission like this; "RRRR GE DR GERALD VY PSED TO MEET YOU ES TNX FER FB RPRT OF 339 339 339 = = = VY FB ON UR QTH OF STAINES STAINES ==== VY FB ON UR G ORP NUMBER 2148 2148 2148 === === WX HERE IS RAINING ES TEMP 10 C 10C 10C ==== MY NAME IS FRED FRED FRED ES MY QTH IS LEEDS==== == MY QRP NUMBER IS 71123 71123 ===== UR FB SIGS ARE RST RST RST 559 == SO BACK TO U ES HW DO U COPY ??? ". Note how the report is only sent once right at the end. My friends that is not an exaggeration. Of course you and I never do things like that do we? In fact you are right that the above example doesn't happen. What happens is the other quy sends it but I don't receive it because he has faded out part way through. result is that neither of us get a full QRP QSO with a club member to put in the log.

As I said at the beginning the secret of good operating is just common sense. What is appropriate under good conditions with a known competent operator at the other end is lid-like operating when the conditions are poor and the other guy is unknown. Slick operating is getting the key information over quickly and accurately and has very little to do with high speed CW, especially if the operator is dotting the i's and crossing the t's, a complaint known as el-bugitis. So lets not relax, get sloppy and set a bad example to the rest of the amateur fraternity. Let's try and make QRP synonymous with first class operating.

LADDER FILTER CRYSTALS: Still available a few sets of 8 crystals on 8913 or 9063KHz plus two carrier crystals, supplied with suitable circuit for $^{£}5.00$ inc. postage from John Haliburton, GM4AQO, 32Glenbervie Rd. Kirkcaldy. Fife.

WANTED: DRAKE 2B, 2C or 9R59DE or similar in GWO and reasonable price. G2BYP, 4 The Crest, Whitehaven, Cumbria. (0946)4910.

FOR SALE: ICOM IC202 2m CW/SSB Portable Transceiver. Complete with mic, whip antenna, Internal Ni-Cads & Charger £80
GOHTR, TEL: Tamworth (0827) 898024 Anytime.

37 Pickerill Road, Greasby, Wirral, Merseyside. L49 3ND

OK/G ACTIVITY WEEKEND 1988 This event generated excellent activity despite the fact that one or two leading Czech QRP men were tied up with work or family matters. Despite this no less that 27 OK QRP stations were worked from the UK, made up of 14 OKls, 6 OK2s, and 7 OK3s. Rather surprisingly the best band turned out to be 3.5 MHz, with 15 different OKs worked from the UK as against on 12 or 14 MHz. 10.1 MHz was certainly not as good as last year, and the muf never got above 14 MHz. Awards have been made to OK3CUG, best 01 log, OK1AYH, runner up, and OK3CPY for the best 14 MHz performance in both 1987 and 1989. UK stations receiving awards from OK are (once again) G43FN for best overall, G4CFS for an outstanding 3.5 MHz performance, and G3VTI. The whole event was very successful and the next one is planned for 21/22 January, 1989. as there was no activity at all reported on 1.8 MHz that band will be dropped for the 1989 event (but before Top Band buffs write and complain, there may be something special for them in the next Winted Sports!)

THE WORK OF OUR 28 MHz Es OBSERVATION TEAM during 1988 has been highly praised by Ron Binns, G30TE, who is carrying out a major study of 28 MHz propogation. Having heard of our work he asked to borrow the logs, which were sent to him. To quote from his letter of thanks "I was going to say that your information supplemented my own - but I rather think the reverse is the case!" Nice to know we were doing something really useful! One important point Ron Makes is that he believes there is strong correlation between very short skip on 28 (allowing inter-G working) and trans-Atlantic openings, so next time the band is full of strong Gs dig down and listen for Ws. Incidentally no less than eight pages in the April, 1988 issue of QST are devoted to Es. What G QRP C did yesterday the world does tomorrow!

CHELMSLEY IROPHY for 1987 goes to John, G3DOP, for an amazing log of results using his loop 6 inches above ground. DX included BY, EA8, EA9, W, VE, and FY5, together with a mass of European countries, all worked with 1 to 3 watts output. Well done John!

IT'S THE SAME THE WHOLE WORLD OVER....." I live in a flat on a housing estate. There are many TVs around, so I try and keep my antennas invisible!". No, the member concerned does not live in London, Birmingham or Glasgow, but in a fairly small town on the other side of the Iron Curtain.

SERVICE WITH A SMILE is the motto of your Communication Department and we do get some strange requests. Recently a member asked us to obtain an important document to help him prove he is a British citizen. Within a couple of weeks it was on its way to him, thanks to some excellent co-operation from Elder Demptster Lines.

COMMORATULATIONS TO PETER, G3X3S, who has confirmed contacts with no less than 50 countries on 3.5MHz when using 3w or less.

DO NOT FORGET THE SUMMER RAMBLE 10-19 JUNE and including International QRP Day on 17th June. Use our QRP frequencies to the full during this period, please.

SAD NEWS OF THE DEATH OF HARRY BLOMQUIST, K6JSS comes in a letter from Bob, NM7M. Harry founded QRP ARCI in 1961, so we are the poorer for his passing.

QRP SUMMER RAMBLE 1988
JUNE 10th to 19th

Including International QRP Day on June 17th
USE THE QRP FREQUENCIES TO THE FULL OVER THIS PERIOD
1843-2569-7030-10106-14060-21060-28060 KHz. CW
3690-7090-14285-21385-28885 KHz. SSB
Logs and Reports to G8PG

THE SQUARE DIPOLE Cut a dipole using 468/f =feet or 143/f =metres to calculate the length. Then erect it in the form of a square, using an insulator to separate the free ends. Feed it with 75 ohm balanced line, or 75 ohm co-ax and a balun, using a transmatch at the rig end of the feeder. Erect it vertically. Gain in the direction of the fed end is within 1dB of a dipole, and at the other end it is about 4 dB down on a dipole. Gain can be reversed by moving the feeder from one end to the other, or you can rotate it. This is easy - the 28 NHz version is only slightly over 4ft square and the 21 Mhz version 5 feet. Hung on a piece of cord across my shack and firing east the 21MHz version worked all Europe, several UA9s and (off the back) W1, W4 and VE3 in a few hours of tests. A 28 MHz version worked well, including my first ever HZ1. version with the 28 MHz antenna inside the 21 MHz antenna was then tried, and worked very well when fed via a common feeder. If made from tubing a rotary version would look like a super TV or vhf fm antenna. It could also be used horizontally, a 7MHz horizontal version only occupying a 17 foot square. will work if cut to formula, but dipping and trimming give it that little extra performance. Power used for the tests was 3 watts.

IF YOU CAN LOCATE YOUR SHACK AT THE TOP OF A WEST-FACING CLIFF then you can do what David, CT4RL/p, did during the 1987 QRP ARCI Contest. David errected a long, narrow loop antenna from the lop of the cliff to two poles down at the bottom. Directivity to the west was terrific - over 40 trans- Λ tlantic QRP/QRP contacts including W6, W7 and HI3 - and with the cliff cutting off signals from the east, virtually no European QRM. At last we may have a rival to those big wires at GM30XX/A

WHY NOT MORE QSY? Taking 3.6 MHz as an example, time and time again one finds QRP stations QRMing each other around 3560 when there are great empty spaces around 3570. Amateurs just seem to be scared to QSY. I agree that modern transceivers do not help in this respect, but one can still move away from the QRM. To do so satisfactorily certain rules must be followed, however. They are these. The station requesting the QSY must state what he wants clearly. "QSY up2 is meaningless - it could be by 10Hz, 10Khz or 10MHz! One must either say "QSY UP (or 100MHz) 3 Khz?" or QSY 10MHz1. Although the frequency is specific, note the question mark, which makes it a request. Whether or not the request is accepted is entirely up to the other operator. He may be XTL, and unable to comply, or he may know a local is blasting away on the proposed frequency. therefore has three courses open to him. He can say "SRI NO QSY, suggest a different frequency to that proposed, or say "OK QSY 3 UP". If he gives either of the first two answers the other station should agree and act accordingly. Once agreement is reached the original proposer should send OSY 3 UP NW. and the other station R UP. The onus is then on the original proposer, who should find a clear spot approximately 3 UP, then call the other station, if necessary doing this at intervals until communication is re-established. Note that before moving it is his responsibility to ensure that the move has been agreed, and that the other station knows the new frequency and is ready to make the change. Used properly a QSY can often help greatly, but if not carried out properly it can lead to disaster. Learn the proper procedure and dodge at least a bit of the QRM.

AWARD NEWS. Congratulations to the following.

QRP COUNTRIES. 200: all cw for GM30XX; well done!!

125: G3XJS. 50:EA3EGY. C4ASL, SV1UY. 25:G4VPV, 5N9GOM.

WROKED G QRP CLUB. 640: all cw, to GM30XX!!

460, G3XJS, 260 G3MBN, 240: G3CQK. 180;G4WZV. 120:G4UGC.

100:G4NBI. G4CFS. 80:G3ZJJ. 60:G4VPV. CWODNR. G4AYS.

40: G4ZGJ. G4UIQ. EA3EGV. G4IJV. 20:UP28FE.

TWO-WAY QRP $\,$ 40:G8PG. 20:G2DAN. 10:G4VPV. UP2BFE. G4UGC. G4CFS. QRP WAC. EA3EGV $\,$

FOR SALE: TEN TEC CENTURY 22 Transceiver with internal keyer board and xtal calibrator as new. £275. G3MBN. TEL: (0225) 810621.

WANTED: BACK ISSUES OF SPRAT before 44. C. Schiotz, K2PGB, RD3 Box 379. Ringoes, N.J. 08551. U.S.A.

124 Belgrave Rd. Wyken, Coventry. CV2 5BH. Tel: (0203) 617367

I'm still trying to get used to my new club number " 4444 " which Dave gave me as the computor didn't like my old one and kept leaving me off the mailing list.

I've not been very active on the bands since last SPRAT but I'm hoping to remedy that at the weekend during the RSGB UHF/UHF contest (May 7/8). I have been in frequent contact with that well known VHF Qrper Dave DOG3A, albeit via the repeater CB3WK. If you are local and want to give me some news then I am uaually within earshot on the repeater between 07:45 & 08:15 local time. The VHF bands seem to be pretty well dead at the moment with not much activity on any of them except the usual waffled on 2m. However, a dedicated few in Warwickshire are doing their best to keep 50 & 70 MHz alive and kicking until the Dx chorus starts up.

I've been trying to improve my 50 MHz sct up and have been experimenting with polyphase audio phase shift networks & 50HHz VXO to generate SSB. This has the advantage that only one crystal is needed for both transmit and receive if a direct conversion Rx is used and a fair chunk of band is covered per \times tal (abt 60 KHz).

It used coaxial phasing lines to phase shift at RF and apart from cutting these to length it requires virtually no setting up if a commercial double balanced mixer (eg MD108) is used. I'm brewing my own from Toroids and BAT 81 diodes.

Also this month is a useful average reading power meter for HF & VHF. It is designed for 75 ohms, but it doesn't take much imagination to make it go at 50 ohms or any other impedance you fancy. Over to Harry Popov LZIBB:

VHF /HF POWER METER HARRY POPOFF LZ1BB

R1 and R4 - 300% /lW. If you need 50% input you should add another two resistors in parallel to R1 and R4. All components are gathered in a small metal box. It could be constructed from PCB. Measurement is made with the base multi-meter with input impedance 30 K % /V. The output power of the transmitter over 75% load should be calculated as follows:

P out =
$$\frac{U^2}{R \text{ load}}$$

75

or in our case:
P out = U²

R1 R3 R3 C1 R5

75. R2 R4 C2 VINETE.

Project was absolutely correct up to

I was very surprised that this simple project was absolutely correct up to 5w output even on 144Mz when compared with commercial watt meter. Powers over 5 watts are dangerous for the load resistor Rl - R4 and Dl - AAZl8. With 8 watts Dl was destroyed. So I think that for our purposes up to 3w out.)this is an ideal cheap weekend project. If the multimeter has different input impedance than $30 k\Omega/V$ then R5 should be calculated as follows; R5=0.414 x z/input impedance of multimeter. Rl - R4, Cl and Dl should be mounted as close as possible to the input socket.

I can send any other information about the wattmeter $% \left(1\right) =1$ and also the diode AAZ18 to all interested members.

Now some information for your column. In 1986 during Perseides I made Ms QSOs with IK2DMF on SSB and RB5EF on CW. The power was 3 watts output and ant was a 9 ele F9FT. So QRPers don't worry so much about your small power for Ms. Have a try.

Harry Popov,LZ1BB,Bratya Bakston,207^A A.6. SOFIA.1618. BULGARIA.

HAVE YOU WRITTEN AN ARTICLE FOR SPRAT YET ?

We do not ask for much. A simple sketch of the circuit, perhaps a layout, and a few notes. Clearly Mark All Component Values. We do the rest.

ROSEMOUNT, CHURCH WHITFIELD, DOVER, KENT.

At last the SSB Net is underway again! At the time of writing there has been no decision about changing time and frequencies but as I write this week by week there may be developments by submission date

I've had a letter from Larry GOHTR and he reports problems with the Rotary Club net, this is always a problem and the morning that it happened I could not hear anything either! Last week I came on early and called the QRP Net and finally managed to form a net of four of us.

Mike G3WWS (894) using a home brew TRX with the famous MLX PCB into an inverted L aerial.

Dave G4XIP (2825) with an Argosy at 5 watts, aerial information not noted. And Graham G4CHK (4317) who could not manage it on his home brew QRP so called in with his FT200 into a 130ft long wire.

I formed the net using 100 watts from my IR7 and then reverted to my "KITIEN". This runs 10 watts PEP and is made of various modules. Am "FT707 R.F. PCB" into an "MLX PCB" forms the heart. "THE KANGO VFO" and "MULTI CHANNEL OSC PCB" forms the local oscilator, and the TX signal amplified using the "CIRCUIT P.A. MODULE" and filtered using the "KANGA L.P.F. PCB". Transmit/receive functions carried out by the Kanga "TR PCB" in tandam with the MLX changeover system. Two of these have been built, the other one by Dick. GOBPS..

How for a real stir, but I am fed up QSL cards!!!!

One of my little foibles!! I consider the QSL card to be a bit of a waste of time!!! (that will ensure that I get a good return of mail for next SPRAT (Hi). My reasons for saying this is that I do not have to prove that I have had a QSO, if someone does not want to believe me that is their hard luck. For awards perhaps there is some need but as an award is for the satisfaction of the person who receives it, it can give no satisfaction if it has been gained dishonestly!!!

Finally I cannot afford the cost of the cards and perhaps more important the time to fill them all in. Anyone who wants confirmation of a $\,$ QSO with me may willingly sent a card with an SAE and 1 will attach my callsign label and sign the card and return it by next post.

I know this is going to cause a stir and perhaps even dislike by some but I am sure that I am not alone in this view.

On a more cheerful note I have had a letter from Chas GW3SB (1221) with a circuit of the homodyne receiver. He recalls in the old days of using the homodyne receiver oscillating hard and keying the H.T. rail for CW transmit and making a transceiver of it!! I remember building a regen detector for 2 metres and increasing the feedback on transmit and grid modulating it.... Using a 1T4 valve I could go portable and work the locals with it. I remember DXing to the next village 4 miles across the valley!!

The big drawback with this system is the radiatin on receive. A form of R.F. amplifier must be employed to reduce this and this would increase the complexity to make the idea non viable... but then perhaps someone will not prove me wrong.

that's all for this time folks, let me know your news and hope that the European QRM keeps at a level that I can work you all on Sunday mornings on 3690 at 0900 local time.

FOR SALE: FT277ZD (101) DC/DC Converter, CW Filter, Fan, Mike. Mint £500 FT290R, Mint, Nicads, Charger, Case, Rubber Duck. £275 Tel: 061-301-3750 Will deal for Argosy QRP Transceiver.

FOR SALE: HW8 complete portable package, in carry case with 12v Nicad supply Key, leads etc. Buyer Collects. Adrian Heath, (0793) 762970

HIFURMATION WANTED: on the HAMMERLUND HQ-120 Receiver by Ron G6SZW 25 Kinloch Way, Immingham, South Humberside, DN40 1PL.

TEN IEC PM3A: Advice wanted on current replacements for the PA transistors. Have been advised 2N3924 but cannot find a supplier H. Bayliss, GDOIDU, 44 Heather Cres. Pulrose. Isle of Man.

EXCHANGE: Argosy for Argonaut 515, must be mint. GOFTO. Tel: Bolton 657410



"Alamosa", The Paddocks, Upper Beeding, Steyning, West Sussex, BN4 3JW

The Yeovil Club once again put on an Members News excellent ORP Convention says G3XJS. wants to know how they even arrange for the excellent weather! The attendance was up on last year with everyone made to feel very welcome. Peter was disappoined that the G-ORP-Club did not offer better support, as the event has so much emphasis on the very ideals that our club stands for. Perhaps I can use Peter's comments as an excuse to explain that everything the club does depends on volunteers and sometimes members are either unable or just unwilling to give up their time for the benefit of the club. If you are going to Yeovil next year or any other event where you feel the G-QRP-Club should be represented, please consider getting together with two or three other members and setting up a club stand. is plenty of material available to help you including items the club has for sale, all we need is you to volunteer. Frank, G3BFR was another member to mention the convention, confirming a great time was had by all.

My planned three week trip to the USA taking in the Visalia Convention, Dayton and the FOC Dinner in Conecticut had to be re-arranged at the last minute due to one of my boys (Gary) going into hospital for an operation. We had been waiting since November and they called him in on 20 April, the day I was booked to fly to California!! Hurried telephone calls to the travel agent resulted in me just visiting Dayton. I took the opportunity to attend in a low key capacity, (QRP that is!), to enable me to get round and see all the other attractions I have missed in previous years. The flea market was as big as ever and those hospitality suites at Stouffers....highlight of them was bumping into WORSP and WB9TEU. Ade sends regards to all his friends in the UK. He was in top form, no doubt due to his temporary QSY to the Florida sunshine. Paula is the editor of the ARCI's ORP Quarterly, and a first class job she is making of it.

The ARCI gang had their club stand in the same position as last year, and it was doing good business each time I visited it. I understand over 85 QRPers attended the QRP Dinner at The Spagetti Warehouse on the Friday evening, and over 100 attended the Boer and Pizza QRP party. The ANCI are already well ahead with QRP events for Dayton 89, information from Jim WIFMR who is the overall coordinator.

Whilst I was at Dayton, my usual USA travelling companion G3VIT was visiting OK land. had a great time, meeting OKICZ and OK2BMA and others from the OK ORP gang. I won't steal his stories as no doubt he will be writing them up for SPRAT. Before we leave the social scene may I remind you of this years Summer QRP Party here at "Alamosa" on 13 August, details on page 25 of SPRAT 54. Come and meet the PA QRP gang, who will now be PA3DMM (new call sign of PDOMAM), PELLIF and PELMHO together with PAOAHS coming with G3VIT.

GASIS has changed his call to ZCAFJ. Frank has been scanning the bands for the QRP gang on 15 and 20m. He will be there several years and hopes to get on 80m when his antenna is G3GTQ, who was CN8CY until recently, is now in Nigeria awaiting a 5NO call. AI2H is now in Delaware from Japan where he held a JA call for two years. During that time Barry worked lots of Korean, Russian and Chinese stations with his HW9! He said getting a JA call is a long and tedious business and he can assist members trying to get one. G4KMY is now G2AGH, Tony having had his original 1939 call re-issued, and yet another change is G4FSP who is now ZIAHB. George has worked into the UK a couple of times on QRO with a temporary bent wire between the trees. Finally G4TEU/2 is now GOJDV as he is now 14 years old and able to obtain his own call - congratulations Ed. His photograph was shown in SPRAT 49 when he was 12 years old and (believed) to be our youngest active member. He is building the Howes TCVR system for 20m.

Now an apology to G4FAI who is NOT the President of FISTS, my informant got it wrong! has, however, been elected Chairman of EUCW and asks me to mention the next Fraternising Party on 19/20 November, more information nearer the event. GBQM has been in hospital and after recuperation has resumed his QRP contacts with VK2AFN on 20m, "to prove the first one was no fluke". Vic has built the Heathkit SW7800 digital read-out GC RX which received signals from the first switch-on. He has a desire to return to SW BC listening and wanted to prove he was still capable of some serious construction work.

GW3FSW takes me to task for not mentioning QRP RTTY in my column. Ian would welcome the opportunity to contact other members interested in RTTY. He intends using an Amstrad 8512 and ST5MC terminal unit. (Look back through my columns Ian as I can recollect at least three occasions when I have mentioned members active on QRP RTTY.) K2FGB, despite working 85 DMCC, does not find many G QRPers around 14060. Chris frequently hears activity from G land on 3560 but no QSOS yet. KD8FR is using an 80m horizontal loop at 20ft for all bands, and has worked Europeans on 15m, VE7 and PY on 10m and NP4A and KV4FZ on 40m with his 2w. Sounds a good antenna. Lowell is QRV in the major contests with his Century 22 in between sending it back to Sevierville! It keeps losing the final transistors and Ten-Tec cannot find out why! VE3FGW is also using a horizontal loop, but in the form of an emergency antenna. Tom has erected a 66ft loop in his basement recreation room. One end is at ground level and the other about 2ft above it, and matching it through an MFJ ATU has given him 28 DXCC including lots of Europeans.

Some of you may have seen my review of the AFtronics Superscaf filter in the May edition of Practical Wireless. In the true G-QRP-Club spirit GOFAH wants to build his own and says the transistors can be obtained from Quardon Electronics, Slack Lane, Derby, DE3 3ED. Bill says the S3528I is £4.26 and the S3529P £3.32 plus VAT. GMIRHV is active on 2m NBFM often using 300mW and has worked members GM4VJY, GM4XQJ and GM4UYE. Mike built the Howes DCRXBO in a biscuit tin and has received VE7 and WI with it. As he says "Not half bad for a £20 kit in a biscuit tin".

GOFTO worked his first JA on 15m with 3w. Bob also had a QSO with G4SIS who was using a helium filled baloon holding up 132ft of wire to an Argonaut. G8IB was pleased to receive a QSL card from UP1BWW who was running .05w to a 7el 20m yagi! Dug has built the W3NQN filter and says it makes his "Argonaut sound like a 940". (From some of the reports I've heard about 940s, I'm not sure that's too much of a compliment!) G3MBN has built a new shack to replace his caravan which he is keeping for /P operation in the Summer. G3XJS reports a long list of DX including PYO, KL7, TI, A9, T22, 8Q7, TY, VK9 and KH6 for new ones. Peter throws down a challenge, now the sun spots are bring us better conditions, the fastest WAC on QRP. To start he offers 3h 35m on 14 March when he worked AXXXA, JG2FDF, PYOFC, UB4INW, EA9GS and KA1MKJ on 15 and 20m. Let me know about your fastest WAC. Not to be outdone G4JFN offers T26, 9Q, KP2, 5L, ZF, TI and HS on 10m, plus ZL on 20m. Bob said he enjoyed the OK Tests very much and made over 200 QRP QSOs in the last Winter Sports.

WF6U is planning his 22nd trip to the UK in September. Hollis will tour the UK on a Britrail ticket and plans attending the AGM of the Huddersfield Canal Society, his other interest. N3IK is planning a cycle tour of the UK this summer and WB2CZB will be part of a DXpedition to Saba Island between 7 and 14 July. They will be on all bands and particular attention will be paid to multip hop paths to the UK, EU and Africa on 6m. Mario will actively solicit CRP contacts on the QRP frequencies. WD9IWP, one of our new members, met K9PNG on 40m and is now part of the W9 group with K5VOL who operate the ARRL Field Day.

G4KKI is using a very much modded HW7. Bill has built a new front end/mixer based on the SO42P from SPRAT 38, RIT as per DJ12B in the Club Circuit Handbook, and switched attenuator. He has replaced the meter with two others, one for RF out and the other as an S meter with the Howes S meter board. The TX/RX relay has been changed for a modern encapsulated one, a four pole switched CW filter fitted and finally a pair of 2N3866s have been fitted to the PA. WIDMD has been worked three times on two-way QRP with it. Bill took it to his local club in Manchester to demonstrate QRP, and using an indoor GSRV he worked HA, SP and UA on 20m, the latter giving him a confirmed 599 report. Needless to say the club members were very impressed. G4XNP is having a problem with stray coupling when changing from RX to TX on his Howes 20m TCVR. Dave has been playing with sloping dipoles based on my SWM articles, and his results will be a separate SPRAT article. N3IK has also been experimenting with antennas. He uses his "Hammer" antenna which has given him WAC on 40m except Asia and EU and SA on 80m. Perhaps Ike will give more information about it so other members can try the "Hammer".


FOR SALE : TRIO TS-130V QRP Transceiver and PS20 Power Supply £395. TEL: 045 36 3994

G3FVC is using a l valve TX giving 2w on all bands and built in 1949. The FSU uses Cossor S130s for voltage stabilisation and Eric says they make a lovely sight flashing in step with his keying. The TX has AM capability with a 6SL7/6L6 choke modulator, plus the original D104 mike, but he hasn't used it on that mode for years! G3ZJJ says his Oner "goes like a dream" and finds he gets just under lw out on 15m. With his 150ft end fed antenna Mike has worked U1.7 and wonders how many other members have successfully used Oners on 15m. He has tried 10m, and although he gets some output he also gets a lovely chirp!

I intend being at NEC both days and also the HF Convention at Oxford in September, perhaps CU there? Let me know how your summer goes, (by 20 August please), and don't forget the fastest ORP WAC.

73

Chris

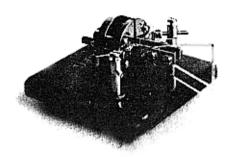

G4ZPY Paddle Keys
41 Mill Dam Lane, Burscough, Ormskirk
Lancs. L40 7TG. (0704) 894299

PUMP KEY (Brass) £26 & £30 (Mickel) £31 & £35, P/P £3
SINGLE PADDLE (Brass) STD:£42, DELUXE;£44,50, P/P £3
SINGLE PADDLE (Mickel) STD:£47, DELUXE;£49,50, P/P £3
TWIN PADDLE (Brass) STD:£48, DELUXE;£50,50, P/P £3
TWIN PADDLE (Nickel) STD:£53, DELUXE;£55,50, P/P £3
IAMBIC KEYERS, Keying 100v,100wA, Pos ;£40 P/P £2
Further Details send SAE or Telephone

DTR3 CW TRANSCEIVER for 80 METRES

This compact and lightweight TX/RX is an ideal QRP rig for the popular 80 Metre band. Great for portable and holiday operation!

Transmitter - Mode : CW

Range : 3.5 - 3.6 MHz

Power : 1.5W output

Receiver

- Direct Conversion

Selectivity - 250 Hz @ 6dB Sensitivity - Better than 1uV

AF Output - up to 250mW to 8 ohm headphones

Power requirements - 450mA (key down) at 12 - 14 Vdc.

ALL parts are included in the Kit. Not only the case, slow motion drive, good quality variable capacitor, knobs, hardware etc., but important features which, in some kits, are regarded as extras – stable VFO, Audio Filter, RIT, Sidetone – PLUS ready printed front and back Panels for that "Professional" finish.

In fact, the only other things you'll have to find are a morse key, headphones and the price - £74.25 plus £2.00 postage and packing. If you prefer, we can supply the Instruction Manual and the five basic PCB's (i.e. boards only) for just £20.00 including postage.

For further details of the DTR3 and other kits in our range, send SAE to



LAKE ELECTRONICS
7 MIDDLETON CLOSE, NUTHALL,
NOTTINGHAM, NG16 1BX
or, ring Alan, 64DVW, (0602) 382509



HAM RADIO NORTH WEST

Props: Kevin Fox GØ DRK, Mrs. A. Fox
23 NEW COURT DRIVE, EGERTON, BOLTON, LANCS, BL7 9XA
TEL: BOLTON (0204) 54808
CALLERS BY APPOINTMENT PLEASE

RALLY PRICE LIST

Catalogue available 50p – Refundable with first order.
Top Quality British Cables, You Will Not Find Better Anywhere!!

		Post/Pkg
Permanoid URM57 75 OHM Low Loss Coax	60p/M	6p/m
Permanoid URM67 50 OHM Low Loss Coax	65p/ M	6p/m
Permanoid URM 50 OHM Coax	23p/M	3p/m
Permanoid URM 75 OHM Coax	30p/M	3p/m
Permanoid RG58/CU 50 OHM Coax	25p/M	3p/m
Permanoid 75 OHM Flat Twin Feeder	18p/M	3p/m
Other Cables		
BOFA (Swedish) 300 OHM Slotted Ribbon GMP6	25p/M	3p/m
POPE H100 (Dutch) 50 OHM Very Low Loss Coax	80p/M	6p/m
TV Coax 75 OHM	20p/M	3p/m
Altronic RG58 per 100 metre Drum	£17.00	£1.50
Equipment and Accessories		
G5RV Multiband Dipole 102ft	£16.25	£2.50
1/2 G5RV Multiband Dipole 51ft	£14.25	£2.50
HB9 CV 2 EI Beam Kit 2m or 70cms	£ 3.95	£2.00
HB9 CV 2 EI Beam Kit 6m	£12.95	£2.00
Gamma Twin 2 mtr (Slim Jim Type Ant.)	£ 8.95	\$2.00
Pair 7.1Mhz Traps	£ 9.50	£1.00
Dipole Centre (Fully Enclosed)	£ 2.25	50p
Plastic Dogbone Insulators	70p ea	25p
Ceramic Egg Insulators	65pea	25p
Plastic Egg Insulators	50p ea	25p
50M/165ft PVC Covered Aerial Wire (24 strand copper)	£ 3.00	£1.40
38mm Ferrite Rings	50pea	25p
High Grade Ferrite Rings (Orange)	60pea	25p
Sun 5/4 2m Antenna (Tilt Base)	£12.95	£2.00
Cast Gutter Mount Black C/W Cable (suitable for above)	£ 9.50	£1.50
Hi-Gain Silver Road CB/10fm Base Antenna	£14.95	£2.00
Revco 5/6 over 1/4 UHF Colinear Mobile Antenna	£ 7.95	£1.50
'AA' Size Ni-Cads – £8.00 per ten	85p ea	25p
Station Log Book (1000QSO)	£ 1.00	25p
Value Component Packs 100's Resistors Mixed	£ 1.00	£1.00
Value Component Packs 100's Capacitors Mixed	£ 1.00	£1.00
G-Comm PSU (British) 8 – 12 amp	£44.25	£2.50
G-Comm PSU (British) 3 – 5 amp	£15.25	£2.00
Universal Ni-Cad Charger	£ 4.95	£1.00

We are now expanding our stock and services!!
e.g. Local Delivery, Bulk Discounts and Special Deals for Clubs etc.
If we haven't got it, we can probably get it, try us first.

* WANTED * Your S/H Equipment, HF, VHF Rigs: Cash Paid.

SPECIAL SPRAT OFFER

PECIAL SPRAI OFFER



CRYSTALS

	QRP						
BAND	CALLING	OTHER	FREQUEN	CIES	MODE	PRICE	
	CHANNEL						All HC-25/U, 30pF.
160m	-	1850			Fundamental	£4.00	
80m	3560	3540	3550		H	3.50	
40m	7030	7025			**	3.50	
30m	10106				**	3.50	
20m	14060	14030	14040	14050	**	3.50	b
17m	-	18080	18090		**	3.50	*
15m	21060				3rd Overtone	3.50	€4 ₆
	21060				Fundamental	4.00	U V
1 2m	-	24910			11	4.00	
10m	28060				3rd Overtone	3.50	
	28060				Fundamental	4.00	

Converter and transverter crystals: HC-18/U, 3rd Overtone, Series resonant. 22.0, 24.0, 31.333, 38.6667, 42.0 MHz, £3.50 each. 65.0(HC25) 94.0 MHz 5 O/T £4.00.

SAE please for lists of stock crystals and TTL oscillators for microprocessors, radio crystals, plus Crystal, Monolithic and Ceramic Filters on 455 kHz, 9.0, 10.7 and 21.4 MHz etc.

VAT and UK postage included. Overseas members please add £1.00 per order.

73 G3EDW

Merriott

Somerset

TA16 5NS

England

Telephone: (0460) 73718



KANGA PRODUCTS

KITS FOR THE AMATEUR, BUDDING AMATEUR AND THE LISTENER

KANGA PRODUCTS offer a range of semi-complete kits for the Radio Amateur and the Listener. They are supplied complete with all those harder to get bits but leaves out those you are likely to have in the junk box.

SPECIAL OFFER TO G-QRP MEMBERS: DEDUCT 10% 17EMS MARKED *** DEDUCT 20% BUT TO QUALIFY YOU HUST QUOTE YOUR MEMBERSHIP MUMBER { PLEASE add 85p P&P to total order }

THE 'ONER' GRP TRANSCEIVER!!! Each kit is supplied with its own i" square board

The G-ORP Clubs own 'ONER' TRANSMITTER kit, either crystal or VFO controlled
The 'ONER' V.F.O. Is this the smallest ever VFO? (see SPRAT 53 for details)
The 'ONER' RECEIVER, yes a working receiver on a 1* sqr PCB (well nearly)
The 'ONER' ANTENNA CHANGEOVER & SIDETONE kit, enough to drive earphones easily
All four kits for £25:00 (8-9RP members £21:00) plus p&p

DUMMY LOAD, Primarily designed for the DRP man, but will take up to 40 Watts in free air, or 100 watts if in a sand or oil bath. Our test units lasted over 3 minutes at 100 Watts in free air. Also fitted with an RF sensor for power measurement. DUMMY LOAD KIT £7:95

DUAL BAND RECEIVER KIT Mainly 20 & BO, but can be used on any of the HF bands. See SPRAT 53 for details and the picture of Georges. Our kit just £35:95 (A less complex, single band version is available for just £19:95)

DIGITAL DIAL / FREQUENCY COUNTER Four offsets available. Use as frequency readout or as a Counter. Guaranteed to 45MHz but mine works up to 64MHz. THE DIGI-DIAL KIT £19195

Our other kits include. 'THE V.F.O.' @ £9195, SIDETONE KIT @ £5:95, P.S.U. kits £9:00 pair, MARKER UNIT @ £9:95, CRYSTAL OSCILLATOR @ £9:45, TX/RX CONTROL BOARD @ £7:95, AF BOARD @ £7:95, 160M FOR THE FT707 & 77 @ £27:50, Resistors, all E12 values @ 50p per 100, 100pf air spaced caps @ £1 each

FOR YOUR FREE COPY OF OUR LATEST CATALOGUE SEND A LARGE SAE TO: KANGA PRODUCTS, 3, LIMES ROAD FOLKESTONE KENT CT19 4AU

Props: I.H. Keyser G3ROD & R.A. Pascoe GOBPS