

low-cost spectrum analyzer with kilobuck features

Build WA2PZO's
useful instrument
for operating position
and lab bench

Although laboratory-grade spectrum analyzers cost \$4500 or more, you can build a spectrum analyzer offering many features of its costlier cousins for about \$50. How can such amazing capabilities be had at such incredibly low cost?

- *Through the use of a commercially mass-produced varactor tuned TV tuner that covers the VHF low, VHF high, and UHF TV bands.* It will tune down through the 2-meter and 6-meter Amateur bands without modification, with better than 1-microvolt sensitivity. By using a crystal-controlled converter and a narrower IF filter, any one of the HF Amateur bands could be viewed as well, by simply upconverting to a TV channel.
- *Through the use of consumer-grade integrated circuits in the oscillator/mixer, dual ceramic filter, IF amplifiers/detector, and audio amplifier (offering audio as well as scope output it is really a spectrum monitor).*
- *Through the use of your own oscilloscope.* Just about any scope may be used; I used a 1951 Heathkit Model OL-1 with its original cathode ray tube.

spectrum analyzer applications

Spectrum analyzers allow the user to observe in real time an adjustable/variable bandwidth of radio frequencies. One of the earliest spectrum analyzers for the ham bands was the "Panadaptor," manufactured by Hallicrafters in the early 1950s. I used one to check for F2 propagation 6-meter band openings in the mid-1950s and credit the panadaptor with my earning the IARU 6-meter WAC award (phone) issued by the ARRL.

The band of frequencies swept by the spectrum analyzer described in this article may be varied from zero up to about 38 MHz on VHF low TV = 50 MHz – 88 MHz, zero up to about 85 MHz on VHF high TV = 135 MHz – 220 MHz, and zero up to about 300

MHz on the UHF TV = 500 MHz – 800 MHz. When the sweep width is set at zero, each of these bands of frequencies may be manually tuned just as in a single-frequency receiver. Both wideband FM and narrowband FM signals, and surprisingly, even amplitude modulated signals are detected quite well by the FM IF amp/detector IC and amplified by the audio IC.

Figure 1 is a block diagram of this spectrum analyzer using a Sanyo varactor tuned TV tuner. A ten-turn, 10k pot with +35 VDC across it is used to adjust the center frequency of the tuner. A low varactor bias yields low frequency and a high varactor bias provides higher frequency on the TV band to which the tuner is set. The sawtooth sweep voltage that is capacitively coupled into the tuner's varactors is the horizontal sweep voltage from the oscilloscope. If your scope doesn't have the horizontal sweep output (the Heathkit OL-1 does not), just mount an RCA phono jack on the front of the scope and bring out the horizontal sweep from the scope's horizontal multivibrator to this point. The 100 kilohm load across the horizontal sweep output should have little or no effect on the scope's operation.

Besides the TV tuner and scope, the rest of the circuit consists of only three integrated circuits. The second mixer/oscillator chip is a Siemens SO42P. The ceramic filter is a Murata SFJ two-section filter at 10.7 MHz. The combination IF amp/detector/AGC amp is a National LM-3089N, and the 1/2-watt audio amp is a National LM-386N.

construction, testing, and alignment

Figure 2 is a schematic of the analyzer. A printed circuit board is available from WA2PZO; I recommend using this and WA2PZO parts kits. (Although the pots, S-meter, and speaker aren't furnished, most are available from Radio Shack.) **Figure 2A** shows the component layout on the WA2PZO printed circuit board (foil side down). Alternatively, you could use perfboard and point-to-point wiring.

Figure 3 is a schematic diagram of the interconnections between the Sanyo tuner, the three-IC printed circuit board, and the scope. Once everything is connected as shown in **fig. 3**, alignment can begin. (It should be easy, since there are only four adjustments,

By Robert M. Richardson, W4UCH, 22 North Lake Drive, Chautauqua, New York 14722

the ferrite cores in L1, L2, L3, and L4.)
 With all the parts hand — and assuming you're using the PCB — assembly time is at most an hour or two. I tuned up my unit using only a grid dip meter as a signal source in about 20 minutes.

Construction of the PCB proceeds as follows:

1. Install the jumper at the lower edge of U3 as illustrated in fig. 2A.
2. Install the 11 resistors as shown in fig. 2A.

3. Install the 16 capacitors as indicated in fig. 2A. Since C6 and C7 are electrolytics, be sure to observe the polarity indicated in fig. 2A.
4. Install the Murata ceramic filter, FL1. Because it's symmetrical, it can be installed in either direction.
5. I recommend carefully installing sockets for U1 (16-pin DIP), U2 (8-pin DIP), and U3 (14-pin DIP).
6. Install L1 through L5, carefully bending the pins slightly so that they fit easily into the PCB's pre-drilled

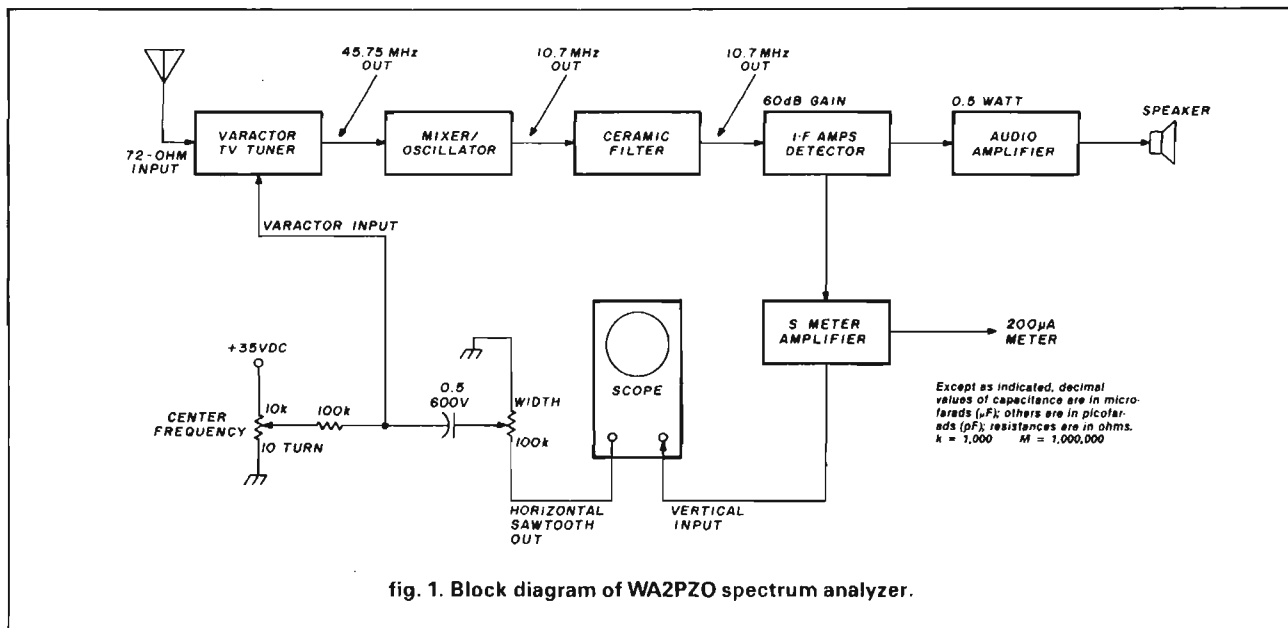


fig. 1. Block diagram of WA2PZO spectrum analyzer.

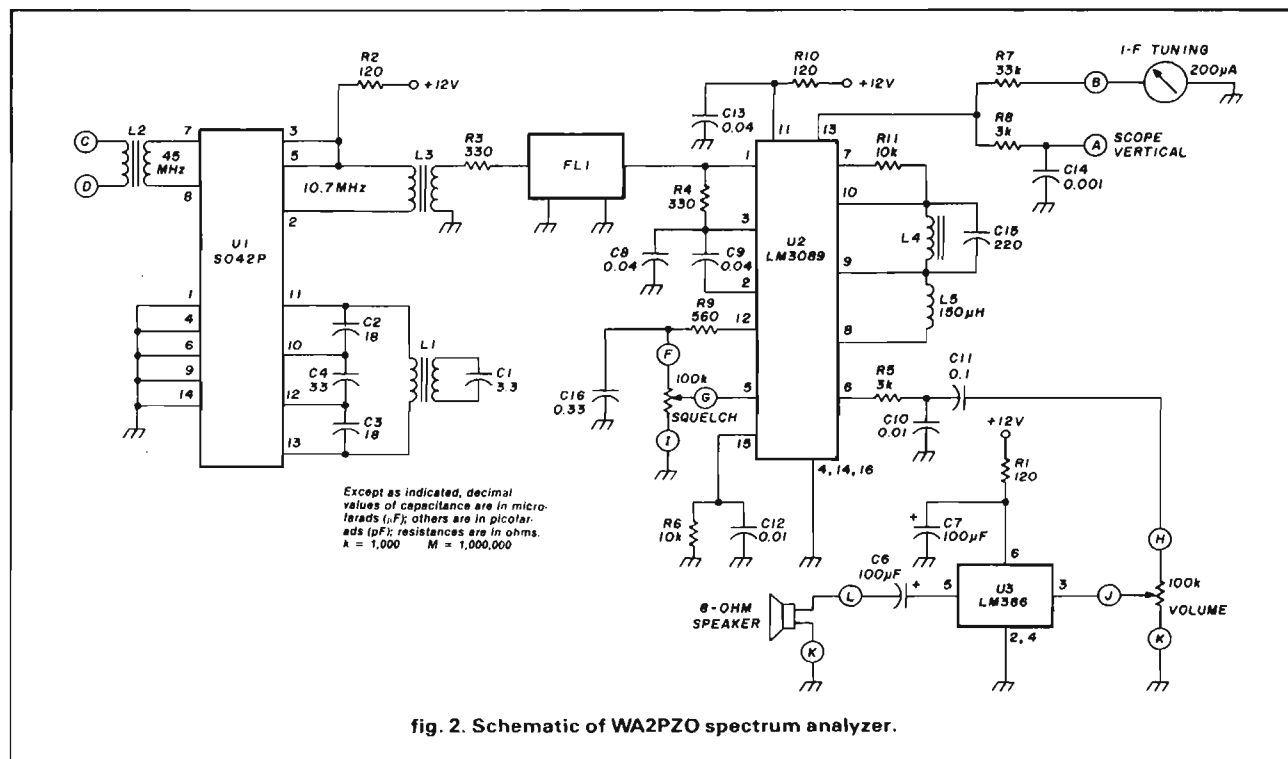


fig. 2. Schematic of WA2PZO spectrum analyzer.



SWL's: Are You Plagued By Phantom Signals?



Meet the Eliminator.

Don't let its small dimensions (4"x3"x2") fool you—the Grove Minituner III is a big weapon against images, intermod and phantom signals on your shortwave receiver!

This short wave/long wave pre-selector is designed to boost performance in the 100 kHz-30 MHz frequency range. If you own one of the popular general coverage communications receivers and are using an outside antenna, you NEED this extra measure of selectivity.

No power required. Simply connect between your receiver and antenna. Equipped for standard PL-259 connections. **Only \$39** (free UPS shipping; \$5 U.S. Mail/Parcel Post). Order TUN-3.



Grove Enterprises
140 Dog Branch Road
Brasstown, N.C. 28902

MC, Visa or COD call:
1-800-438-8155

Shop Grove for fantastic values in shortwave receivers, antennas, cable, performance boosting accessories and literature.

Call (704) 837-9200 or write to above address for free catalog!

33 cm. • 23 cm. • 13 cm.

LOOP YAGIS AND AMPLIFIERS FROM DOWN EAST MICROWAVE

• TROPO	• WEAK SIGNAL
• EME	• OSCAR MODE L & MODE S
• 902	• 2304
• 1269	• 2400 MHz
• 1296	
2345LY	45 el loop Yagi 1296 MHz 20 + dBi \$85
2445LY	45 el loop Yagi 1269 MHz 20 + dBi \$85
1345LY	45 el loop Yagi 2304 MHz 20 + dBi \$75
3333LY	33 el loop Yagi 902 MHz 18.5 dBi \$85

above antennas are assembled and tested. All aluminum and stainless construction. Kits also available. Add \$8 (\$11 west of Rockies) per antenna for UPS shipping.

2 & 4 way power dividers, complete arrays available
2316 PA Linear Amp 10w in 18w out 1296 MHz 13.5 V \$245
2335 PA Linear Amp 10w in 36w out 1296 MHz 13.5 V \$295
include \$5 for UPS Blue — 48 states.

Write about Higher Power, 2304 linears, GaAs Fet preamps
Free catalog

DOWN EAST MICROWAVE

Bill Olson, W3H01

Box 1655A, RFD 1, Burnham, ME 04922
(207) 948-3741

✓ 155

ANTENNA And TOWER ACCESSORIES

MAST ADAPTERS
MA-2 \$27.50 NEW
MA-3 \$29.50

BEAM MOUNT
BM 1 \$34.50

STANDOFFS
SO-1 \$34.50
SO-2 \$64.50
SO-3

Commercials: Antenna Standoff \$99.50

NEW FREE CATALOG NOW AVAILABLE

IIX EQUIPMENT LTD.
P.O. Box 9 Oaklawn, IL 60454
(312) 423-0605

✓ 156

BRAND NEW — JUST RELEASED

HOT OFF THE PRESS!!!

GET *** CONNECTED to Packet Radio

by Jim Grubbs, K9EI

Beginners' guide to Packet Radio operation.

Packet communications is one of the hottest subjects in Amateur Radio these days. Noted computer author Jim Grubbs, author of the *Commodore Ham's Companion* and *Command Post*, has put together one of the first books on how to get on Packet Radio. Packet basics are fully discussed in a step-by-step manner. Subjects also covered are: selecting a TNC, setting up your computer, Packet organizations and publications, protocol, networking, Packet answering machine, file transfers, accessories and more! 1986 208 pages 1st Edition.

JG-PR

Softbound \$12.95

Also available *The Commodore Ham's Companion*, Order code JG-CC, \$15.95, and *Command Post*, Order code JG-CP, \$9.95.

Please add \$3.50 for shipping and handling

Ham Radio's Bookstore

Greenville, NH 03048

Want to
Advertise in
HAM RADIO?

Call Rally Dennis
(603) 878-1441
today for more
information

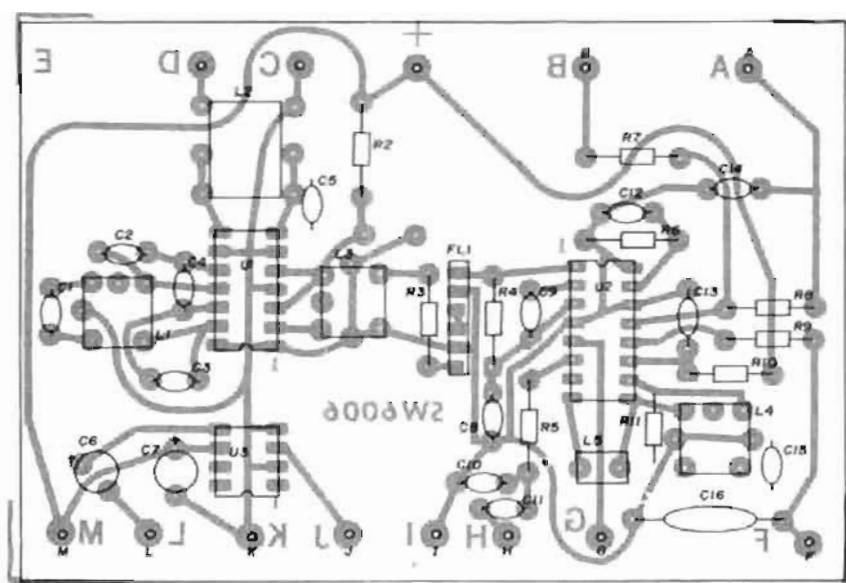


fig. 2A. Component layout on the WA2PZO printed circuit board (foil side down).

holes. Because L5, the 150 μ H inductor, is symmetrical it can be installed in either direction.

7. Most important: lubricate the small ferrite cores of L1, L2, L3, and L4 with a drop or two of WD-40 before attempting adjustment. These cores are extremely brittle; use a plastic or nylon tuning tool matched to the width of the ferrite slots (using a metal one will guarantee their destruction).

8. If you're not using a 200- μ A S-meter, install a jumper from 'A' to ground.

Testing and alignment proceed as follows:

1. Connect the TV tuner's VHF input to your 2-meter antenna.
2. Set the VHF/UHF switch to the VHF position.
3. Set the Hi/Lo switch to *Hi*.
4. Make sure the top of the ferrite core in L1 is exactly even with the top of its shielded housing.
5. Set the squelch control to zero and adjust the volume control for a slight hiss from the speaker with the gain control at maximum resistance (10 kilohms).
6. Set the width control (sawtooth sweep from scope) to zero.
7. Connect a voltmeter to pin 10 of the TV tuner (varactor input). Use the +30-volt voltmeter range (adjust the center frequency 10k-turn pot so that varactor bias is below +30 VDC).
8. Turn the center frequency pot slowly down (reducing varactor bias voltage) until a local TV video carrier is both heard on the speaker (buzz) and seen on the scope. If no TV stations are nearby, use a signal generator with modulated output or a grid dip meter.

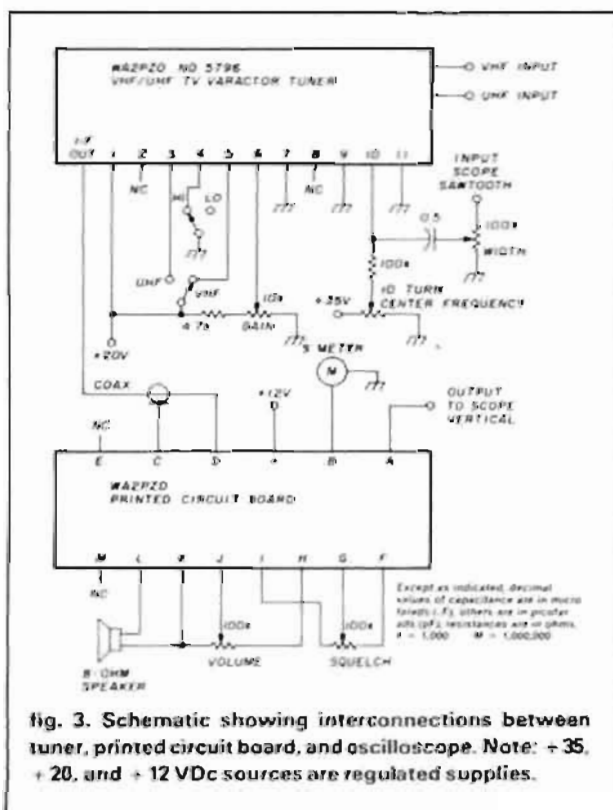


fig. 3. Schematic showing interconnections between tuner, printed circuit board, and oscilloscope. Note: +35, +20, and +12 VDC sources are regulated supplies.

9. Peak the ferrite slugs in L2 and L3 for maximum signal output on the scope.
10. Continue tuning the center frequency pot until a TV audio signal is found, then adjust L4 for maximum

NEW
DVK-100

ANNOUNCING THE DIGITAL VOICE KEYS



Mic not included

Now for the first time you can enjoy the truly unique operation of a Digital Voice Announcement System, designed specifically for Amateur Radio communications. The DVK-100 represents the latest technology in digital audio processing. Create your own natural voice contest calls, CO's etc. Your voice is stored in digital memory, ready to be played back at the touch of a key. The Digital Voice Keyer is not a tape recorder or robotic sounding synthesizer but a true full fidelity natural voice record/playback system.

The DVK-100, is a must for the avid contesteur and great audio accessory for any Ham Shack.

FEATURES

- Superior natural voice quality
- Micro processor controlled
- 32 seconds of message time
- PTT/VOX operation
- Dynamic/condensor mic input
- Selectable monitor amplifier with preset level controls
- Selectable audio compressor
- Sealed membrane keyboard
- 4 independent voice memories
- Positive/negative keyed PTT
- ESD/EMI/RFI shielding
- Selectable end of transmission tone generator

The sound of the future is here today. Contact your local Amateur Radio dealer or NTE for further information.


\$349⁰⁰ SUGGESTED NET AMATEUR PRICE

✓ 157

DEALER INQUIRIES INVITED



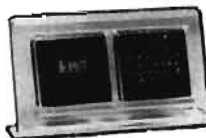NEL-TECH LABS, INC.
28 DEVONSHIRE LANE • LONDONDERRY, NH 03053
603-434-8234



RECEIVE THIS LCD CALENDAR/CLOCK FREE WITH YOUR SUBSCRIPTION

WHAT'S REALLY HAPPENING IN HOME SATELLITE TV?

STVSM THE HOME SATELLITE TELEVISION MAGAZINESM

A monthly of 100-plus pages—has everything you need to know about where to find equipment, how to install it, system performance, legal viewpoints, and industry insights! With your subscription to STVSM you will receive a FREE LCD Calendar/Clock.

- Only \$19.95 per year (12 monthly issues)
- \$1.00 for sample copy

IF YOU HAVE A SATELLITE SYSTEM, THEN YOU REALLY NEED ...



OnSat

The best in satellite programming! Featuring: ★All Scheduled Channels ★Weekly Updated Listings ★Magazine Format ★Complete Movie Listing ★All Sports Specials ★Prime Time Highlights ★Specials Listing and ★Programming Updates!

- Only \$45.00 per year (52 weekly issues)
- 2 Years \$79.00 (104 weekly issues)
- \$1.00 for sample copy

VisaSM and MasterCardSM accepted (subscription orders only). All prices in US funds. Write for foreign rates.

Send this ad along with your order to:

STVSM/OnSatSM

P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384
SUBSCRIPTION CALLS ONLY
TOLL FREE 1-800-438-2020



INTERNATIONAL MONTHLY MAGAZINE BY AND FOR ACTIVE RADIOAMATEURS

RADIOSPORTING

A magazine dedicated to quality and sportsmanship in amateur radio operating. Fresh, timely, practical and down to earth reading for little pistols and big guns. Written by world's best in their fields.

Includes DX News, QSL Info, 160 m, DXpeditioning, Propagation, Awards, contest rules and results, Traffic-Emergency, FCC News, New Products, Antennas, technical articles, equipment reviews and modifications, computer programs, Radio Funnies, Club Life, YL, RTTY, VHF/UHF, Mail Room, Classified Ads and much more in a magazine format with the speed of a bulletin.

RADIOSPORTING sponsors DX Century Award, Contest Hall of Fame, World Contest Championship and World Radio Championship contest.

"Your publication is superb! Keep it up!"

Joe Reisert, W1JR

"Your W2PV articles are priceless. Your magazine is super!"

Rush Drake, W7RM

"Let me congratulate you on a very impressive magazine. Just what I've been looking for as a DXer and Contesteur!"

Dick Moen, W7RO

"RADIOSPORTING, once received, cannot be tossed aside until it is read from cover to cover. Then reviewed again and again."

Chas Browning, W4PKA

Subscription rates: 1 year USA \$18, Canada CDN\$24, Overseas US\$21; 2 years \$33, \$44, \$39 respectively. Single issue \$2.

TRY US! SUBSCRIBE OR SEND \$1 FOR YOUR SAMPLE COPY.

RADIOSPORTING Magazine
PO Box 282, Pine Brook, NJ 07058, USA



audio output and minimum background noise from the speaker.

11. Though each varactor tuned TV tuner will have somewhat different voltage versus frequency response, see **fig. 10** to see the response we obtained using a Sanyo varactor tuned TV tuner.

Figure 4 is a photo of our finished spectrum analyzer. The tuner and PCB are mounted on top of a 2

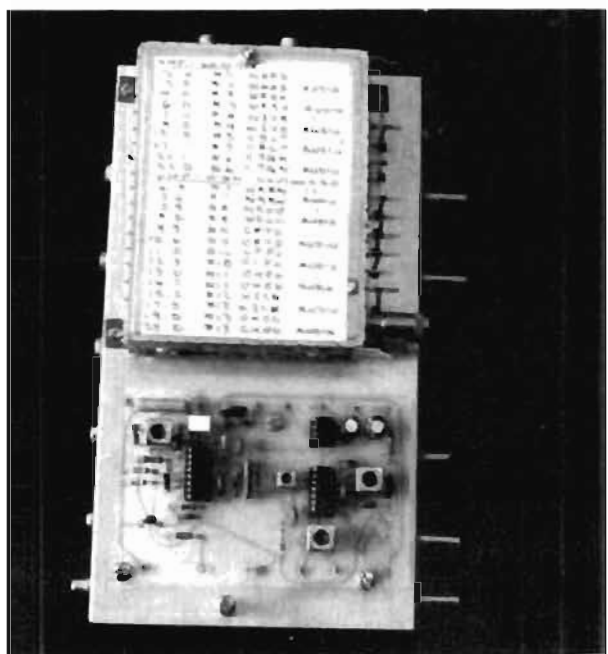
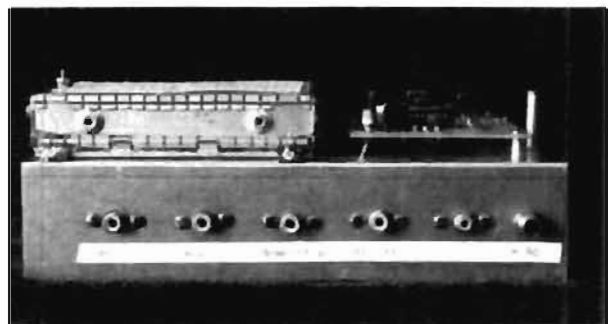
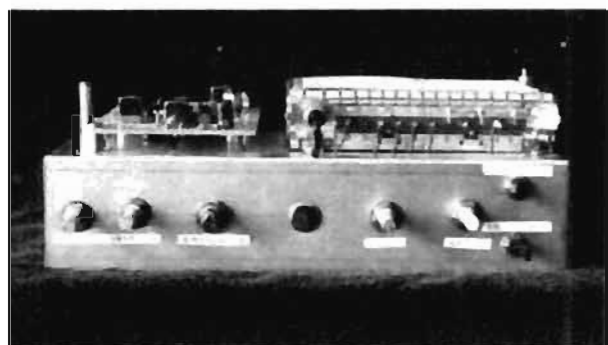


fig. 4. Completed spectrum analyzer: (A) front, (B) rear, (C) top.

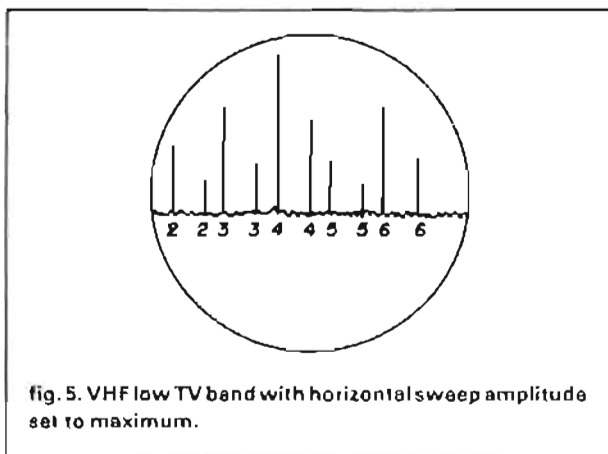


fig. 5. VHF low TV band with horizontal sweep amplitude set to maximum.

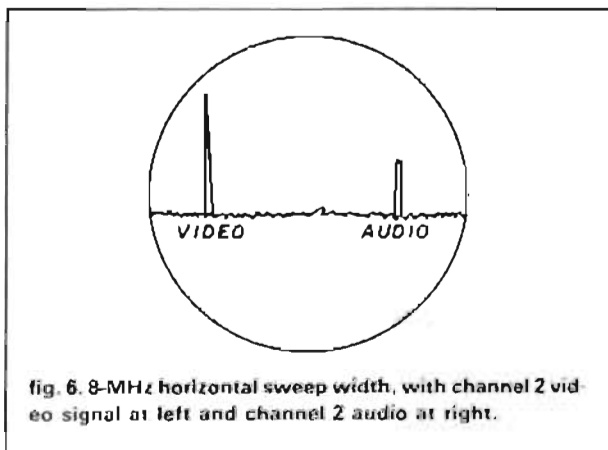


fig. 6. 8-MHz horizontal sweep width, with channel 2 video signal at left and channel 2 audio at right.

x 5 x 9-inch (5 x 13 x 23 cm) aluminum chassis. The PCB is mounted on 1/2-inch (1.3 cm) threaded standoffs. Left to right, the five pots are: volume, squelch, center frequency, sweep width, and tuner gain. The two mini-toggle switches on the right of **fig. 4** are VHF-UHF (top) and VHF LOW – VHF HIGH (bottom). On the rear of the chassis are six RCA phono jacks: +35 VDC for tuner center frequency; +20 VDC for tuner; +12 VDC for oscillator/mixer, second IF amps, U3 audio amp; horizontal sweep from scope; vertical output to scope; and audio output to the 8-ohm speaker.

operation

Now the fun really begins. For antennas, I used my two 23-element Cushcraft 2-meter "Boomers." (No, I don't bounce signals off the moon with them, but I can work into 2-meter repeaters in Toronto, some 125 miles away. My QTH is on the south shore of Chautauqua Lake, some 65 miles southwest of Buffalo; because of this distance, and the presence of a range of hills about 300 feet (90 meters) high between Buffalo and Chautauqua, TV signals aren't par-

MICROWAVE MODULES LTD.

A Connoisseurs Choice in VHF/UHF

CONVERTERS SOLID STATE AMPLIFIERS

TRANSVERTERS

VMT 111/2RR

144Mhz. TRANSVERTER
High Quality DBM
Repeater Offset
GaAsFET Receiver
25 WATTS OUTPUT

\$335.00

Selectable Input:
3w, 10w, 25w



1mw to 300mw 28Mhz. Drive

VML 111/200-S

144Mhz. SOLID-STATE LINEAR
GaAsFET Pre-Amp
Bargraph Display
200 WATTS OUTPUT

\$385.00



MODELS AVAILABLE FOR
50Mhz. 432Mhz
1296Mhz
OSCAR MODE B & L
AMATEUR TELEVISION

AVAILABLE FROM:

THE "PX" SHACK

VHF/UHF
EQUIPMENT



14445 Lanchutms KC2PX
52 Stonewyck Drive
Belle Mead, New Jersey 08502
(201) 874-6013



MICROWAVE
MODULES LTD.

Hours: 11am - 3pm
4pm - 10pm



✓ 161

NEMAL ELECTRONICS

Your Authorized
Distributor For



BELDEN

INTRODUCTORY SALE!

Belden No.	Nemal No.	Description	Per 100 ft.	Per ft.
8214	1102B	RG8 /U Foam 96%	\$45.00	.50
8237	1100B	RG8/U Poly 96%	39.00	.44
8241	1500B	RG59/U Poly 96%	13.00	.15
8267	1130B	RG213/U Poly 96%	53.00	.59
9269	1800B	RG82A/U Poly 96%	15.00	.17
8218	1450B	RG174/U Poly 96%	12.00	.14
9913	1180	Low Loss 50 Ohm	46.00	.58

OTHER QUALITY CABLES

Nemal No.	Description	Per 100 ft.	Per ft.
1110	RG8X 95% Shield (mini 8)	15.00	.17
1130	RG213/U MII Spec 96% Shield	34.00	.36
1140	RG214/U MII Spec Silver	155.00	1.65
1705	RG142B/U Teflon Silver	140.00	1.50
1310	RG217/U 5/8" 60 Ohm Dbl Shld.	80.00	.85
1470	RG223/U MII Spec. - Silver	80.00	.85

ROTOR CABLE - 8 COND.

8C1822	2-18 Ga., 6-22 Ga.	19.00	21
8C1620	2-16 Ga., 6-20 Ga. Heavy Duty	34.00	36

FXA12	Smooth Alum. w/black jacket	79.00	89
FLC12	Corrug'd. Copper (EO, Helix LDF)	159.00	1.69

CONNECTORS - MADE IN U.S.A.

NE720	Type N for Belden 9913	4.75	
PL259	Standard Plug for RG8, 213	.65	
PL259AM	Amphenol PL259	.89	
PL259TS	PL259 Teflon/Silver	1.59	
UG21D	Type N for RG8, 213, 214	3.00	
UG17S	Adapter for RG58	.22	

Call or write for complete Price List
Shipping: Cable - \$3.00 per 100 ft. Florida Residents add 5%
Connectors - and 12%, \$3.00 minimum Orders under \$20 Add \$2 Handling

Nemal's new 32-page Cable & Connector Selection Guide now available at no charge with orders of \$50 or more or for a cost of \$4.00 individually.

NEMAL ELECTRONICS

12240 N.E. 148th Ave., Dept. Q, Miami, FL 33161

Telephone (305) 893-3924

✓ 162

DO YOU KNOW WHERE TO FIND REAL BARGAINS



on NEW and USED ELECTRONIC Equipment?

**You'll Find Them
in the Nation's No. 1
Electronic Shopper Magazine**

NUTS & VOLTS

Now in Our 5th Year

Nuts & Volts is published MONTHLY and features:
**NEW STATE-OF-THE-ART PRODUCTS •
SURPLUS EQUIPMENT • USED BARGAINS •
LOW COST AD RATES • PRIVATE AND
COMMERCIAL CLASSIFIEDS • NATIONAL
CIRCULATION • NEW PRODUCT NEWS
SECTION • AND A FREE CLASSIFIED AD
WITH YOUR SUBSCRIPTION**

SUBSCRIPTION RATES

- One Year - 3rd Class Mail \$10.00
- One Year - 1st Class Mail \$15.00
- One Year - Canada & Mexico (in U.S. Funds) .. \$18.00
- Lifetime - 3rd Class Mail (U.S. Only) \$35.00

ORDER NOW!

- SEND: CHECK MONEY ORDER
 VISA MASTERCARD

TO: **NUTS & VOLTS MAGAZINE**
P.O. BOX 1111-H
PLACENTIA, CALIFORNIA 92670
(714) 632-7721

Name _____
Address _____
City _____
State _____ Zip _____
Card No _____
Exp. Date _____

**IF YOU'RE INTO ELECTRONICS,
THIS MAGAZINE WILL SAVE YOU MONEY!**

Dealer Inquiries Invited

✓ 163

ticularly strong. Nevertheless, all the TV channels on both the VHF low TV and VHF high TV bands were displayed on the first try. Both the vestigial sideband video signal and its accompanying FM audio signal were clearly displayed for each channel.

Figures 5 through 10 are sketches of the oscilloscope display in the noted modes of operation. (Oscilloscope cameras cost about \$300; I chose not to add one to my \$39.95 Heathkit scope.)

Figure 5 shows the VHF low TV band with the horizontal sweep amplitude set to maximum. Each TV channel pair displayed (video and audio) is noted. The height of each signal is proportional to signal strength; some Canadian TV stations really pack a wallop even though they're 125 miles away.

Figure 6 illustrates about 8 MHz horizontal sweep width (left side of CRT to right side of CRT) with the video signal of Channel 2 on the left and the audio from Channel 2 on the right side.

Figure 7 displays the sweep width reduced to about 2 or 3 MHz with the center frequency set to Channel 2's video carrier. Note the blanking and vertical sync pulse riding on top of the carrier.

Figure 8 is the Channel 2 video carrier with the horizontal sweep set to zero. The blanking pulse with the vertical sync pulse on top is on the left side. The eight squiggles to the right of the vertical sync pulse are the color burst; all the hazy, wavy signals to the right are the video information. The top of the vertical sync pulse represents 100 percent modulation and the bottom of the video information represents the white level of video at about 15 percent modulation.

Although some scope photos or sketches show 100 percent modulation at the bottom, I prefer it at the top. If you insist on having it at the bottom, simply turn the figure upside down and view it in a mirror.

Figure 9 illustrates the 2-meter band with horizontal sweep representing about 3 MHz. The left side of the CRT is at 145 MHz and the right side of the CRT is at 148 MHz. Spread between 146 and 148 MHz, we can see about six 2-meter repeaters located in the Buffalo and Toronto areas.

Figure 10 is a plot of varactor tuning voltage versus frequency on my Sanyo TV tuner. The 10-turn, 10-ohm pot used for setting the varactor voltage is an absolute "must" for fine tuning.

By reducing the sweep width to zero and single-signal tuning across each band, I was able to copy the audio on the VHF TV low band from the following stations: WGRZ-TV (Channel 2, Buffalo) WPSX-TV (Channel 3, Rochester), WIVB-TV (Channel 4, Buffalo), CBLT-TV (Channel 5, Canada), and CTGN-TV, (Channel 6, Canada). On the VHF TV high band we copied audio from air-to-ground and air traffic control stations; 2-meter repeaters in western New York

and the Toronto area; commercial FM pagers; Toronto Coast Guard marine weather on 161.775 MHz; the Erie, Pennsylvania, weather bureau on 162.40 MHz; the Buffalo, New York, weather bureau on 162.55 MHz; WKBW-TV (Channel 7, Buffalo); WROC-TV (Channel 8, Rochester); CFTO-TV (Channel 9, Canada); CFPL-TV (Channel 10, Canada); CHCH-TV (Channel 11, Canada); WICU-TV, (Channel 12, Erie); and CKCO-TV (Channel 13, Canada). On the UHF TV

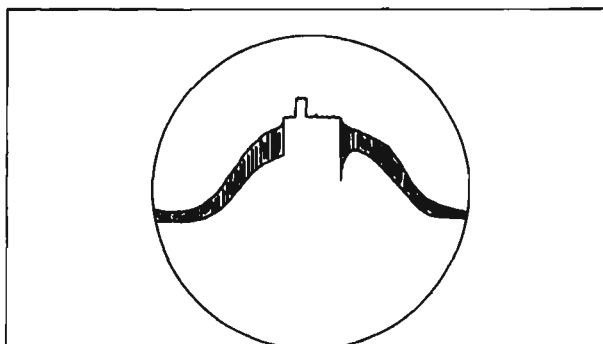


fig. 7. Sweep width reduced to about 2 or 3 MHz with center frequency set to channel 2's video carrier.

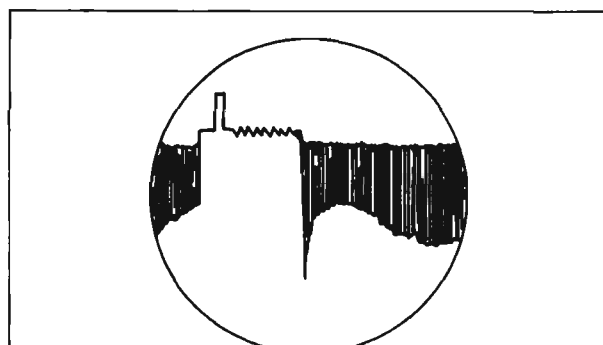


fig. 8. Channel 2 video carrier with horizontal sweep set to zero.

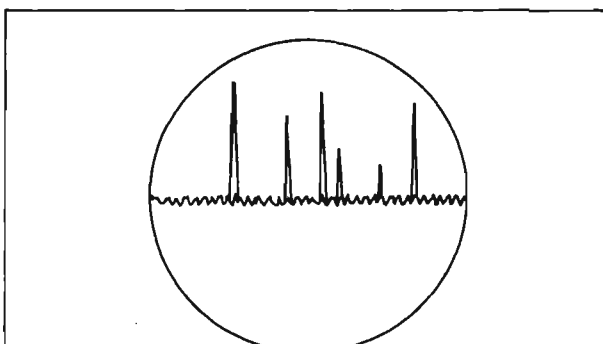


fig. 9. 2-meter band with horizontal sweep representing about 3 MHz.

Fig. 10. Varactor voltage versus frequency (will vary from tuner to tuner).

VHF low band	
voltage	frequency MHz
0.5	50.00 6-meter band
2.0	55.25 channel 2 video
3.5	59.75 channel 2 audio
4.0	61.25 channel 3 video
6.0	65.75 channel 3 audio
7.0	67.25 channel 4 video
9.5	71.75 channel 4 audio
13.5	77.55 channel 5 video
17.1	81.75 channel 5 audio
20.1	83.25 channel 6 video
34.8	87.75 channel 6 audio
VHF high band	
0.5	135.00 air to ground
1.0	144.00 2-meter band
2.0	148.20 commercial paging
4.0	162.55 Buffalo weather
6.5	175.25 channel 7 video
7.6	179.75 channel 7 audio
7.9	181.25 channel 8 video
9.0	185.75 channel 8 audio
9.3	187.25 channel 9 video
10.6	191.75 channel 9 audio
11.0	193.25 channel 10 video
12.3	197.75 channel 10 audio
13.0	199.25 channel 11 video
14.7	203.75 channel 11 audio
15.2	205.25 channel 12 video
17.5	209.75 channel 12 audio
19.0	211.25 channel 13 video
25.5	215.75 channel 13 audio

band we copied about six TV stations from Channel 17 through Channel 26, including a French language Canadian TV station. The Sanyo TV tuner is one super little box with excellent sensitivity — i.e., much better than 1 microvolt. All these stations were copied using only 2-meter antennas.

other uses

Once you become accustomed to using it, the spectrum analyzer is probably the greatest trouble-shooting aid since Volta invented the voltmeter. With the proper probes, attenuators, and converters it can be used as an RF voltmeter; as a signal tracer in transmitters and receivers; and for transmitter alignment, harmonic measurement, deviation measurement, oscillator injection measurement, IF alignment, and spurious radiation measurement, to name but a few of its applications. If you want to dig deeper, Cushman Electronics (2450 North First Street, San Jose, California 95131) publishes a neat little book entitled *Using The Spectrum Monitor* Priced at \$7.25 (postpaid), it's easily understood by the average Radio Amateur.

acknowledgement

I wish I could claim authorship for this unique design, but credit goes entirely to my friend, Murray Barlowe, WA2PZO, who not only created the design but has generously made a partial kit of parts, TV tuner, and printed circuit board available to Amateurs at virtually his cost.

For more information send an SASE to Murray Barlowe, WA2PZO, P.O. Box 393, Bethpage, New York 11714. Once you try it, you'll never understand how you got along without it.

ham radio



Crystal Filters TRIPLE DISCOUNT SALE

The more filters you buy, the more you save! 10% Off on one, 20% on two, 30% on 3 or more. For example, one \$60 filter costs \$54; two \$54+48; three \$54+48+42; four \$54+48+42+42. One \$110 filter costs \$99; two \$88, etc. Figure each price group separately. For combos (matched pairs only) see prices below.

8.83MHz 8-POLE FT FILTERS FOR KENWOOD - Reg. \$60 ea.

Bandwidths: CW 250, 400Hz; SSB 1.8, 2.1; AM 6.0KHz. Suitable for all models from TS120 through TS940. TS440S introductory. Take \$5 off sale price for two.

Filter Cascading Kits with FT Filter

TS430S - Discounted 2 1 filter plus \$20 for amp board
TS820S - Discounted 2 1 filter plus \$5 for parts

455KHz 8-POLE FT FILTERS FOR KENWOOD - Reg. \$110 ea.

Bandwidths available: CW 400Hz; SSB 2.1KHz. Suitable for R820, TS830, TS930, TS940. Matched Filter Pairs for Above Models - Reg. \$170 ea. SSB: 2.1KHz (455 and 8.83); CW: 400Hz: (455 and 8.83). Discounted Pairs: one for \$147, \$279 for both.

3.395MHz FILTERS FOR TS520, 511, R599 - Reg. \$60 ea.

Bandwidths available: 250, 400Hz, 1.8", 2.1KHz. *1.8 special - Take \$10 off list, then discount!

Same deal for YAESU, DRAKE, ICOM, and HEATH filters!

Check your GREEN SHEET for List prices, or PHONE

LIMITED QUANTITIES — ORDER NOW TO AVOID DELAY

When ordering, specify Make and Model Number of your Rig; Frequency and Bandwidth of filter(s) desired.

SHIPPING: \$5 US and Canada, \$12 elsewhere

Order by Mail or Phone. VISA/MC or COD accepted

GO FOX - TANGO — TO BE SURE! GET THE BEST — FOR LESS!

FOX-TANGO Corp. Box 15944, W. Palm Beach, FL 33416
Telephone: (305) 683-9587

1986-87 ARRL REPEATER DIRECTORY

\$3 + \$2.00
shipping and handling

Send \$5.00 to:
Ham Radio's Bookstore
Greenville, N. H. 03048