# H-bridge modification for the OE5JFL controller

(by Walter Crauwels ON4BCB January 2016)

#### Introduction:

Many of us are using the well known OE5JFL antenna controller.

Some of us are struggling with the limited motor current of the L6203 H-bridge from SGS Thomson.

Following the datasheet 5A max peak current .

I worked out a solution using a double high power motor driver based on two BTS7960 chips.

Those are available from various ebay vendors as they are used for many arduino projects:

IBT-2 H-bridge.



# Input port

1	2	1、RPWM	Forward level or PWM signal input, active high
	0	2、LPWM	Inversion level or PWM signal input, active high
0	0	3、R_EN	Forward drive enable input, high enable, low close
0	0	4、 L_EN	:Reverse drive enable input , high enable , low close
O	0	5、 R_IS	: Forward drive -side current alarm output
0	0	6、L_IS	Reverse drive -side current alarm output
$\sim$		7、VCC	:+5 V power input, connected to the microcontroller 5V power supply
7	8	8、GND	: Signal common ground terminal

Usage one:

VCC pick MCU 5V power supply, GND connected microcontroller GND R\_EN and L\_EN shorted and connected to 5V level, the drive to work. L\_PWM, input PWM signal or high motor forward R\_PWM, input PWM signal or high motor reversal

Usage two:

VCC pick MCU 5V power supply, GND connected microcontroller GND R\_EN and L\_EN short circuit and PWM signal input connected to high-speed L\_PWM, pin input 5V level motor is transferred R\_PWM, pin input 5V level motor reversal

## Modification:

Following the OE5JFL original schematic:

- 1) Remove the L6203 for Azimuth IC1, and IC2 for Elevation carefully
- 2) Connect the following wires between the pads where the L6203 was and the IBT2 H-bridge:

### Azimuth:

IC1 Pin5 (CW) → IBT-2 azimuth Pin 1 (R\_PWM)

IC1 Pin7 (CCW) → IBT-2 azimuth Pin 2 (L\_PWM)

IC1 Pin11 (PWM) → IBT-2 azimuth Pin 3+4 (R\_EN + L\_EN)

IC1 Pin6 (GND) → IBT-2 azimuth Pin 8 (GND)

R15 & R16 junction (+5V) → IBT-2 azimuth Pin 7 (VCC)

### Elevation:

IC2 Pin5 (UP) → IBT-2 elevation Pin 1 (R\_PWM)

IC2 Pin7 (DOWN) → IBT-2 elevation Pin 2 (L\_PWM)

IC2 Pin11 (PWM)  $\rightarrow$  IBT-2 elevation Pin 3+4 (R\_EN + L\_EN)

IC2 Pin6 (GND) → IBT-2 elevation Pin 8 (GND)

R15 & R16 junction (+5V) → IBT-2 elevation Pin 7 (VCC)





