


Hints & Kinks

by DJ9BV

DB6NT's 24 GHz-Transverter

Hints for construction (Aufbauhinweise):

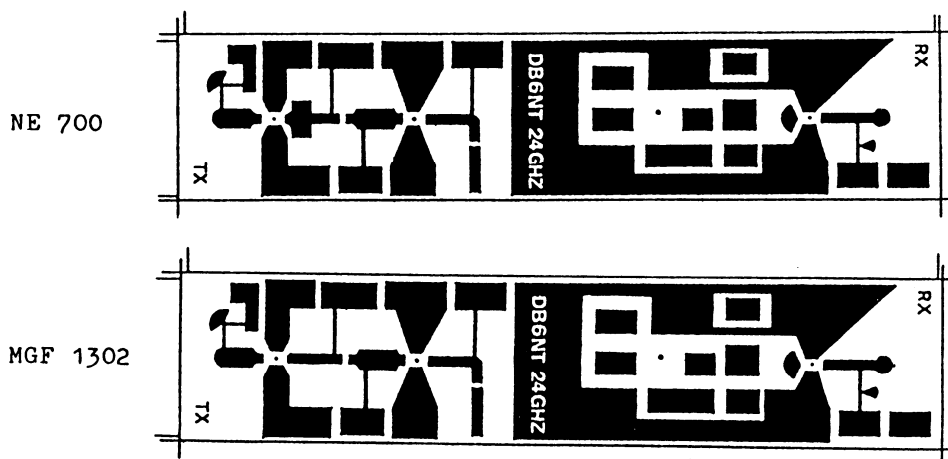1. New PCB for change of T4 from NE700 into MGF-1302:



2. Change of 150 k resistor in IF-Amp into 100k or 82 k:

