

Technician Licensing Class

**Electrical components,
semiconductors,
circuit diagrams,
component functions**

T6A - T6D

Valid

July 1, 2018 Through June 30, 2022

T 6 A

Topics


- Electrical components:
 - fixed and variable resistors;
 - capacitors and inductors;
 - fuses;
 - switches;
 - batteries

T 6 A

- The electrical component which opposes the flow of current in a DC circuit is the resistor. T6A01
- The component often used as an adjustable volume control is the potentiometer. T6A02
- The electrical parameter controlled by a potentiometer is resistance. T6A03

T 6 A

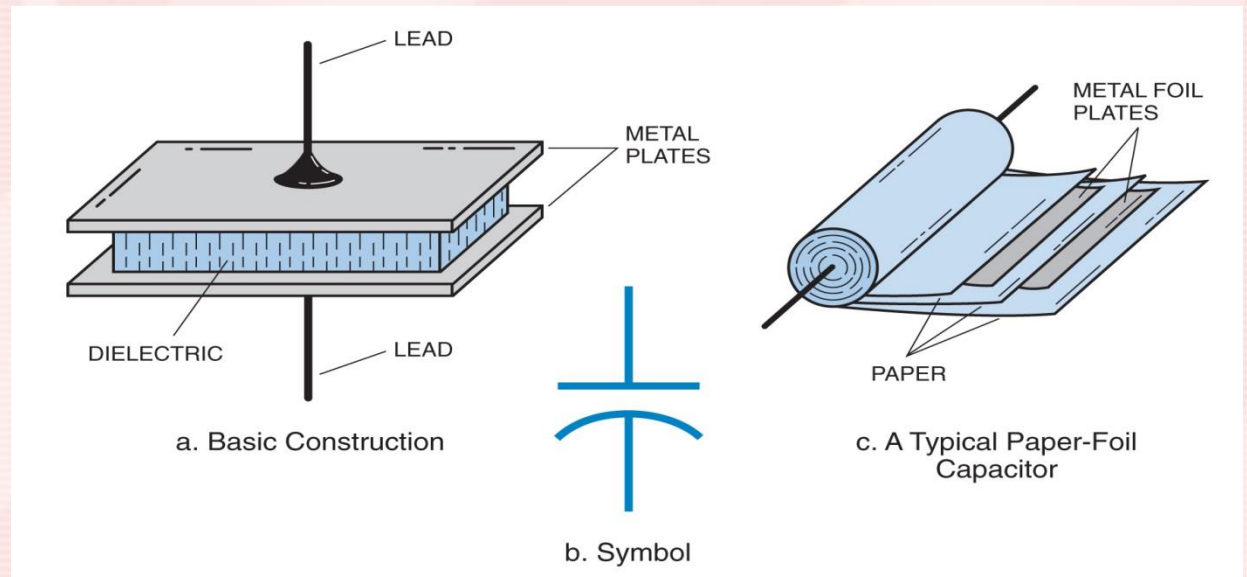- The electrical component that stores energy in an electric field is the capacitor. T6A04
- The type of electrical component that consists of two or more conductive surfaces separated by an insulator is a capacitor. T6A05



T 6 A

- The electrical component that stores energy in a magnetic field is an inductor. T6A06
- The electrical component usually composed of a coil of wire is an inductor. T6A07

T 6 A

- The electrical component used to connect or disconnect electrical circuits is the switch. T6A08
- The electrical component used to protect other circuit components from current overload is the fuse. T6A09

T 6 A

- These battery types are rechargeable:
 - Nickel-metal hydride;
 - Lithium-ion;
 - Lead-acid gel-cell

✓ All of these choices are correct. T6A10
- This type of battery is not rechargeable: Carbon-zinc. T6A11

T 6 B

Topics

- Semiconductors:
 - basic principles and applications of solid state devices;
 - diodes and transistors

T 6 B


- The class of electronic components that uses a voltage or current signal to control current flow are transistors. T6B01
- The electronic component that allows current to flow in only one direction is the diode. T6B02
- The component that can be used as an electronic switch or amplifier is the transistor. T6B03

T 6 B

- The component that consists of three layers of semiconductor material is the transistor. T6B04
- The transistor is an electronic component that can amplify signals. T6B05
- The cathode lead of a semiconductor diode is usually identified with a stripe. T6B06



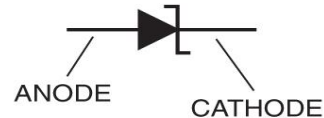Here is the schematic symbol of a diode. Current will only flow ONE WAY in a diode. You can remember this diode diagram as a one-way arrow (key words).




Here is the schematic symbol of a Zener diode. Since a diode only passes energy in one direction, look for that one-way arrow, plus a "Z" indicating it is a Zener diode. Doesn't that vertical line look like a tiny "Z"?

T 6 B

- The abbreviation LED stands for Light Emitting Diode.


T6B07

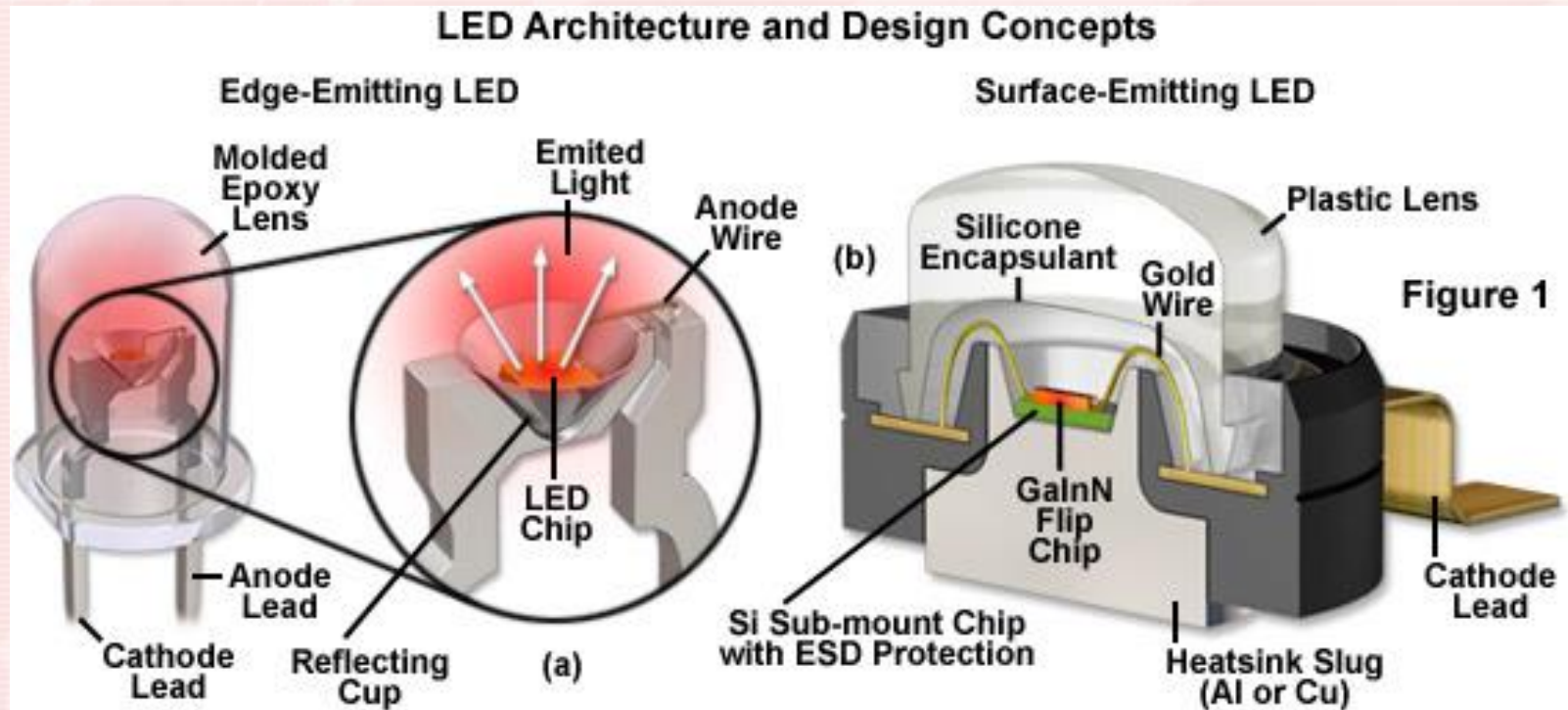

T 6 B

- The abbreviation FET stands for Field Effect Transistor.

T6B08

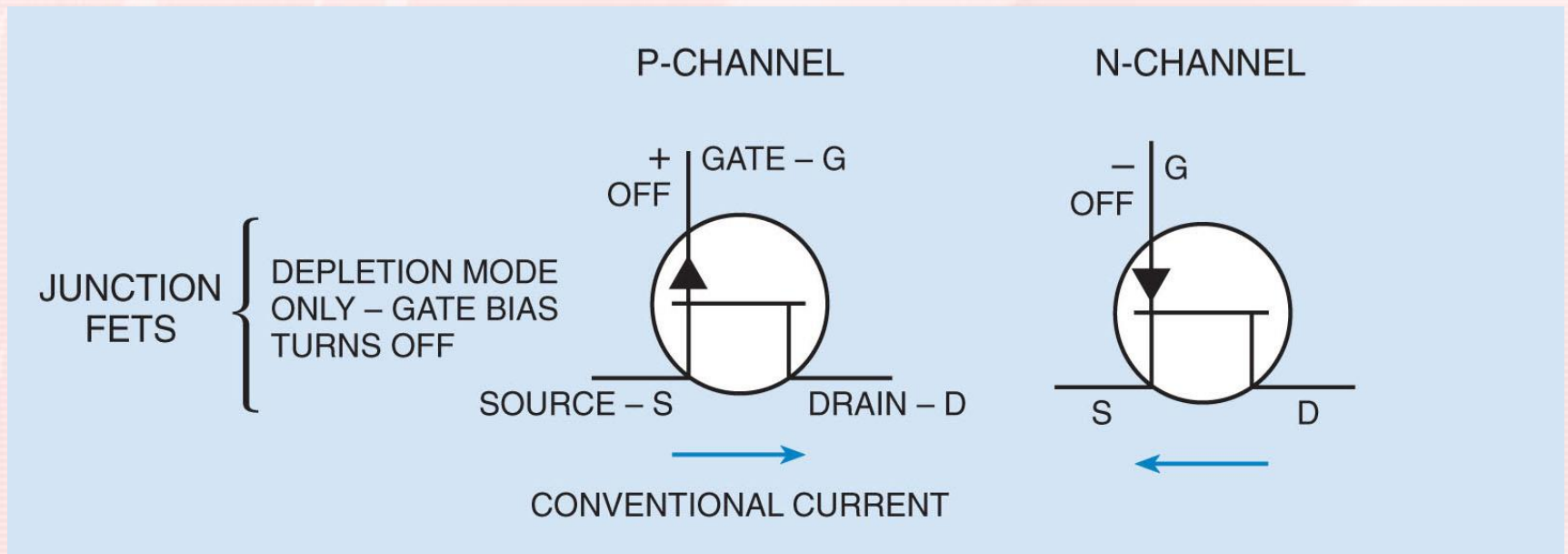

T 6 B

- The two electrodes of a diode are the anode and cathode. T6B09
- The primary gain-producing component in an RF power amplifier is the transistor. T6B10
- The term that describes a transistor's ability to amplify a signal is gain. T6B11

T 6 C

Topics

- Circuit diagrams;
 - schematic symbols

T 6 C

- The name of an electrical wiring diagram that uses standard component symbols is a schematic. T6C01

T 6 C

- Component #1 in Figure T1 is a Resistor T6C02

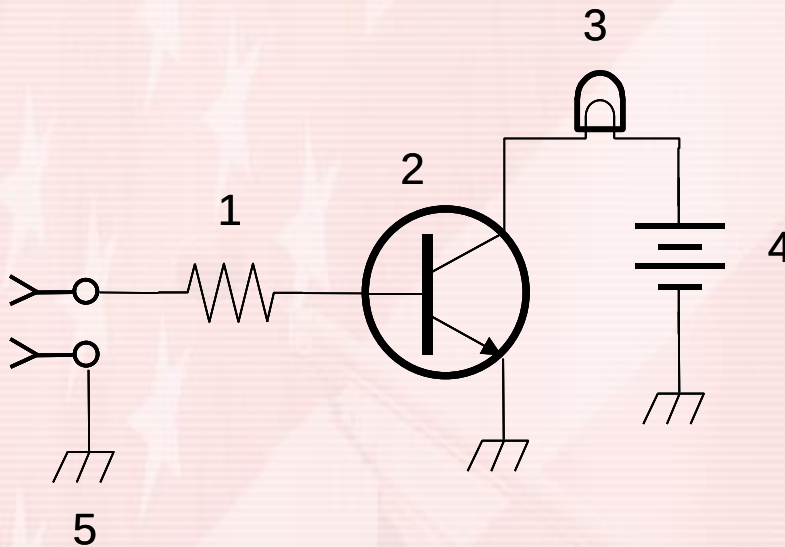


Figure T1

- Component #2 in Figure T1 is a Transistor. T6C03

T 6 C

- Component #3 in Figure T1 is a Lamp. T6C04

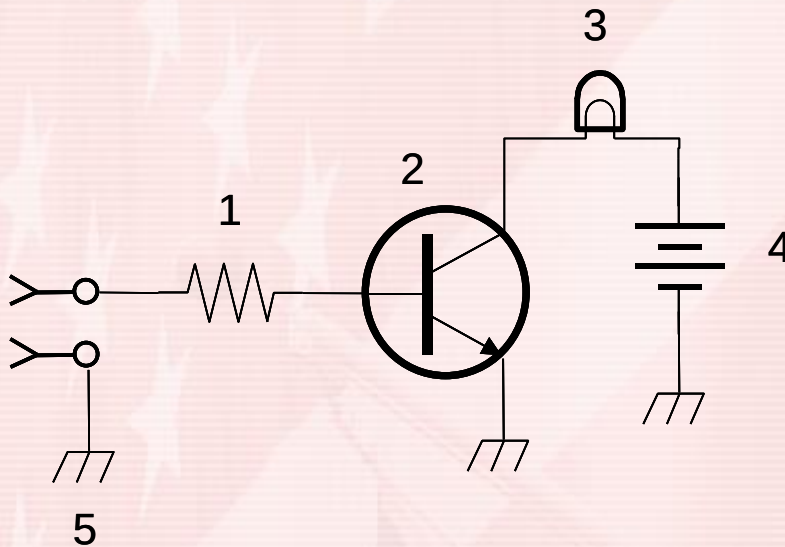


Figure T1

- Component #4 in Figure T1 is a Battery. T6C05

T 6 C

- Component #6 in Figure T2 is a capacitor. T6C06

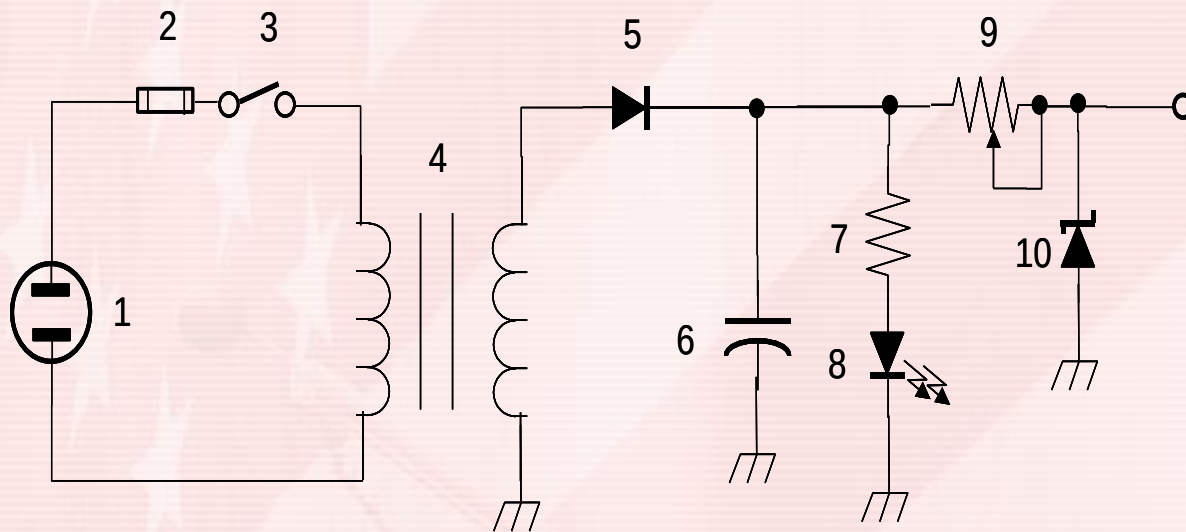


Figure T2

- Component #8 in Figure T2 is a light emitting diode. T6C07
- Component #9 in Figure T2 is a variable resistor. T6C08

T 6 C

- Component #4 in Figure T2 is a transformer. T6C09

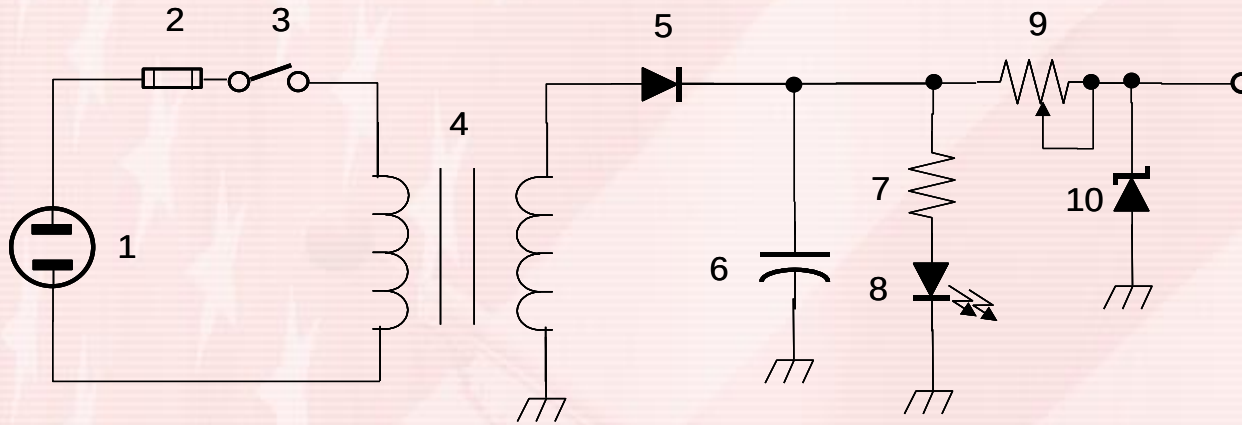


Figure T2

T 6 C

- The component #3 in figure T3 is a variable inductor. T6C10

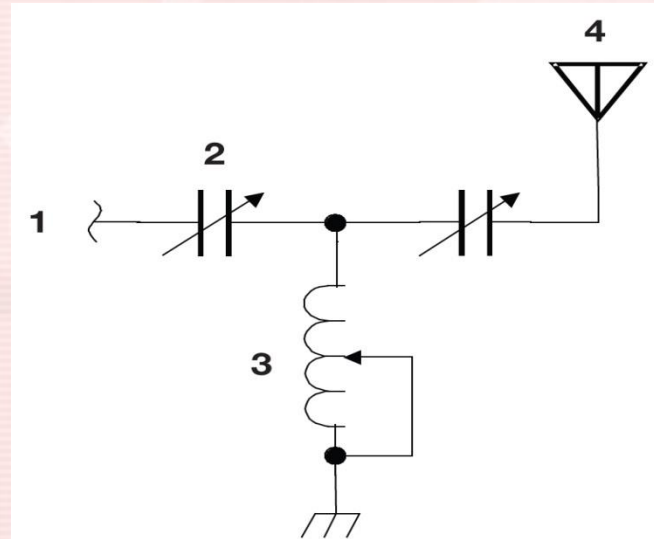


Figure T3

- The component #4 in figure T3 is an antenna. T6C11

T 6 C

- The symbols on an electrical circuit schematic diagram represent electrical components. T6C12
- The way components are interconnected is accurately represented in electrical circuit schematic diagrams. T6C13

T 6 D

Topics

- Component functions:
 - rectification;
 - switches;
 - indicators;
 - power supply components;
 - resonant circuit;
 - shielding;
 - power transformers;
 - integrated circuits

T 6 D

- The device or circuit that changes an alternating current in to a varying direct current signal is the rectifier. T6D01
- A switch controlled by an electromagnet is a relay. T6D02
- Component #3 in Figure T2 is a single-pole, single-throw switch. T6D03


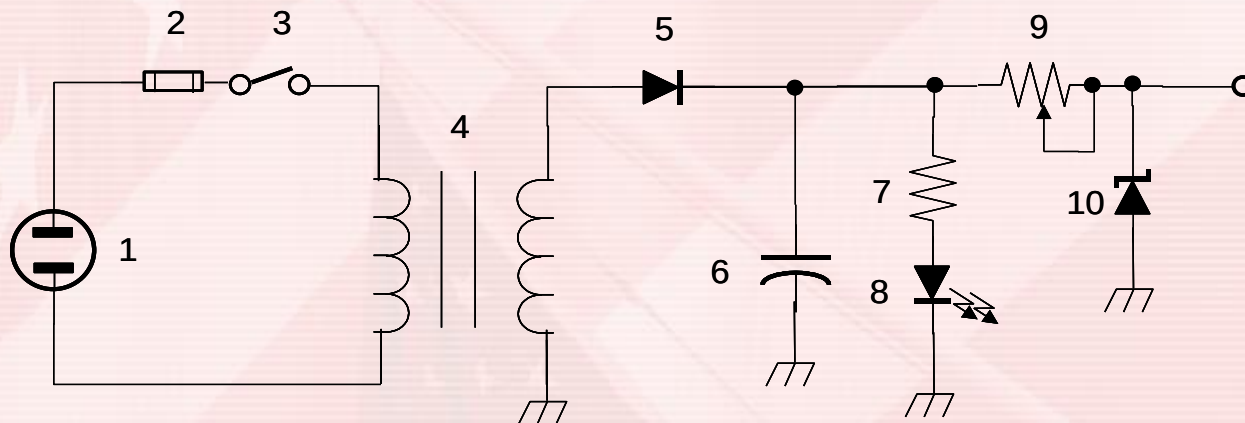
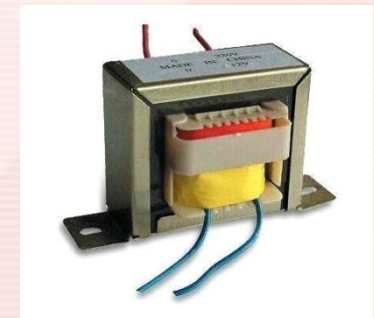


Figure T2

T 6 D

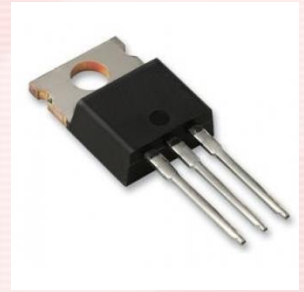- A meter can be used to display signal strength on a numeric scale. T6D
- A regulator is a type of circuit that controls the amount of voltage from a power supply. T6D05
- The component commonly used to change 120V AC house current to a lower AC voltage for other uses is a transformer. T6D06




T 6 D


- A device commonly used as a visual indicator is an LED. T6D07
- A capacitor is used together with an inductor to make a tuned circuit. T6D08

T 6 D

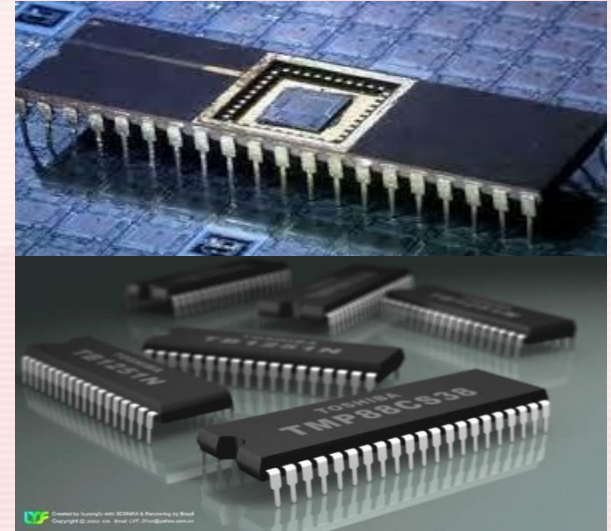- The device that combines several semiconductors and other components into one package is an integrated circuit. T6D09




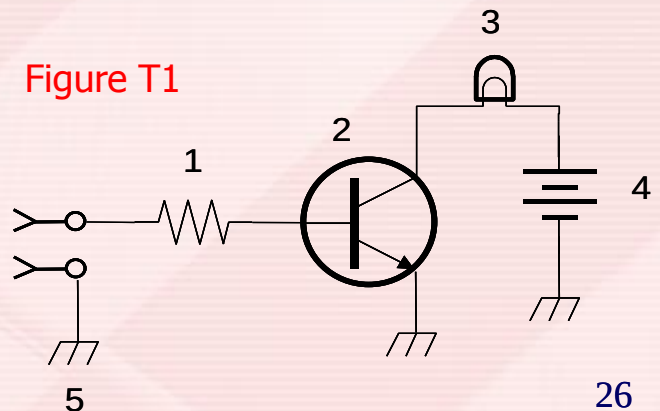- The function of component #2 in Figure T1 is to control the flow of current. T6D10



T 6 D

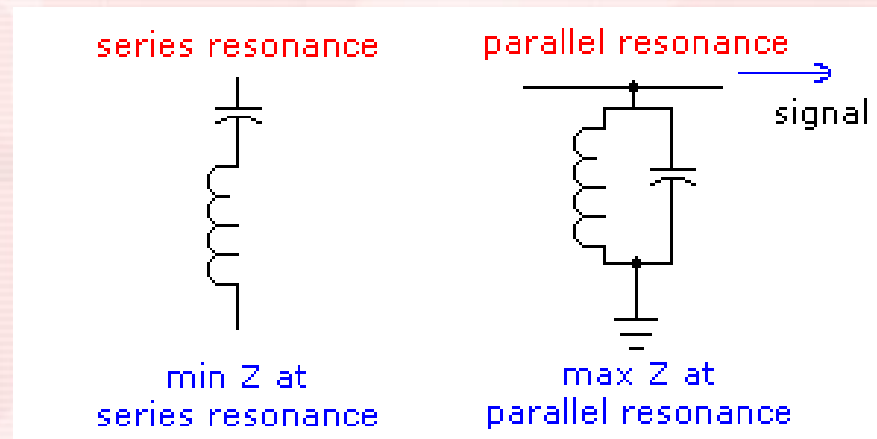- A simple resonant or tuned circuit consists of an inductor and a capacitor connected in series or parallel to form a filter. T6D11



- A common reason to use shielded wire is to prevent coupling of unwanted signals to or from the wire. T6D12

Element 2 Technician Class Question Pool

T 6 A - T 6 D

T6A01

What electrical component opposes the flow of current in a DC circuit?

- A. Inductor
- B. Resistor
- C. Voltmeter
- D. Transformer

What type of component is often used as an adjustable volume control?

- A. Fixed resistor
- B. Power resistor
- C. Potentiometer
- D. Transformer

T6A03

What electrical parameter is controlled by a potentiometer?

- A. Inductance
- B. Resistance
- C. Capacitance
- D. Field strength

T6A04

What electrical component stores energy in an electric field?

- A. Resistor
- B. Capacitor
- C. Inductor
- D. Diode

What type of electrical component consists of two or more conductive surfaces separated by an insulator?

- A. Resistor
- B. Potentiometer
- C. Oscillator
- D. Capacitor

T6A06

What type of electrical component stores energy in a magnetic field?

- A. Resistor
- B. Capacitor
- C. Inductor
- D. Diode

T6A07

What electrical component is usually composed of a coil of wire?

- A. Switch
- B. Capacitor
- C. Diode
- D. Inductor

What electrical component is used to connect or disconnect electrical circuits?

- A. Magnetron
- B. Switch
- C. Thermistor
- D. All of these choices are correct

What electrical component is used to protect other circuit components from current overloads?

- A. Fuse
- B. Capacitor
- C. Inductor
- D. All of these choices are correct

T6A10

Which of the following battery types is rechargeable?

- A. Nickel-metal hydride
- B. Lithium-ion
- C. Lead-acid gel-cell
- D. All of these choices are correct

T6A11

Which of the following battery types is not rechargeable?

- A. Nickel-cadmium
- B. Carbon-zinc
- C. Lead-acid
- D. Lithium-ion

What class of electronic components is capable of using a voltage or current signal to control current flow?

- A. Capacitors
- B. Inductors
- C. Resistors
- D. Transistors

What electronic component allows current to flow in only one direction?

- A. Resistor
- B. Fuse
- C. Diode
- D. Driven element

Which of these components can be used as an electronic switch or amplifier?

- A. Oscillator
- B. Potentiometer
- C. Transistor
- D. Voltmeter

T6B04

Which of the following components can consist of three layers of semiconductor material?

- A. Alternator
- B. Transistor
- C. Triode
- D. Pentagrid converter

Which of the following electronic components can amplify signals?

- A. Transistor
- B. Variable resistor
- C. Electrolytic capacitor
- D. Multi-cell battery

How is cathode lead of a semiconductor diode often marked on the package?

- A. With the word “cathode”
- B. With a stripe
- C. With the letter C
- D. With the letter K

T6B07

What does the abbreviation "LED" stand for?

- A. Low Emission Diode
- B. Light Emitting Diode
- C. Liquid Emission Detector
- D. Long Echo Delay

- A. Field Effect Transistor
- B. Fast Electron Transistor
- C. Free Electron Transition
- D. Field Emission Thickness

What are the names of the two electrodes of a diode?

- A. Plus and minus
- B. Source and drain
- C. Anode and cathode
- D. Gate and base

Which of the following could be the primary gain-producing component in an RF power amplifier?

- A. Transformer
- B. Transistor
- C. Reactor
- D. Resistor

T6B11

What is the term that describes a transistor's ability to amplify a signal?


- A. Gain
- B. Forward resistance
- C. Forward voltage drop
- D. On resistance

What is the name of an electrical wiring diagram that uses standard component symbols?

- A. Bill of materials
- B. Connector pinout
- C. Schematic
- D. Flow chart


T6C02 What is component 1 in figure T1?

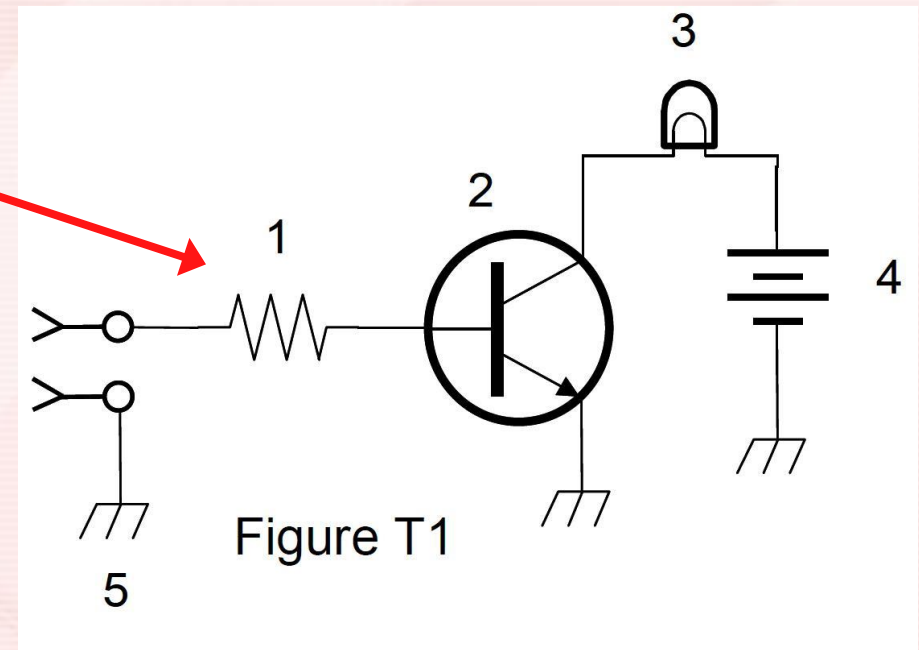- A. Resistor
- B. Transistor
- C. Battery
- D. connector




T6C03 What is component 2 in figure T1?

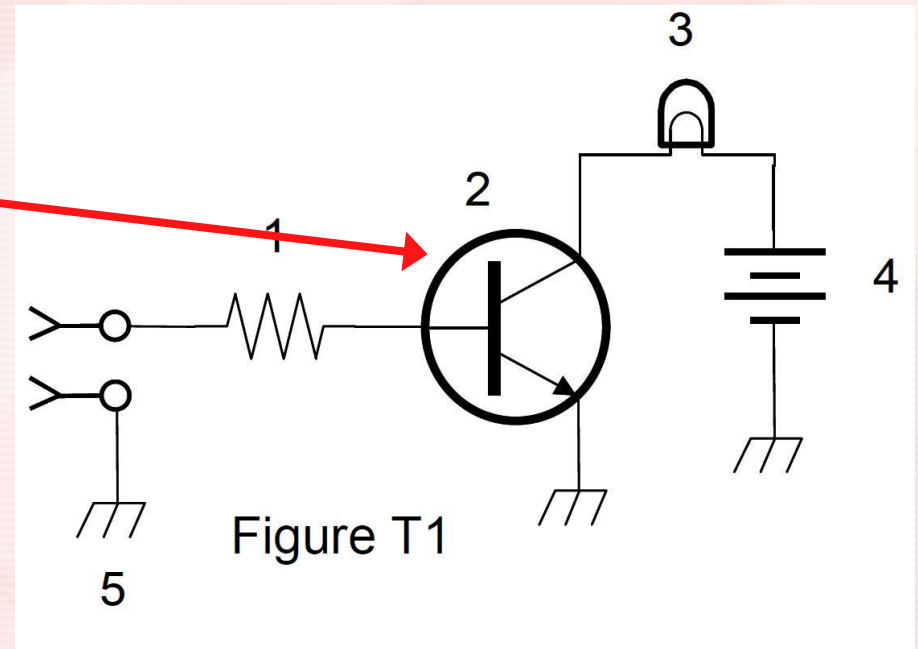- A. Resistor
- B. Transistor
- C. Indicator lamp
- D. Connector




T6C04 What is component 3 in figure T1?

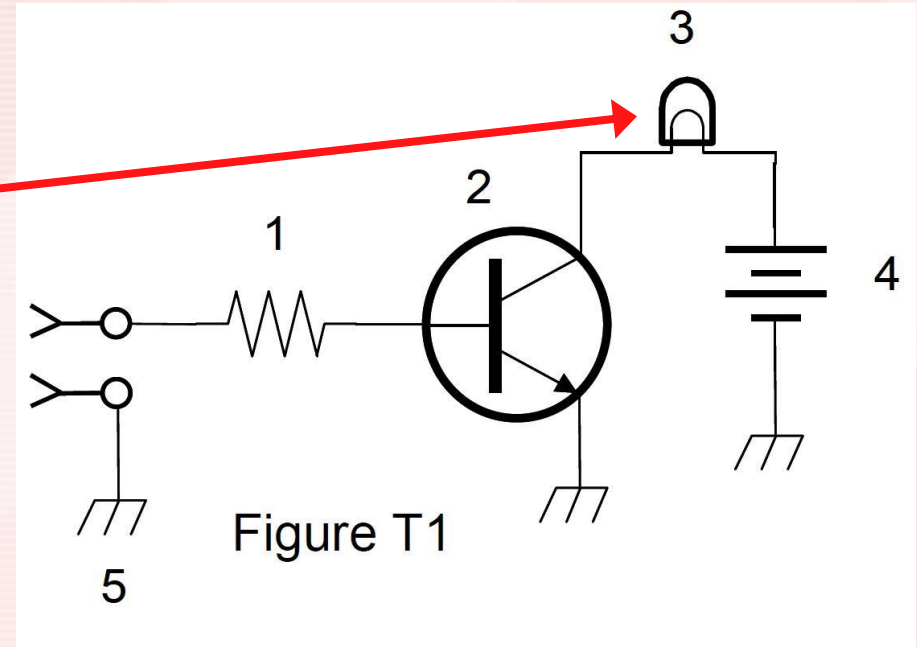- A. Resistor
- B. Transistor
- C. Lamp
- D. Ground symbol



T6C05 What is component 4 in figure T1?

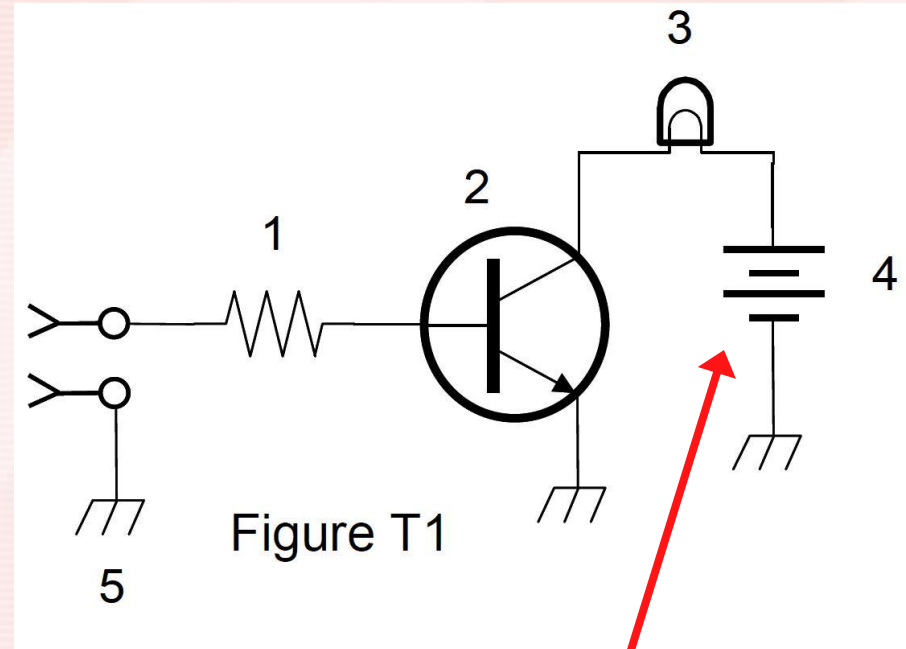- A. Resistor
- B. Transistor
- C. Battery
- D. Ground symbol



T6C06 What is component 6 in figure T2?

- A. Resistor
- B. Capacitor
- C. Regulator IC
- D. Transistor

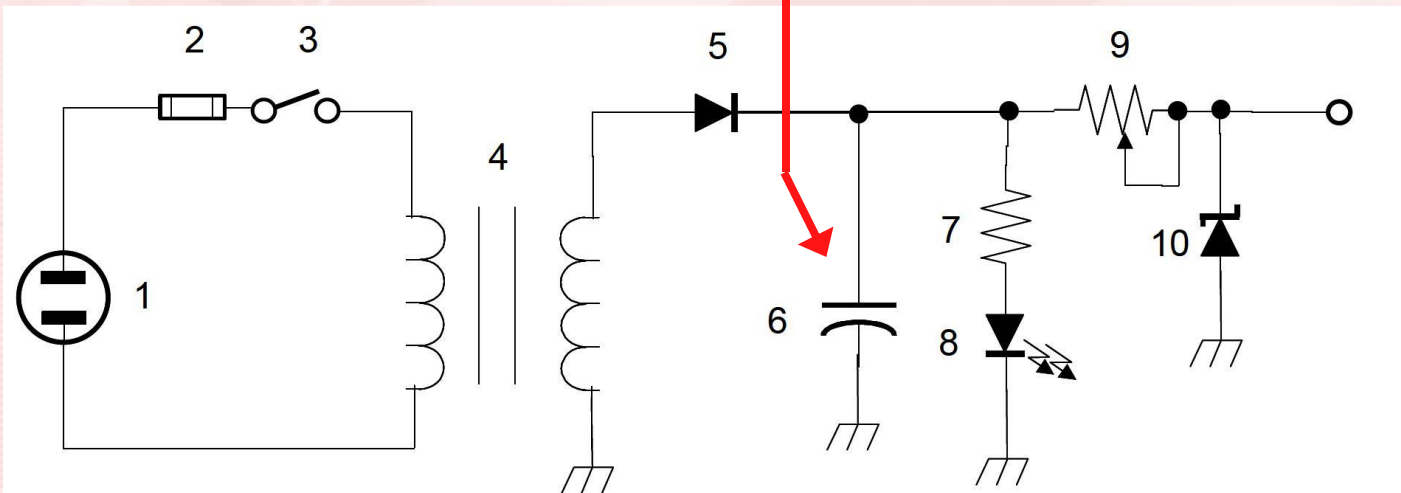


Figure T2

T6C07 What is component 8 in figure T2?

- A. Resistor
- B. Inductor
- C. Regulator IC
- D. Light emitting diode

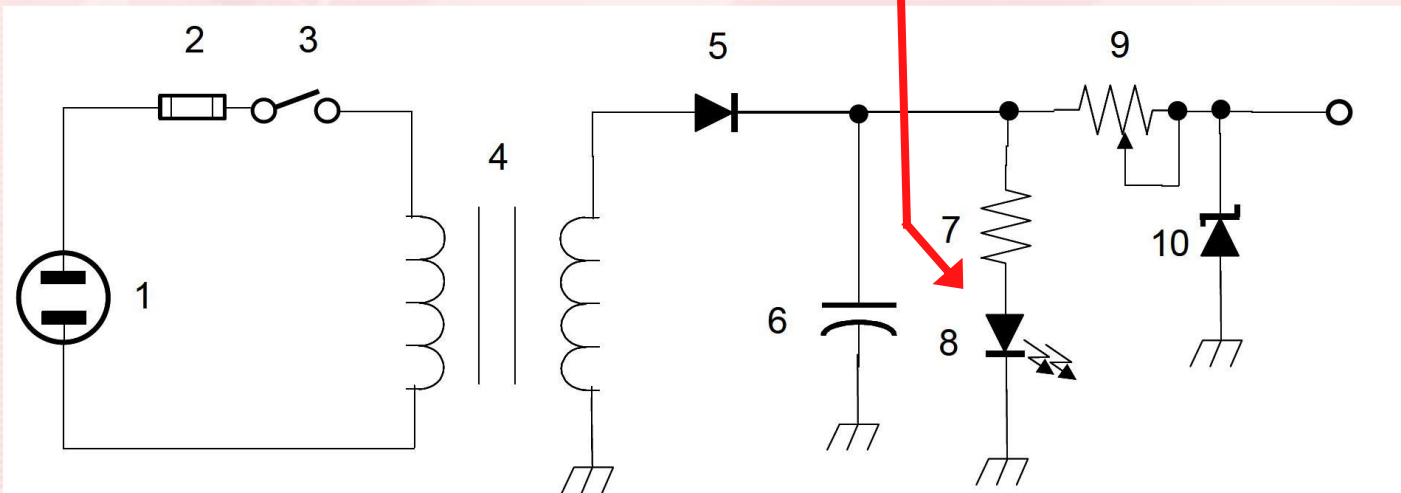


Figure T2

T6C08

What is component 9 in figure T2?

- ### A. Variable capacitor

- ## B. Variable inductor

- ### C. Variable resistor

- ### D. Variable transformer


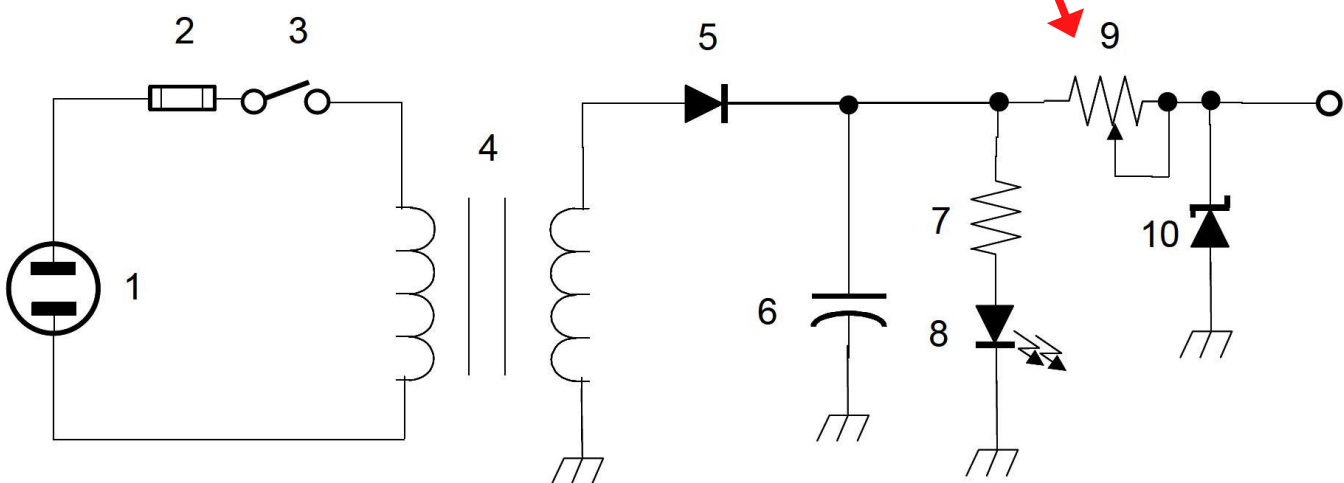


Figure T2


T6C09 What is component 4 in figure T2?

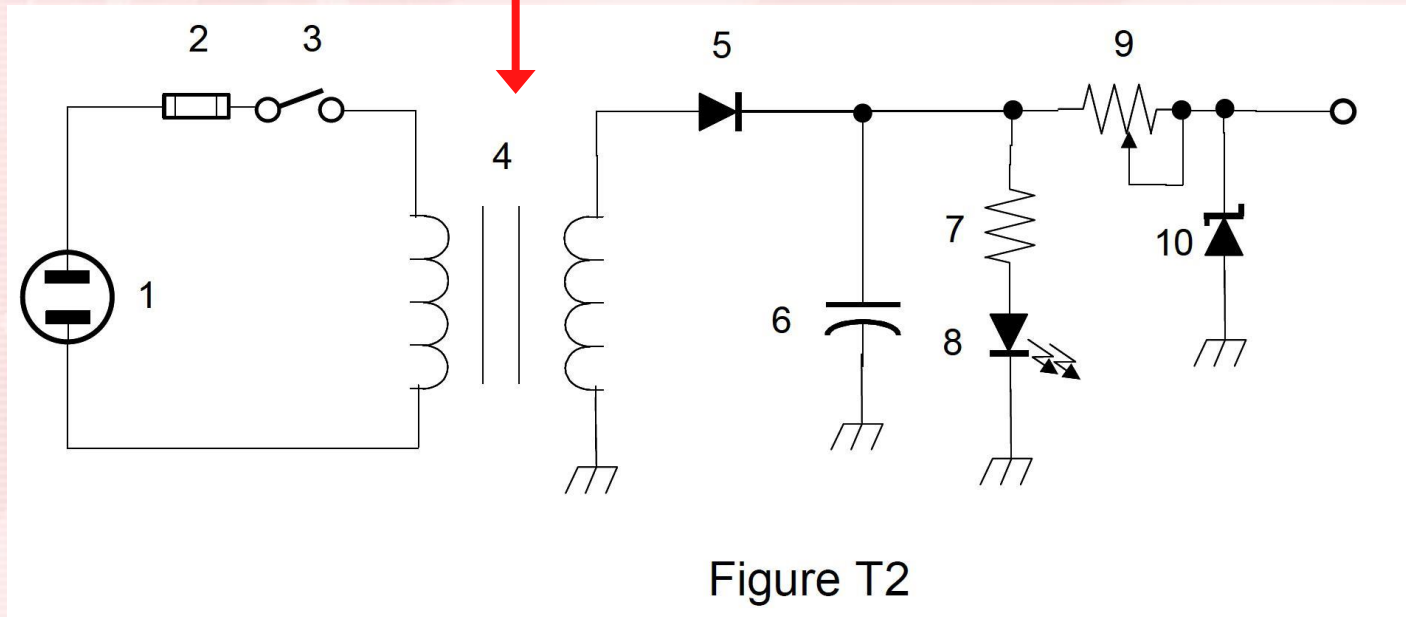- A. Variable inductor
- B. Double-pole switch
- C. Potentiometer
- D. Transformer



T6C10 What is component 3 in figure T3?

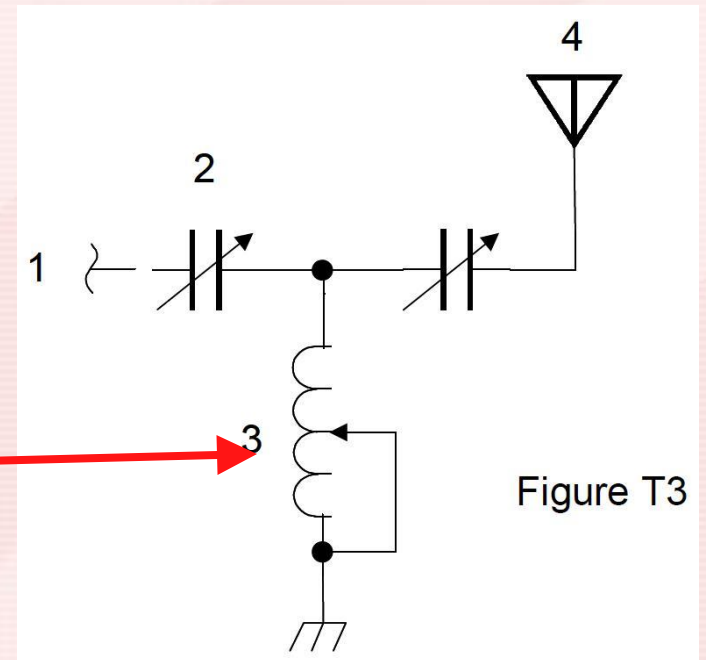- A. Connector
- B. Meter
- C. Variable capacitor
- D. Variable inductor



T6C11 What is component 4 in figure T3?

- A. Antenna
- B. Transmitter
- C. Dummy load
- D. Ground

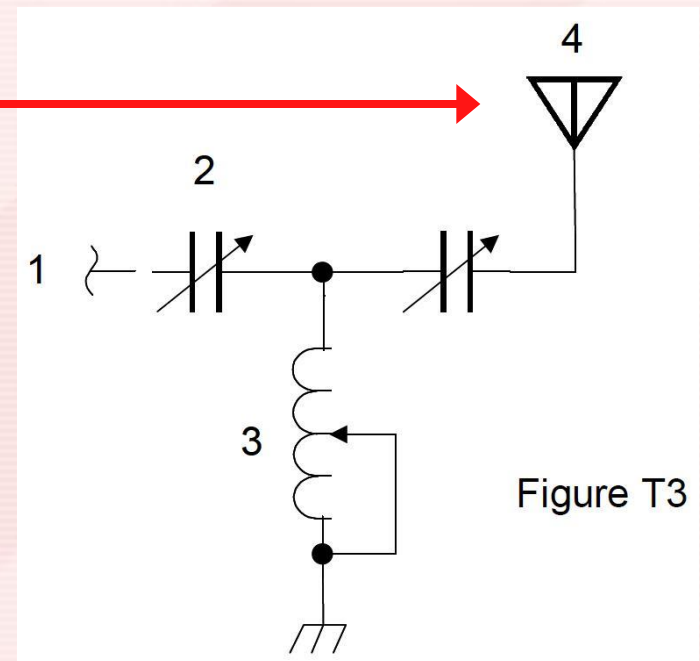


Figure T3

What do the symbols on an electrical circuit schematic represent?

- A. Electrical components
- B. Logic states
- C. Digital codes
- D. Traffic nodes

Which of the following is accurately represented in electrical circuit schematic diagrams?

- A. Wire lengths
- B. Physical appearance of components
- C. The way components are interconnected
- D. All of these choices

Which of the following devices or circuits changes an alternating current into a varying direct current signal?

- A. Transformer
- B. Rectifier
- C. Amplifier
- D. Reflector

T6D02 What is a relay?

- A. A switch controlled by an electromagnet
- B. A current controlled amplifier
- C. An optical sensor
- D. A pass transistor

What type of switch is represented by item 3 in figure T2?

- A. Single-pole single-throw
- B. Single-pole double-throw
- C. Double-pole single-throw
- D. Double-pole double-throw

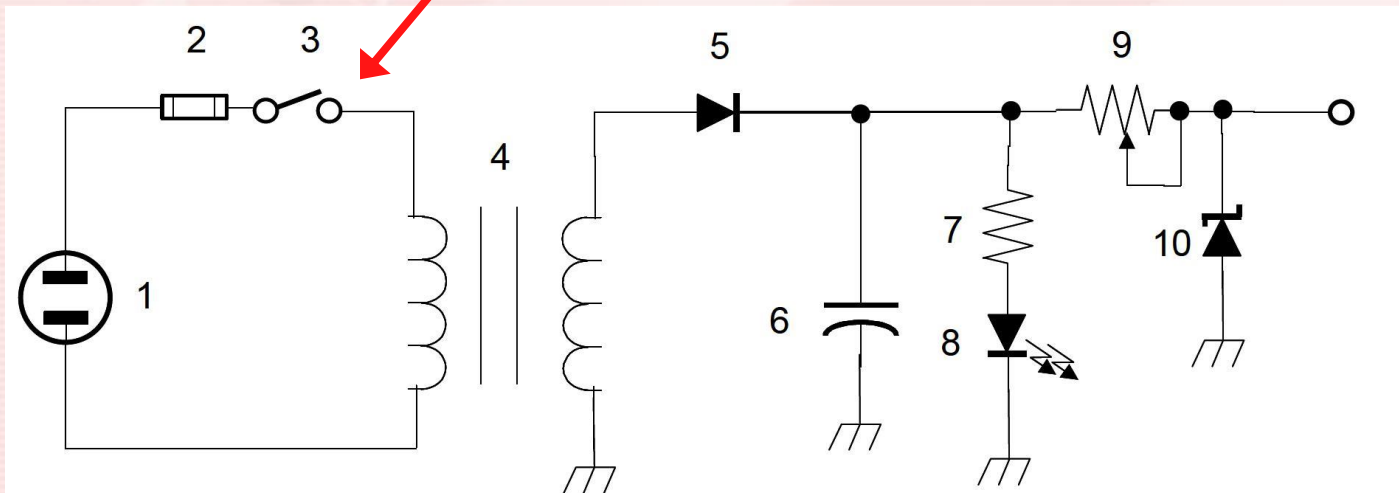


Figure T2

Which of the following displays an electrical quantity as a numeric value?

- A. Potentiometer
- B. Transistor
- C. Meter
- D. Relay

T6D05

What type of circuit controls the amount of voltage from a power supply?

- A. Regulator
- B. Oscillator
- C. Filter
- D. Phase inverter

What component is commonly used to change 120V AC house current to a lower AC voltage for other uses?

- A. Variable capacitor
- B. Transformer
- C. Transistor
- D. Diode

T6D07

Which of the following is commonly used as a visual indicator?

- A. LED
- B. FET
- C. Zener diode
- D. Bipolar transistor

T6D08

Which of the following is combined with an inductor to make a tuned circuit?


- A. Resistor
- B. Zener diode
- C. Potentiometer
- D. Capacitor

What is the name of a device that combines several semiconductors and other components into one package?

- A. Transducer
- B. Multi-pole relay
- C. Integrated circuit
- D. Transformer

T6D10 What is the function of component 2 in Figure T1?

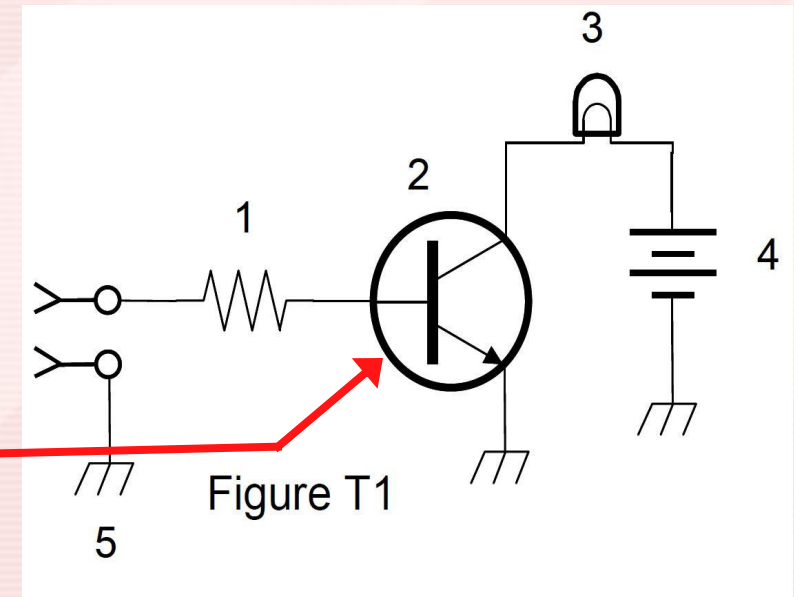- A. Give off light when current flows through it
- B. Supply electrical energy
- C. Control the flow of current
- D. Convert electrical energy into radio waves



What of the following is a resonant or tuned circuit?

- A. An inductor and a capacitor connected in series or parallel to form a filter
- B. A type of voltage regulator
- C. A resistor circuit used for reducing standing wave ratio
- D. A circuit designed to provide high fidelity audio

T6D12 Which of the following is a common reason to use shielded wire?

- A. To decrease the resistance of DC power connections
- B. To increase the current carrying capability of the wire
- C. To prevent coupling of unwanted signals to or from the wire
- D. To couple the wire to other signals