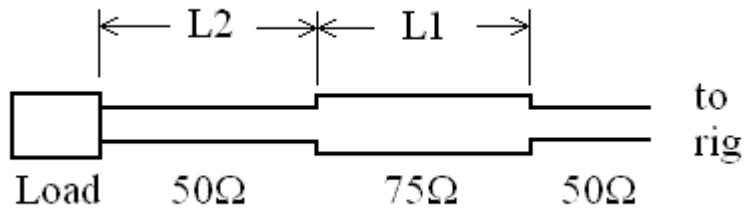


A Matching Technique Using 50 & 75 Ohm Cables


Steve Kavanagh, VE3SMA

June 19, 2010

The following shows how to use sections of 50 and 75 ohm cables in series to match resistive loads of less than 50 ohms to a 50 ohm transmission line. This can be useful particularly for feeding vertical and Yagi antennas. The general configuration is shown in the following figure.



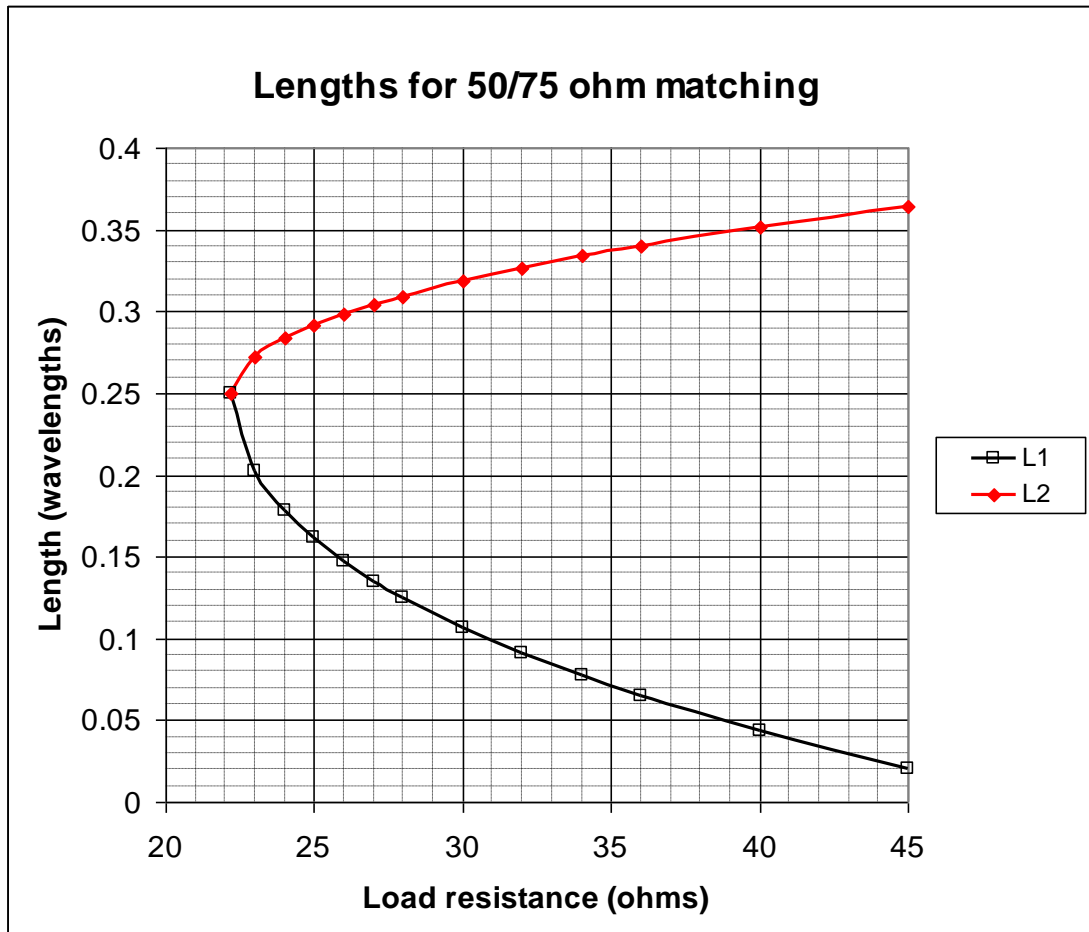A section of 75 ohm line is inserted in the 50 ohm line to the antenna. For load impedance between 22.2 and 45 ohms the required lengths to give a perfect match are given by the following curves. A perfect match is not possible for loads under 22.2 ohms.



For example let's say we want to match a Yagi which has an input impedance of 25 ohms (with no reactance) at 50.150 MHz, using sections of RG-58C/U (50 ohms) and RG-59B/U (75 ohms). From the chart the lengths needed are

$$L1 = 0.161 \lambda$$
$$L2 = 0.291 \lambda .$$

Since the wavelength at this frequency is 5.98 m and both of these cables have velocity factors of 66%, the actual cable lengths required will be

$$L1 = 63.5 \text{ cm (25.0 inches)}$$
$$L2 = 114.8 \text{ cm (45.2 inches)}.$$

If it is desired to use a balun at the load, a portion of the cable, including the matching sections L1 and L2, may be coiled up to create a choke, or ferrite beads can be slipped over the load end of L2 to create a W2DU-type balun.