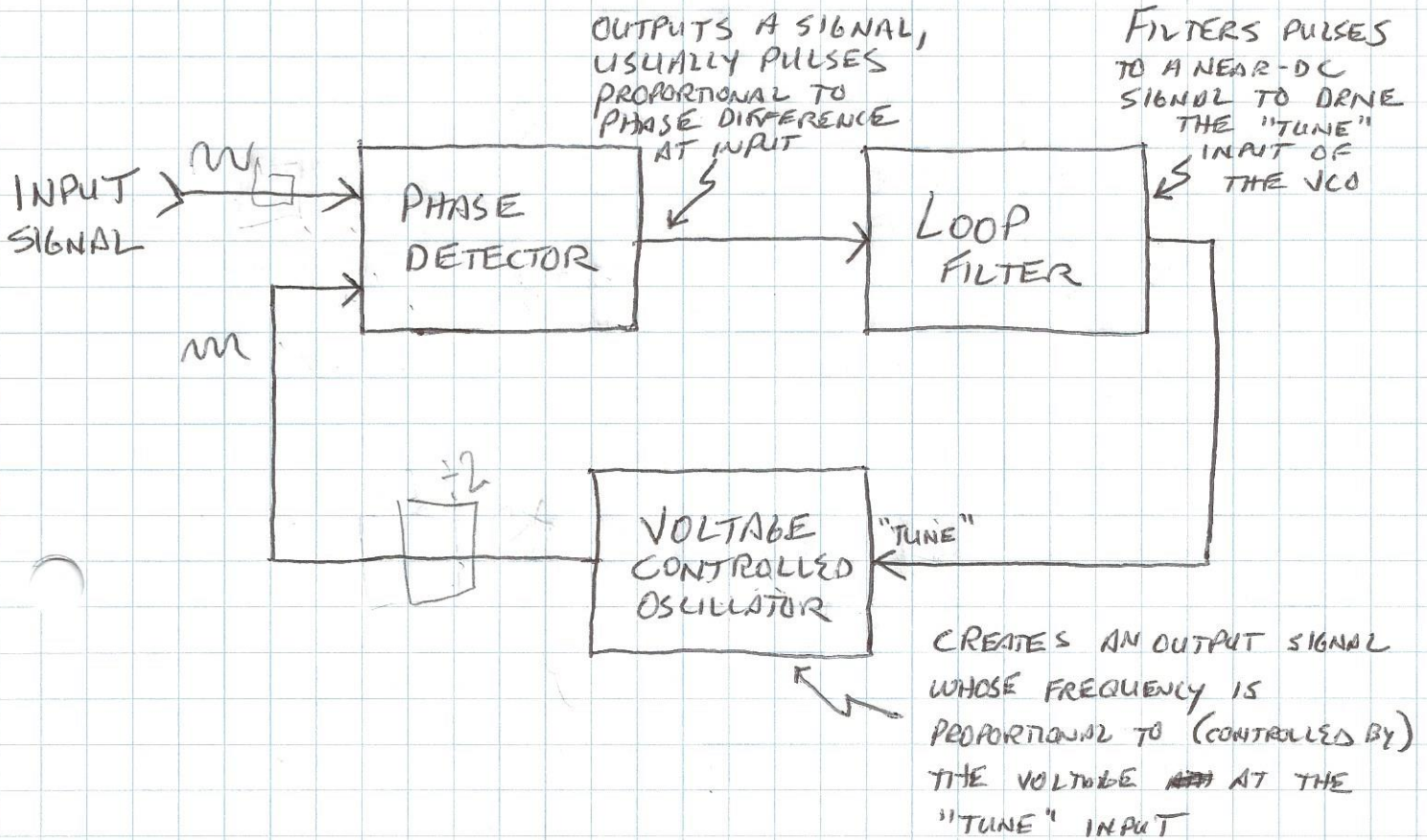


WZAEW

PHASE LOCKED LOOPS





APPLICATIONS INCLUDE:

- DEMODULATION + MODULATION
- FM DISCRIMINATION
- FREQUENCY SYNTHESIS
- TUNING CONTROL
- TONE DECODING
- CLOCK RECOVERY

WZAEW

VOLTAGE CONTROLLED OSCILLATOR: VCO


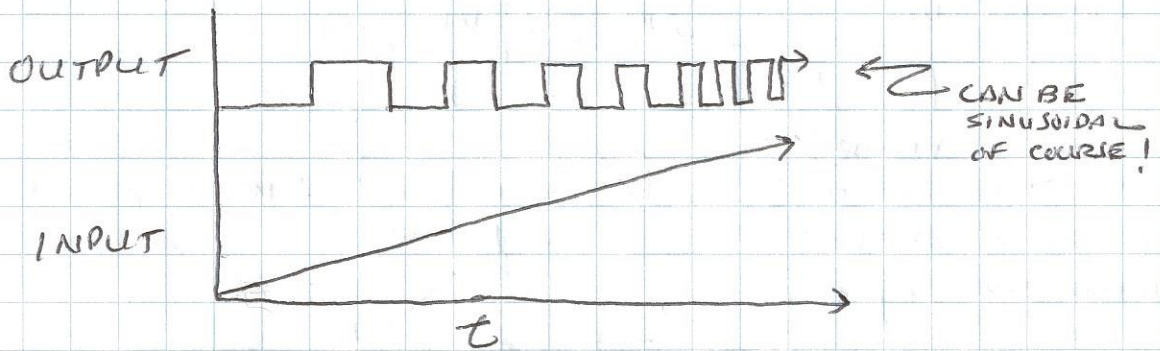
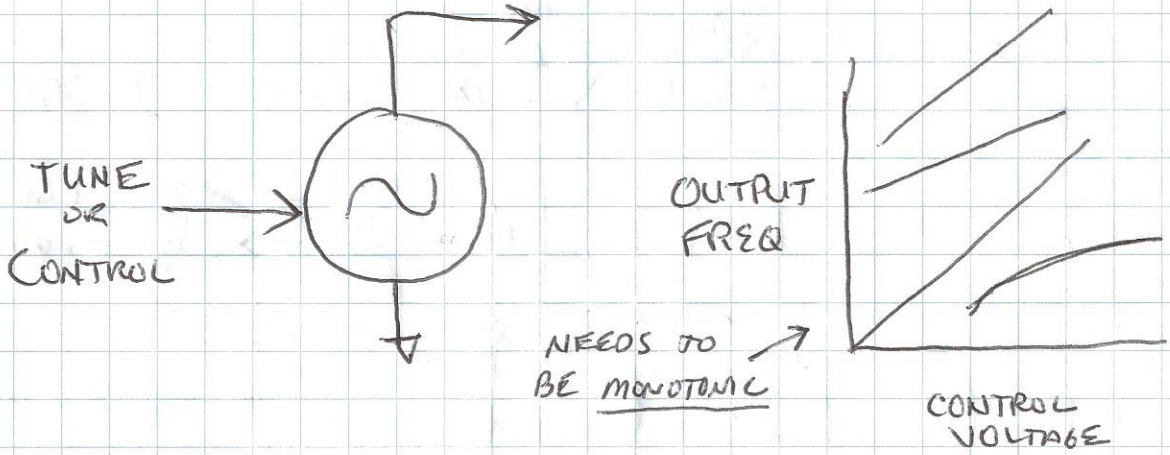


W2AEW

PHASE DETECTOR

TYPE I: SIMPLE XOR / MIXER

DIGITAL APPS
RF APPS

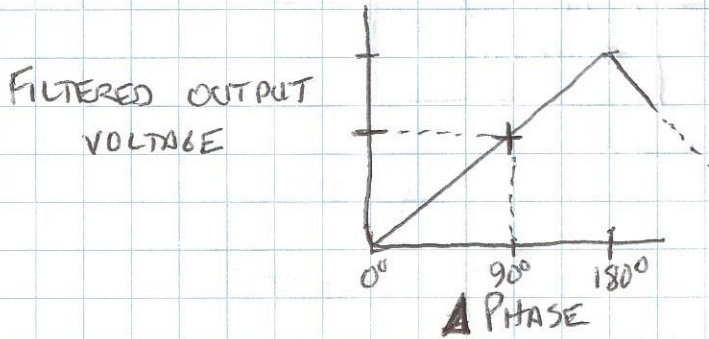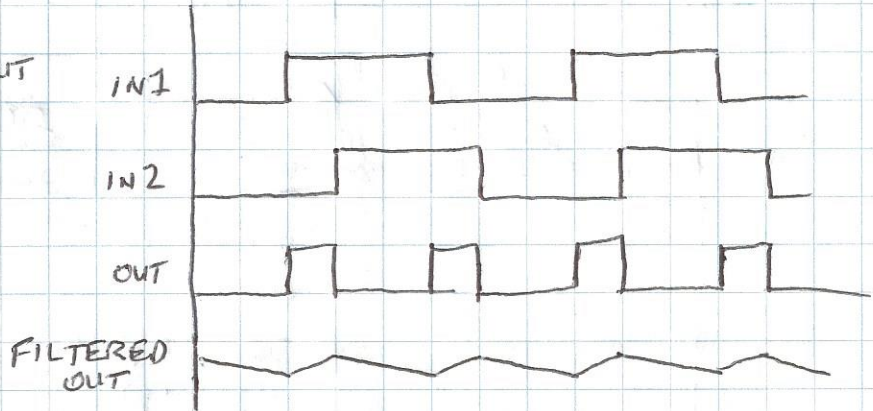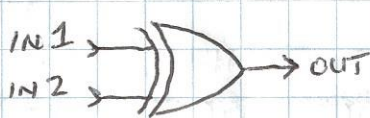

USUALLY DESIGNED
SO MID-POINT (90°)
VOLTAGE IS DESIRED
TUNE VOLTAGE WHEN
LOCKED

GOOD

- GOOD WITH NOISY INPUTS
- SIMPLE



BAD

- CAN LOCK ON A HARMONIC
- PHASE AT LOCK CAN BE $0-180^\circ$
- INPUTS SHOULD BE 50% DUTY CYCLE
- NO REAL FREQUENCY DETECTION

WZAEW

PHASE DETECTOR

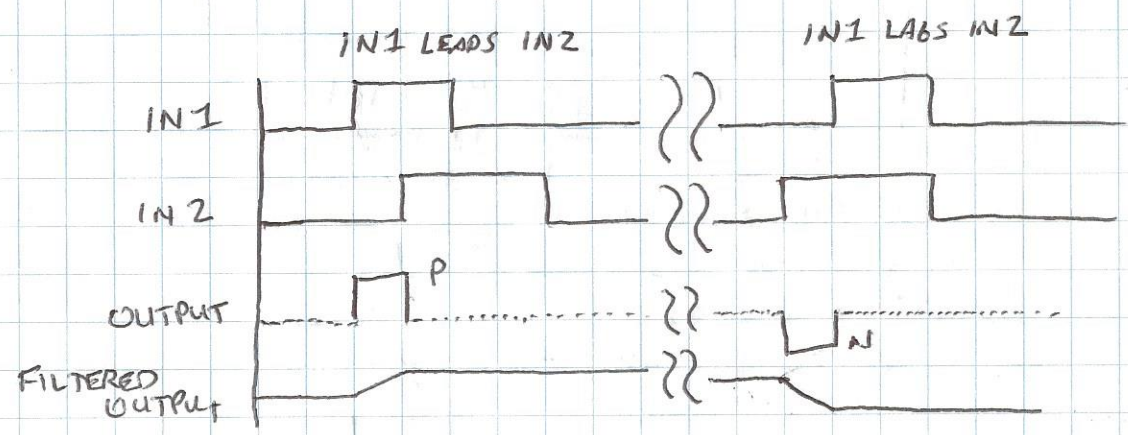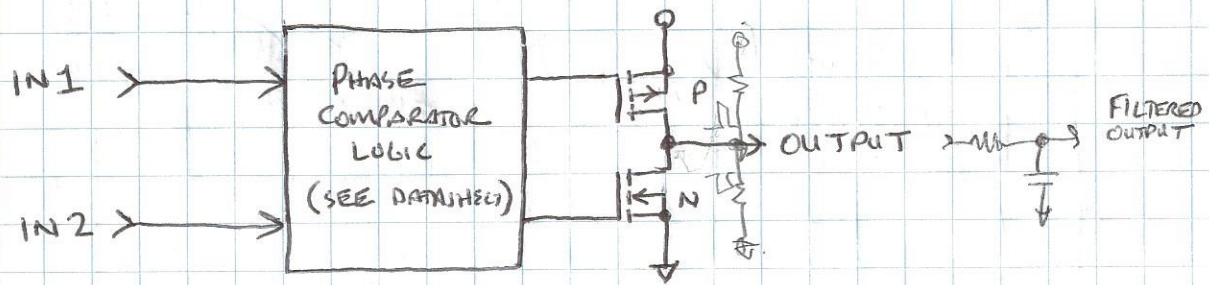TYPE II : ALSO CALLED PHASE FREQUENCY DETECTOR



GOOD

- GOOD FREQUENCY DETECTOR
- WON'T LOCK ON HARMONIC
- SIGNALS DON'T HAVE TO BE 50% D/C
- LOCKS A (NEAR) 0° PHASE

BAD

- MORE COMPLEX
- NOT AS GOOD WITH NOISY INPUTS