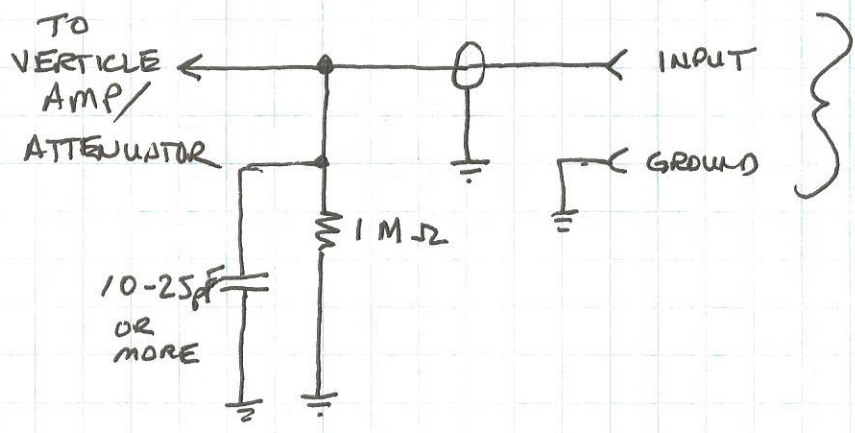


OSCILLOSCOPE INPUT



HOW DO WE CONNECT THIS TO THE CIRCUIT?


OSCILLOSCOPE INPUT

TO
VERTICAL
AMP/
ATTENUATOR

10-25pF
OR
MORE

1 MΩ

WHY NOT SIMPLY USE WIRES?

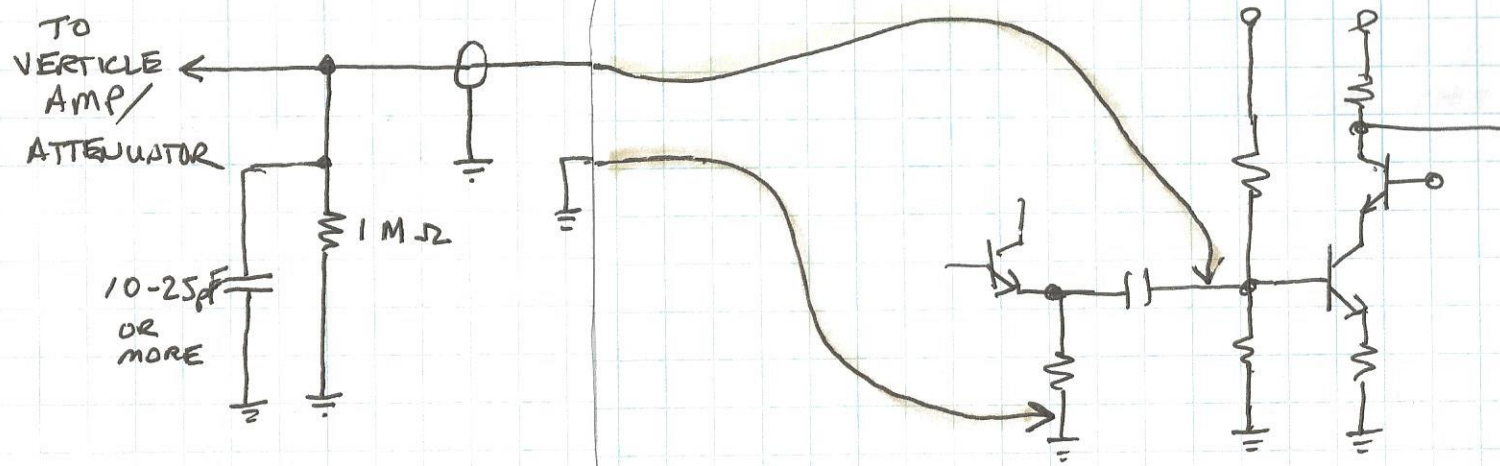

- LOTS OF STRAY INDUCTANCE


→ - WIRES ARE ANTENNAS, WILL
PICK UP ALL SORTS OF NOISE

- WIRES WILL COUPLE TO OTHER PARTS
OF THE CIRCUIT

- OK FOR LOW FREQUENCY, LARGE SIGNALS


OSCILLOSCOPE INPUT

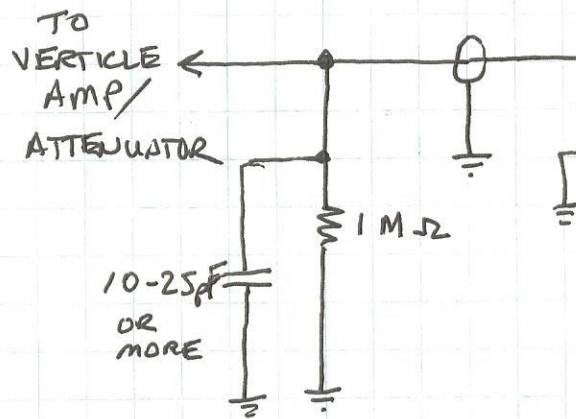REPLACING THE WIRES WITH COAXIAL CABLE
SOLVES SOME OF THE PROBLEMS



THIS IS YOUR BASIC
1X PROBE DESIGN!

OK TO A FEW MHz
DEPENDING ON CIRCUIT

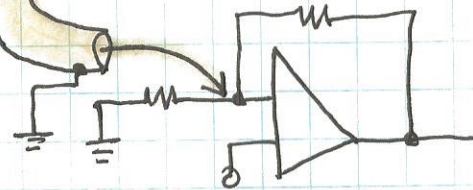

THE GOOD:

- MINIMIZES STRAY SIGNAL PICKUP
- MINIMIZES COUPLING TO OTHER PARTS OF CIRCUIT


THE BAD:

- ADDS TO CAPACITIVE LOADING
COAX IS TYPICALLY $\approx 30\text{pF}$ PER FOOT!


2.5' OF COAX + SCOPE INPUT CAPACITANCE
CAN EASILY BE 100pF!

100pF IS $\approx 50\Omega$ @ 30MHz!

OSCILLOSCOPE INPUT

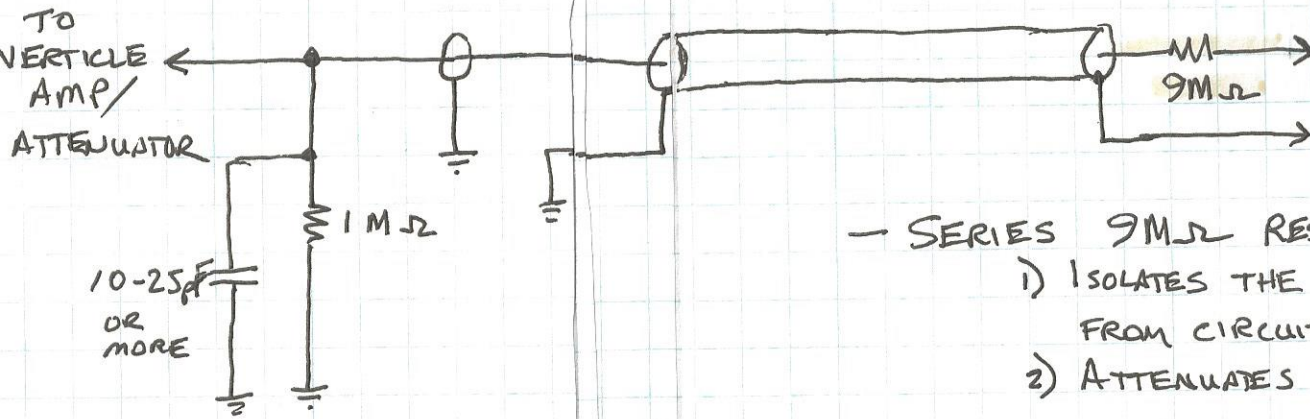

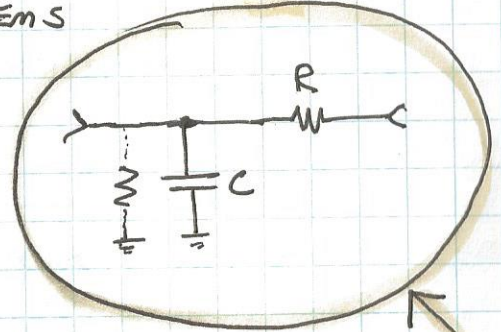10X PROBE SOLVES SOME OF THE
LOADING & CAPACITANCE PROBLEMS




- SERIES 9MΩ RESISTOR DOES 2 THINGS
 - 1) ISOLATES THE COAX + SCOPE CAPACITANCE FROM CIRCUIT
 - 2) ATTENUATES THE SIGNAL BY 10X

... BUT ...

- THE 9MΩ RESISTOR & THE COAX + SCOPE CAPACITANCE FORM A RC LOW PASS FILTER!
- THE 10X ATTENUATION GETS WORSE AS FREQUENCY INCREASES

→ THERE IS A SIMPLE FIX FOR THIS!

OSCILLOSCOPE INPUT

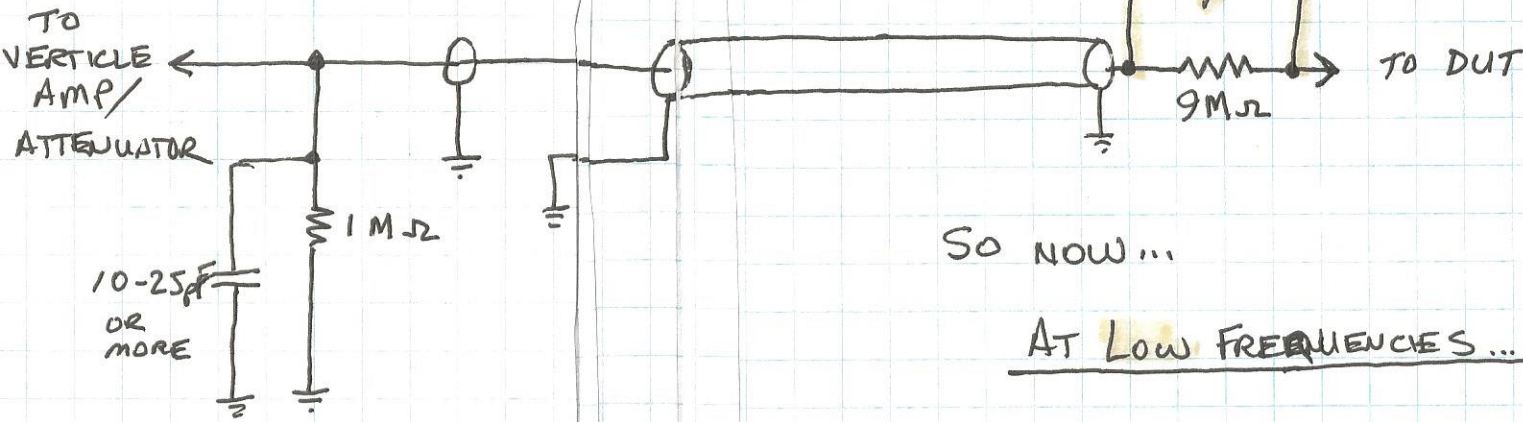

A TRIMMER CAPACITOR IS ADDED TO THE PROBE TO COMPENSATE THE FREQUENCY RESPONSE

THE COMPENSATION CAPACITOR IS VARIABLE TO ACCOUNT FOR DIFFERENT SCOPE INPUT CAPACITANCES!


SO NOW...

AT LOW FREQUENCIES...



... THE RESISTORS FORM THE 10X ATTENUATION

AT HIGH FREQUENCIES...

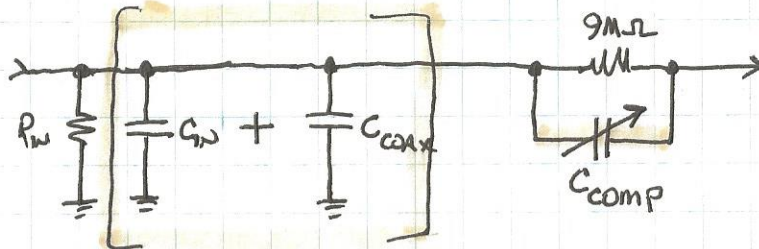

... THE COMPENSATION CAP AND COAX/SCOPE CAP FORM THE 10X ATTENUATION