
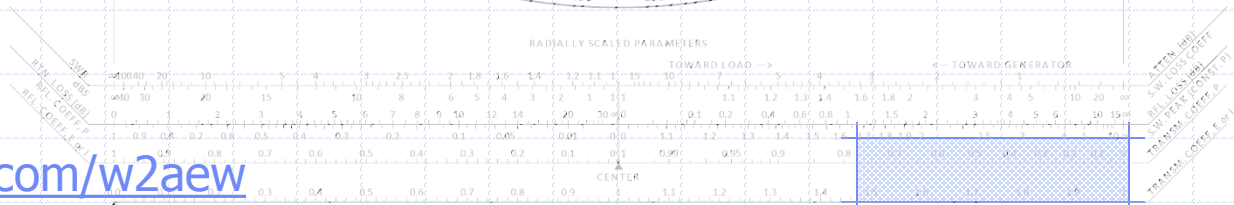


# Basics of Smith Charts


Alan Wolke – W2AEW

ARRL NNJ Technical Coordinator

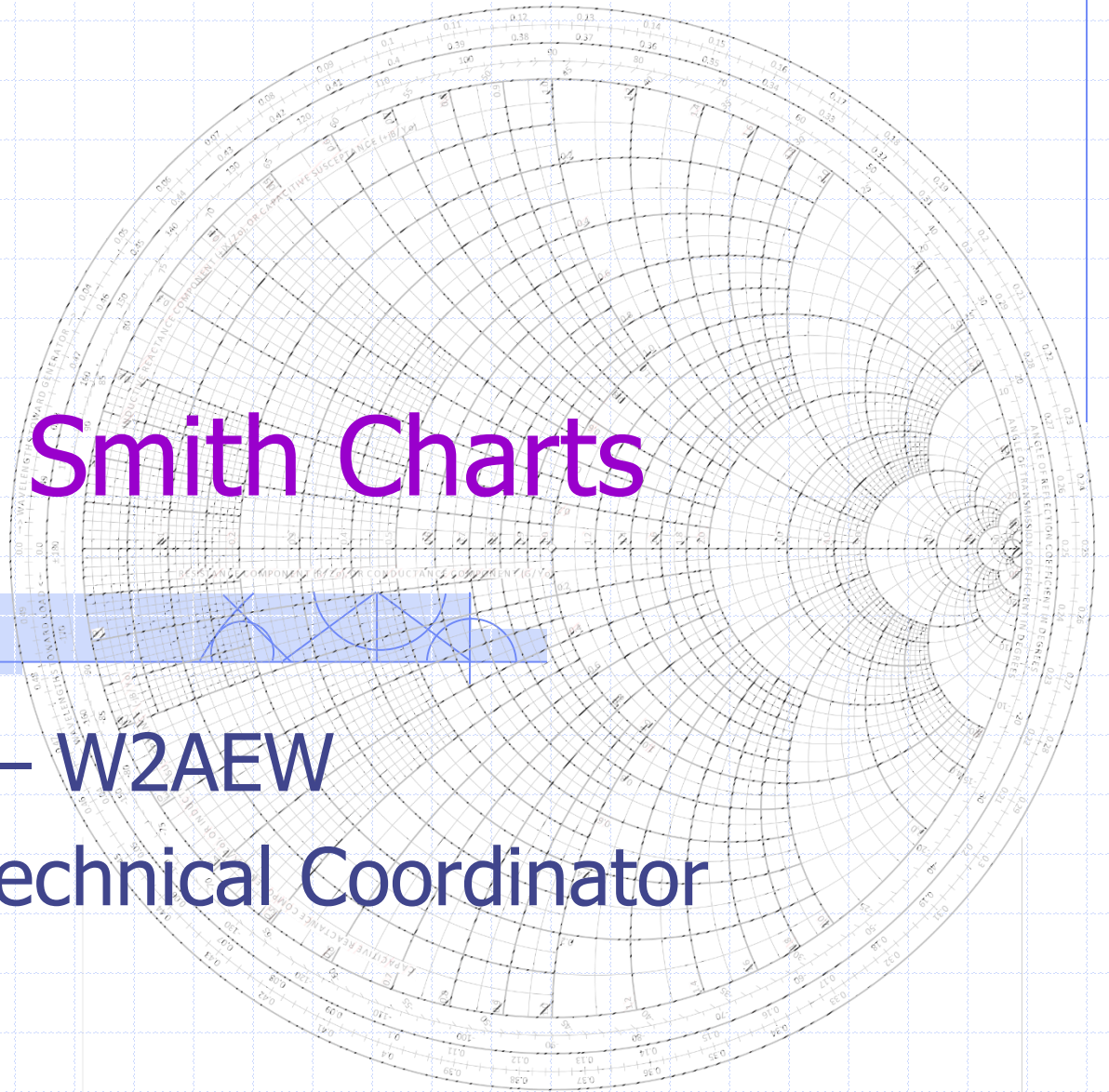
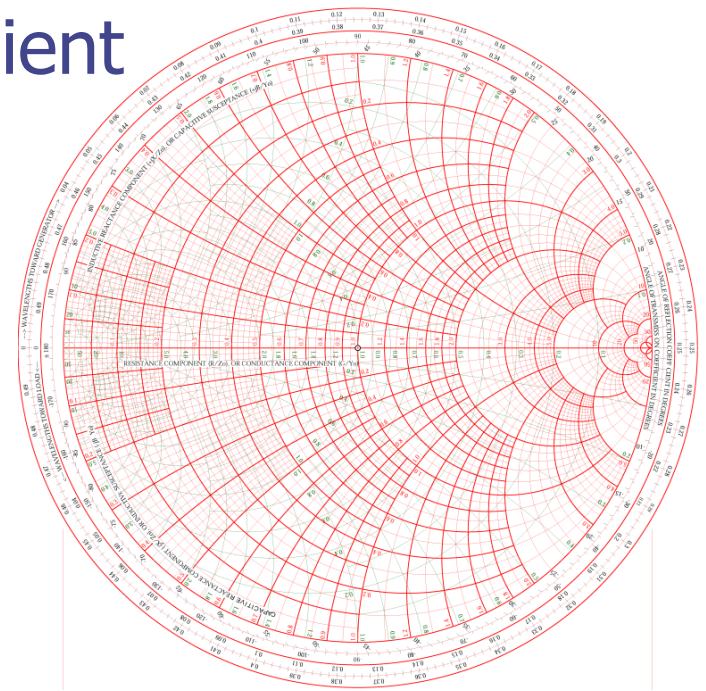
# What is a Smith Chart

- A graphical tool to plot and compute:
  - Complex impedance
  - Complex reflection coefficient
  - VSWR
  - Transmission line effects
  - Matching networks
  - ...and more
- Let's break it down....



# Normalized Impedance

- Normalized  $Z = \text{Actual } Z / \text{System } Z_0$ 
  - For  $Z_0 = 50\Omega$ , divide values by 50
- Example:

- $Z = 37 + j55$

- $Z' = \frac{37}{50} + j \frac{55}{50}$

- $Z' = 0.74 + j1.10$

*This is what we plot on the chart*

- **Makes it usable for any system  $Z_0$**

# Z Regions on the Smith Chart


$$R + jX$$

**+j Inductive**

Purely Resistive  
 $jX = 0$

$$R - jX$$

**-j Capacitive**

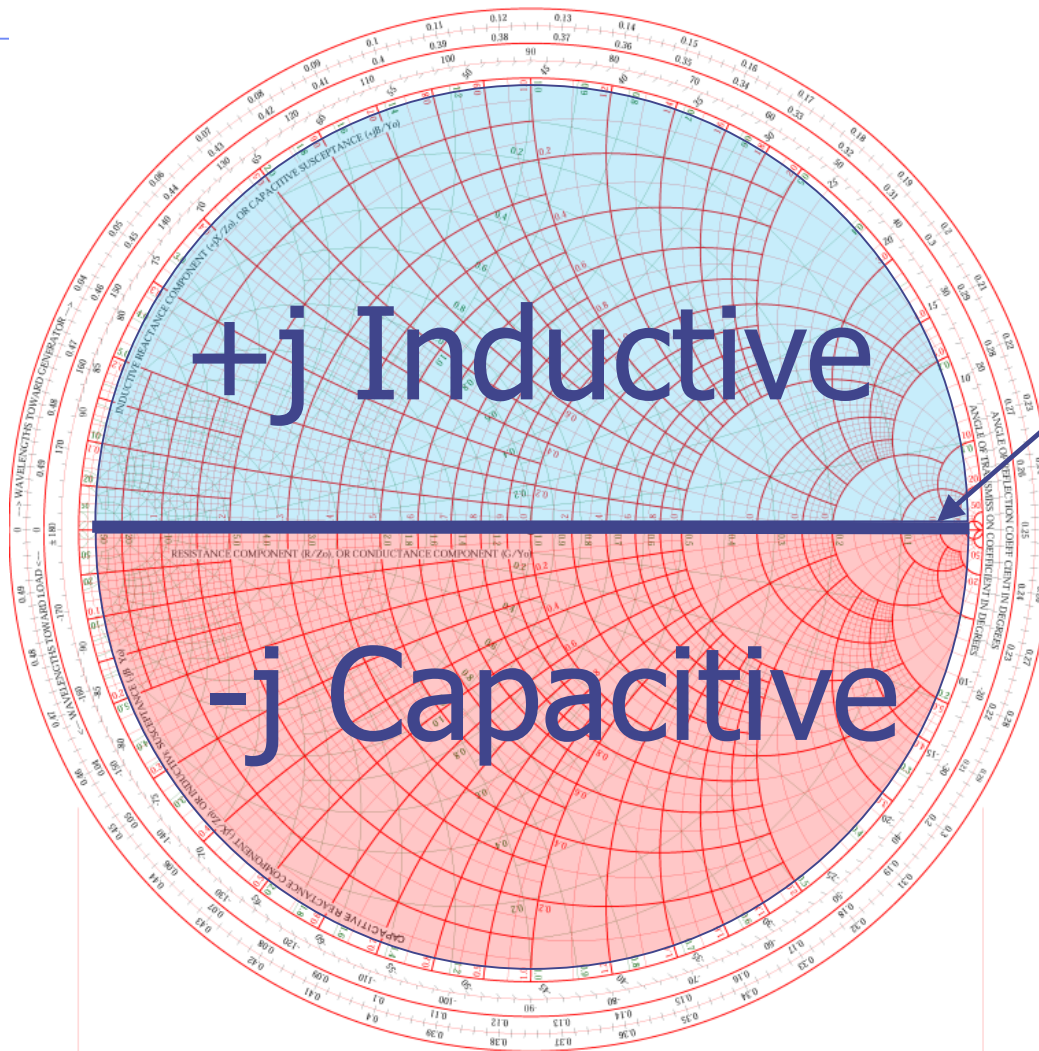




# Key Values on the chart


Short  
Circuit

$Z_0$   
(system impedance)


Open  
Circuit

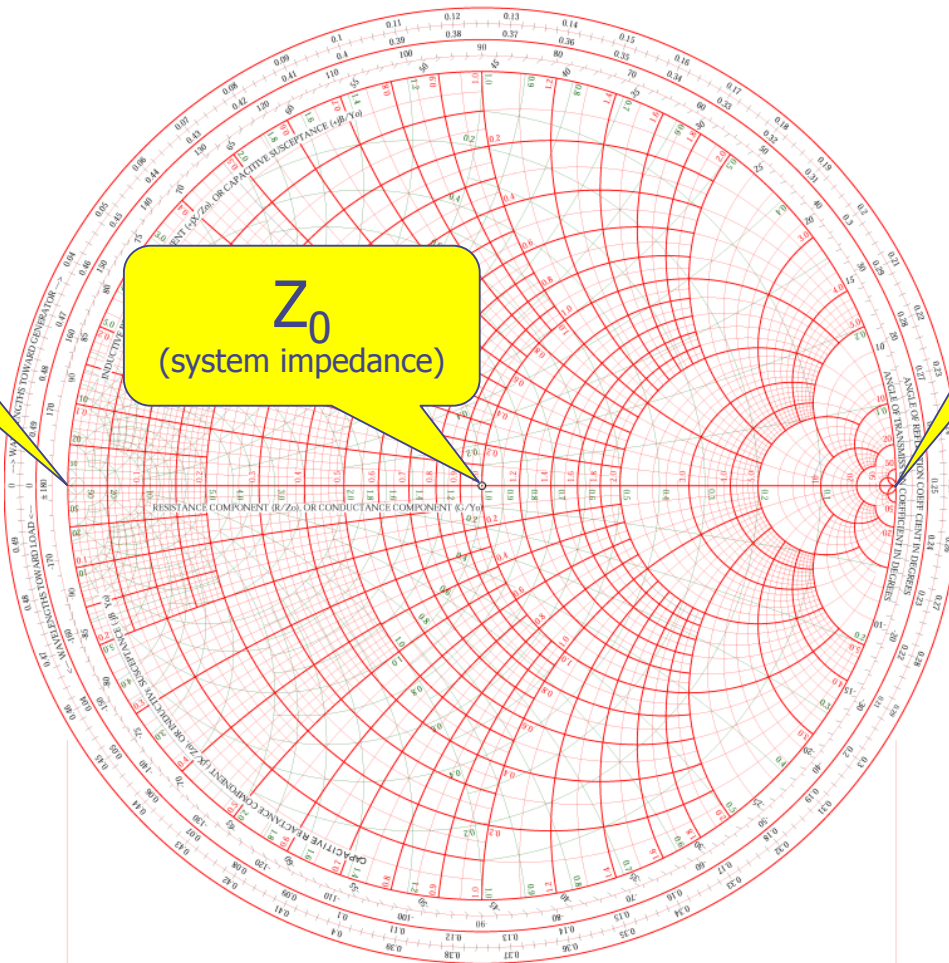

# Constant Resistance Circles

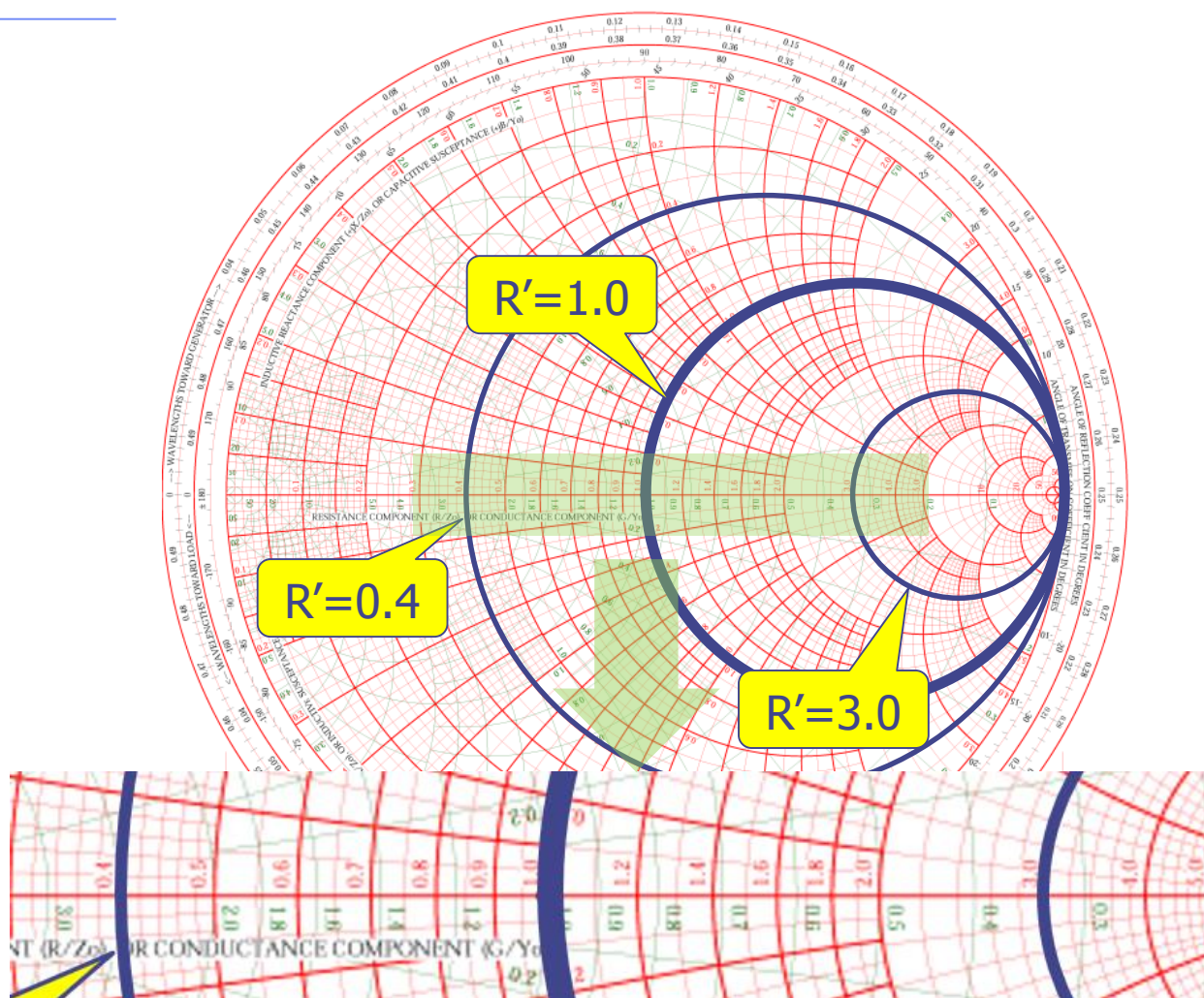


# Constant Reactance 'Arcs'

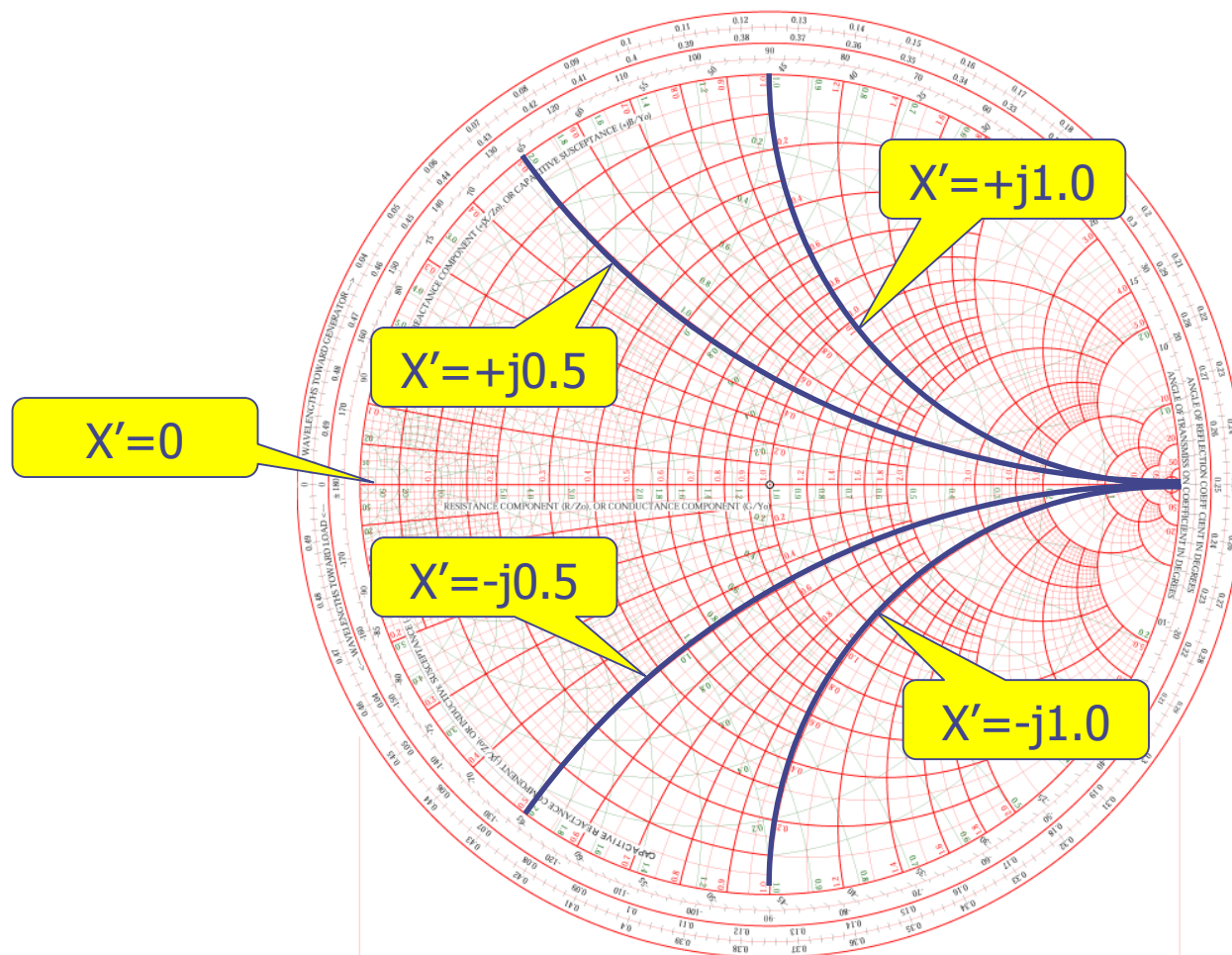
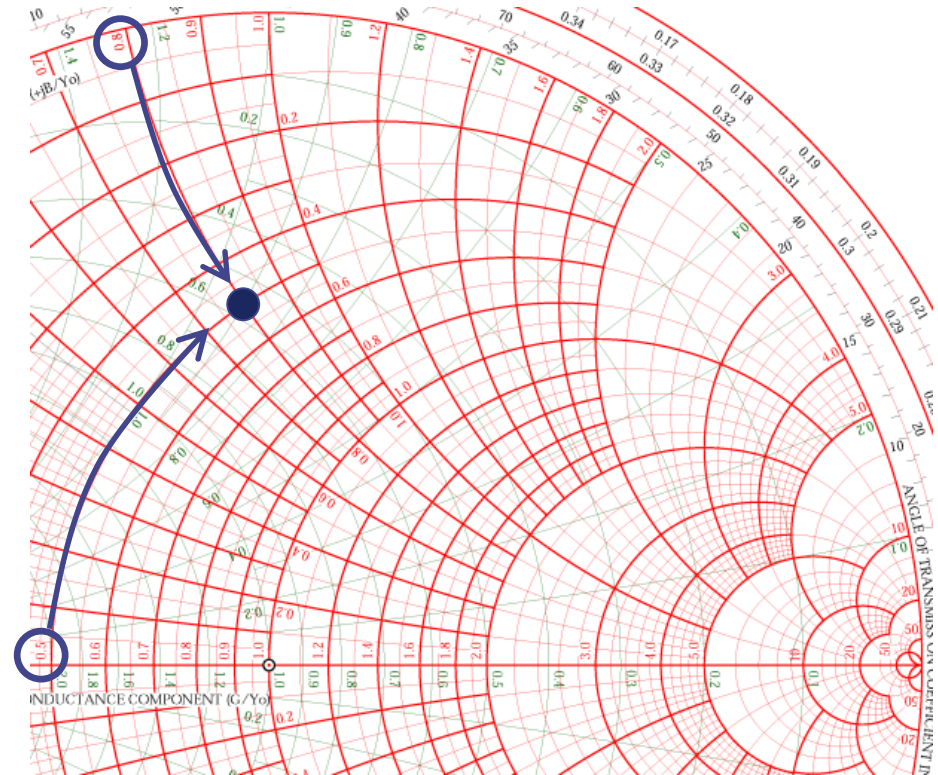
# Plot a Complex Impedance


- $Z = 25 + j40$
- Divide by 50 to normalize...
- $Z' = 0.5 + j0.8$
- Find intersection of  $R'=0.5$  circle and  $X'=0.8$  arc




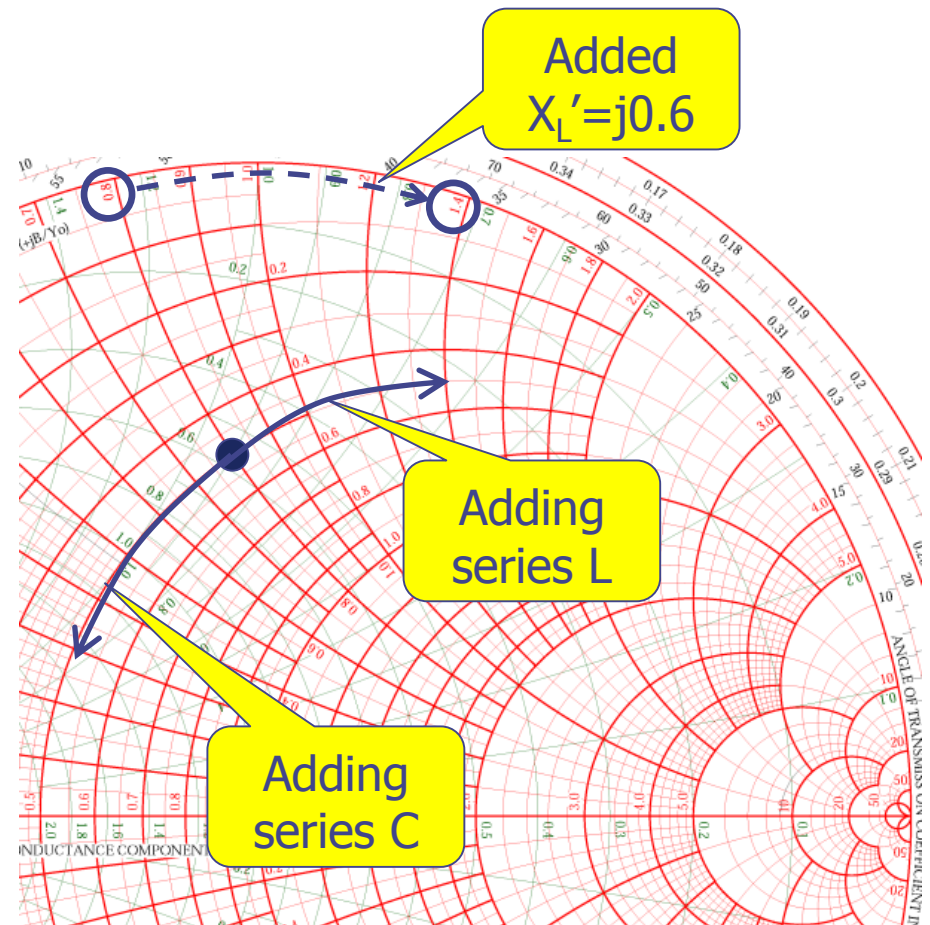
# Adding Series Elements

- Add components to move around the Smith Chart
- Series L & C move along constant-R circles
  - Series L moves CW
  - Series C moves CCW



# What about Admittance?

- Admittance is handy when adding elements in parallel

$$\text{Admittance: } Y = \frac{1}{Z}$$

- Converting Impedance to Admittance is easy with Smith Chart

$$\text{Conductance: } G = \frac{1}{R}^*$$

$$\text{Susceptance: } B = \frac{1}{X}^*$$


\* (when "real" component = 0)

# Converting to Admittance

- Draw circle centered on  $Z_0$  that crosses through Z point
- Bisect circle thru Z and  $Z_0$
- Y is  $180^\circ$  away on circle


$$Z' = 1 + j1.1$$

$$Y' = 0.45 - j0.5$$

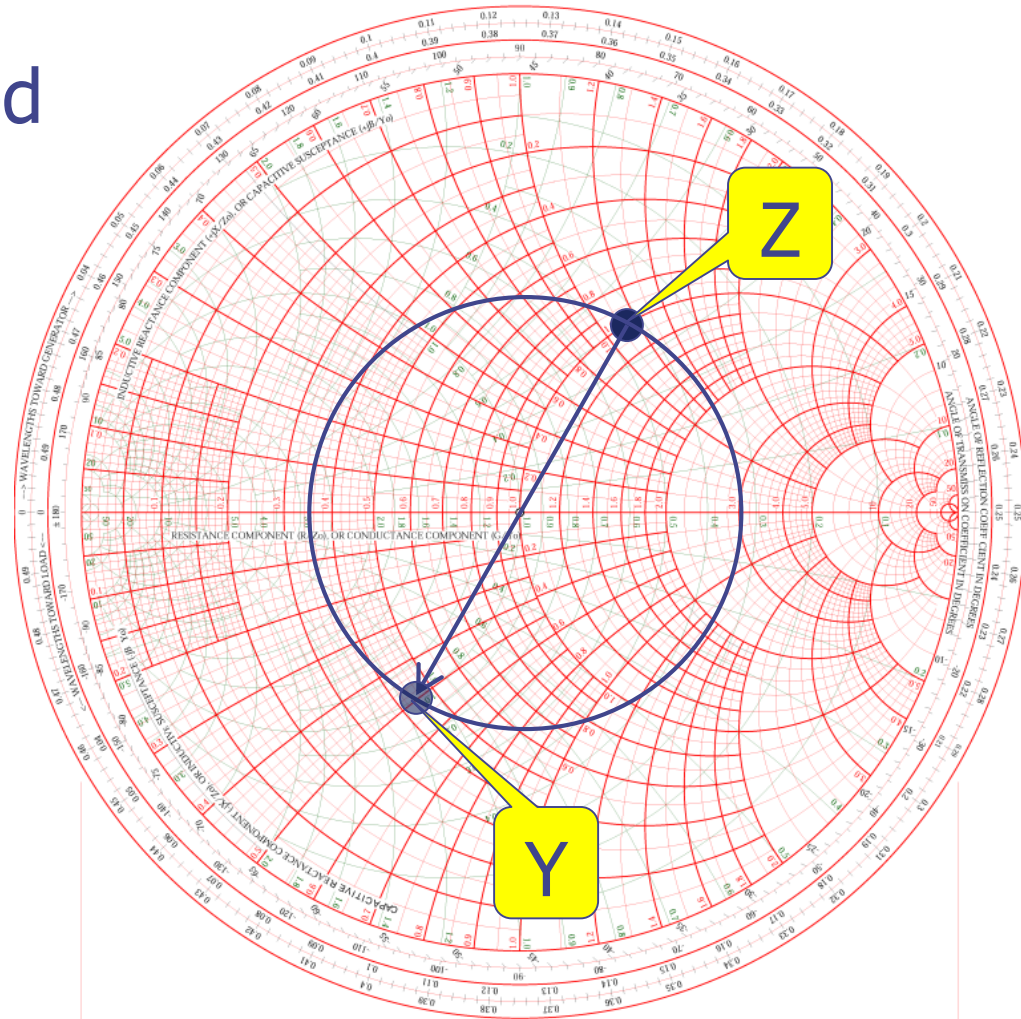
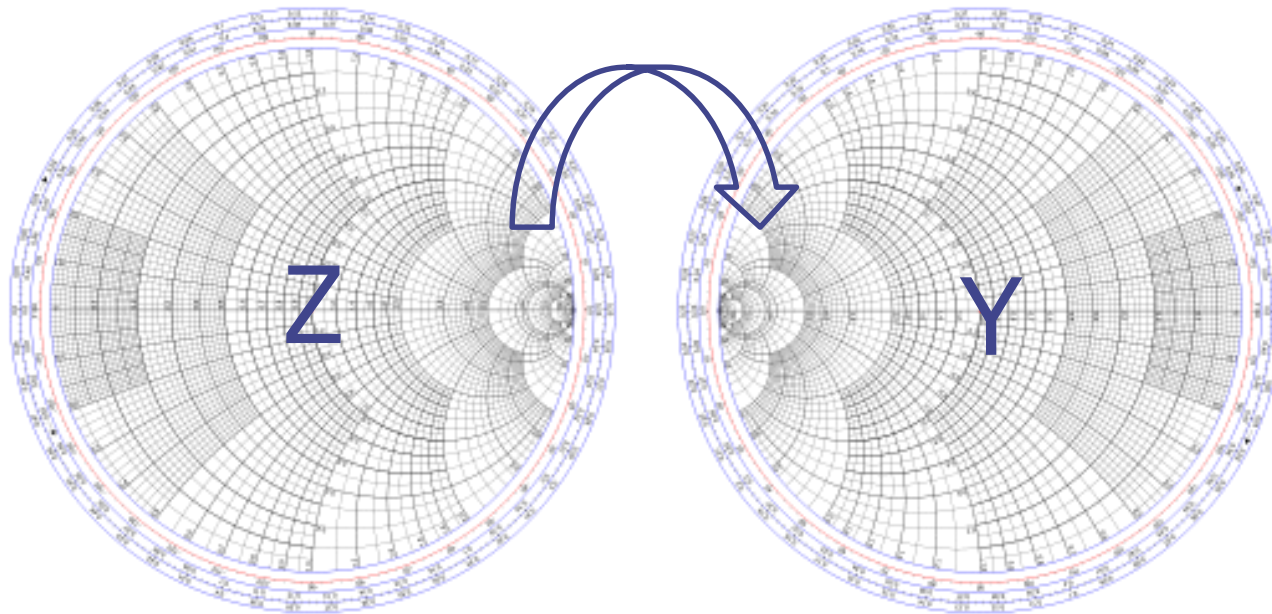
# Admittance Curves


Admittance Curves are obtained by simply rotating the Smith Chart by  $180^\circ$





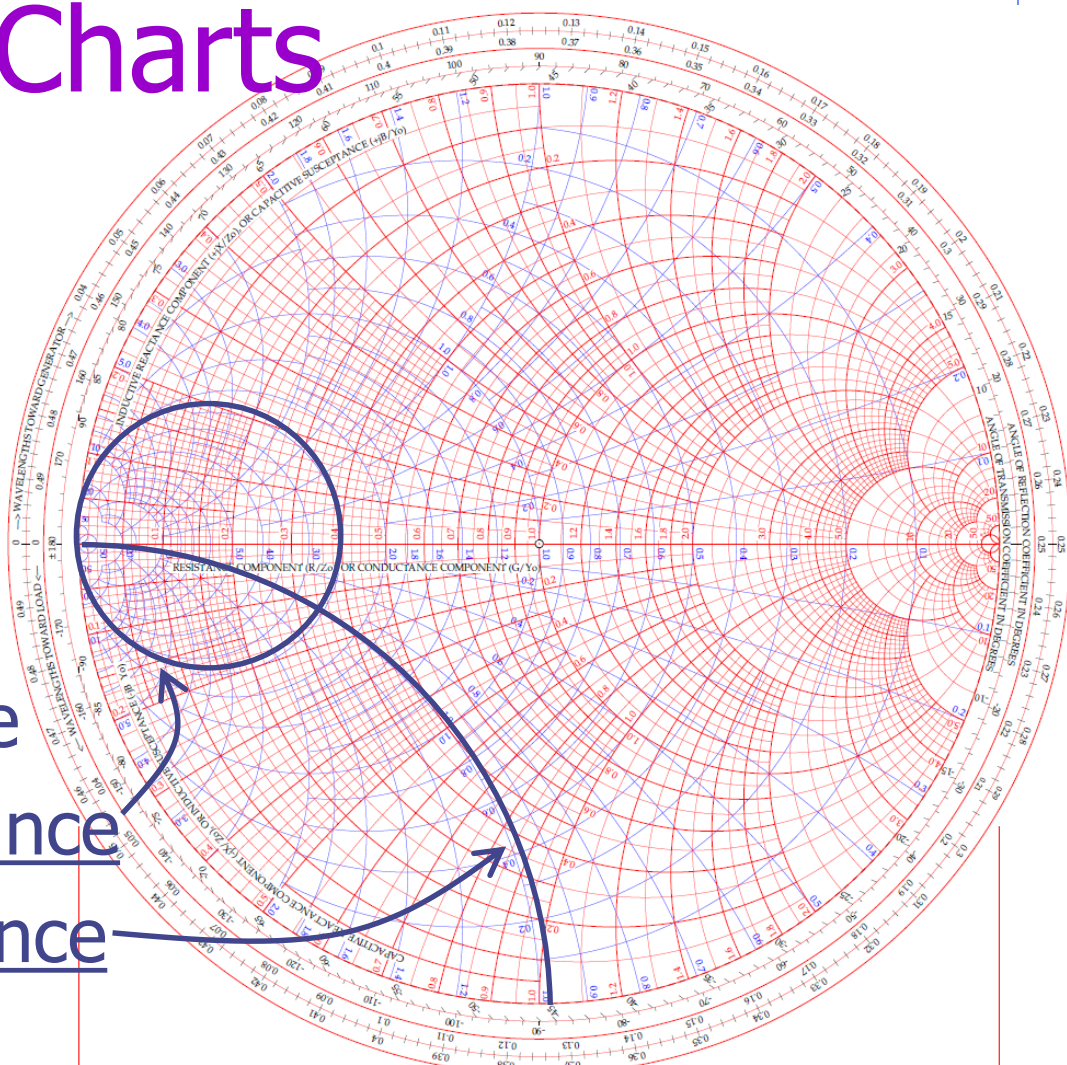
# Combination Charts

- Look carefully – Admittance curves are here!
- Both **Z-only** and **combo** charts are available
- Constant Conductance
- Constant Susceptance



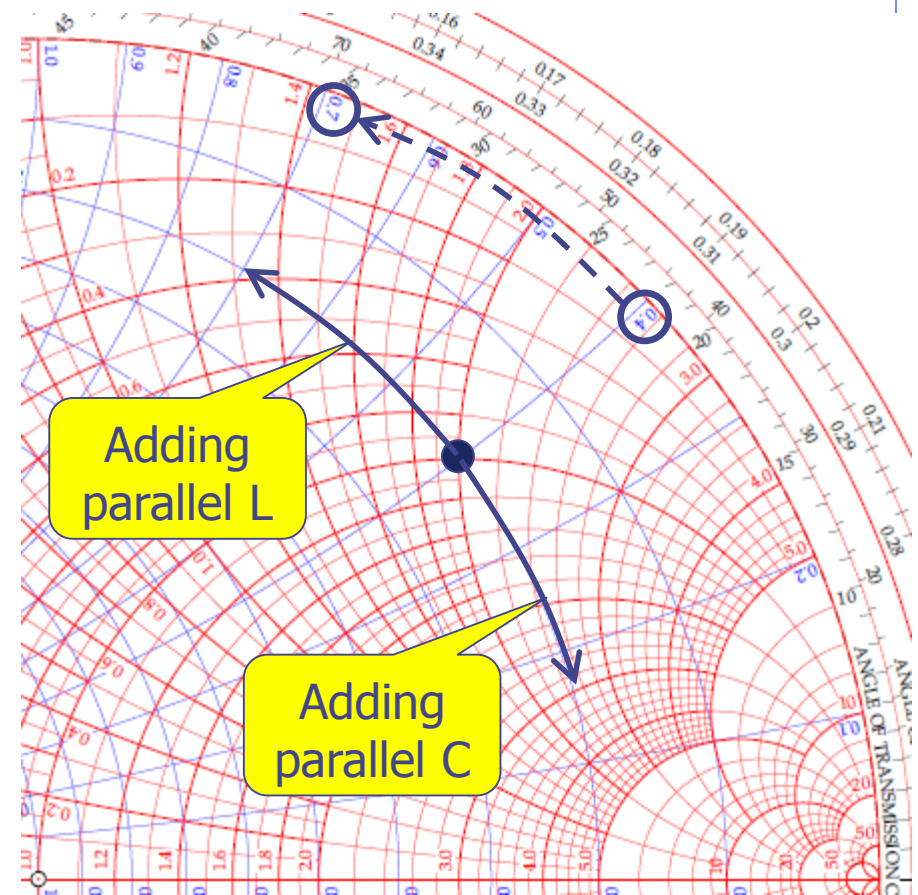
# Adding elements in parallel

- Adding parallel or shunt L & C moves along constant conductance circles
- Easiest to do with "combo" Smith Chart
  - Shunt L with  $B'_L = j0.3$  is shown


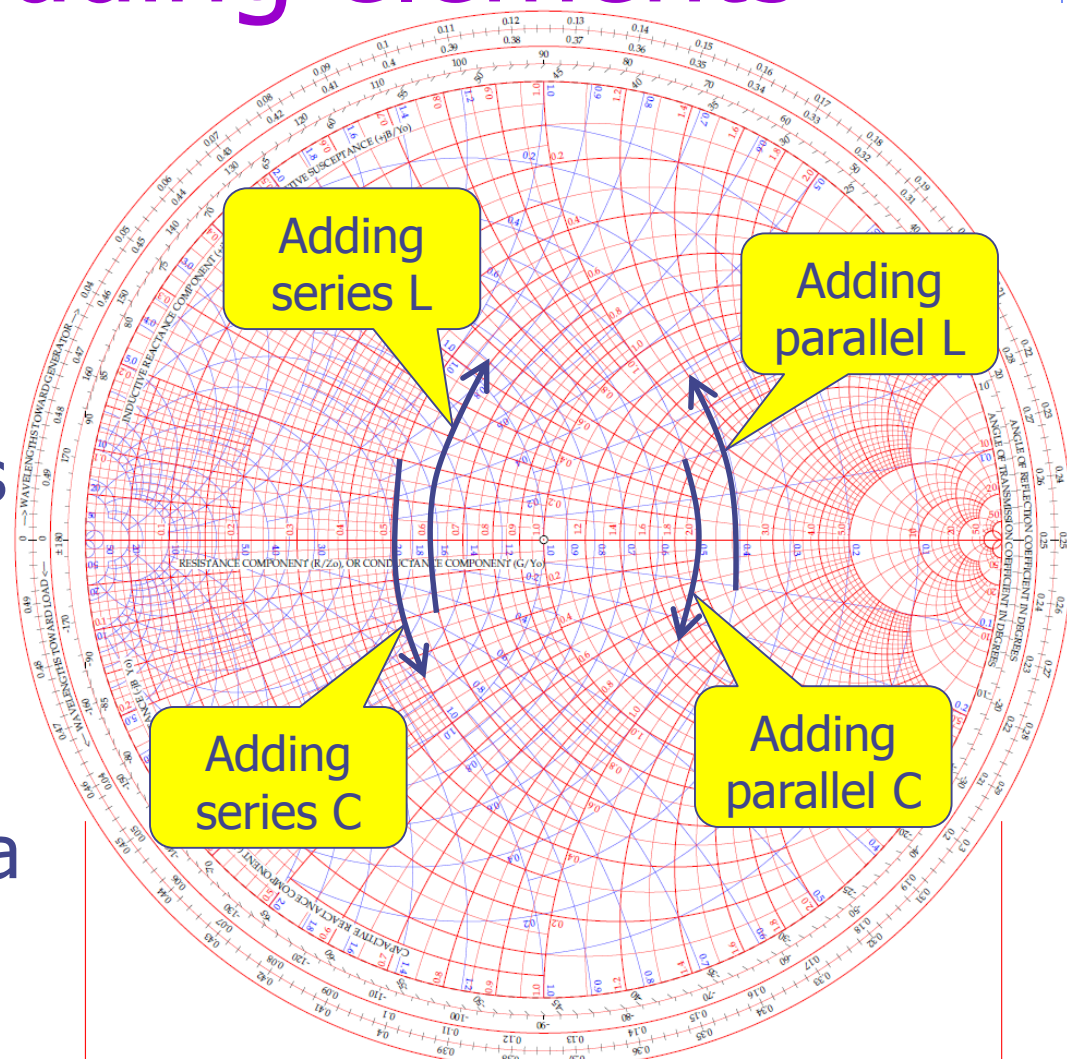
# Quick tip – adding elements


- Adding inductors “e**L**evate” thru real axis
- Adding capacitors “**C**rash” down thru real axis
- Remember this when we design a matching circuit!




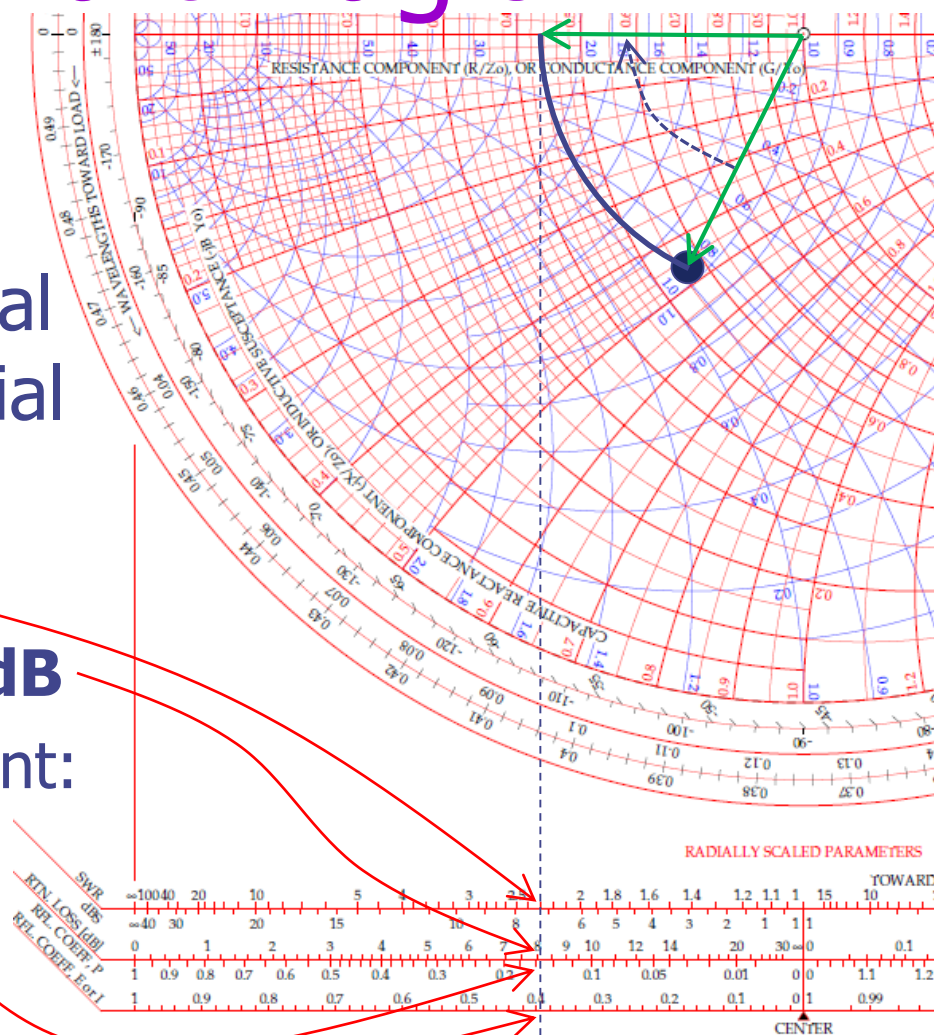
# More Smith Chart Magic


- **Radially Scaled Parameters**
- Rotate vector to real axis, extend to radial scales:
  - VSWR: **2.3:1**
  - Return Loss: **8.10dB**
  - Reflection Coefficient: Power: **0.155**  
V or I: **0.39**





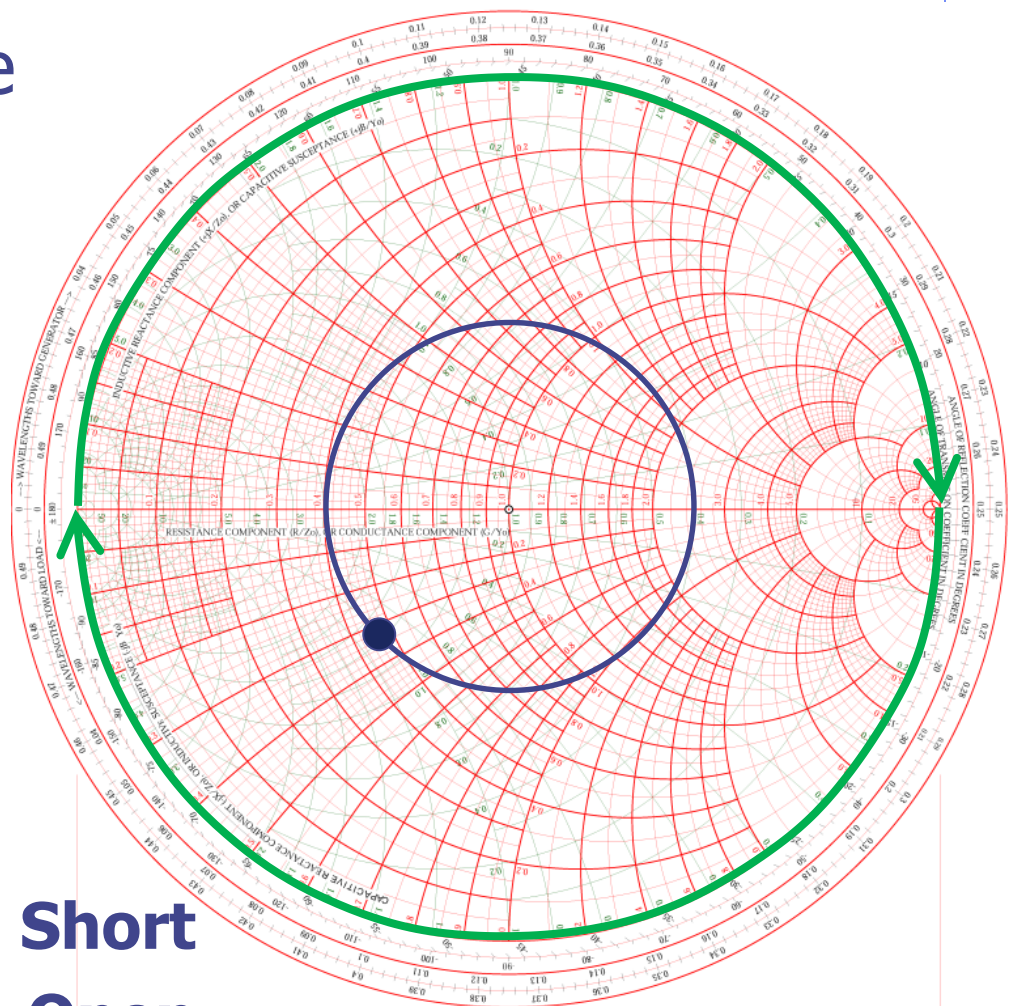
# VSWR and Transmission Lines

- Constant VSWR circle
  - Impedance varies
  - VSWR stays same
- One trip around Smith chart is  $\frac{1}{2}$  wavelength
  - Impedance **repeats**
- Half-way around is  $\frac{1}{4}$  wavelength:
  - **Open** transformed to **Short**
  - **Short** transformed to **Open**








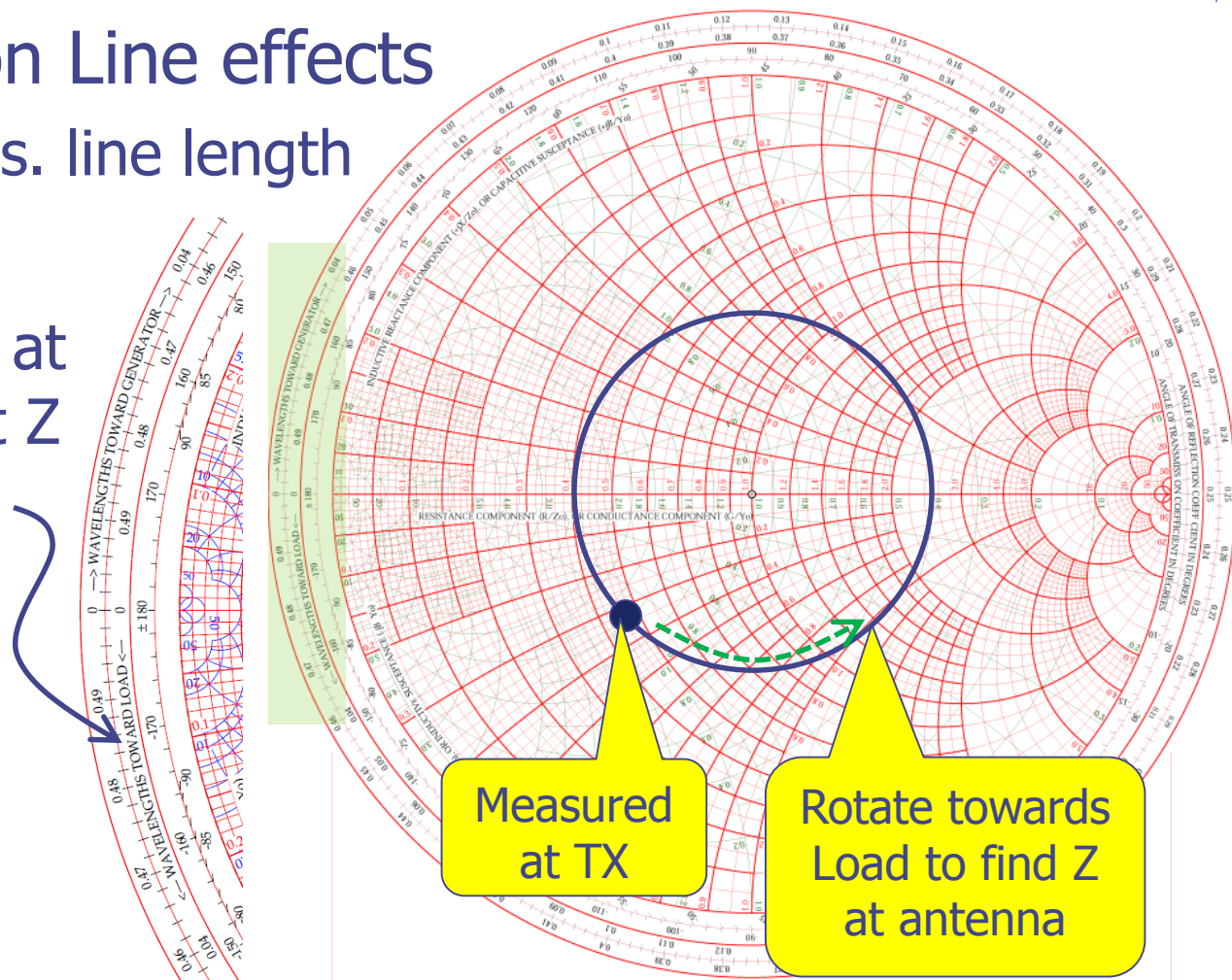
# VSWR and Transmission Lines

- Transmission Line effects
  - Predict  $Z$  vs. line length
- Example:
  - Measure  $Z$  at TX, predict  $Z$  at antenna


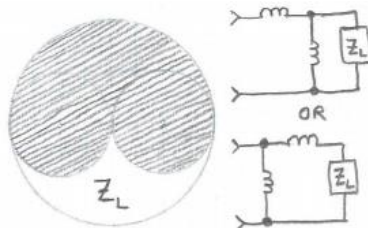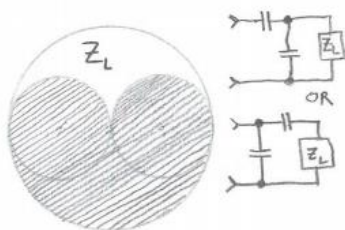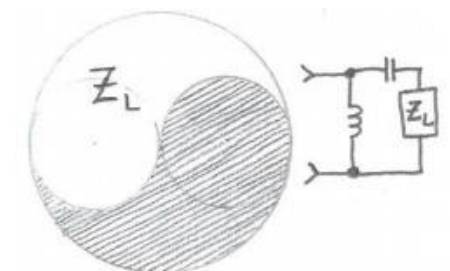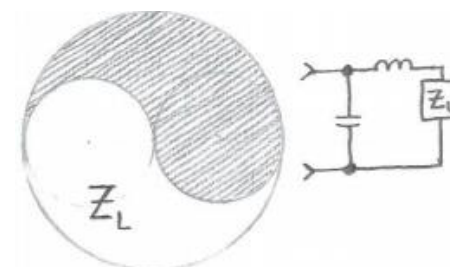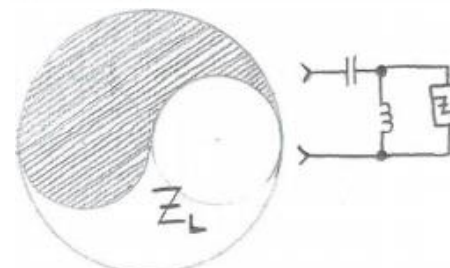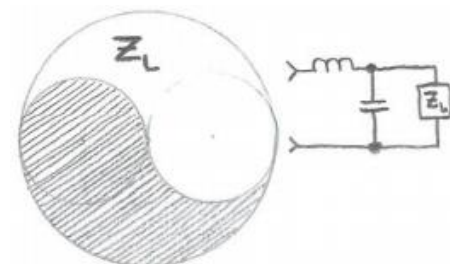
# Impedance Matching: L-Network


- Add series/parallel inductor/capacitor to move  $Z_L$  to  $Z_0$
- L-Network topology based on where  $Z_L$  is on the Smith Chart
- Sometimes more than one network topology works




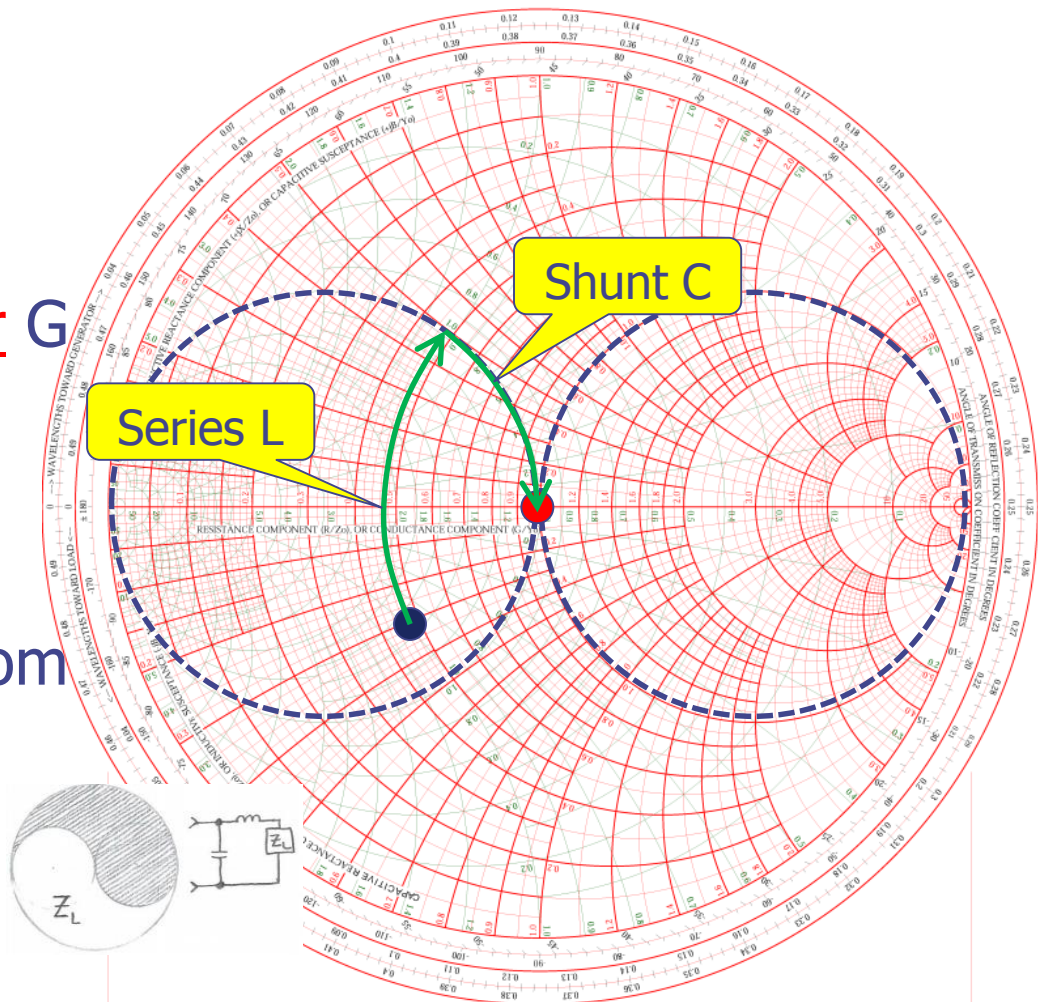
# L-Network Design Process



- Pick a topology
- Process:
  - Add ser/par L/C to rotate to unity R or G circle
  - Add ser/par L/C to rotate to  $Z_0$
  - Compute values from  $\Delta X'$  and  $\Delta B'$
- Example:
  - Series L, shunt C





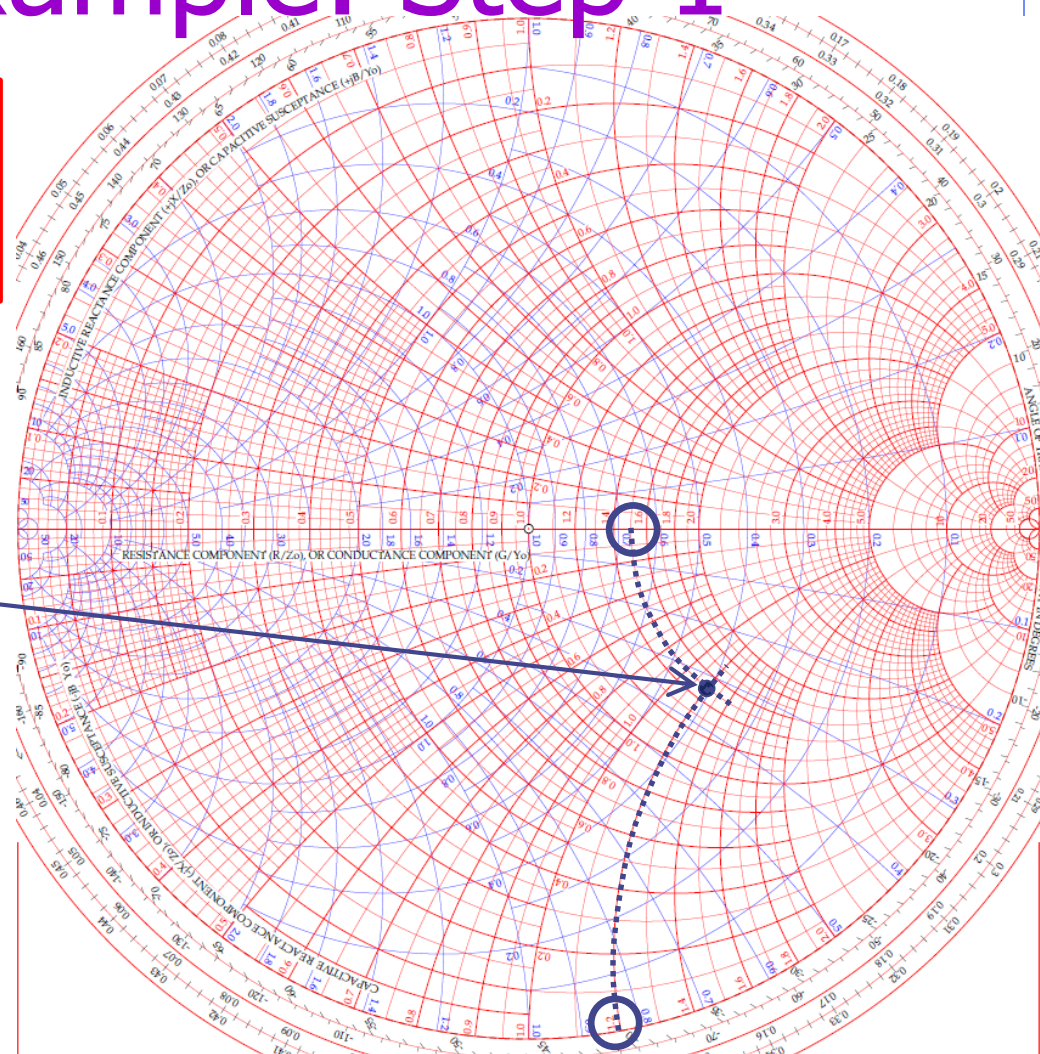
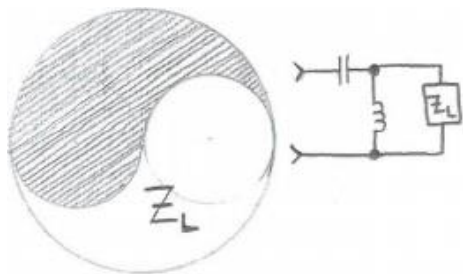
# L-Network Example: Step 1

- Freq = 432.1MHz
- $Z_L = 75 - j60$
- Normalize...
- $Z'_L = 1.5 - j1.2$
- Plot it
- Pick a topology:


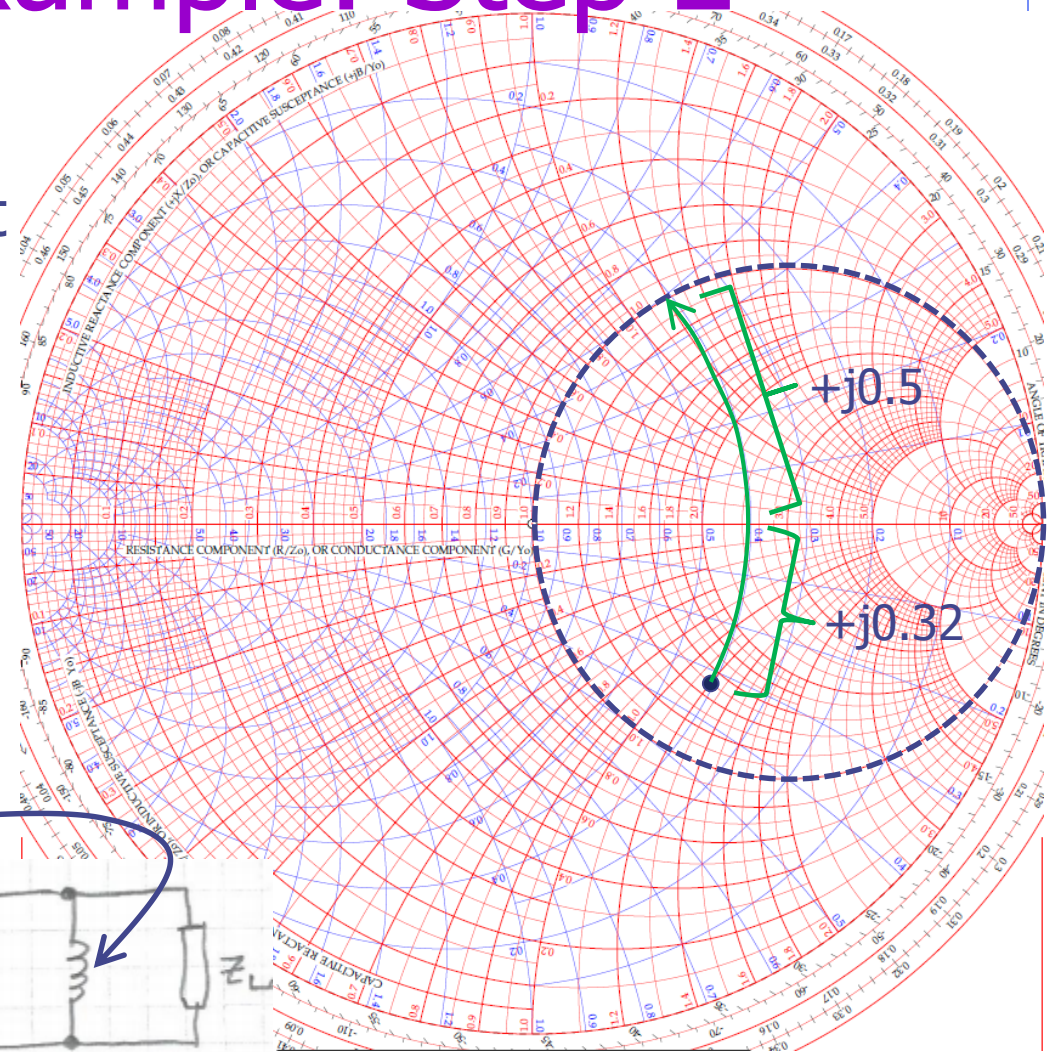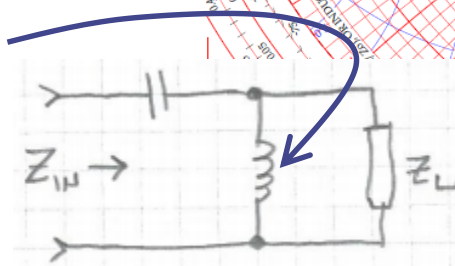
# L-Network Example: Step 2



- Add Shunt L
  - Rotate on constant G until hit  $R'=1$
  - Added  $B'_L$  is  $0.32+0.5=\mathbf{j0.82}$
  - $X'_L=j1.22$
  - $X_L=j61$
  - $L=X_L/(2*\pi*F)$
  - **$L=22.5\text{nH}$**





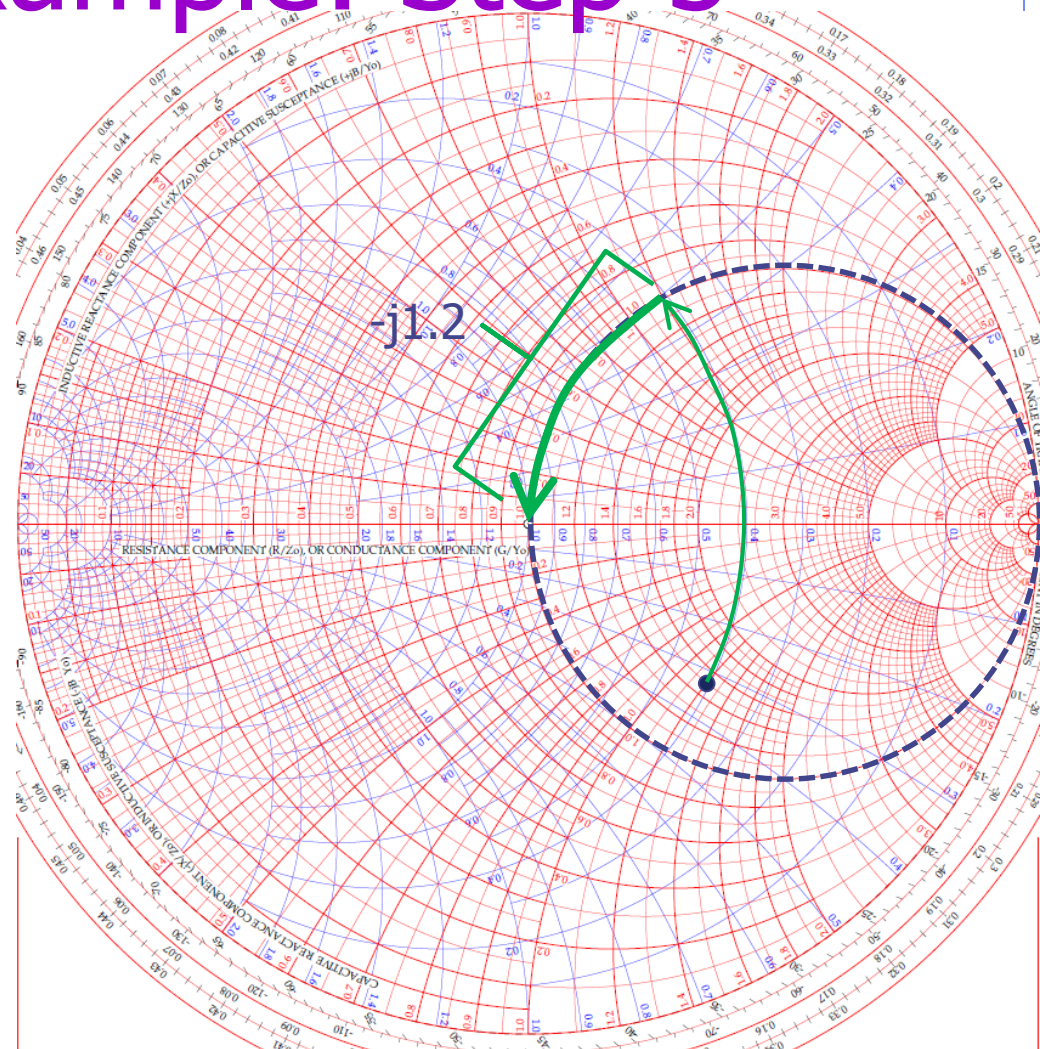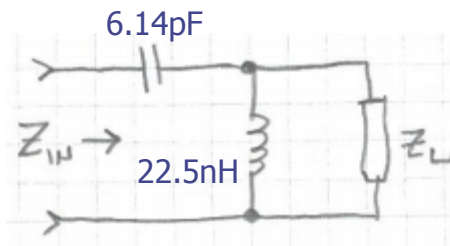
# L-Network Example: Step 3

- Add Series C
  - Rotate on  $R'=1$  until hit  $Z_0$
  - Added  $X'_C = -j1.2$
  - $X_C = -j60$
  - $C = 1/(X_C * 2 * \pi * F)$
  - **$C = 6.14\text{pF}$**



# Extra Credit: Z-only chart

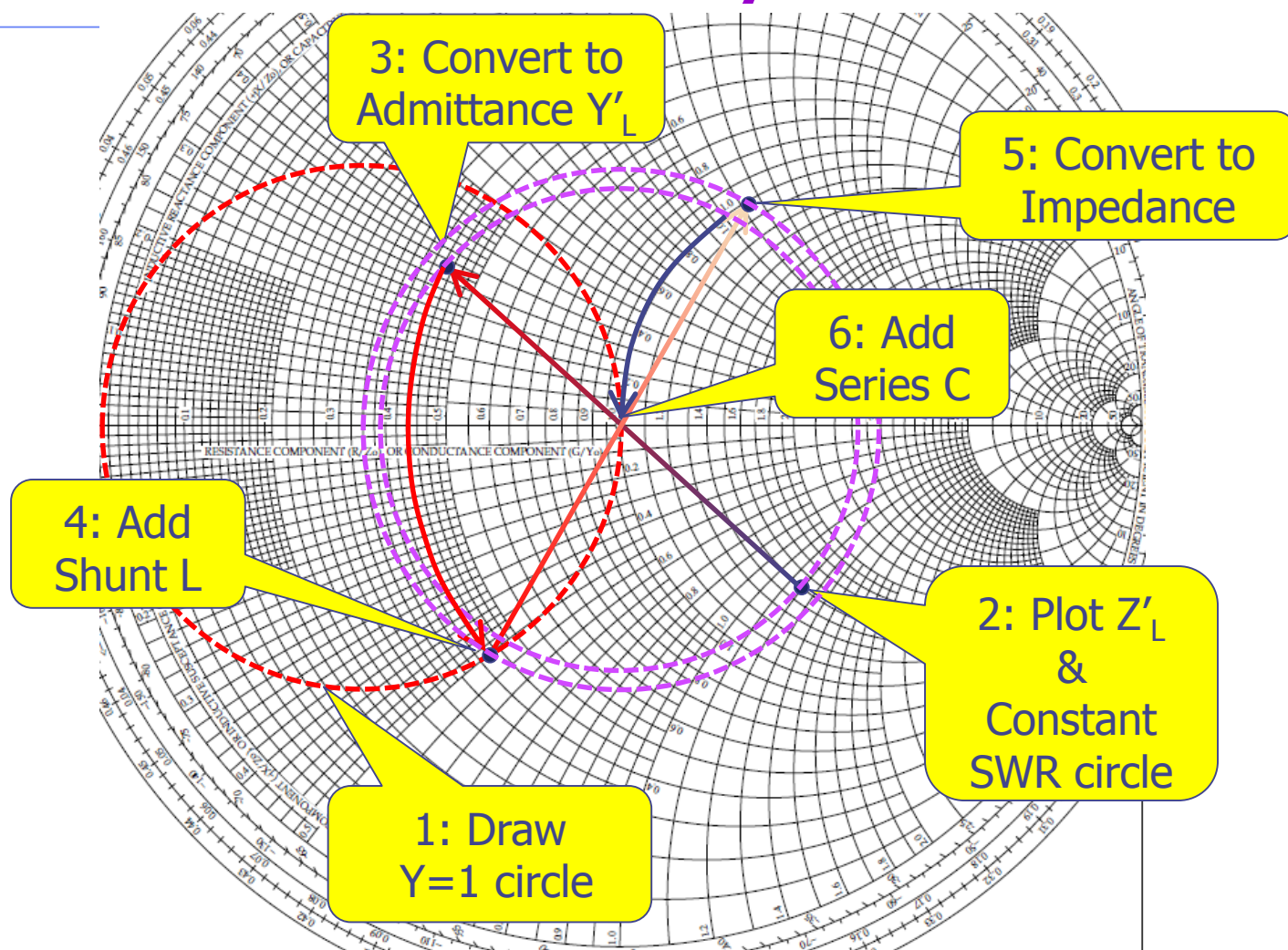



# Summary

- The Smith Chart is a highly useful tool:
  - Complex Impedance Transformations
  - Determining VSWR, RL, and much more
  - Transmission Line impedance transformations
  - Matching Network Design
  - ...and a lot more that we haven't touched on
- Check out SimSmith – PC based tool
  - [http://www.ae6ty.com/Smith\\_Charts.html](http://www.ae6ty.com/Smith_Charts.html)
  - <http://www.w0qe.com/SimSmith.html>