

BACK TO BASICS

# BASICS OF THE BIPOLAR TRANSISTOR

W2AEW  
①



AKA: BJT - BIPOLAR JUNCTION TRANSISTOR

- TWO BASIC TYPES: NPN & PNP




SEE #219 FOR FET BASICS

COMMON PINOUTS  
(BUT NOT UNIVERSAL)


NPN:

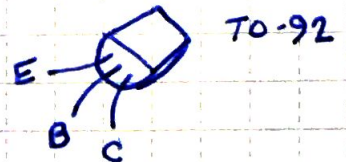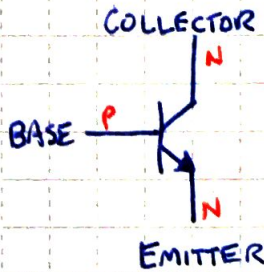

PNP:

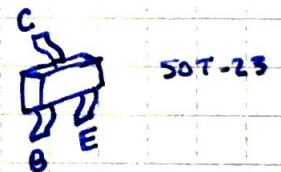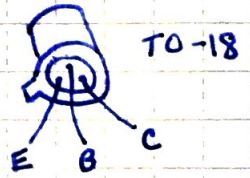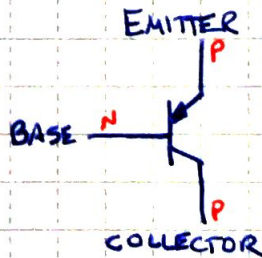

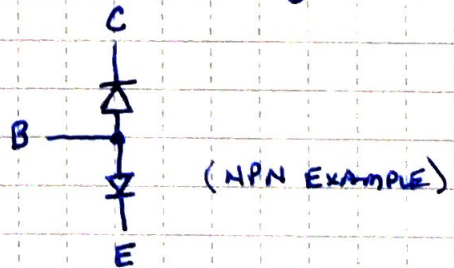
- IT IS COMMON TO SEE A DIAGRAM LIKE THIS TO SHOW THE "JUNCTIONS" OF A BJT




\* - WHILE THIS DOES ILLUSTRATE THE PN JUNCTIONS, IT DOES **NOT** DESCRIBE THE OPERATION OF THE BJT (EXCEPT FOR B-E JUNCTION)
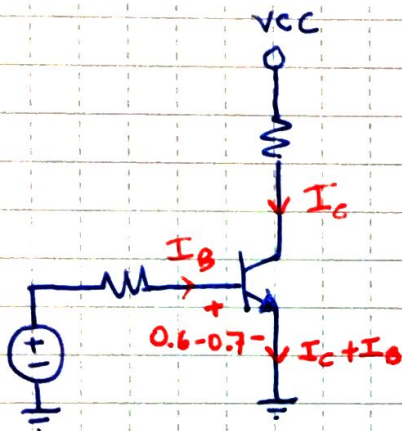
# BASIC OPERATING PRINCIPLES


- THE BASE-EMITTER JUNCTION BEHAVES LIKE A DIODE
- WHEN BASE-EMITTER IS FORWARD-BIASED...  
... CURRENT CAN FLOW BETWEEN COLLECTOR & EMITTER
- WHEN BASE-EMITTER IS **NOT** FORWARD-BIASED...  
... **NO** CURRENT FLOWS BETWEEN COLLECTOR & EMITTER



"ON"

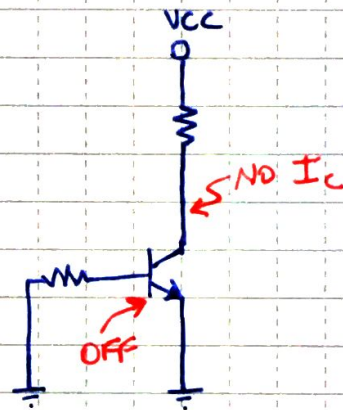

"OFF"

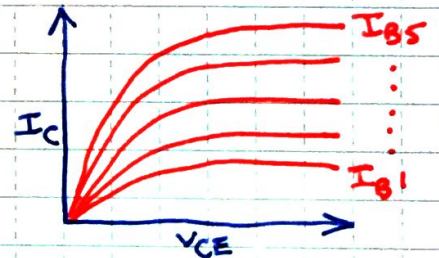

- "LINEAR" OPERATION
  - B-E FORWARD BIASED
  - C-B REVERSE BIASED!

← HOW DO WE GET CURRENT FLOW THRU A REVERSE BIASED PN JUNCTION?


(STAY TUNED)

- "SWITCH" OPERATION (SATURATION)
  - B-E FORWARD BIASED
  - C-B FORWARD BIASED  
(VCE VERY SMALL)




- SWITCH OPERATION : TRANSISTOR IN SATURATION MODE

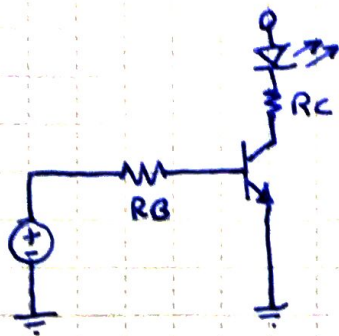- BASE - EMITTER IS FORWARD-BIASED
- VOLTAGE DEVELOPED ACROSS THE LOAD IN THE COLLECTOR PATH DRIVES THE COLLECTOR VOLTAGE BELOW THE BASE
- THIS FORWARD-BIASES THE BASE-COLLECTOR JUNCTION
- TRANSISTOR  $\beta$  (CURRENT GAIN) DROPS - TYPICALLY TO  $\approx 10-20$
- THUS, BASE CURRENT INCREASES



EXAMPLE

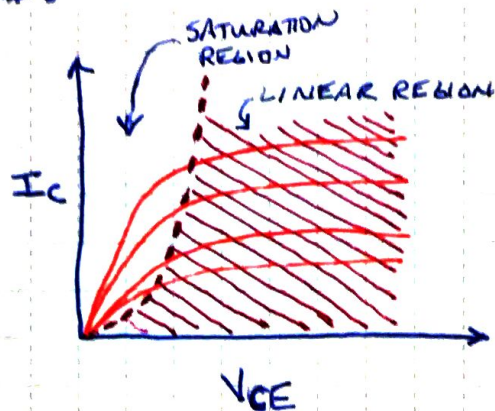

- IN SATURATION,  $V_{CE}$  IS A FEW HUNDRED mV
- $I_C$  DETERMINED BY SUPPLY VOLTAGE & LOAD IN COLLECTOR PATH  
&  $I_B \approx I_C / 10$  or 20

MORE VIDEOS ON BIPOLAR TRANSISTOR CIRCUITS & APPLICATIONS

#185: BIPOLAR TRANSISTOR BIAS CONSIDERATIONS & BETA DEPENDENCE

#113: BIPOLAR TRANSISTOR AMPLIFIER BIAS & CLASS OF OPERATION

#114: COMMON EMITTER, COMMON BASE & COMMON COLLECTOR AMPLIFIERS

#273: COMMON EMITTER AMPLIFIER TIPS & TRICKS

#67: COMMON EMITTER AMPLIFIER GAIN & FREQUENCY RESPONSE

#356: BASICS OF THE EMITTER FOLLOWER AMPLIFIER

#198: V<sub>BE</sub> MULTIPLIER TUTORIAL & APPLICATIONS

#190/191: CURRENT MIRROR BASICS

#327: CURRENT MIRRORS & EARLY EFFECT


#193: BASICS OF THE EMITTER COUPLED DIFFERENTIAL PAIR AMP




... A FEW MORE DETAILS ...

WRAEW  
③

- FOR LINEAR OPERATION

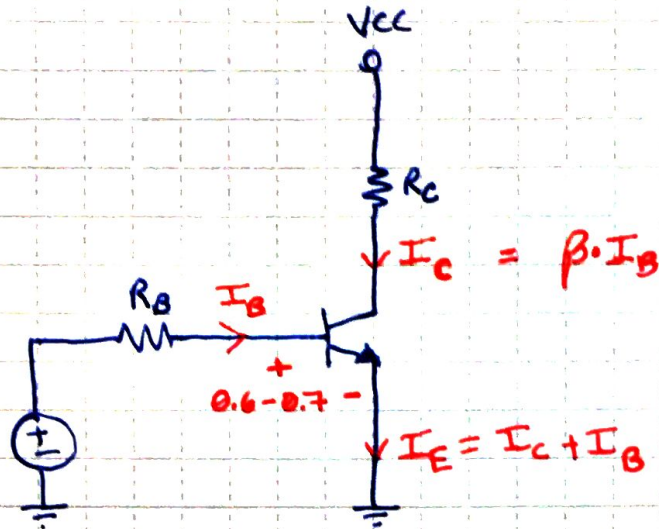

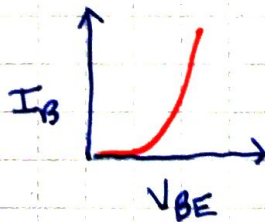- $V_{BE}$  TYPICALLY  $0.6V$  TO  $0.7V$
- $I_C = \beta \cdot I_B$  ,  $\beta$  TYPICALLY  $\approx 100 - 200$
- $I_E = I_C + I_B$
- BASE-EMITTER BEHAVES LIKE A DIODE:




- COLLECTOR CURRENT DETERMINED BY BASE CURRENT



1 SQUARE =

- HOW DOES CURRENT FLOW THROUGH THE REVERSE-BIASED COLLECTOR-BASE JUNCTION?


- LOOK AT VERY BASIC STRUCTURE & PHYSICS

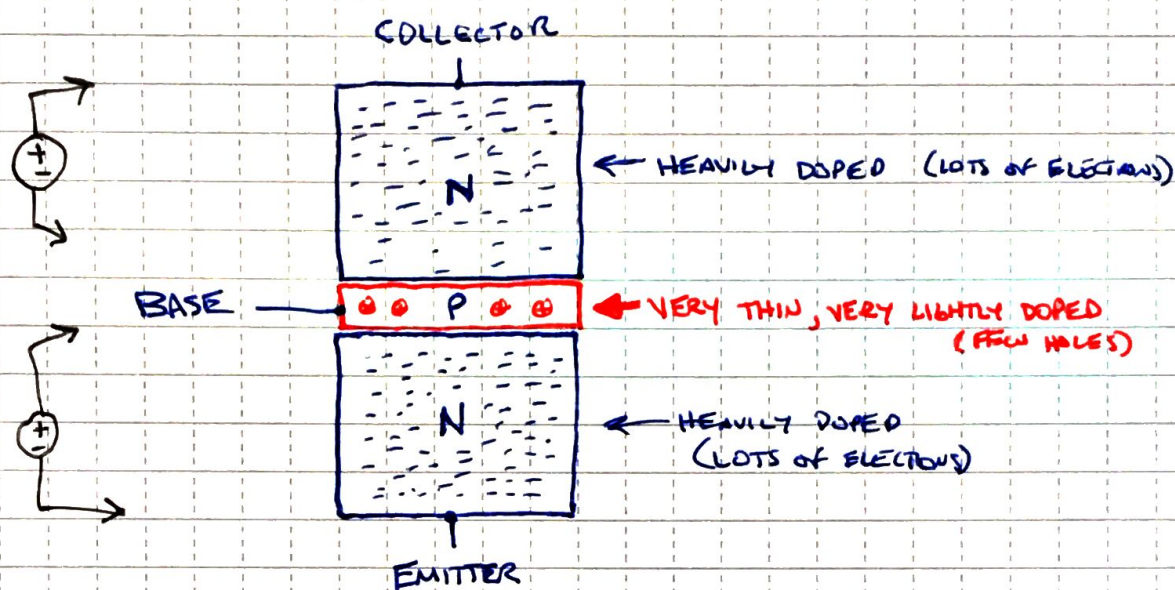

- BASE VOLTAGE HIGHER THAN EMITTER
- FORWARD BIAS B-E JUNCTION
- LOTS OF ELECTRONS DRAWN INTO BASE REGION
- SINCE BASE IS VERY LIGHTLY DOPED - FEW ELECTRONS RECOMBINE WITH HOLES
- SINCE BASE IS SO THIN, A LOT OF ELECTRONS TRAVEL ACROSS THE BASE, DRAWN BY THE POSITIVE POTENTIAL OF THE COLLECTOR
- THESE ELECTRONS CROSS THE C-B DEPLETION REGION AND BECOME THE COLLECTOR CURRENT
- ONLY ABOUT 1% OF THE ELECTRONS RE-COMBINE AND MAKE UP BASE CURRENT
- $\approx 99\%$  OF ELECTRONS FROM EMITTER TRAVEL THROUGH THE BASE REGION AND BECOME COLLECTOR CURRENT




# TEST CIRCUIT DIAGRAM

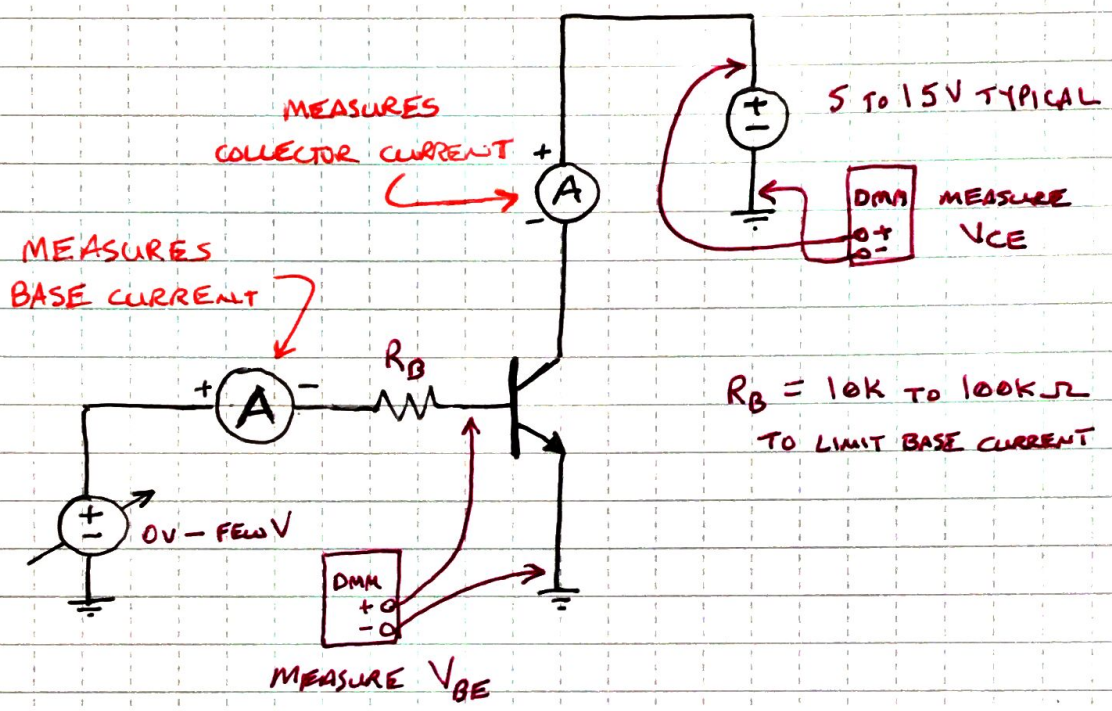

- 2 VARIABLE POWER SUPPLIES
- 2 AMMETERS
- 2 VOLTMETER / DMM
- 1 RESISTOR

## FOR SATURATION

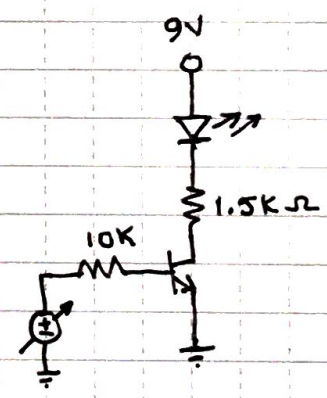

1 SQUARE =