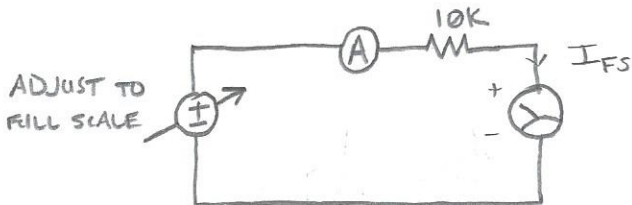


USING A CURRENT SHUNT TO
CHANGE THE FULL SCALE READING
OF AN AMMETER


WRAEW

① MEASURE FULL SCALE CURRENT OF THE METER:



$$I_{FS} = 200 \mu A$$

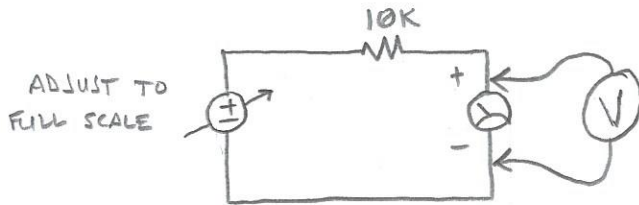
② MEASURE THE METER'S VOLTAGE DROP AT FULL SCALE:



$$V_{FS} = 185 mV$$

③ CALCULATE SHUNT RESISTOR FOR DESIRED FULL SCALE CURRENT: I_{FSD}

$$I_{FSD} = 0.6 A$$

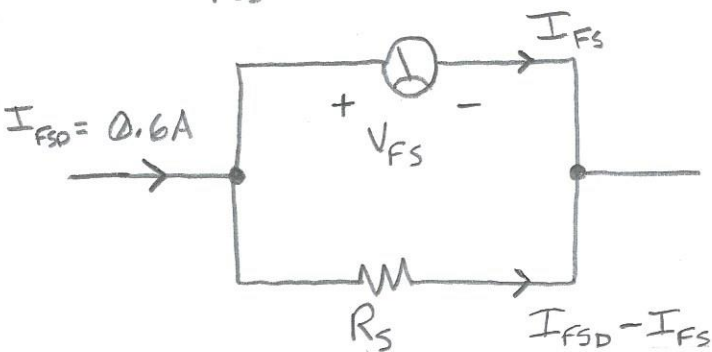

$$R_S = \frac{V_{FS}}{I_{FSD} - I_{FS}}$$

$$R_S = 308 m\Omega$$