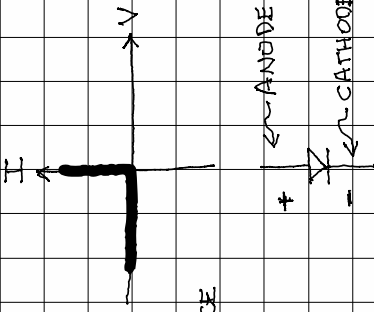


# PRACTICAL GUIDE TO DIODES

①


WZAEW




— FROM IDEAL TO REAL —

— THE IDEAL DIODE — THE ONE-WAY CHECK VALVE

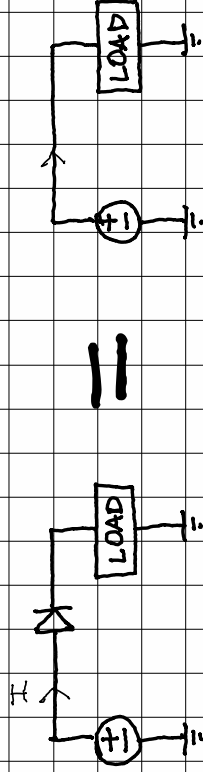• FORWARD DIRECTION = SHORT CIRCUIT, NO RESISTANCE



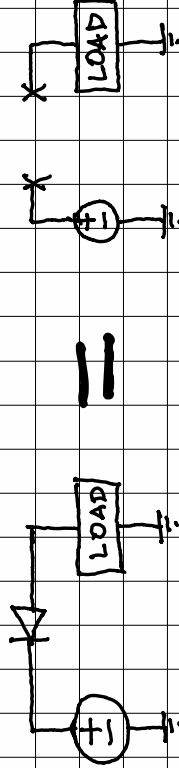• REVERSE DIRECTION = OPEN CIRCUIT, INFINITE RESISTANCE




• IDEAL DIODE DOESN'T EXIST

# LET'S START TO GET REAL...

② W2AEW


• FORWARD DIRECTION (FORWARD BIAS)

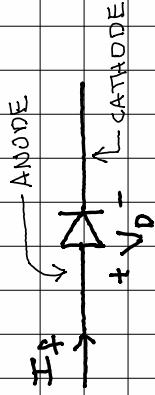


- IF  $V_D < V_f$  : OPEN CIRCUIT, NO CURRENT
- $V_D = V_f$  : SHORT CIRCUIT, CURRENT FLOWS
- $V_D$  CAN'T BE GREATER THAN  $V_f$

- DIODE LOOKS LIKE A CONSTANT VOLTAGE DROP



- CURRENT LIMITED BY LOAD

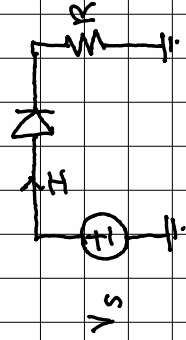

$$I = \frac{V_S - V_f}{R}$$

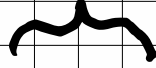

MANY CIRCUITS CAN BE ANALYZED LIKE THIS

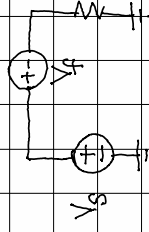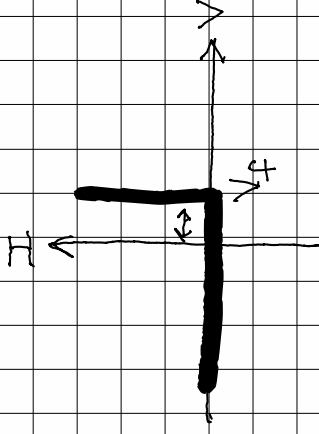

## A LITTLE MORE REAL...


③

W2AEW

- FORWARD BIAS

-  $V_D$  INCREASES "SLIGHTLY" AS CURRENT INCREASES


- APPEARS LIKE:

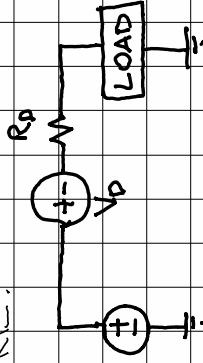

-  $R_D$  IS THE "DYNAMIC RESISTANCE"

- AKA: SMALL-SIGNAL OR INCREMENTAL RESISTANCE

- TYPICALLY JUST A FEW / SEVERAL OHMS

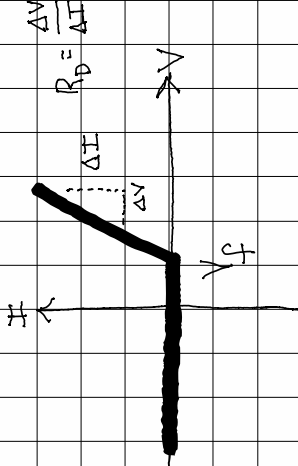


# A FEW MORE DETAILS ...

④



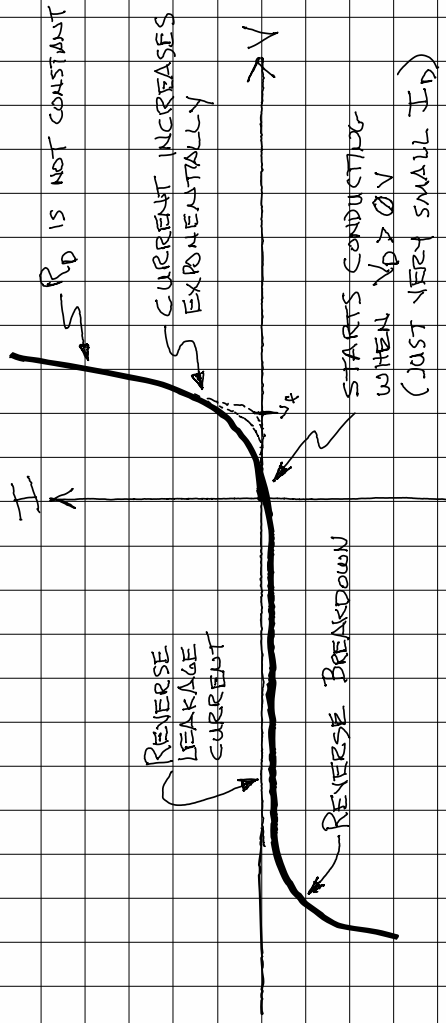

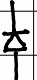
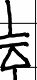

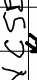

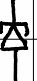

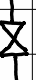
WRAEW

MUCH MORE ACCURATE  
V-I CURVE FOR DIODES



- ALL CHARACTERISTICS ARE TEMPERATURE DEPENDENT

# MORE DIODE REALITIES...

- JUNCTION CAPACITANCE
  - BIAS DEPENDENT
- CHARGE STORAGE
  - REVERSE CURRENT WHEN SWITCHING OFF (BRIEFLY)
  - SEE VIDEO LINK (VIDEO #201)
- MANY DIFFERENT TYPES OF DIODES
  - RECTIFIER / GENERAL PURPOSE 
  - SWITCHING DIODES  (VIDEO # 82)
  - SCHOTTKY DIODES 
  - ZENER / AVALANCHE DIODES  (VIDEO # 289)
  - PIN DIODES  (VIDEOS #118 & #200 & #130)
  - VARACTOR / VARI-CAP DIODES  (VIDEO # 147)
  - LIGHT EMITTING DIODES 
  - LASER DIODES / VCSELS 
  - PHOTO DIODES 
  - \* - TUNNEL DIODES  (VIDEO # 204)
  - STEP-RECOVERY / SWAP DIODES 
  - \* - GUNN DIODES 

MORE DIODE VIDEOS  
 #302 #77  
 #183 #161  
 #104 #167

\* STRANGE I-V CURVES

2 MORE

## COMMON DIODE SPECIFICATIONS

⑥

W2AEW

•  $V_f$  - FORWARD VOLTAGE

SILICON PN DIODES:  $0.6 - 0.7V$  TYP.

GERMANIUM DIODES:  $\approx 0.3V$

SCHOTTKY DIODES:  $\approx 0.2V$

•  $I_f$  - FORWARD CURRENT (OPERATING)

•  $I_R$  - REVERSE CURRENT

TYPICALLY FEW  $\mu A$   
GE & SCHOTTKY WORSE

•  $V_{BR}$  - REVERSE BREAKDOWN VOLTAGE

VOLTAGE WHERE REVERSE CURRENT INCREASES RAPIDLY - USUALLY DON'T GO THERE!

$V_Z$  = ZENER VOLTAGE - DESIGNED FOR OPERATION IN THIS REGION (VIDEO #289)

PN = PEAK INVERSE VOLTAGE - SPEC FOR POWER DIODES, MAX REVERSE OPERATING VOLTAGE

•  $t_{rr}$  - REVERSE RECOVERY TIME (VIDEO #201)

TIME DURATION OF REVERSE CURRENT FLOW WHEN SWITCHING OFF

RANGES FROM  $< 1ns$  TO MANY  $\mu S$  OR MORE

SCHOTTKY & SWITCHING DIODES ARE FAST

POWER RECTIFIERS, PWS DIODES ARE SLOW

