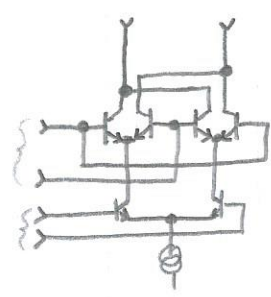


# THE GILBERT CELL

- NAMED AFTER BARRIE GILBERT (TEKTRONIX, ANALOG DEVICES, PRESSEY)
- EXTENSIONS ON CIRCUIT FIRST PUBLISHED BY HOWARD JONES IN 1963, US PATENT 3,241,078 (1966)




## USES & APPLICATIONS

- FOUR QUADRANT ANALOG MULTIPLIER
- VARIABLE GAIN AMPLIFIER
- AUTOMATIC GAIN CONTROL CIRCUITS
- BALANCED MODULATOR
- FREQUENCY MIXER
- PHASE DETECTOR

### PRE REQUISITE

#193: BACK TO BASICS: THE DIFFERENTIAL AMPLIFIER, AKA LONG-TAILED PAIR, DIFF-PAIR
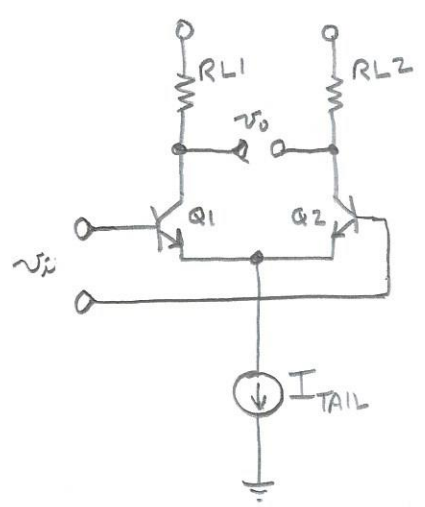
## FOUNDATION: THE DIFFERENTIAL AMPLIFIER (REVIEW VIDEO #193)



WHEN  $v_i = 0$ :  $I_{C1} = I_{C2} = \frac{I_{TAIL}}{2}$

$V_{RL1} = V_{RL2}$ , so  $v_o = 0$

SMALL SIGNAL DIFFERENTIAL GAIN

$A_{V_{DIFF}} = \frac{v_o}{v_i} = g_m R_L$

$v_o = v_i \cdot g_m \cdot R_L$


$g_m = \frac{I_C}{V_T} = \left(\frac{I_{TAIL}}{2}\right) / V_T$

$V_T = 26mV @ \text{ROOM TEMP}$

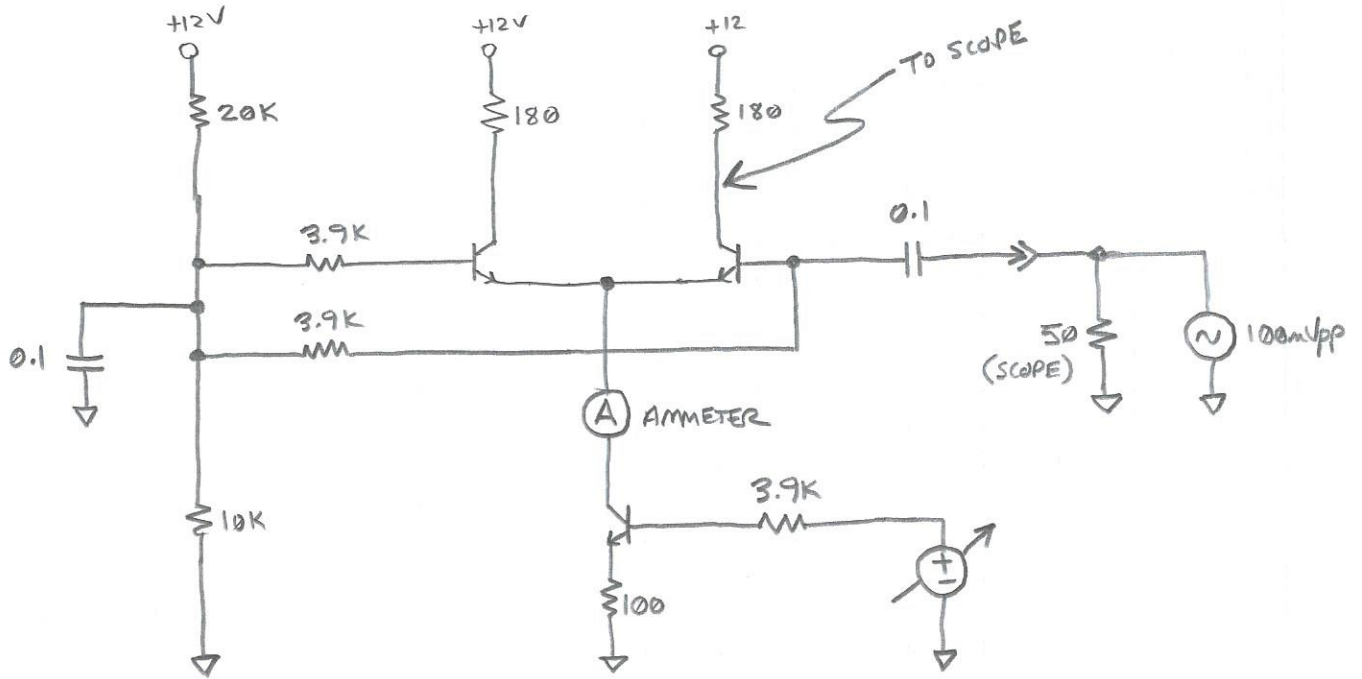**KEY POINT: GAIN IS A FUNCTION OF  $I_C$**


↑ REMEMBER THIS FOR LATER!

TEST CIRCUIT TO SHOW DIFF-AMP  
GAIN VS. TAIL CURRENT



ALL TRANSISTORS 2N3904


SUMMING THE OUTPUTS OF TWO DIFF-PAIRS

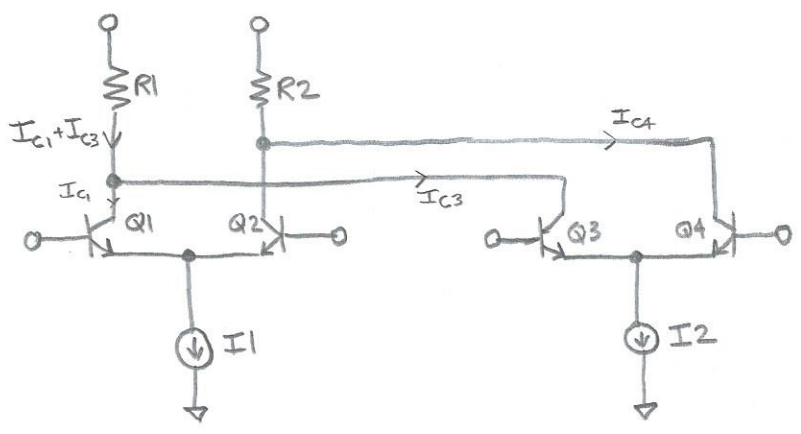

$$V_{R1} = I_{c1} \cdot R1 + I_{c3} \cdot R1$$

$$V_{R2} = I_{c2} \cdot R2 + I_{c4} \cdot R2$$

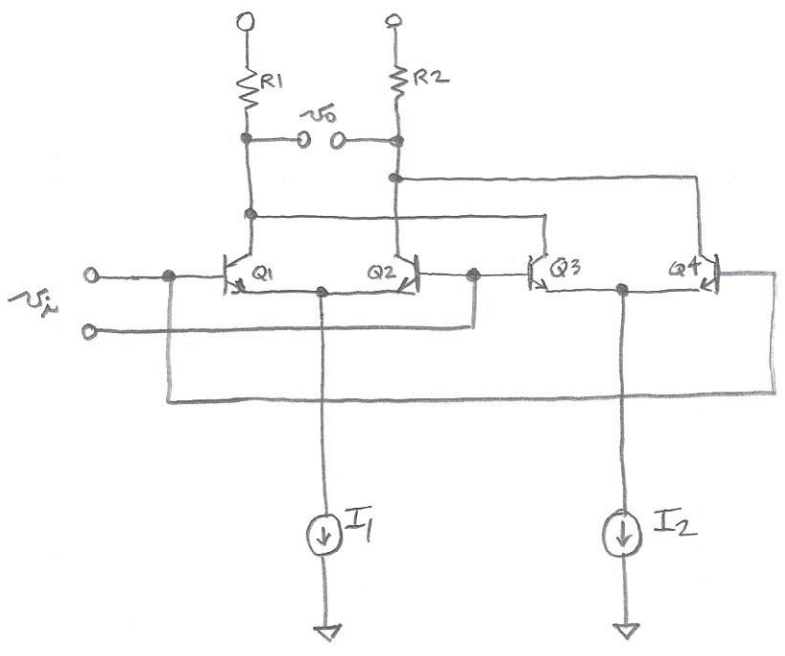NEXT, EXAMINE WHAT HAPPENS WHEN WE CROSS-CONNECT THE INPUTS...



IF  $I_1 = I_2$ :  $V_{R1} = V_{R2}$

$$V_o = 0$$

REGARDLESS OF  $v_i$

IF  $I_1 \neq I_2$ :  $v_o$  WILL VARY  $\propto v_i$

DIFFERENTIAL GAIN IS PROPORTIONAL TO THE DIFFERENCE BETWEEN  $I_1$  &  $I_2$


- INVERTING OR NON-INVERTING

- VARIABLE GAIN

$$v_o = K v_i$$

$\propto$  DIFFERENCE IN  $I_1$  &  $I_2$   
CAN BE + OR -

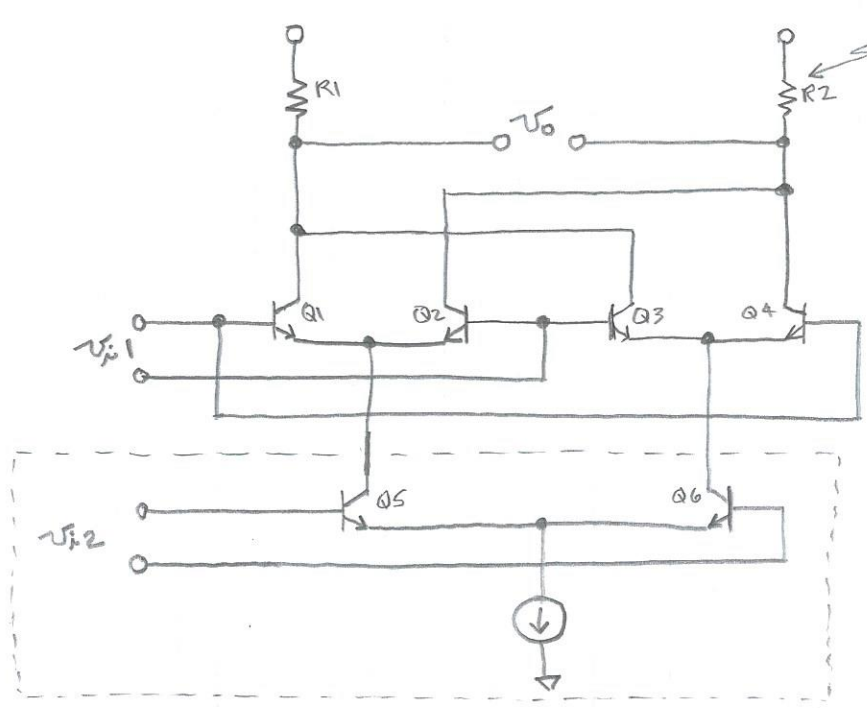FINAL STEP: REPLACE  $I_1$  &  $I_2$  WITH A DIFF-PAIR



(NOTE: SIMPLY REPOSITIONED R2)

$$V_0 \approx K \cdot V_{i1} \cdot V_{i2}$$

IF  $V_{i1} = 0$ ,  $V_0 = 0$


IF  $V_{i2} = 0$ ,  $V_0 = 0$

THIS IS THE FUNDAMENTAL GILBERT CELL

FOUND IN NUMEROUS INTEGRATED CIRCUITS INCLUDING:

- NE 602
- NE 612
- MC1496

TEST CIRCUIT

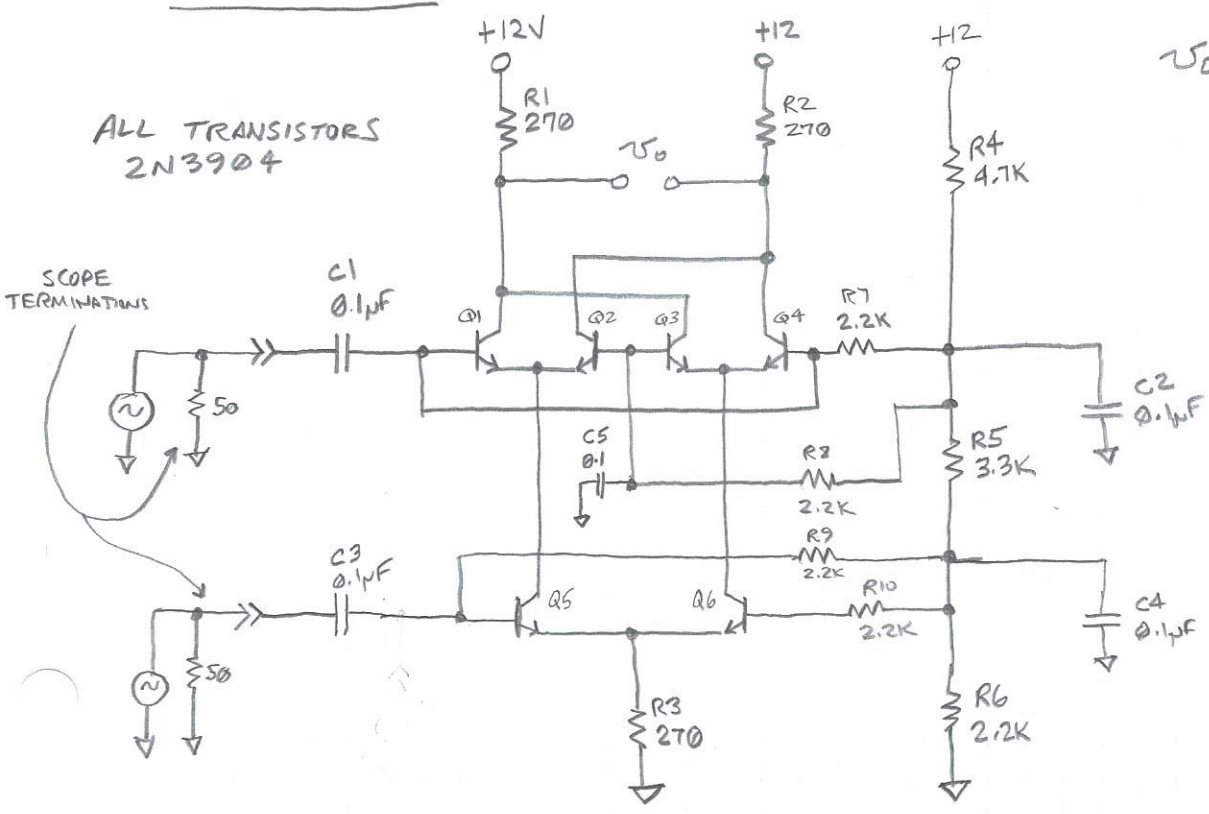

$V_0 = V_{R1} - V_{R2}$

ALL TRANSISTORS 2N3904

SCOPE TERMINATIONS