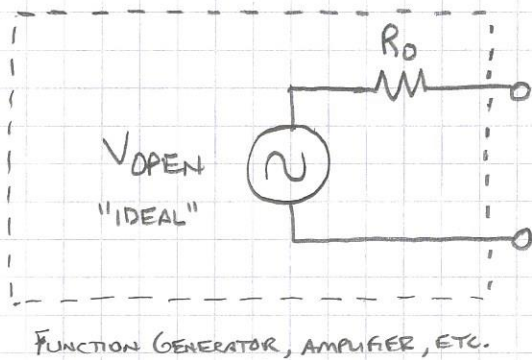



HOW TO MEASURE OUTPUT IMPEDANCE



- IN GENERAL - MEASURE THE CHANGE IN OUTPUT VS. CHANGING LOAD RESISTANCE

- IN MANY CASES YOU CAN USE THE "OPEN" & "LOADED" CASE

① MEASURE "OPEN CIRCUIT"

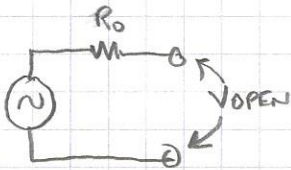

③ CALCULATE R_O


$$R_O = R_L \left(\frac{V_{OPEN}}{V_L} - 1 \right)$$

≡ SPECIAL CASE ≡

$$V_L = \frac{V_{OPEN}}{2} \text{ WHEN } R_L = R_O$$

YOU CAN VARY R_L UNTIL $V_L = \frac{V_{OPEN}}{2}$
AND MEASURE R_L


② MEASURE "LOADED" CIRCUIT

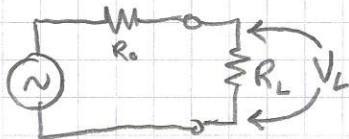

IN SOME CASES - THIS MIGHT NOT WORK WELL

- IF AMPLIFIER / CIRCUIT / ETC DOESN'T WORK WELL UNLOADED
- IF OUTPUT IMPEDANCE CHANGES WITH BIG CHANGES IN LOAD
- ETC.

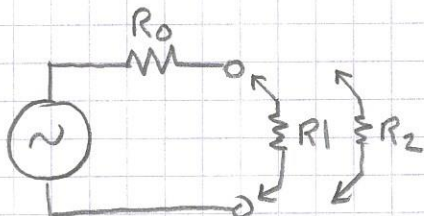- IN THESE CASES - MEASURE OUTPUT WITH TWO DIFFERENT LOADS



$$R_O = \frac{R_1 - R_1 \cdot \frac{V_1}{V_2}}{\frac{V_1}{V_2} - \frac{R_1}{R_2}}$$