
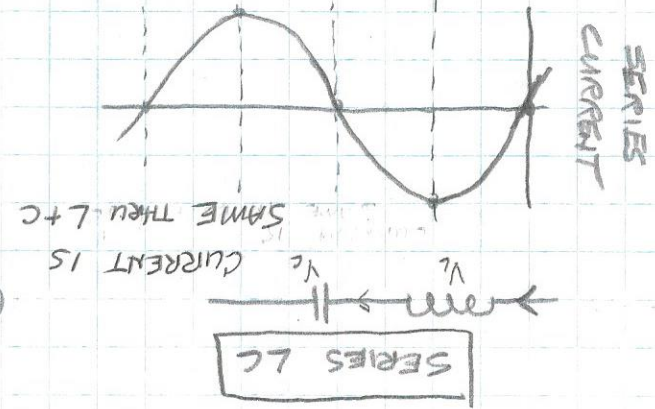




A LOOK AT LC RESONANCE

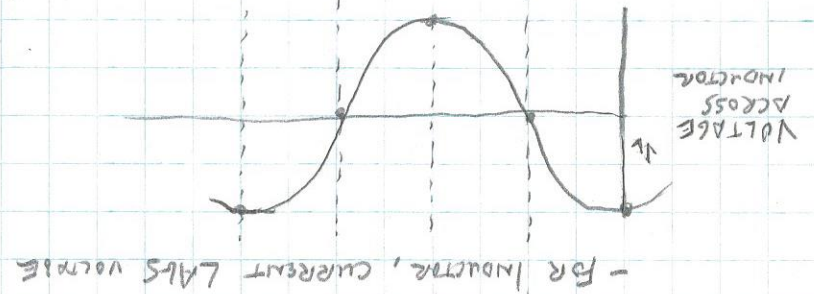


... LET'S LOOK AT VOLTAGES



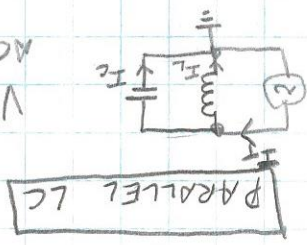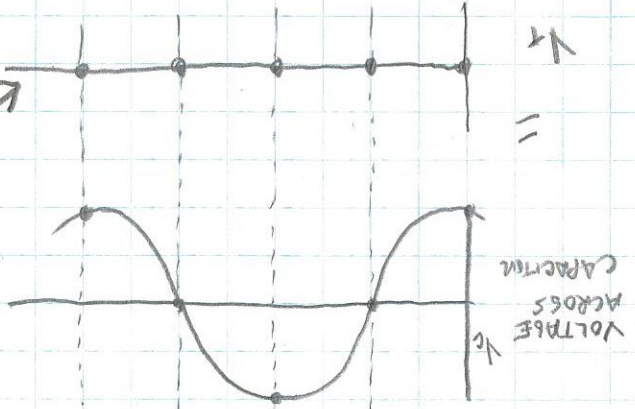
SERIES L-C LOOKS LIKE A SHORT CIRCUIT AT RESONANCE



VOLTAGE ACROSS L+C

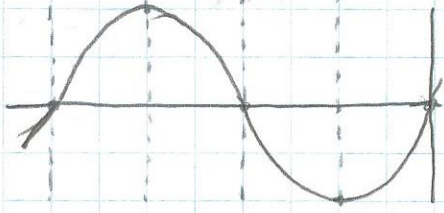

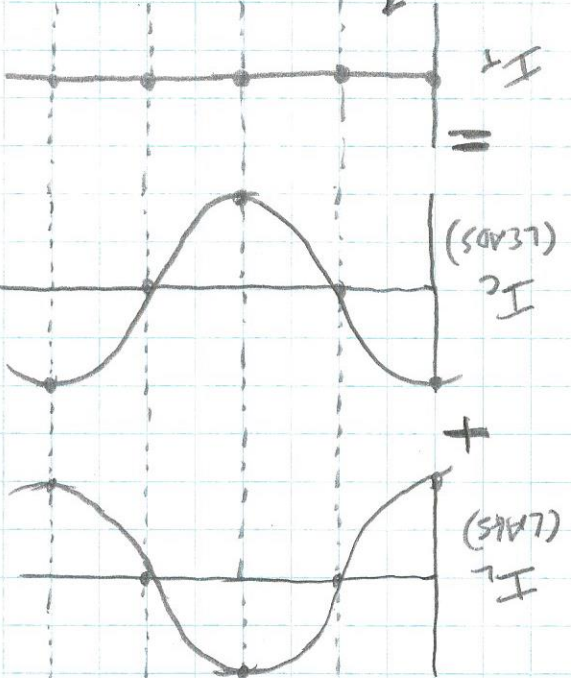PARALLEL LC LOOKS LIKE AN OPEN CIRCUIT AT RESONANCE




VOLTAGE IS SAME ACROSS L+C

RESONANT CIRCUITS - PART II

VIDEO 55

W2AEW (2)

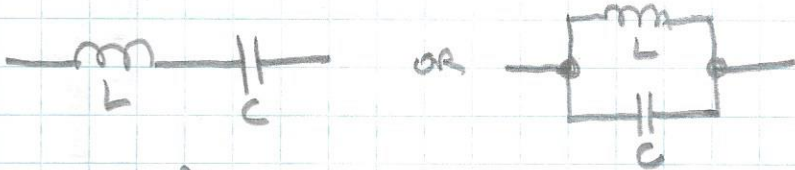

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

RESONANCE IS WHEN $X_L = X_C$

OR,,

$$2\pi fL = \frac{1}{2\pi fC}$$

$$L = \frac{1}{(2\pi)^2 f^2 C}$$

SOLVE FOR L

$$L = \frac{1}{39.48 \cdot f^2 \cdot C}$$

SOLVE FOR C

$$C = \frac{1}{39.48 \cdot f^2 \cdot L}$$

SOLVE FOR f

$$f = \frac{1}{2\pi \cdot \sqrt{LC}}$$

IN AN IDEAL WORLD, THERE ARE INFINITE COMBINATIONS OF L & C VALUES THAT WILL RESONATE AT ANY GIVEN FREQUENCY.

EXAMPLE: $f = 10\text{MHz}$ RESONANT FREQUENCY

START WITH 1pF CAPACITOR,,,

$$f_R = 10\text{MHz} \rightarrow L = \underline{253\mu\text{H}}$$

OR

$$\underline{1\mu\text{F}}$$
 CAPACITOR, $L = \underline{253\text{pH}}$

$$1\text{pF} \begin{cases} \approx 253\mu\text{H} \\ = \end{cases}$$

$$1\mu\text{F} \begin{cases} \approx 253\text{pH} \end{cases}$$

- PRACTICAL, NON-IDEAL FACTORS DETERMINE WHAT TO DO,,,