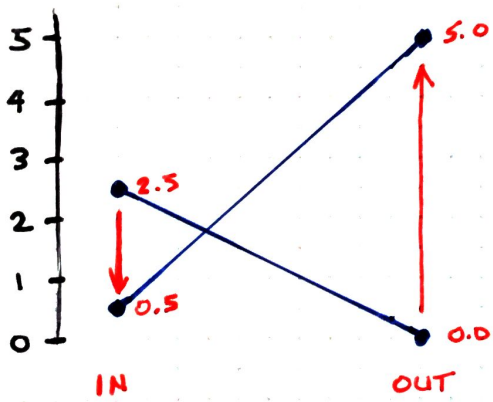



SENSOR SIGNAL CONDITIONING WITH AN OP AMP (A PRACTICAL EXAMPLE)

SENSOR OUTPUT	DESIRED OUTPUT
+2.5V	0V
+0.5V	5V



A GRAPHICAL VIEW

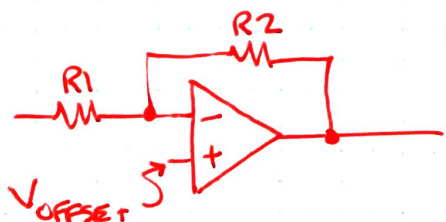- A -2V CHANGE AT INPUT → +5V CHANGE AT OUTPUT
- INVERTING OP GAIN STAGE
- GAIN = -2.5x



$$\frac{R2}{R1} = 2.5$$

R1 + R2 SELECTION CRITERIA...

(2)
WZAEW

- SENSOR OUTPUT IMPEDANCE (LOADING)
- LOAD AT OP AMP OUTPUT
- OTHER FACTORS.

PICK $R1 = 33K$

THEN $R2 = R1 * 2.5$

$R2 = 82K$

(USING NEAREST STD VALUES)

V_{OFFSET} = VOLTAGE NEEDED AT NON-INVERTING INPUT TO SHIFT O/P UP TO DESIRED RANGE

- GRAPH GIVES THE VALUE!
- OR - SIMPLE CALCULATION...

- CONSIDER ONE OF THE STATES

$2.5V \text{ IN} \rightarrow 0V \text{ OUT}$

- SIMPLE VOLTAGE DIVIDER



$$\frac{(2.5V) R2}{R1 + R2} =$$

$V_{\text{offset}} = 1.78V$

FINISH DESIGN DETAILS

③
WZAEW

$$\underline{V_{CC} = 5V}$$


- NEED SINGLE-SUPPLY OP AMP WITH RAIL-RAIL OUTPUT SWING
- INPUT COMMON-MODE INCLUDES 1.78V

- USING MCP6002

- V_{SUPPLY} MAX 6V
- R-R INPUT + OUTPUT
- DIP PACKAGE

GENERATE $V_{OFFSET} = 1.78V$

- USE RESISTOR DIVIDER

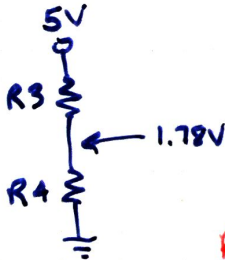

$$V_{R3} = 5 - 1.78 = 3.22$$

$$V_{R4} = 1.78$$


$$\frac{R3}{R4} = \frac{V_{R3}}{V_{R4}} = \frac{3.22}{1.78} = 1.8$$

PLAY WITH STD VALUES...


$$R3 = 27K$$

$$R4 = 15K$$

FINAL CIRCUIT

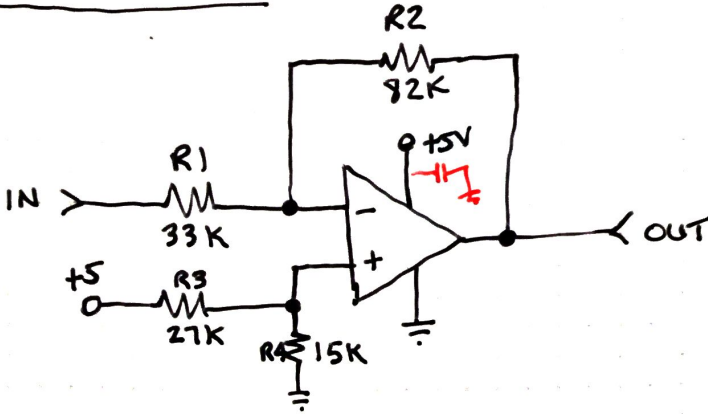

SIMULATE SENSER WITH...

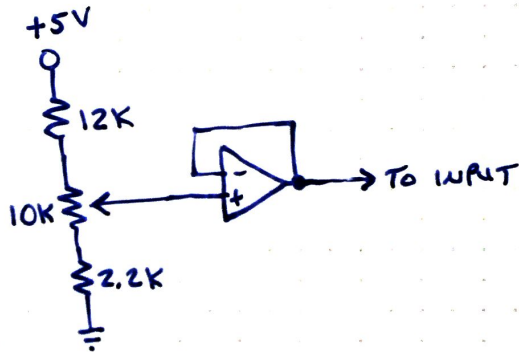

FINAL THOUGHTS

- POWER SUPPLY DECOUPLING (ALWAYS)
- TRIMMERS TO TRIM GAIN + V_{OFFSET}
- INPUT CURRENT CONSIDERATIONS
- INPUT OFFSET TRIMMING