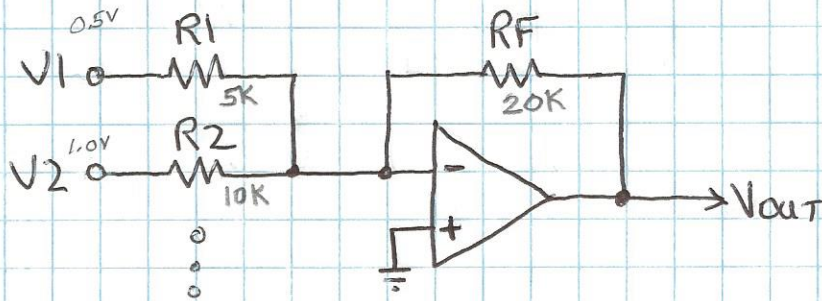


# THE OP AMP SUMMING AMPLIFIER

(LESSON IN SUPERPOSITION)

## ① INVERTING CONFIGURATION

W2AEW




$$V_{out} = -\frac{V_1 \cdot R_f}{R_1} - \frac{V_2 \cdot R_f}{R_2} \dots$$

## CHARACTERISTICS

- EACH INPUT "SEES" A FIXED LOAD TO "VIRTUAL GROUND"
- NO INTERACTION FROM ONE INPUT TO ANOTHER
- EASY TO CALCULATE RESPONSE WITH ADDITIONAL INPUTS

## ② NON-INVERTING CONFIGURATION

W2AEW

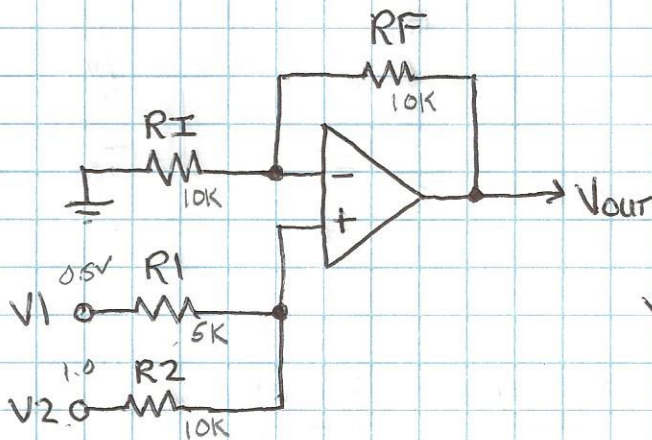

$$V_{out} = (V_+) \left( \frac{R_F}{R_I} + 1 \right)$$

(TWO INPUT CASE)

$$V_{out} = \left( \frac{R_F}{R_I} + 1 \right) \cdot \left( V_1 \cdot \frac{R_2}{R_1 + R_2} + \frac{V_2 \cdot R_1}{R_1 + R_2} \right)$$

### CHARACTERISTICS

- THE "LOAD" ON EACH INPUT DEPENDS ON THE OTHER INPUTS
- THERE CAN BE INTERACTION BETWEEN INPUTS, DEPENDING ON SOURCE'S OUTPUT IMPEDANCE
- A LITTLE MORE COMPLICATED TO CALCULATE

(SOMETIMES NICER TO DO THE "INVERTED" CASE, THEN FOLLOW THIS WITH ANOTHER "INVERT" STAGE)