

SMITH CHART EXAMPLE

W2AEW
①

- IMPEDANCE
 - REFLECTION COEFFICIENT
 - VSWR, RETURN LOSS
 - TRANSMISSION LINE EFFECTS
-



... OPERATING AT 14.2 MHz ...

$$Z_{LOAD} = R + jX$$

$$R = 33 \Omega$$

$$X_C = -\frac{1}{2\pi f C} \quad (\text{NEGATIVE BECAUSE CAPACITIVE})$$

$$\underline{Z_{LOAD} = 33 - j51}$$

TO PLOT ON THE SMITH CHART: NORMALIZE TO Z_0

(Z_0 IS OUR SYSTEM IMPEDANCE = 50Ω)

$$Z_L = \frac{Z_{LOAD}}{Z_0}$$


$$Z_L = \frac{33 - j51}{50}$$

$$\boxed{Z_L = 0.66 - j1.02}$$


↙ PLOT THIS!

$Z_L = 0.66 - j1.02$

Smith Chart

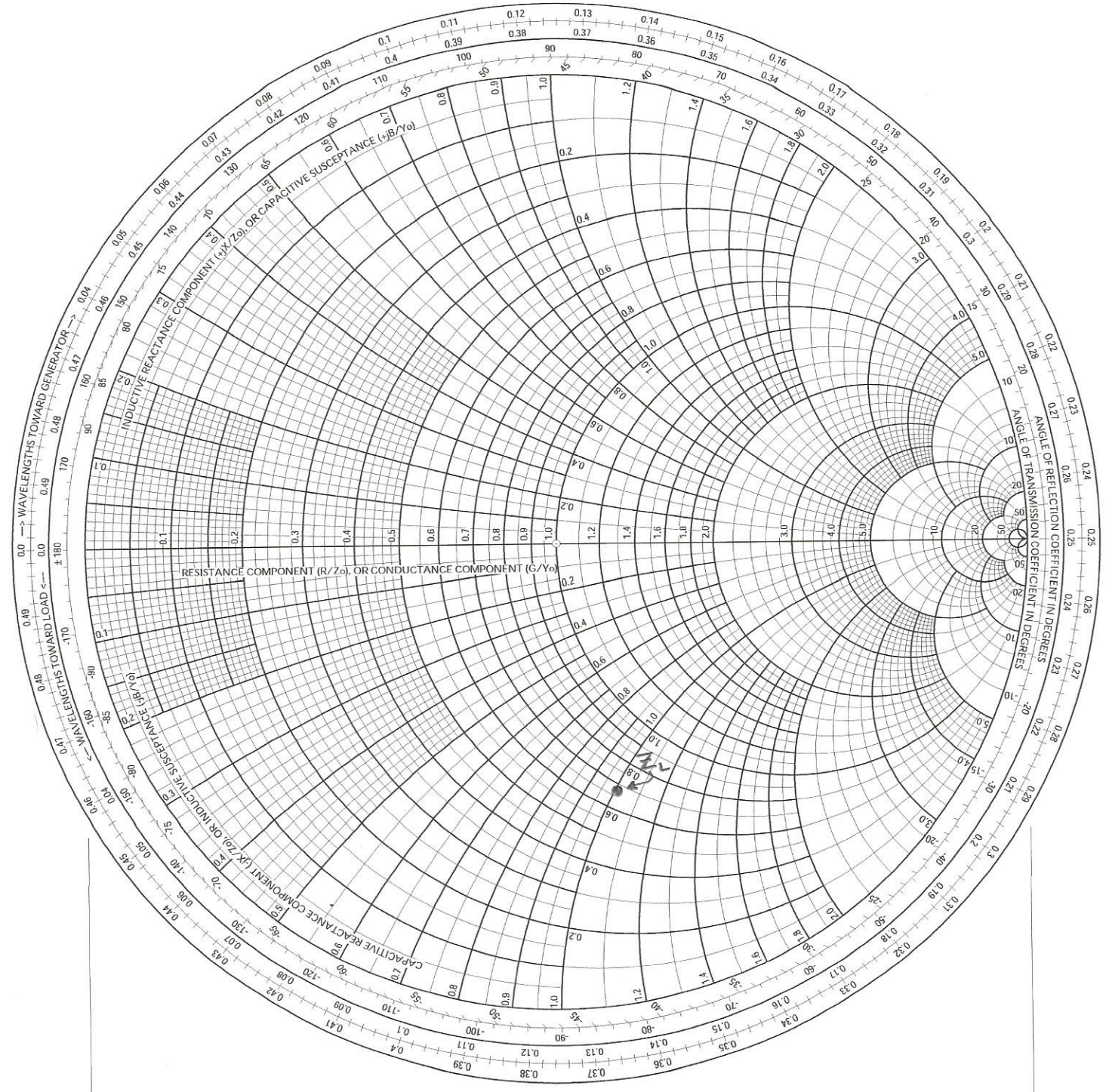

RADIALLY SCALED PARAMETERS

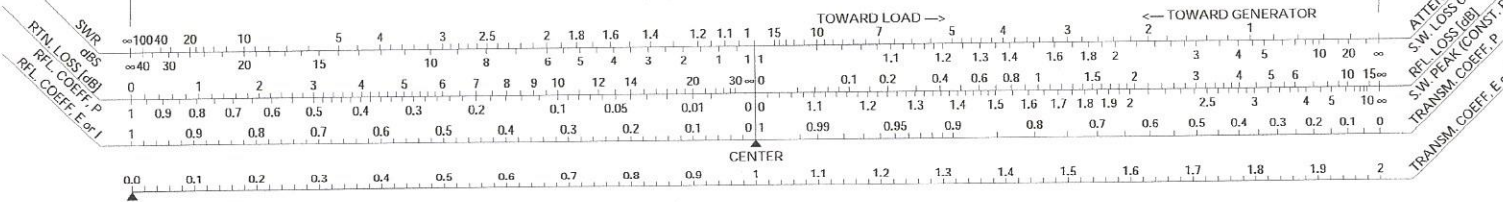

ONCE WE KNOW Z_{LOAD} ($33 - j51$)...

... WE "COULD" CALCULATE :

- COMPLEX REFLECTION COEFFICIENT (VOLTAGE OR CURRENT)

$$\Gamma = \frac{Z_{LOAD} - Z_0}{Z_{LOAD} + Z_0}$$

NOTE: $Z + \Gamma$ ARE COMPLEX VALUES

- REFLECTION COEFFICIENT (MAGNITUDE)

$$\rho = |\Gamma|$$

- VOLTAGE STANDING WAVE RATIO

$$VSWR = \frac{1 + \rho}{1 - \rho}$$

- POWER REFLECTION COEFFICIENT

$$\Gamma_{PWR} = |\Gamma|^2$$

- RETURN LOSS


$$RL = 20 \log_{10} \left(\frac{VSWR + 1}{VSWR - 1} \right)$$

$$= 10 \log_{10} (\Gamma_{PWR})$$


OR, SIMPLY READ THEM OFF THE SMITH CHART !

$Z_L = 0.66 - j1.02$

Smith Chart

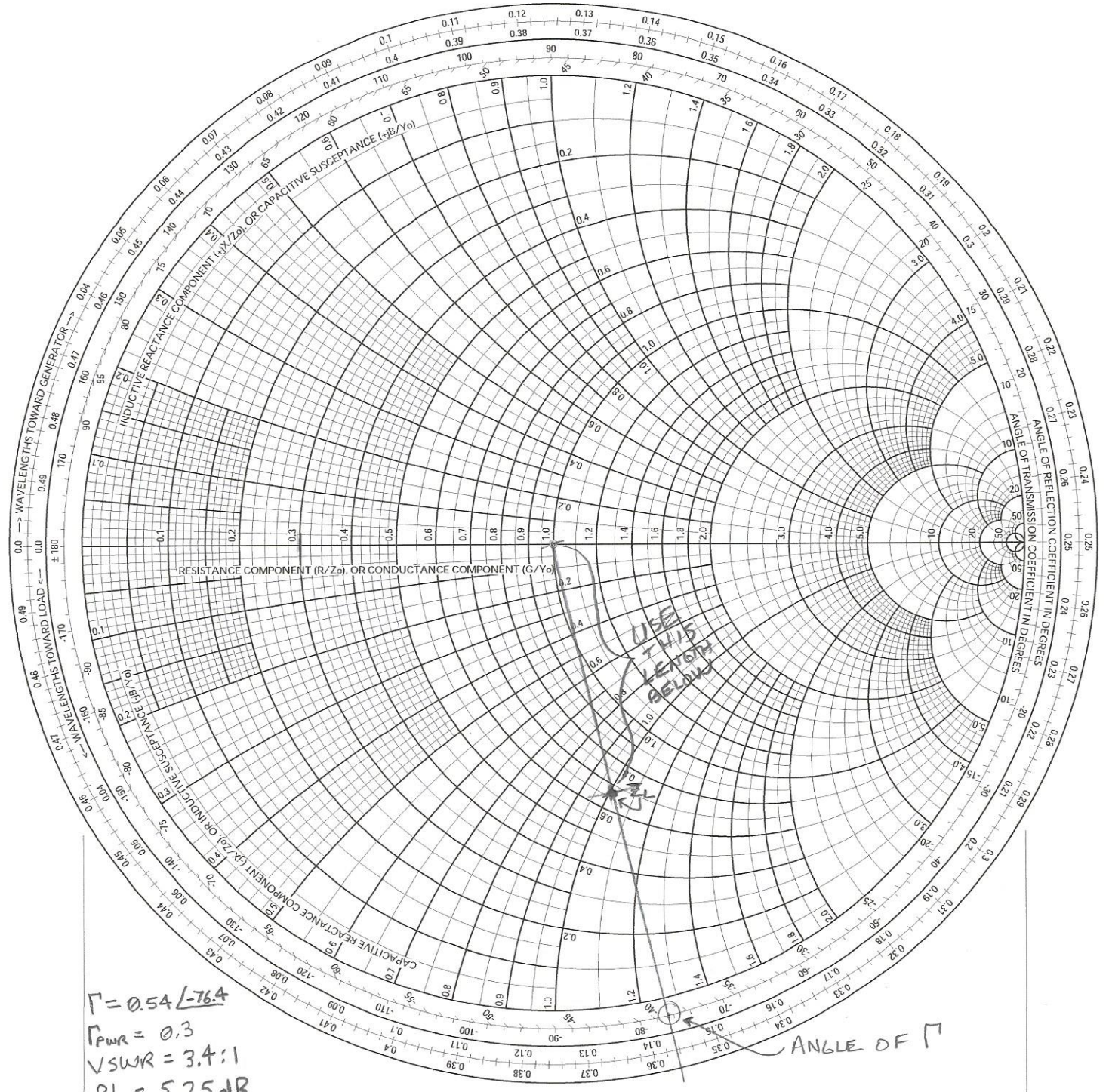

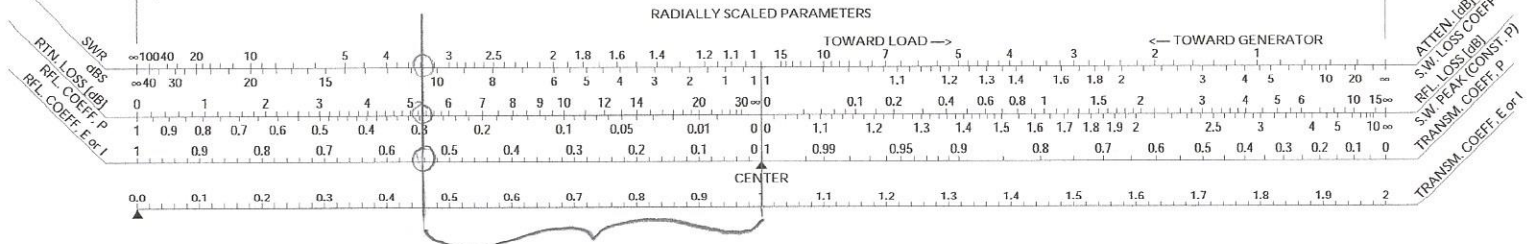$\Gamma = 0.54 \angle -76.4$
 $\Gamma_{PWR} = 0.3$
 $V_{SWR} = 3.4:1$
 $RL = 5.25 \text{ dB}$



TRANSMISSION LINE EFFECTS

W2AEW

③

- WHEN YOU ADD A Z_0 TRANSMISSION LINE BETWEEN THE SOURCE (GENERATOR) AND THE LOAD...

- THE VSWR SEEN BY THE SOURCE IS CONSTANT* (IGNORING LOSSES)

- THE IMPEDANCE SEEN BY THE SOURCE CHANGES

[EXAMPLE: Z_{LOAD} OF 25Ω OR 100Ω
BOTH RESULT IN $VSWR = 2.0:1$]

- SAME HOLDS TRUE FOR COMPLEX Z ...

- CALCULATION OF Z_{INPUT} IS UGLY...

... SO WE USE THE MAGIC OF SMITH CHART !

TRANSMISSION LINE LENGTH ON THE SMITH CHART

P3

- ROTATING AROUND CHART REPRESENTS ADDING/SUBTRACTING LINE LENGTH

- COMPLETE TRIP AROUND CHART = $\frac{1}{2}$ WAVELENGTH (λ)

∴ $Z_{INPUT} = Z_{LOAD}$ WHEN LENGTH IS MULTIPLE OF $\frac{\lambda}{2}$
(REGARDLESS OF Z_0 & Z_{LOAD})

- HALFWAY AROUND CHART = $\frac{\lambda}{4}$ (QUARTER WAVELENGTH)

- $\frac{\lambda}{4}$ LINE THAT IS OPEN AT END LOOKS LIKE A SHORT

- $\frac{\lambda}{4}$ LINE THAT IS SHORTED AT END LOOK LIKE OPEN

- FOR ANY Z , DRAW CIRCLE THRU Z TO SHOW HOW Z_{IN} VARIES w/ LINE LENGTH

Smith Chart


$Z_L = 0.66 - j1.02$

$\Gamma = 0.54 \angle -76.4^\circ$

$\Gamma_{pwr} = 0.3$

VSWR = 3.4 : 1

RL = 5.25 dB

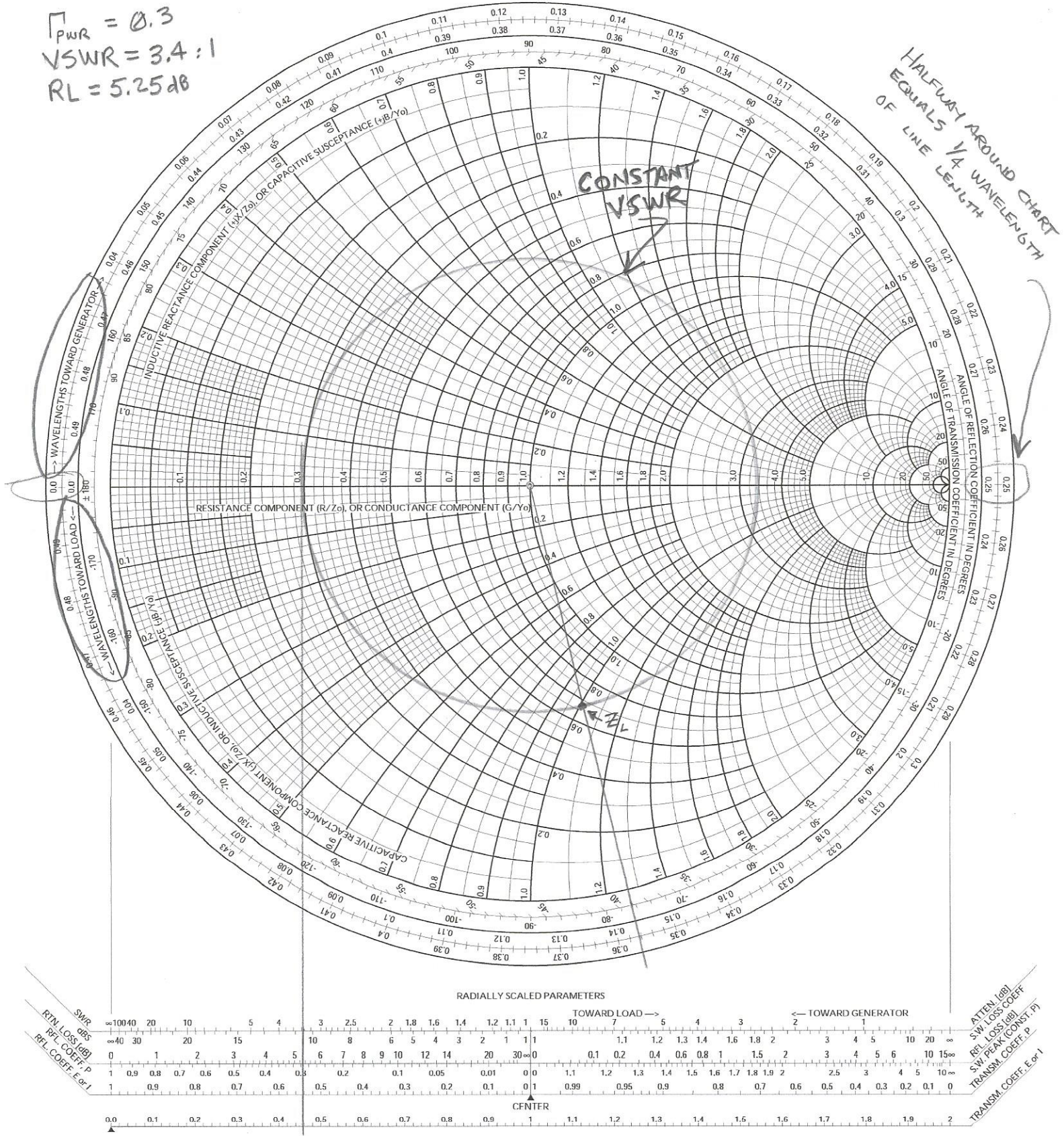

HALFWAY AROUND CHART
EQUALS 1/4 WAVELENGTH
OF LINE LENGTH

TRANSMISSION LINE EXAMPLE

$$f = 14.2 \text{ MHz}$$

$$\text{COAX VELOCITY FACTOR} = 0.66$$

$$\text{COAX LENGTH} = 1 \text{ METER}$$

$$\lambda_{\text{FREE SPACE}} = \frac{300}{14.2} = 21.13 \text{ m}$$

$$\lambda_{\text{COAX}} = \text{V.F.} * \lambda_{\text{FREE SPACE}}$$

$$= 0.66 * 21.13 \text{ m}$$

$$\lambda_{\text{COAX}} = 13.95 \text{ m}$$

$$\therefore 1 \text{ METER OF COAX IS } \frac{1}{13.95} = \underline{\underline{0.0717\lambda}}$$

... LETS GO TO THE SMITH CHART...

P4

COMMON USE CASE

- MEASURE Z_{INPUT} AT THE TRANSMITTER
- KNOWING LINE LENGTH, ROTATE "TOWARD LOAD" TO GET Z_{LOAD}
- DESIGN MATCHING NETWORK TO PLACE AT ANTENNA FEEDPOINT
(KEEPS VSWR ON THE LINE NEAR 1:1 TO MINIMIZE LOSS)

Smith Chart


$$Z_L = 0.66 - j1.02$$

$$\Gamma = 0.54 / 76.4^\circ$$

$$\Gamma_{pwr} = 0.3$$

$$VSWR = 3.4:1$$

$$RL = 5.25dB$$

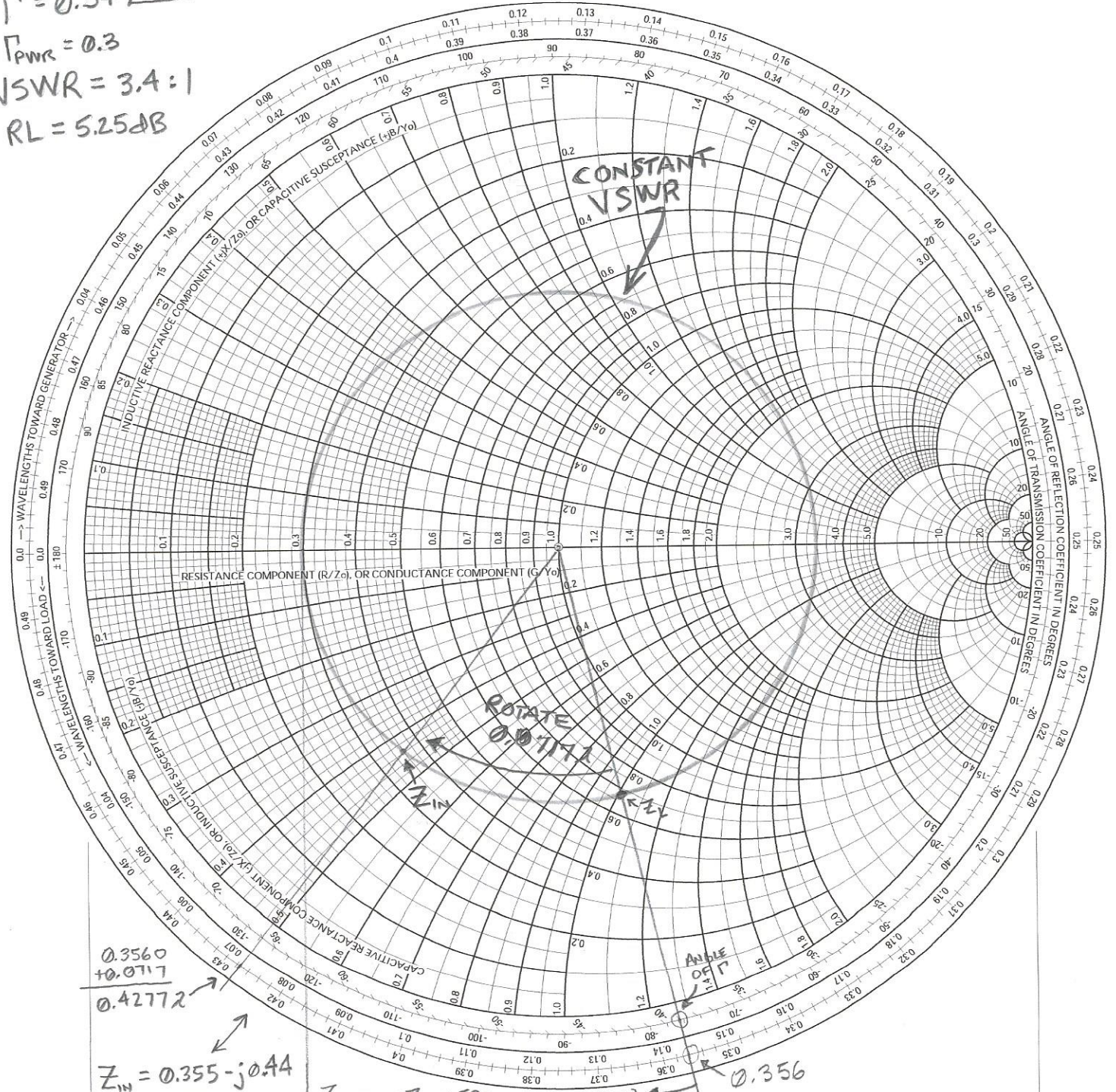

$$0.3560 + j0.0717$$

$$0.42772$$

$$Z_{IN} = 0.355 - j0.44$$

$$Z_{INPUT} = 17.8 - j22$$

$$Z_{INPUT} = Z_{IN} * 50\Omega$$

RADIALLY SCALED PARAMETERS

