



DIODE REVERSE RECOVERY TIME

IN2AEW

#201

- WHEN A DIODE IS SWITCHED FROM FORWARD TO REVERSE BIAS, A REVERSE CURRENT FLOWS FOR A SHORT TIME.

↓
I.E. IT DOESN'T BLOCK LIKE A DIODE!

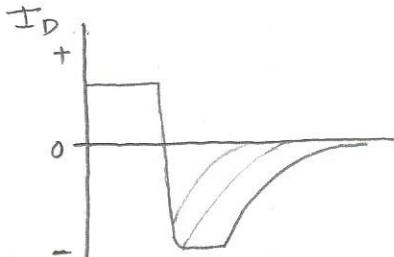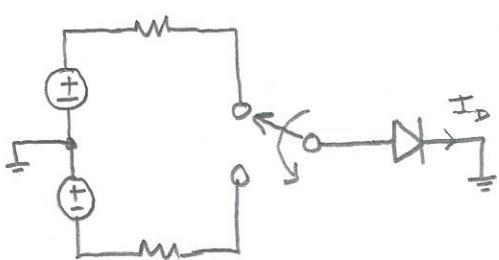

- DUE TO STORED CHARGE (SPACE CHARGE) IN THE JUNCTION WHICH TAKES TIME TO REMOVE & RECOMBINE
- REVERSE RECOVERY TIMES CAN RANGE FROM A FEW μs OR LESS, TO A FEW μs OR MORE - DEPENDENT ON THE DEVICE & CURRENT LEVELS

- ↓ - CAN BE A SIGNIFICANT SOURCE OF LOSS IN SWITCHING REGULATORS
 ↑ - CAN BE BENEFICIAL IN SOME SIGNAL SWITCHING APPLICATIONS
 (SEE VIDEO ON PIN DIODES & RF SWITCHING)

QUICK MEASUREMENT SETUP

