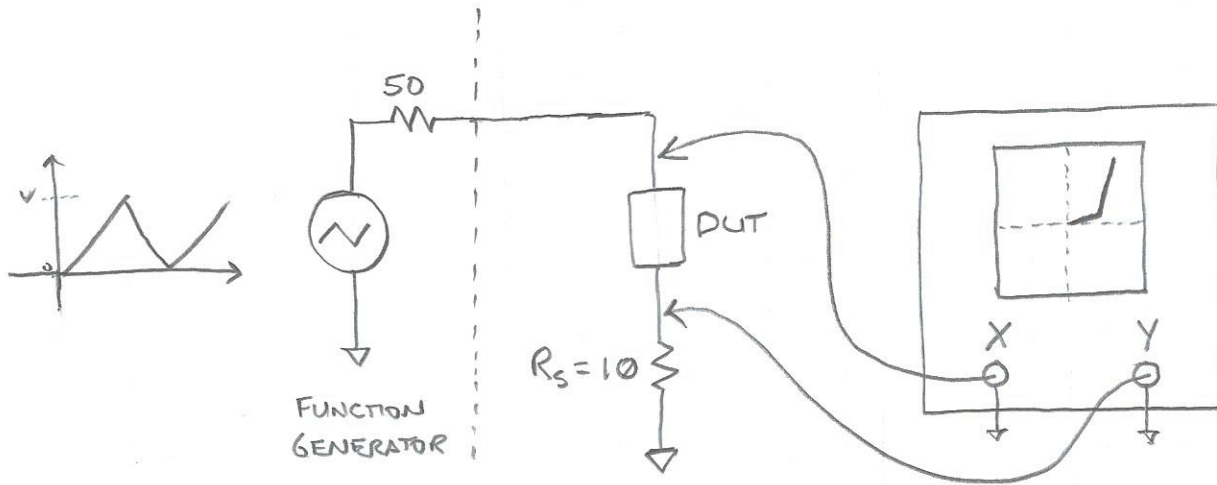


SIMPLE V-I TRACER



(NOT PERFECT BECAUSE CURRENT SENSE Y IS ADDED TO DUT VOLTAGE X)

- BETTER WOULD BE ...

- CURRENT PROBE FOR Y
- OR
- SWAP DUT & R_s , USE DIFFERENTIAL PROBE ACROSS R_s FOR Y
- OR
- USE MATH TO SUBTRACT V_{R_s} FROM V_x