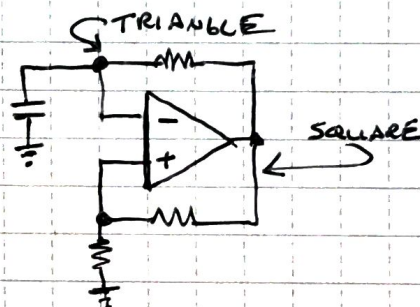


CIRCUIT FUN: THE TWIN-TEE OSCILLATOR
 + ONLY R'S & C'S (NO INDUCTORS)
 + SINUSOIDAL OUTPUT


- NOT EASILY TUNABLE
- SOME MINOR TRIMMING FOR LOWEST DISTORTION

^{"RC"}
OTHER OP AMP BASED OSCILLATORS

- RELAXATION OSCILLATOR
- NOT SINUSOIDAL




- RC PHASE SHIFT OSCILLATOR

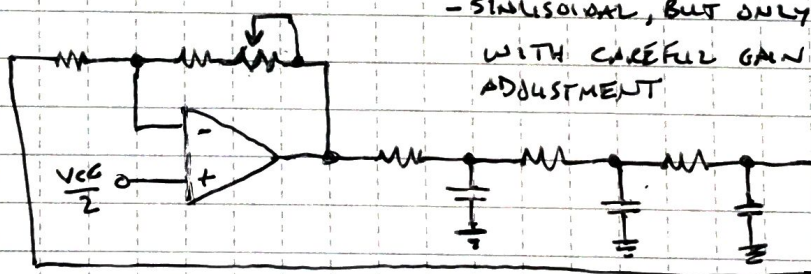


- SINUSOIDAL, BUT ONLY WITH CAREFUL GAIN ADJUSTMENT

- WIEN-BRIDGE OSCILLATOR


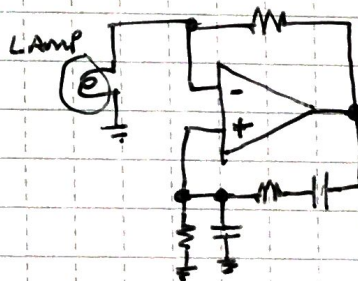
- SINUSOIDAL, BUT NEEDS SPECIAL GAIN CONTROL FOR LOW DISTORTION
- LAMP
- A/GC w/ FET, ETC.





THE TWIN-TEE NETWORK

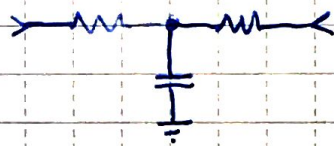


LOW-PASS NETWORK

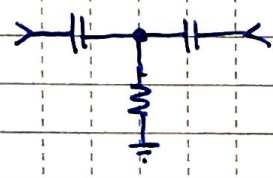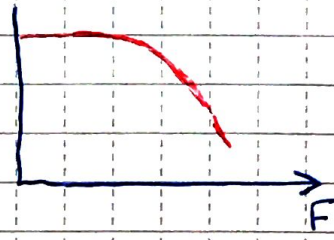

HIGH-PASS NETWORK

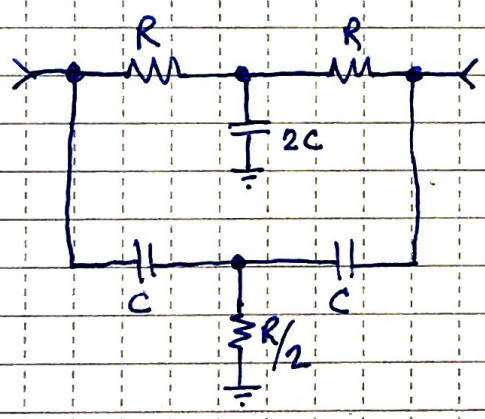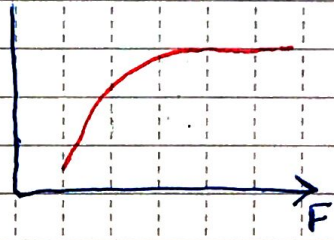


NOTCH FILTER

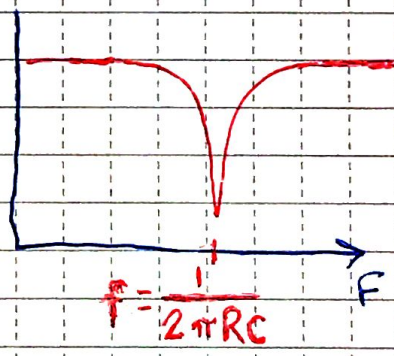

TWIN-TEE OP AMP OSCILLATOR

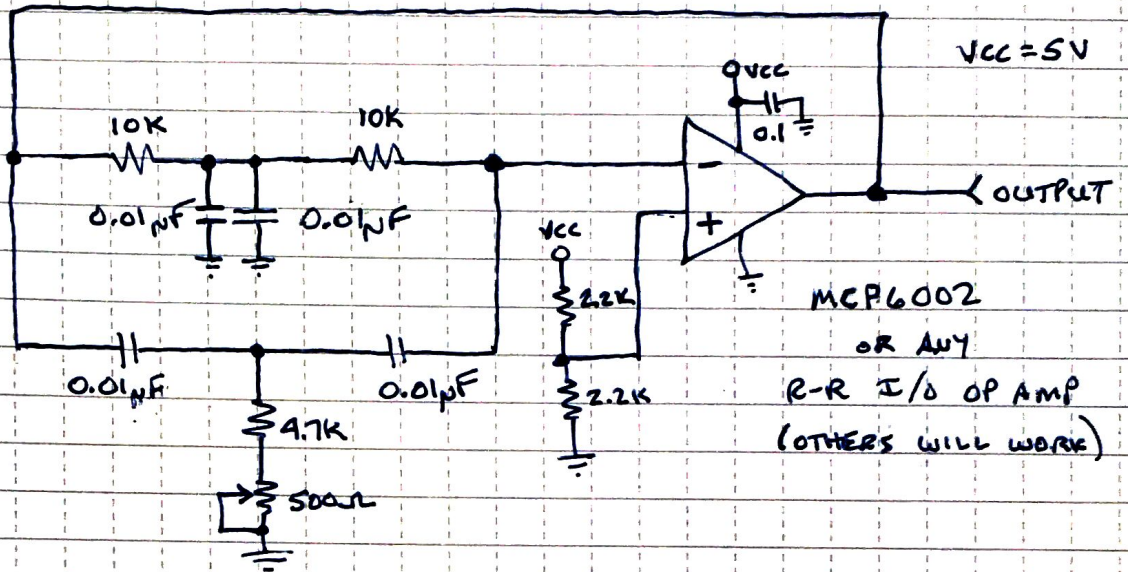- PUT TWIN-TEE "NOTCH" IN FEEDBACK LOOP
(MAKES IT A "PEAKING" CIRCUIT)



- EASY TO GET $\ll 1\%$ THD