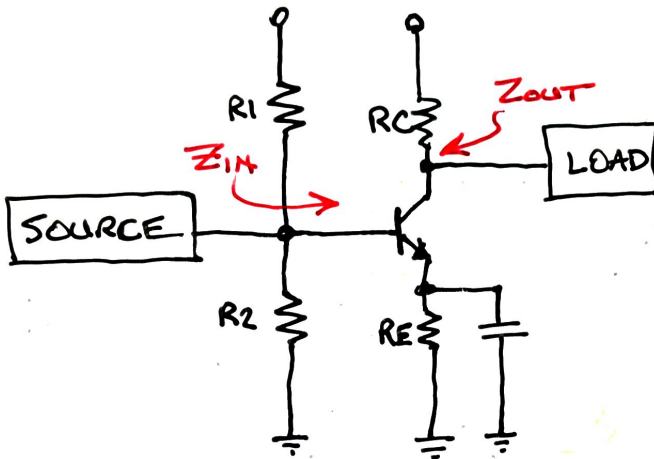



INPUT & OUTPUT IMPEDANCE OF COMMON-EMITTER AMPLIFIERS



WHY WE CARE...



- THE **INPUT IMPEDANCE** MAY LOAD DOWN THE SOURCE THAT IS PROVIDING THE INPUT SIGNAL
- THE **LOAD** MAY LOAD-DOWN THE OUTPUT (**Z_{out}**) AND CHANGE THE GAIN OF THE AMPLIFIER

TEST CIRCUIT #1

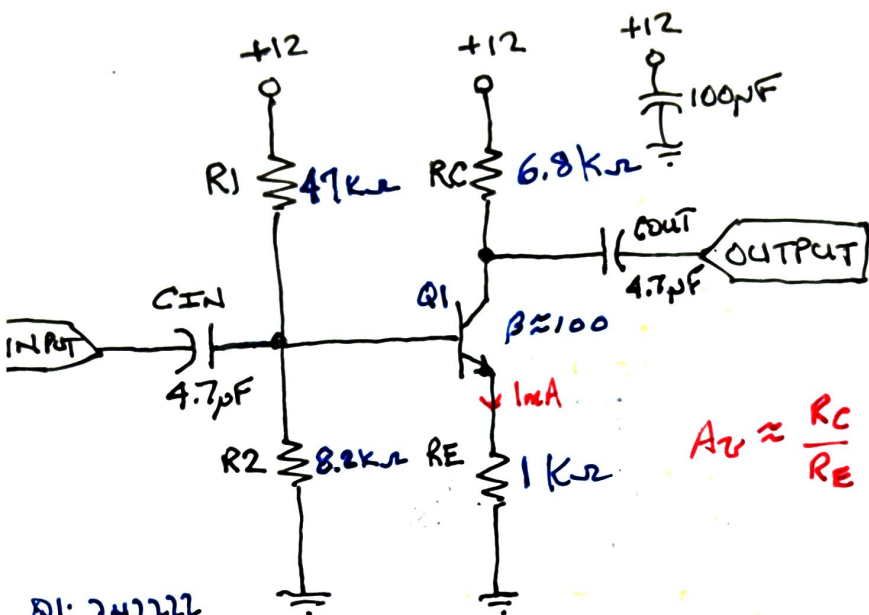


$$A_v \approx \frac{R_C}{R_E}$$

Q_1 : 2N2222
2N3904
ETC.

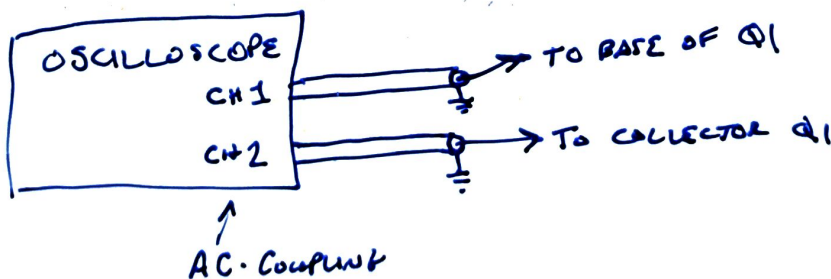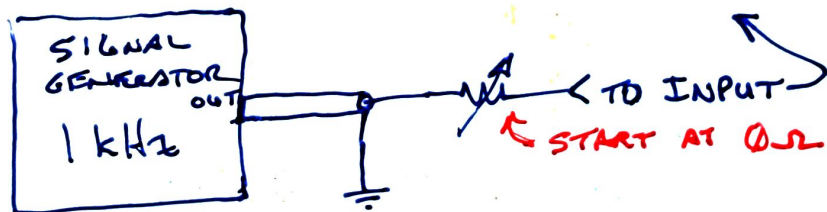

- LOOK AT OUTPUT IMPEDANCE

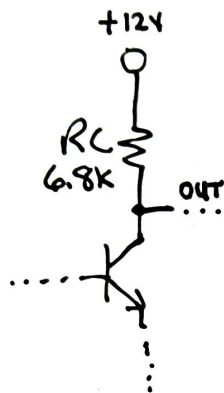

- COLLECTOR "LOOKS LIKE" A CURRENT SOURCE
 $\therefore$ VERY HIGH IMPEDANCE

- OUTPUT IMPEDANCE IS BASICALLY JUST R_C

- IMPLICATIONS - ANY LOAD CONNECTED APPEARS IN PARALLEL TO R_C

- THIS REDUCES R_C

- THIS, REDUCES GAIN


$$\left(\approx \frac{R_C}{R_E} \right)$$

THUS: ANYTHING CONNECTED TO OUTPUT CAN AFFECT GAIN

- INCLUDING A CASCADED AMPLIFIER!

- SO - INPUT IMPEDANCE OF AMPLIFIERS MATTERS ALSO!

INPUT IMPEDANCE

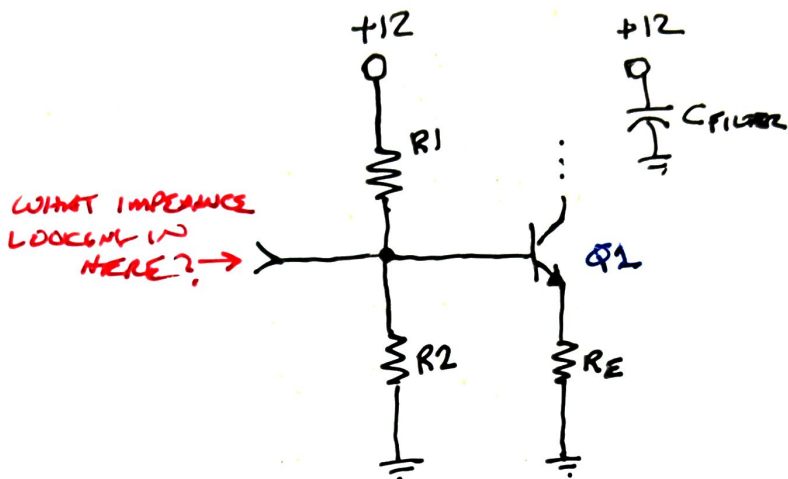

STEP 1:

$R1 \parallel R2$ ARE IN PARALLEL DUE TO C_{FILTER}

STEP 2:

THIS COMBO IS IN PARALLEL WITH INPUT IMPEDANCE OF THE BASE OF Q1


THIS IS TYPICALLY DOMINATED BY:

$$\boxed{\beta * R_E} * (\text{ACTUALLY } (\beta + 1) * R_E)$$

THEREFORE: INPUT IMPEDANCE IS

$$\approx R1 \parallel R2 \parallel \beta * R_E$$

MEASUREMENT OF INPUT IMPEDANCE

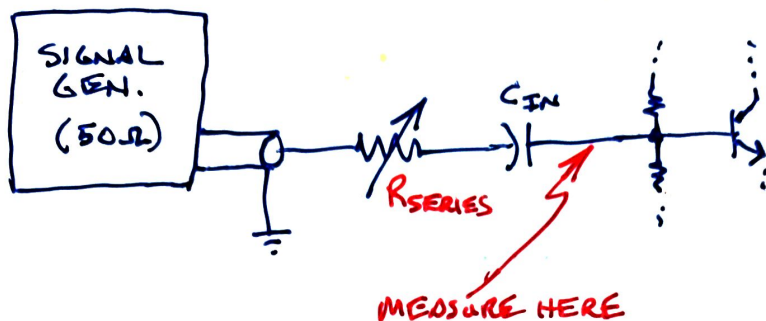


- ADJUST R_{series} UNTIL MEASURED SIGNAL DROPS TO $\frac{1}{2}$ OF VALUE WHEN $R_{\text{series}} = 0\Omega$

THE EFFECT OF INPUT IMPEDANCE IS NOT REDUCING GAIN, BUT RATHER ATTENUATING THE INPUT SIGNAL BEFORE IT IS AMPLIFIED.

- OF COURSE, IT COULD BE DOING THIS BY REDUCING GAIN OF THE PREVIOUS STAGE OF CIRCUIT.

ADVANCED TOPIC

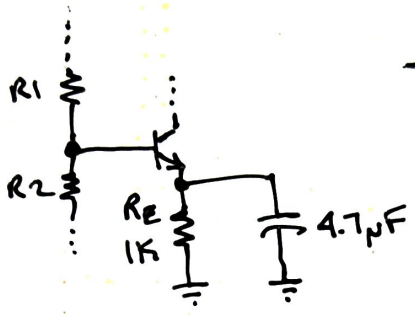- WHAT IF THE EMITTER IS BYPASSED TO MAXIMIZE GAIN?



- WHAT IS THE INPUT IMPEDANCE OF THE BASE IN THIS CASE?

- FROM MY PREVIOUS VIDEOS, WE KNOW THE SMALL SIGNAL EMITTER RESISTANCE (r_e)

IS EQUAL TO:
$$\frac{1}{g_m} = \frac{V_T}{I_C}$$
 (V_T TYPICALLY 26mV @ ROOM TEMP.)

- THUS, INPUT IMPEDANCE OF BASE IS $\beta * r_e$ *

OVERALL WPUT IMPEDANCE:

$$R_1 \parallel R_2 \parallel (\beta * r_e)$$

CALCULATIONS

OUTPUT IMPEDANCE

$$R_C = 6.8K$$

$$R_{LOAD} = 10K$$

$$6.8K \parallel 10K \approx 4K\Omega$$

$$A_v = \frac{4K}{1K} \approx 4$$

INPUT IMPEDANCE

$$47K \parallel 8.2K \approx 7K\Omega$$

$$\beta \approx 100$$

$$\beta * R_E = 100K\Omega$$

$$7K \parallel 100K \approx \underline{6.5K\Omega}$$

INPUT IMPEDANCE w/ EMITTER BYPASSED

$$47k \parallel 8.2k \parallel \beta * 26\Omega$$

$$\approx 1.9K\Omega$$