

THIS CIRCUIT IDENTICAL FOR EACH OUTPUT YOU WANT A CONTACT CLOSURE. EQUIP 1 TO 16 OUTPUTS AS DESIRED.

NOTE 1: A VALID DTMF TONE MUST BE A MINIMUM OF 35MS IN DURATION.

NOTE 2: EACH TIME A VALID DTMF TONE IS DETECTED, THAT OUTPUT STAYS ON (RELAY CONTACTS CLOSED) UNTIL ANOTHER TONE IS RECEIVED. FOR THAT REASON, DO NOT EQUIP OUTPUT Y0 (THE "D" TONE). SEND A "D" TONE AS A DISCONNECT TONE TO OPEN ANY CLOSED CONTACTS.


NOTE 3: VALUE OF BASE RESISTOR IN DRIVER CIRCUIT WILL CHANGE DEPENDING ON RELAY COIL RESISTANCE. THIS IS DUE TO THE CURRENT SOURCE CAPABILITIES OF THE '4514  
 For relay coils with a resistance of 130 ohm R=1200 ohm  
 For relay coils with a resistance of 50 ohm R=470 ohm

75T204 Logic Table					74HC4514 Logic Table (74HC4515 is the same but outputs inverted from this table)																						
DTMF DIGIT	D8	D4	D2	D1	Inputs				Outputs												DTMF DIGIT						
					E	D	B	C	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7	Y8	Y9	Y10	Y11	Y12	Y13	Y14	Y15		
1	1	0	0	0	H	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
2	0	1	0	0	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	D
3	1	1	0	0	L	H	L	L	L	L	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	1
4	0	0	1	0	L	L	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	2
5	1	0	1	0	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	3
6	0	1	1	0	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	4
7	1	1	1	0	L	L	L	H	L	L	L	L	H	L	L	L	L	L	L	L	L	L	L	L	L	L	5
8	0	0	0	1	L	H	L	H	L	L	L	L	L	L	H	L	L	L	L	L	L	L	L	L	L	L	6
9	1	0	0	1	L	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	7
0	0	1	0	1	L	H	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	8
*	1	1	0	1	L	L	L	H	L	L	L	L	L	L	L	L	L	L	H	L	L	L	L	L	L	L	9
#	0	0	1	1	L	H	L	H	L	L	L	L	L	L	L	L	L	L	L	H	L	L	L	L	L	L	0
A	1	0	1	1	L	L	H	L	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	*
B	0	1	1	1	L	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	#
C	1	1	1	1	L	L	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	A
D	0	0	0	0	L	H	L	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	B
					L	L	H	H	H	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	L	C

Valid Digit, High on detection of a true DTMF tone  
 0=LOW 1=HIGH

LATCH ENABLE MUST BE HIGH. L=LOW H=HIGH X=DONT CARE

Date	Revision/Addition/ Note	by
Oct. 4, 2007	CONCEPT AND ORIGINAL DRAWING PC SOFTWARE TO GENERATE DTMF TONES FROM AUDIO CARD. <a href="http://www.comtekk.us/">http://www.comtekk.us/</a>	WD4BIS
Oct. 7, 2007	Added Package Outlines	WD4BIS

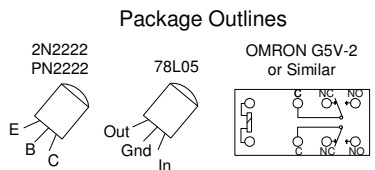

Drawn By: <b>Gerald Crenshaw WD4BIS</b>	Date: <b>Oct. 4, 2007</b>	<b>From the bench of:          Amateur Radio Station WD4BIS</b>	Page <b>1</b>
Engineer: <b>Gerald Crenshaw WD4BIS</b>	Date: <b>Oct. 4, 2007</b>		of <b>1</b>
Checked By: <b>Janet Crenshaw WB9ZPH</b>	Date: <b>Oct. 4, 2007</b>		Title: <b>DTMF to Relay Decoder</b>