



# The Simple Sixty

Ian Liston-Smith G4JQT shows how you can get on the air with a simple two-transistor design.

**A**fter a minor modification one afternoon to make a Pixie transceiver operate on 60m, I made some CW QSOs with it almost immediately. This spurred me on to design a really simple transmitter to see what could be worked with significantly more output on 5262kHz – the UK CW QRP centre of activity for the 60m band. Incidentally, if you're not familiar with the G-QRP Club Pixie design, do a Google search or follow the link below. [www.gqrp.com/The\\_Sprat\\_Pixie\\_File.pdf](http://www.gqrp.com/The_Sprat_Pixie_File.pdf)

This two-transistor circuit, **Fig. 1**, is what I eventually came up with. The circuit is quite conventional and, to keep it simple, I have left out some of the enhancements usually seen in similar circuits. For example, there is no Tx/Rx changeover switch or relay and the keying is in the emitter of Tr1 rather than indirectly keying its supply via a PNP keying transistor. Neither have I included any components to pull the crystal for a little frequency agility. Nevertheless, there's no reason why all these additions and more can't be added. The only embellishments I

have included are an LED to give an indication of RF output and a power-on LED.

### Circuit Description

The crystal oscillator circuit is a Pierce type. The Colpitts oscillator is probably more familiar and has some advantages but the Pierce design enables the oscillator to drive the PA directly. The minor disadvantage of this design is the possibility of slight chirp if the antenna load is incorrect or the supply voltage is much higher than, say, 14V.

The PA device is the ubiquitous IRF510 power MOSFET. They tend to run out of steam beyond 10 to 15MHz but are more than happy at 5MHz. As with most transmitters, it's not recommended that it is keyed for more than 15 to 20 seconds during tune-up, particularly without any RF load!

The circuit easily produces 5W of RF output but with careful selection of RF chokes, transformers and inductors I have managed over 15W output.

I've had plenty of QSOs with this little rig and 60m is ideal for daytime inter-G working, even with a modest antenna. The 60m band

is available to full licence holders but unlike the other bands it is split into sub-bands so if you're unfamiliar with this part of the spectrum it's worth checking the link below. <http://rsgb.org/main/operating/band-plans/hf/5mhz>

### Construction

I didn't bother making a PCB layout so the photo, **Fig. 2**, shows my prototype using 'ugly construction'. Most of the components are not particularly critical but the transistors are driven pretty hard so do require heat-sinks, particularly Tr2.

L1 is about 10 to 15 turns around a large ferrite bead but again it's not critical. If a ready-made choke is used, it must be able to easily withstand a current of 25mA and have a value of 100µH to 500µH.

T1 is not critical either. I wound eight bifilar turns through a small 15mm square pig-nose ferrite block but an FT50-10 core or even a short piece of ferrite rod works nearly as well. Wire type is not critical but I'd suggest something between 24 and 34SWG enamelled copper wire.



