

Modification of 24GHz Wavelab TRX to reduce RX current


YO4HFU – 2023, rev.1

1. Internal disconnection of +5V_A TX chain supply from +5V_LO bus.
Total consumption during RX state will be reduced.

+5V_LO = external supplied from +5V common RXTX.

+5V_A = external supplied from +5V TX

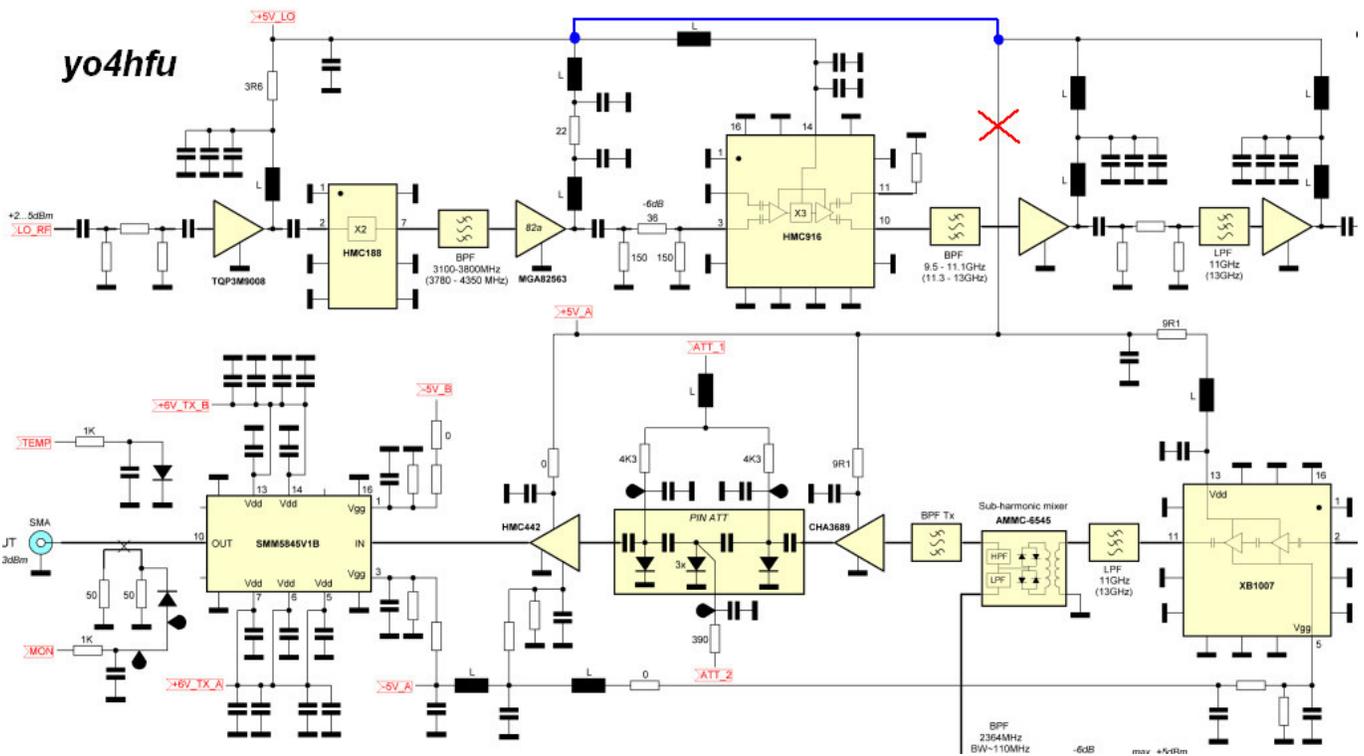+5V_RX= external supplied from +5V RX (not visible in the bellow diagram)



2. Open Wavelab TRX module and proceed with next modifications:

