
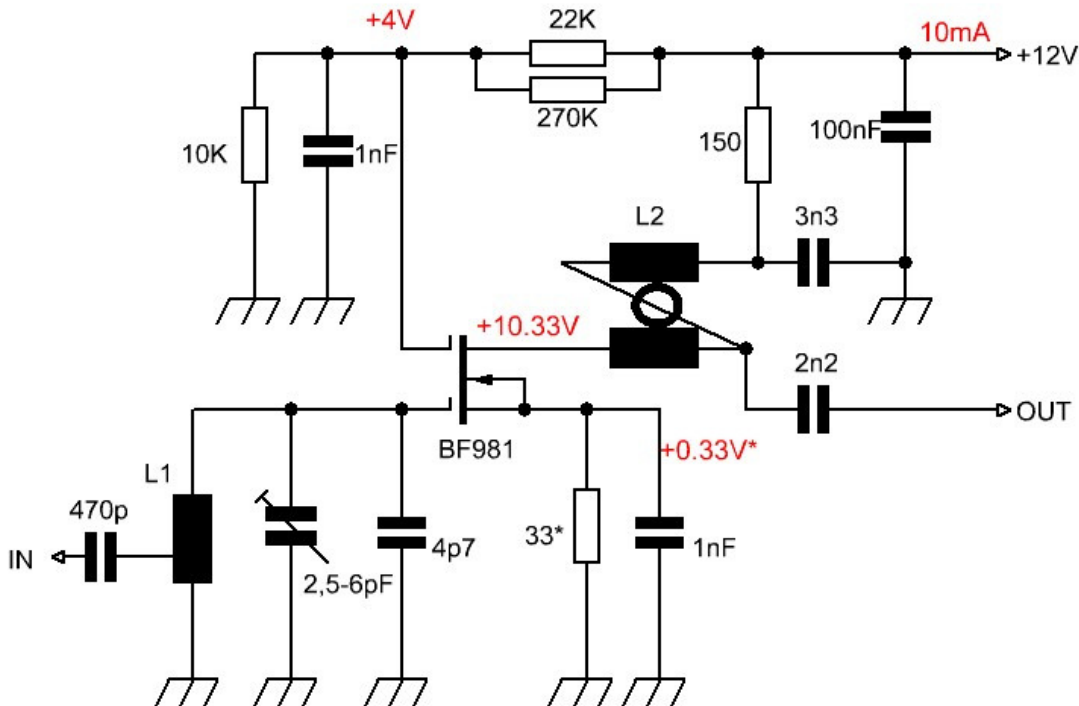




YO4HFU / 2010


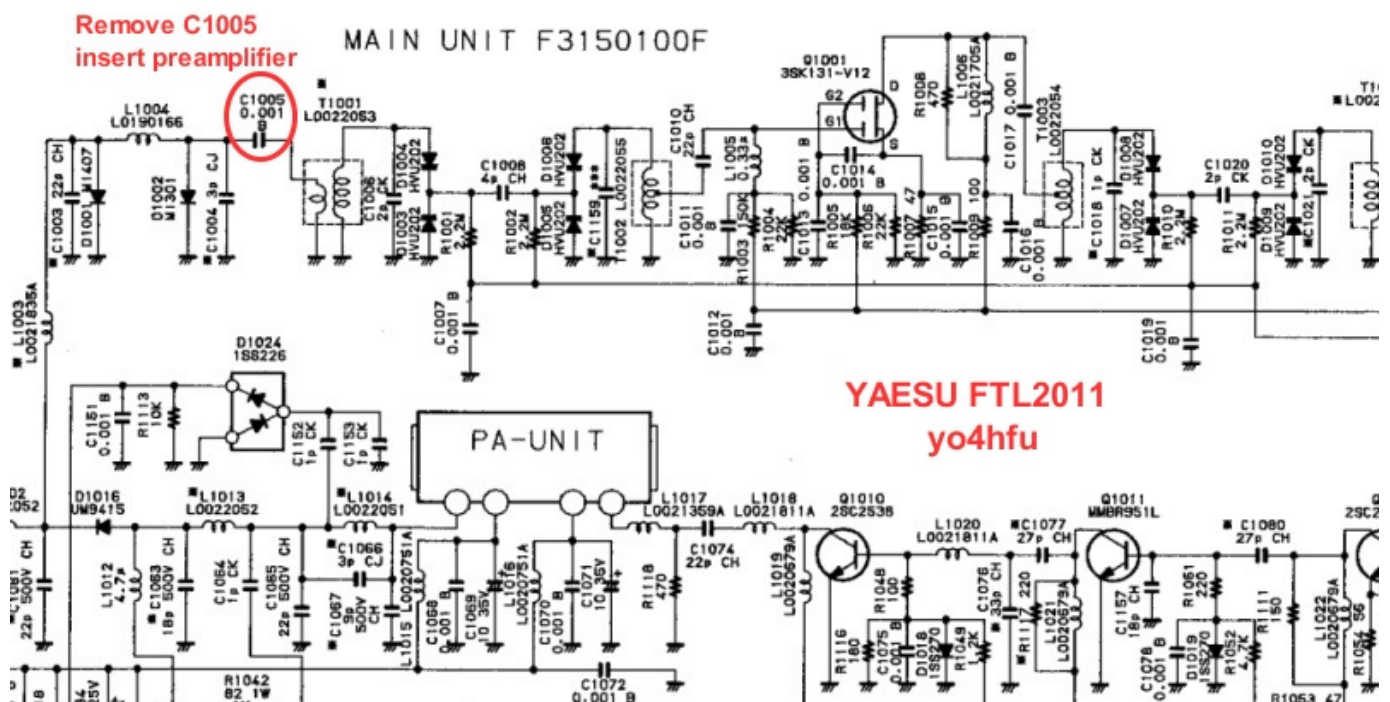



L2= 2x2 turns, CuEm 0,3mm, binocular VHF

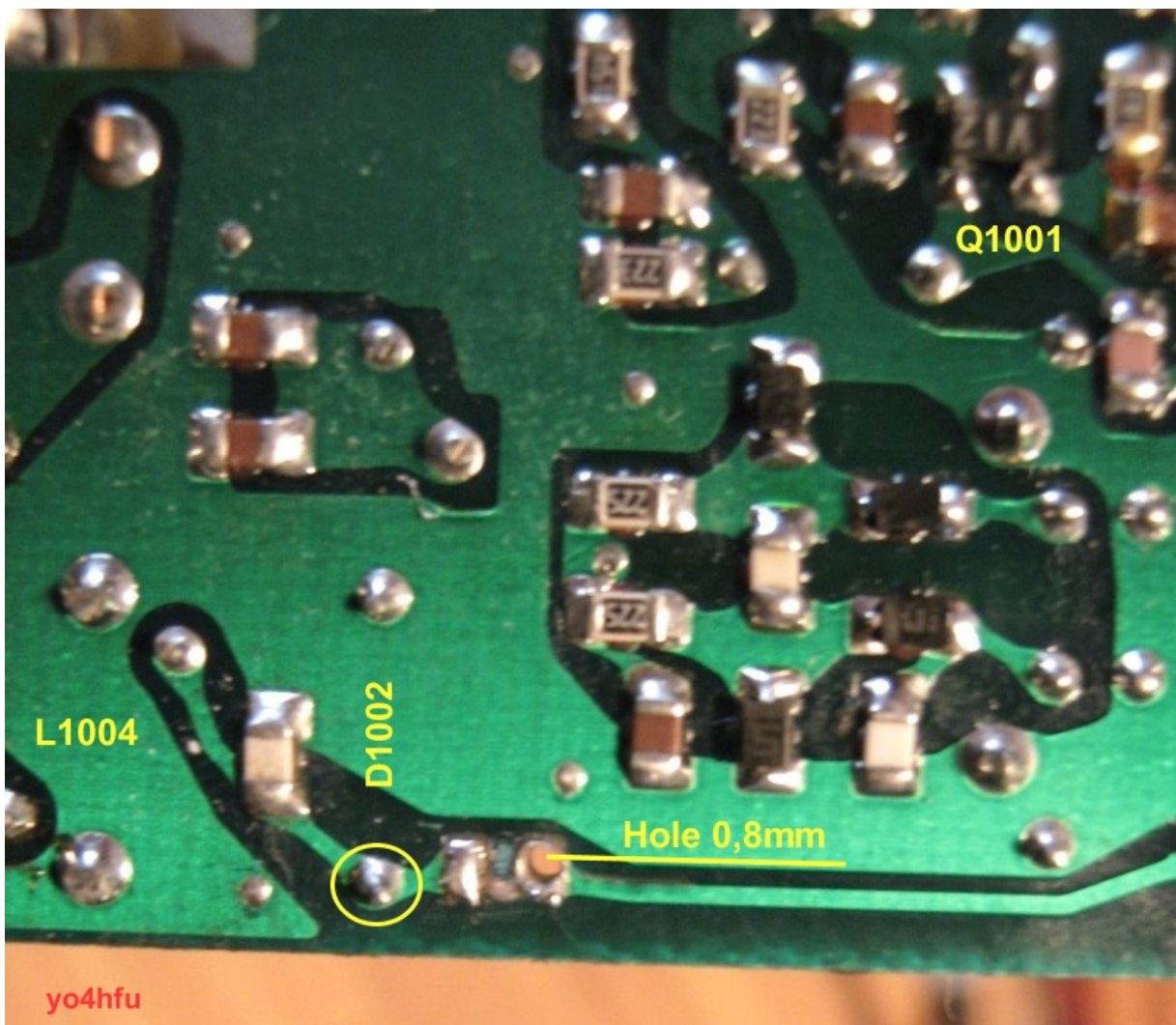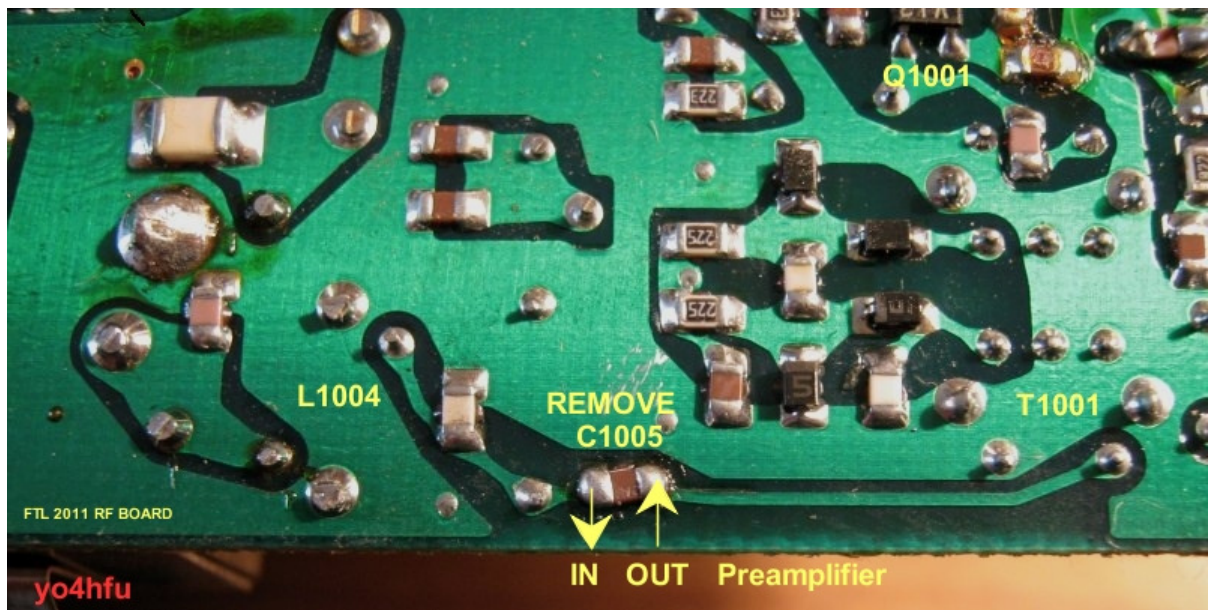
BF981 Preamplifier
Yaesu FTL2011
YO4HFU@2010





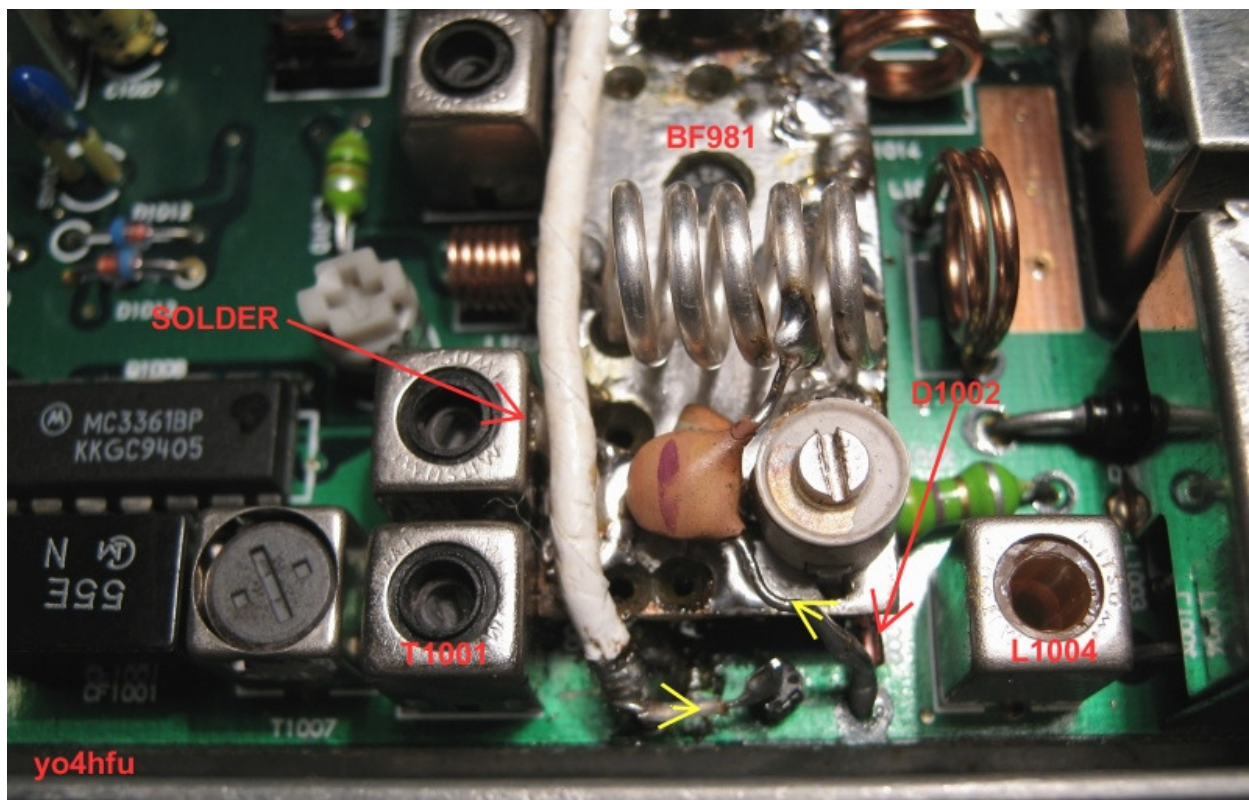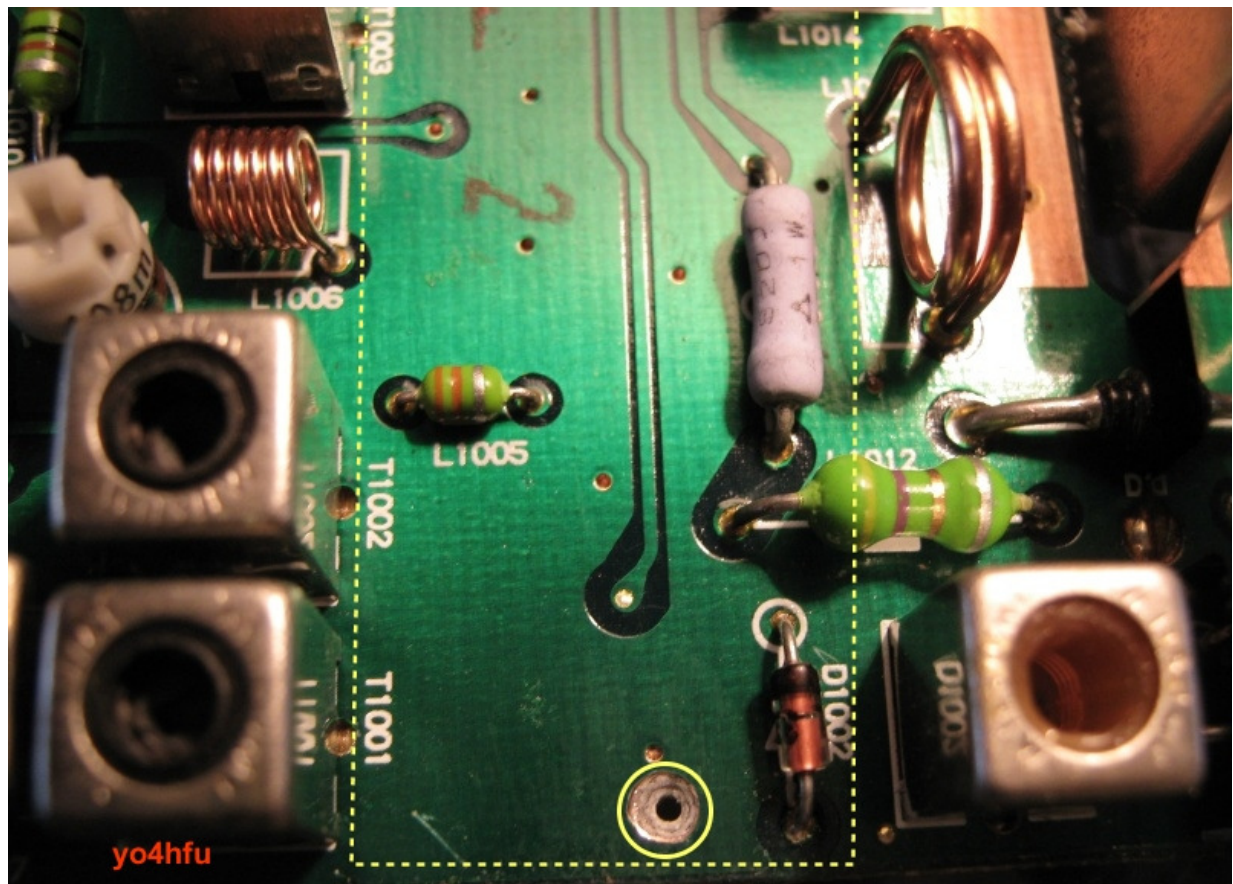

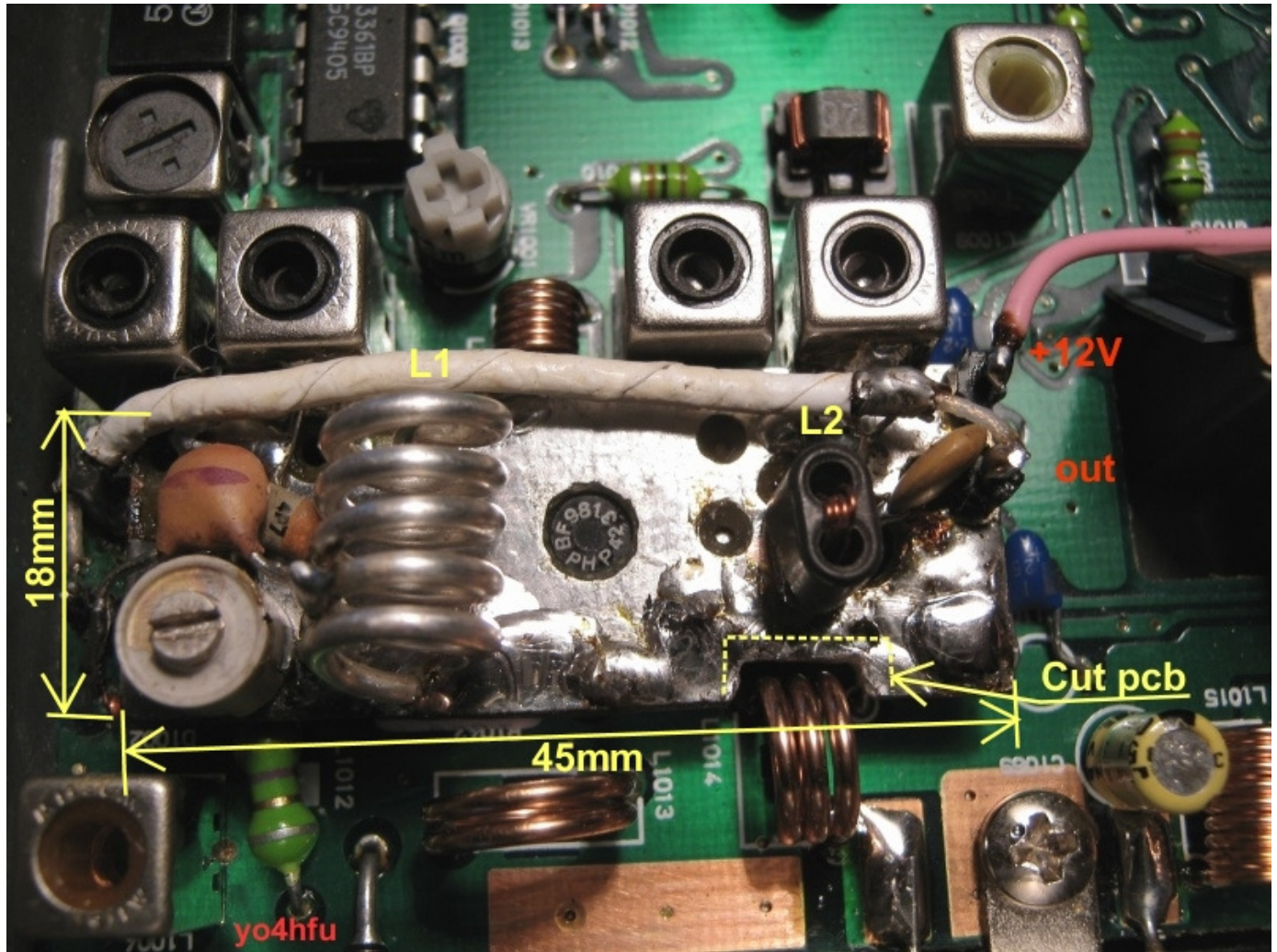

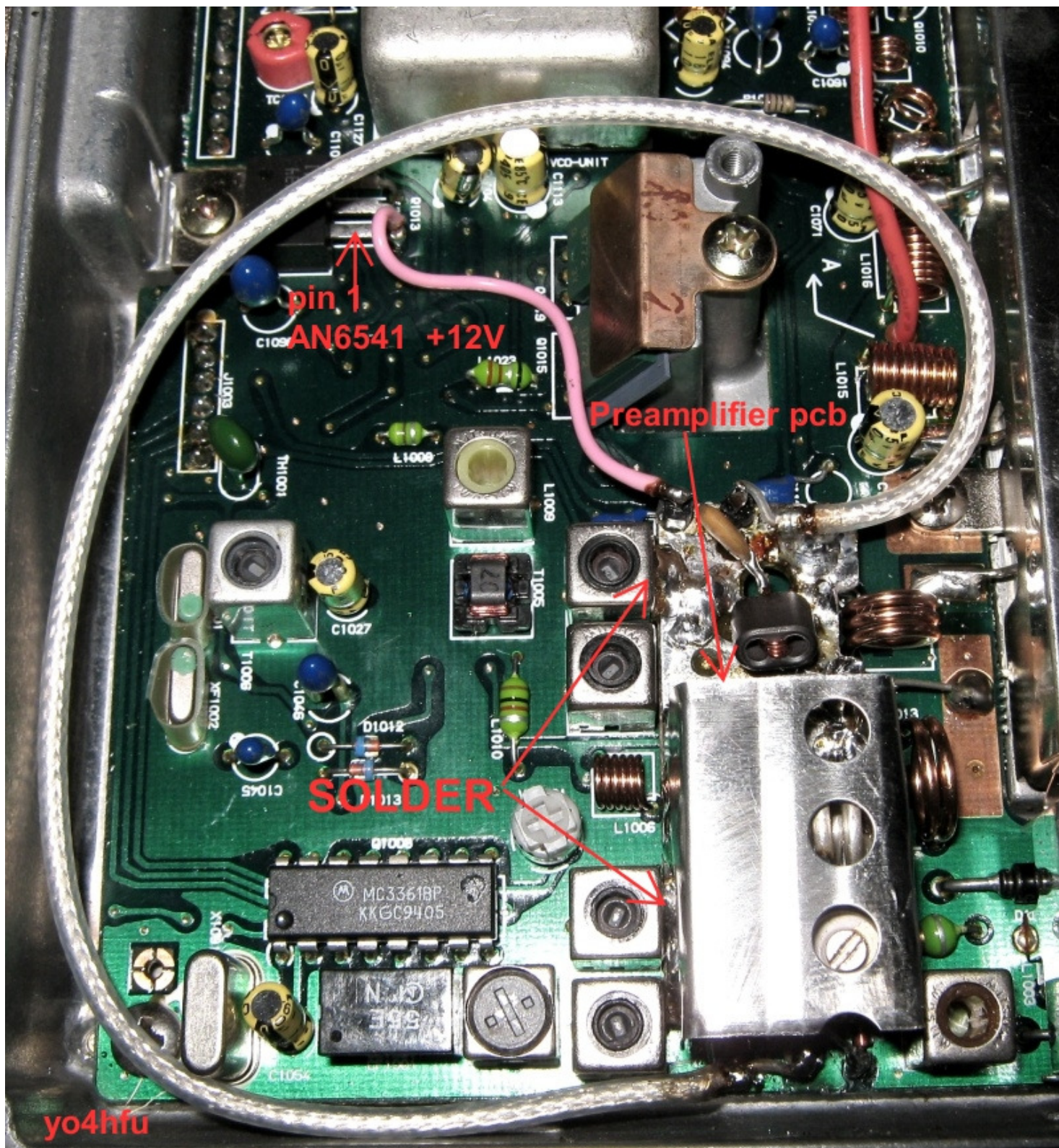

yo4hfu

